

2. Operational Amplifiers


An integrated ckt (IC) amplifier. It is used in countless circuits.

early amplifiers: Vacuum tubes, discrete transistors

mid 60s: The first IC opamp $\mu A 709$ expensive


Today: high-quality opamp - dirt cheap!

2.1 The OPAMP Terminals

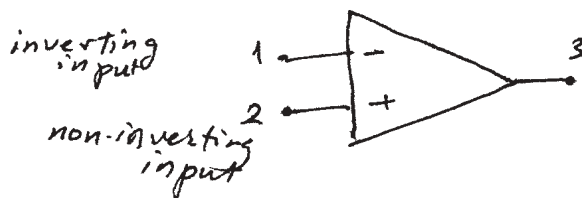

1, 2 : input terminals
3 : output terminal


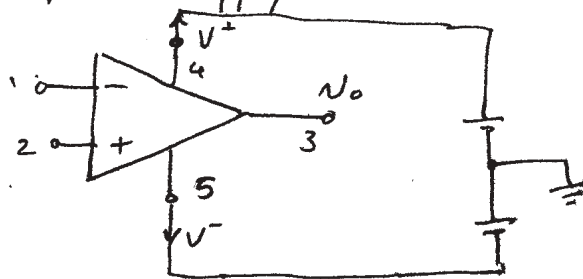
Because it needs DC power, sometimes the power supply leads are also shown:



← This is the voltage-reference for inputs and output


There are other terminals for specific purposes: e.g., frequency compensation, offset nulling.

2.2 The ideal OPAMP

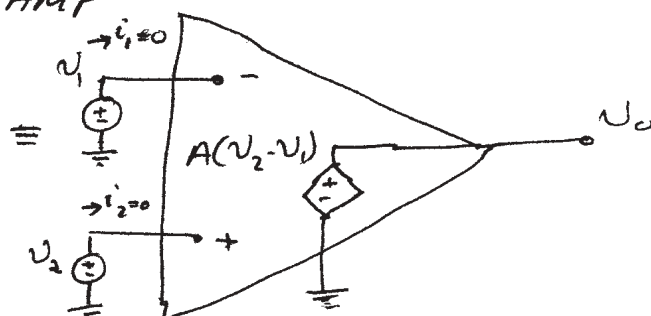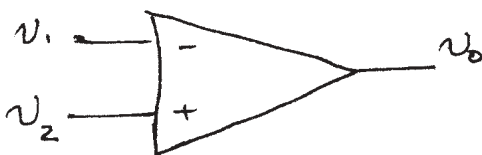


no currents go in at the input
 no limit on the output current
 $V_o = A(V_2 - V_1)$, $A \rightarrow \infty \Rightarrow$ needs negative f.b.

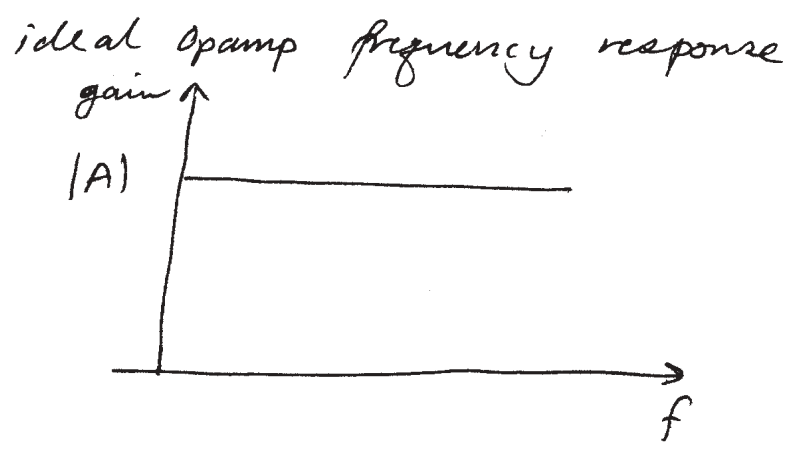Opamp is a differential-input, single-ended amplifier.
 A : differential gain, Open-loop gain
 Overall gain of the amplifier circuit $\rightarrow$ closed-loop gain




2.3 OPAMP in Inverting Configuration

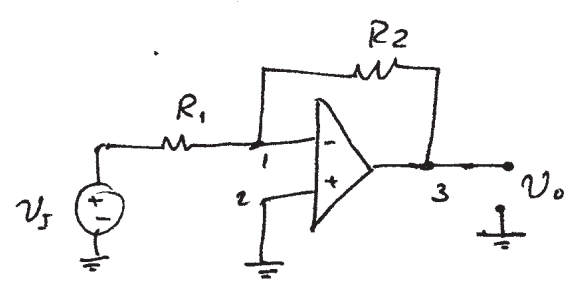

R_2 provides negative feedback because a portion of the output voltage is brought to the inverting input.

Closed-loop gain (overall circuit gain) $G \equiv \frac{V_o}{V_I}$

Equivalent ckt for the amplifier

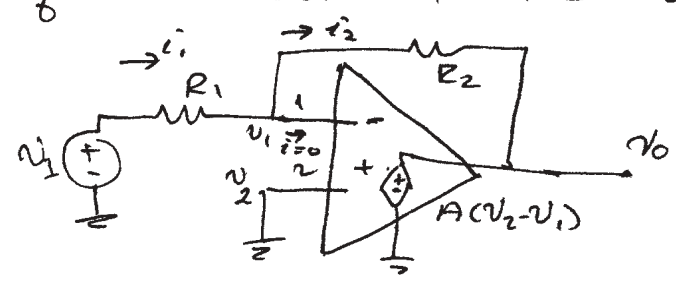

(3)

ideal opamp, finite output $\rightarrow v_o = A(v_2 - v_1)$
 $v_2 - v_1 = \frac{v_o}{A} \approx 0$

Since v_2 is connected to the ground, v_1 has the same potential $\rightarrow$ virtual ground.
 No current goes into the opamp at the input terminals.

$$i_1 = \frac{v_I - v_1}{R_1} = \frac{v_I}{R_1}, \quad i_2 = i_1, \quad v_o = v_1 - i_2 R_2$$

$$v_o = -i_2 R_2 = -i_1 R_2$$

$$v_o = -\frac{R_2}{R_1} v_I$$

$$G = \frac{v_o}{v_I} = -\frac{R_2}{R_1}$$

example: $R_1 = 1 \text{ k}\Omega$
 $R_2 = 10 \text{ k}\Omega$
 $G = -10$

$$A \rightarrow \infty, \quad G = -10$$

Finite open-loop gain $\rightarrow v_2 - v_1 = \frac{v_o}{A}$
 $v_2 = 0 \Rightarrow v_1 = -\frac{v_o}{A}$

$$i_1 = \frac{v_I + \frac{v_o}{A}}{R_1}, \quad i_2 = i_1, \quad v_o = -\frac{v_o}{A} - \left(\frac{v_I + \frac{v_o}{A}}{R_1} \right) R_2$$

$$G = \frac{v_o}{v_I} = \frac{-R_2/R_1}{1 + (1 + \frac{R_2}{R_1})/A}$$

$$A \rightarrow \infty \Rightarrow G = -R_2/R_1$$


$(1 + \frac{R_2}{R_1})/A$ in the denominator should be made small so that variations in A does not affect the overall gain.

$$1 \gg \frac{1 + R_2/R_1}{A}$$

Example $R_1 = 1 \text{ k}\Omega, R_2 = 100 \text{ k}\Omega$

$A =$	10^3	10^4	10^5	∞
$G =$	90.83	99.00	99.90	100

input resistance of the amplifier:

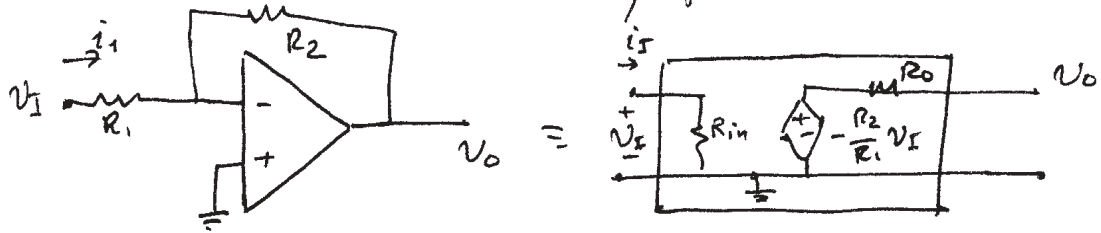

$$R_{in} = \frac{V_i}{i_i} = R_1$$

$$R_o = 0$$


Design problem: An inverting amplifier is to be designed. Specs: $R_{in} = 1 \text{ M}\Omega$, $|G| = 100$.

Solution: $R_1 = 1 \text{ M}\Omega$ $R_2 = 100 \text{ M}\Omega$.

↑ this is very large!

In practice we keep the resistors in $\text{k}\Omega$ range preferable not to exceed $1 \text{ M}\Omega$.

Here is a configuration:

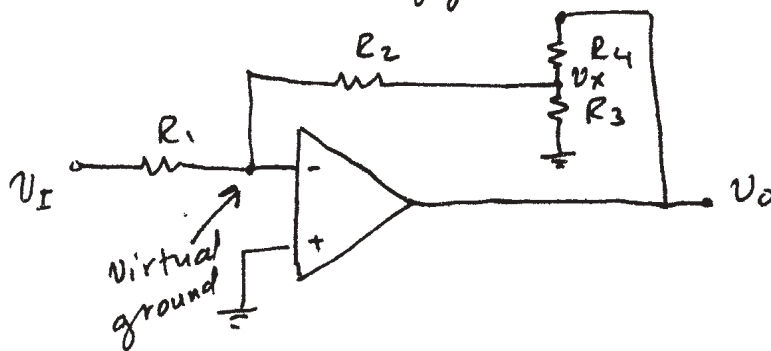

R_3 and R_4 work almost like a voltage divider.

$$V_x = V_o \frac{R_2 \parallel R_3}{R_4 + R_2 \parallel R_3}$$

$$V_x = -\frac{R_2}{R_1} V_i$$


$$\therefore \frac{V_o}{V_i} = -\frac{R_2}{R_1} \left(1 + \frac{R_4}{R_2} + \frac{R_4}{R_3} \right) \text{ is obtained.}$$

$$R_{in} = R_1 = 1 \text{ M}\Omega, \quad R_2 = 1 \text{ M}\Omega, \quad R_4 = 1 \text{ M}\Omega \Rightarrow R_3 = 10.2 \text{ k}\Omega$$

5

2.4 Other Inverting Amp Configurations

In general

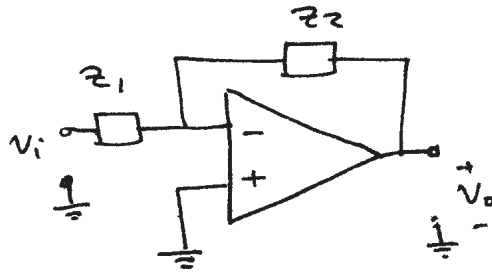

$$\frac{V_o}{V_i} = -\frac{Z_2}{Z_1}$$

Specific examples: $Z_1 = R$, $Z_2 = \frac{1}{sC}$


$$\frac{V_o}{V_i} = -\frac{1}{sCR}$$

$$\text{or } \frac{V_o}{V_i} = -\frac{1}{j\omega CR}$$

in time domain


$$i_i = \frac{V_i(t)}{R}$$
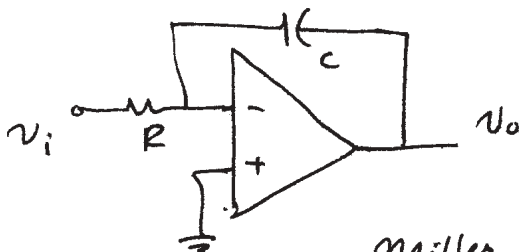
$$V_o = -\frac{1}{C} \int_0^t \frac{V_i(t)}{R} dt + V_c(0)$$




Miller integrator
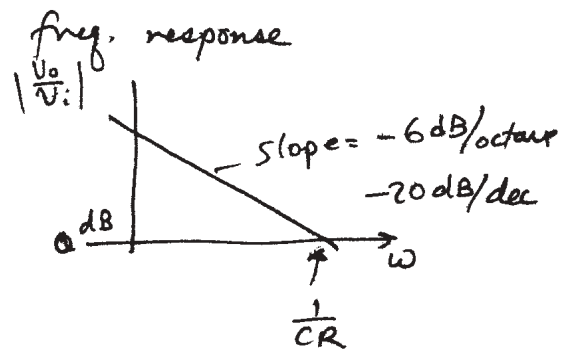
$$= -\frac{1}{RC} \int_0^t V_i(t) dt + V_c(0)$$




Differentiator:

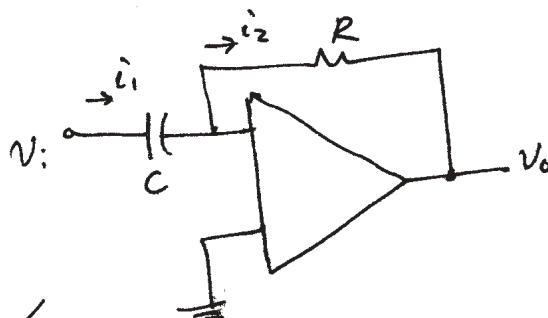

$$i_i = C \frac{dV_i}{dt}$$


$$V_o = -i_i R$$

$$V_o = -RC \frac{dV_i}{dt}$$

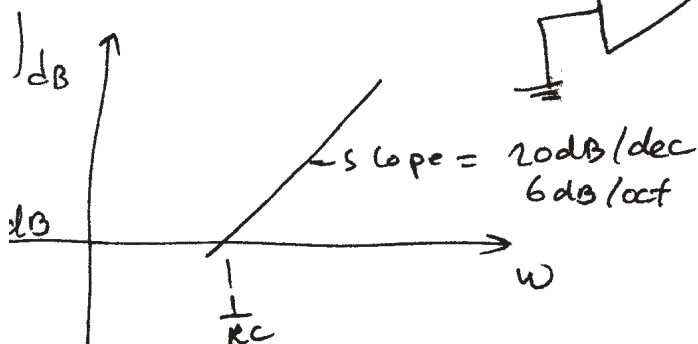

⑤

Summer (weighted summer)

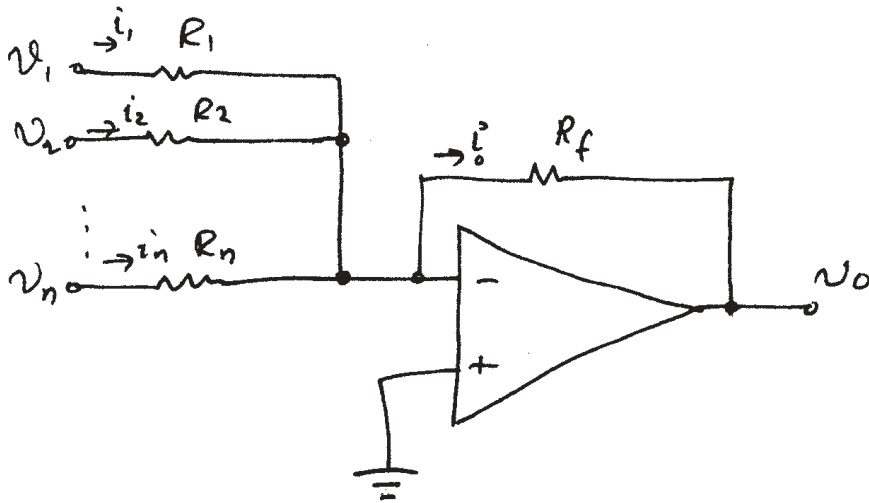


$$\begin{aligned} i_o &= i_1 + i_2 + \dots + i_n \\ &= \frac{V_1}{R_1} + \frac{V_2}{R_2} + \dots + \frac{V_n}{R_n} \Rightarrow V_o = -R_f \left(\frac{V_1}{R_1} + \frac{V_2}{R_2} + \dots + \frac{V_n}{R_n} \right) \end{aligned}$$

if $R_1 = R_2 = \dots = R_n = R_f \Rightarrow V_o = -(V_1 + V_2 + \dots + V_n)$

5 Non-inverting Configuration

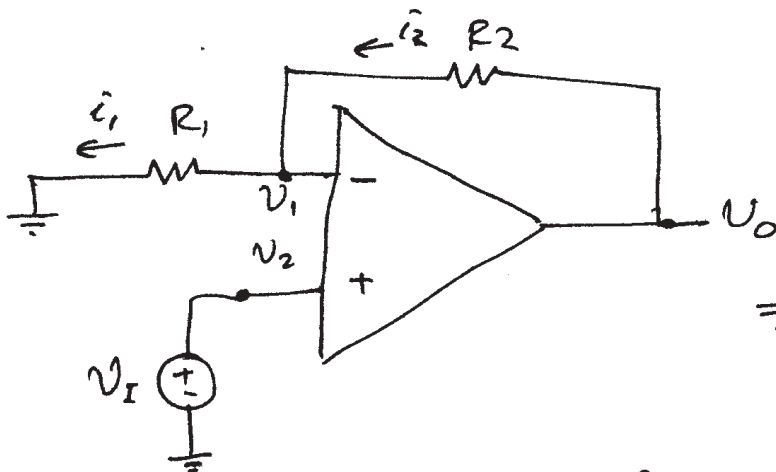
- still need negative feedback for linear operation



Negative feedback $\rightarrow V_1 = V_2$
voltage divider
 $\Rightarrow V_1 = V_o \frac{R_1}{R_1 + R_2} = V_2 = V_i$


$$V_i = V_o \frac{R_1}{R_1 + R_2} \Rightarrow \frac{V_o}{V_i} = \frac{R_1 + R_2}{R_1} = 1 + \frac{R_2}{R_1}$$

eg. clt:

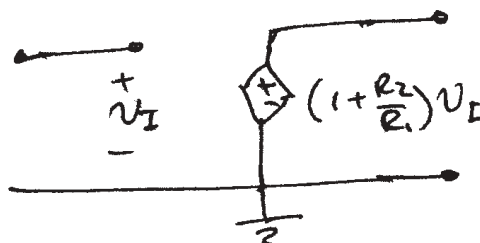


useful as
buffer amplifier

7

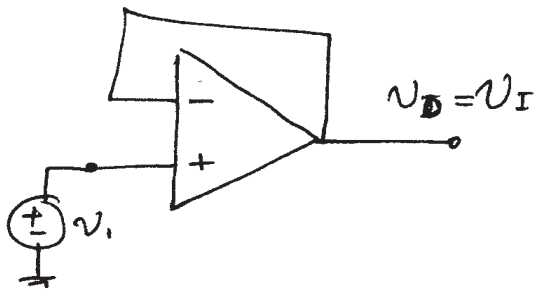

voltage follower.

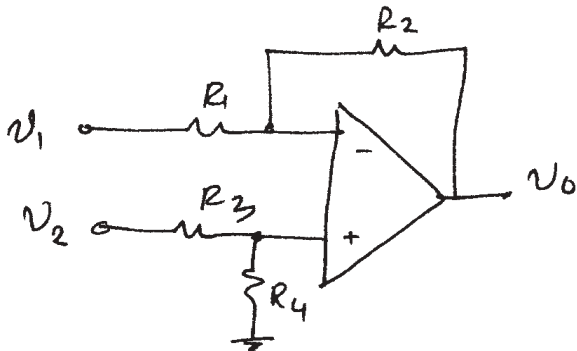2.6 Other Examples: of Op Amp applications



Difference amplifier


$$V_o = -\frac{R_2}{R_1} V_1 + \frac{1 + R_2/R_1}{1 + R_3/R_4} V_2$$

if $\frac{R_4}{R_3} = \frac{R_2}{R_1} \Rightarrow V_o = \frac{R_2}{R_1} (V_2 - V_1)$

Since there are two inputs, a "differential" input resistance is defined:

$$R_{in} \equiv \frac{V_2 - V_1}{i}$$


$$R_{in} = R_1 + R_1 = 2R_1$$

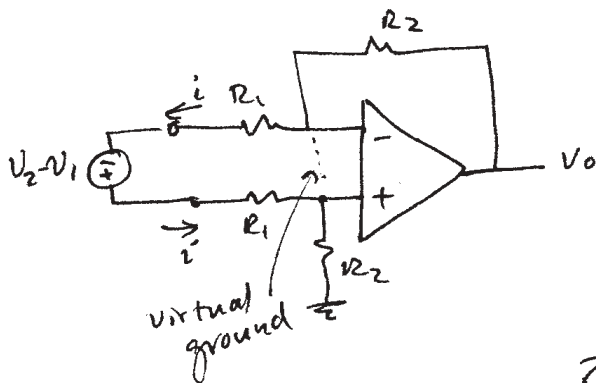

(instrumentation amplifier)

To improve the input resistance (i.e. to increase it) buffers may be placed before the inputs.

(Negative impedance converter)

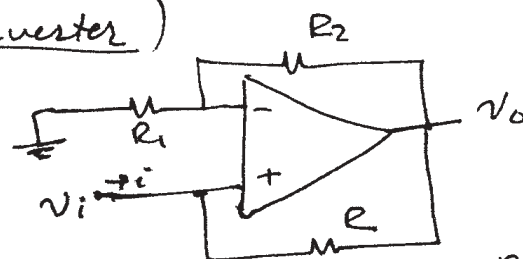

$$i = -\frac{(V_o - V_i)}{R} = -\frac{V \left(1 + \frac{R_2}{R_1}\right)}{R}$$



$$\frac{V}{i} = \frac{-R}{\left(1 + \frac{R_2}{R_1}\right)} = -R \frac{R_1}{R_2}$$

8


$$\text{if } R_1 = R_2 \Rightarrow R_{in} = \frac{V_i}{i} = -R$$

That means the ckt above is equivalent to a negative resistance. (The resistance may be replaced by an impedance.)

Consider the following:

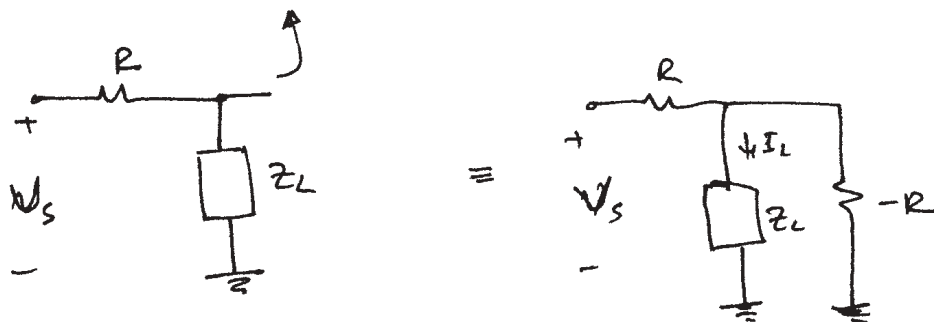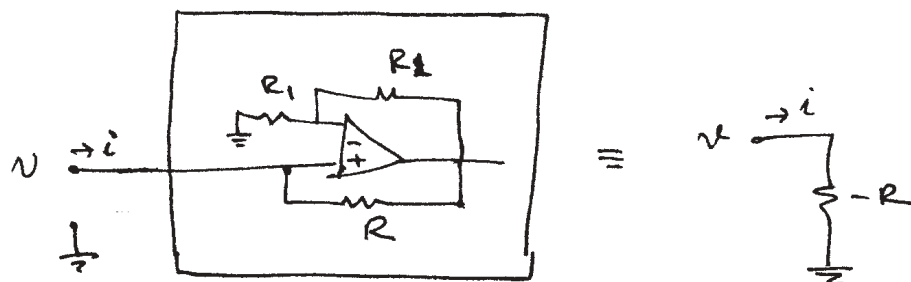

Convert Thevenin to Norton $\rightarrow$

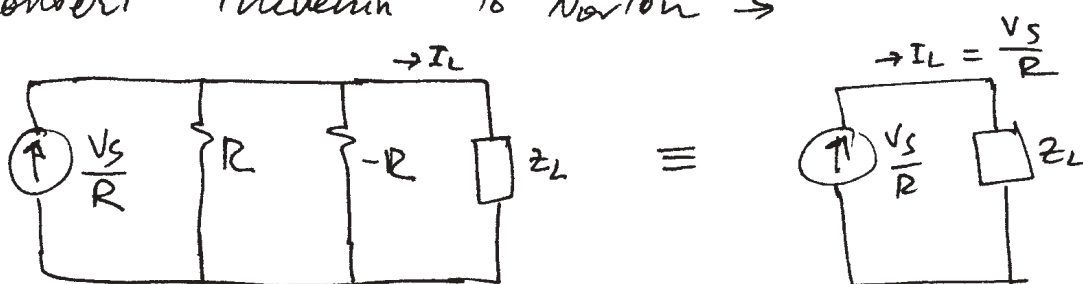


Read section 2.6 (pp. 67-76)

2.7 Nonideal Performance of OP AMPs

it is important to know the limitations so that one designs the ckt better.

Finite Open-Loop Gain and Bandwidth

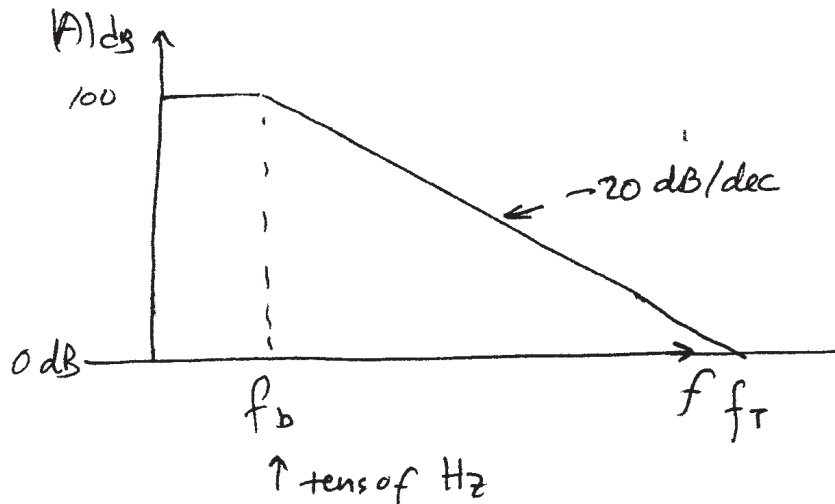

internally
frequency compensated
opamp
(including a capacitor)

$$A(s) = \frac{A_0}{1 + s/\omega_b}$$

$$s = j\omega, \quad A(j\omega) = \frac{A_0}{1 + j\omega/\omega_b}$$

A_0 : dc gain

ω_b : "break" frequency

high cut-off frequency

3 dB cut-off freq.

$$\omega \gg \omega_b \Rightarrow A(j\omega) \approx \frac{A_0 \omega_b}{j\omega}$$

$$\omega_t = A_0 \omega_b = \text{unity-gain bandwidth} \\ = \text{gain-bandwidth product.}$$

$$A(j\omega) \approx \frac{\omega_t}{j\omega}$$

$$A(s) \approx \frac{\omega_t}{s} \leftarrow \text{integrator} \\ \text{time constant } \tau = \frac{1}{\omega_t}$$

(10)

Frequency Response of Closed-loop Amplifiers:

The inverting amplifier gain was found to be


$$\frac{V_o}{V_i} = \frac{-\frac{R_2}{R_1}}{1 + (1 + \frac{R_2}{R_1})/A}$$

$$A(s) = \frac{A_0}{1 + s/\omega_b}$$

This makes $\frac{V_o}{V_i} = \frac{-\frac{R_2}{R_1}}{1 + \frac{1}{A_0} \left(1 + \frac{R_2}{R_1}\right) + \frac{s}{\omega_b / (1 + \frac{R_2}{R_1})}}$

$$A_0 \gg 1 + \frac{R_2}{R_1} \Rightarrow$$
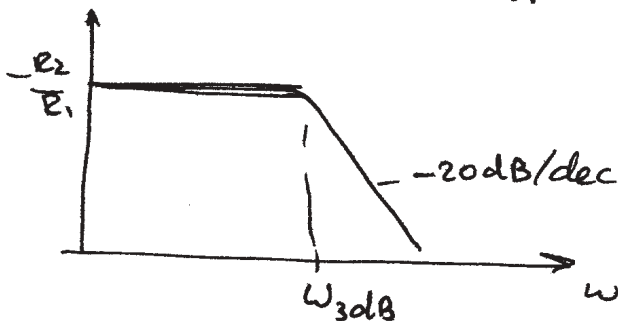
$$\frac{V_o}{V_i} \approx \frac{-R_2/R_1}{1 + \frac{s}{\omega_b / (1 + \frac{R_2}{R_1})}}$$



$$\omega_{3dB} = \frac{\omega_b}{1 + \frac{R_2}{R_1}}$$

For the non-inverting amplifier


$$\frac{V_o}{V_i} = \frac{1 + \frac{R_2}{R_1}}{1 + (1 + \frac{R_2}{R_1})/A}$$

$$A_0 \gg 1 + \frac{R_2}{R_1} \Rightarrow$$

$$\frac{V_o}{V_i} \approx \frac{1 + R_2/R_1}{1 + \frac{s}{\omega_b / (1 + \frac{R_2}{R_1})}}$$

$$\omega_{3dB} = \frac{\omega_b}{1 + \frac{R_2}{R_1}}$$

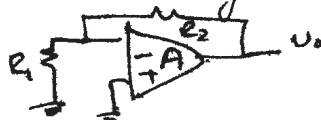The feedback loop of the inverting and noninverting configurations are the same:



Forward path gain $\rightarrow -A$

Feedback path voltage divider
(feedback factor, β)

$$\frac{R_1}{R_1 + R_2} = \beta$$

The loop gain $= -A\beta$

amount of feedback (return difference) $\equiv 1 - \text{loop gain}$
 $= 1 + A\beta$


3 dB bandwidth $f_{3dB} = \beta f_t$

Large Signal Operation of OPAMPS

Output Saturation


The output voltage of an opamp is limited by the power supply. However, not all of the voltage of the supply is available for the output. It is 1-3 V less than the supply voltages in magnitude.

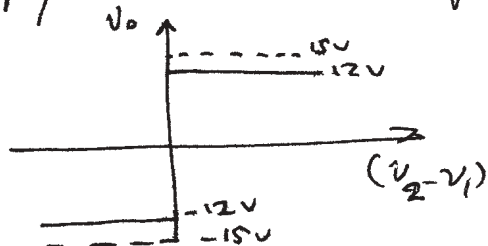± 15 V supply $\rightarrow \pm 12$ V output (rated output voltage)



Slew Rate

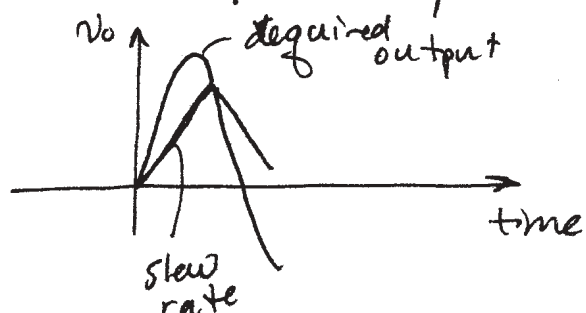
The output voltage has a limit in increasing or decreasing. This is due to the internal capacitors of the operational



amplifier and the limited current to charge them
Sine/square wave $\Rightarrow$ triangular wave.

(12)

Consider the following unity gain ampl.

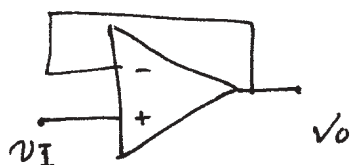

$$\frac{V_O}{V_i} = \frac{1}{1 + s/\omega_t} \quad (\text{low pass})$$




Step input $\rightarrow V_O(t) = V(1 - e^{-t/\tau})$

$$\tau = \frac{1}{\omega_t}$$

initial slope: V/τ

sw Rate $SR = \left. \frac{dV_O}{dt} \right|_{\max}$

data sheets $\rightarrow V/\mu s$

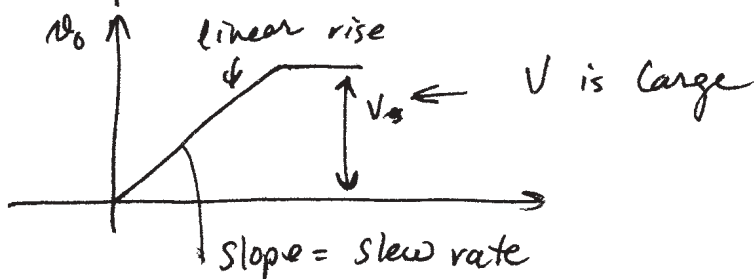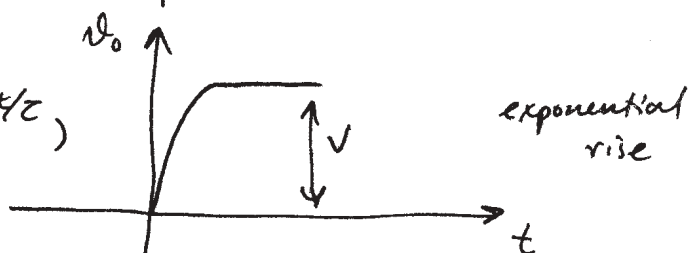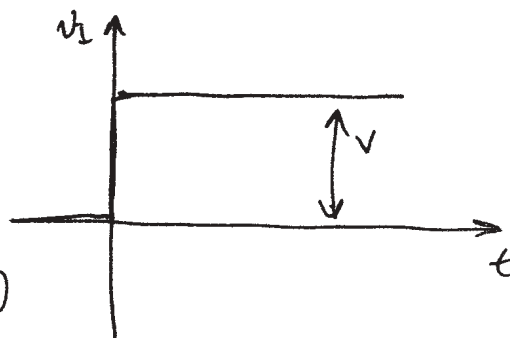

Full Power Bandwidth

consider the unity gain amplifier.


input signal $v_i = \hat{V}_i \sin \omega t$

$$\frac{dv_i}{dt} = \omega \hat{V}_i \cos \omega t$$

max slope = $\omega \hat{V}_i$

at the zero crossing

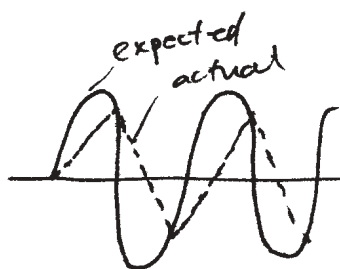if $\omega \hat{V}_i$ exceeds the slew rate, the output waveform will be distorted.



Data sheets $f_m = \text{full power bandwidth}$


(max operating freq)

output voltage: V_{Omax}

$$\omega_m V_{Omax} \equiv SR \Rightarrow f_m = \frac{SR}{2\pi V_{Omax}}$$

⇒ if $\omega > \omega_m$, $V_o = V_{omax} \left(\frac{\omega_m}{\omega} \right)$
 max amplitude of the output w/o distortion.

Common mode Rejection

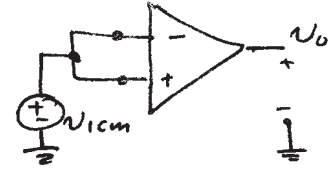

$$\left. \begin{aligned} V_{Idm} &= V_2 - V_1 \\ V_{Icm} &= \frac{V_1 + V_2}{2} \end{aligned} \right\}$$

$$V_o = A_{dm} V_{Idm} + A_{cm} V_{Icm}$$

$$A_{dm} \rightarrow A$$


$$A_{cm} = \frac{V_o}{V_{Icm}}$$

Common mode rejection ratio

$$CMRR = \frac{|A|}{|A_{cm}|} \quad \text{or} \quad 20 \log \left| \frac{A}{A_{cm}} \right|$$



80 - 100 dB @ low freq.

Input and Output resistances

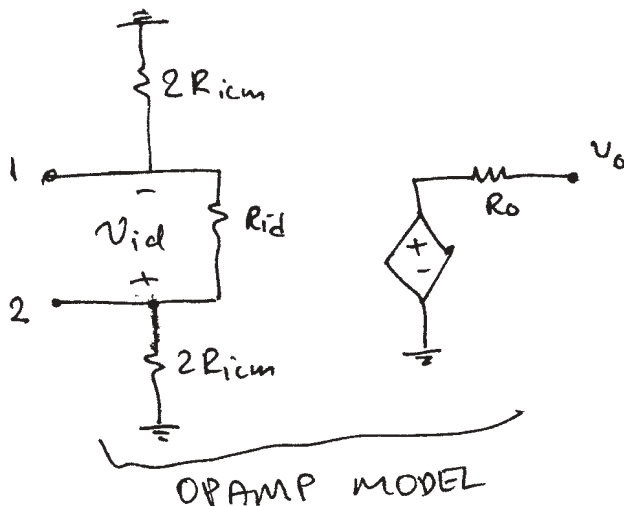

Typical values (bipolar general purpose)
 $R_{id} = 1 \text{ M}\Omega$
 $R_{icm} = 100 \text{ M}\Omega$

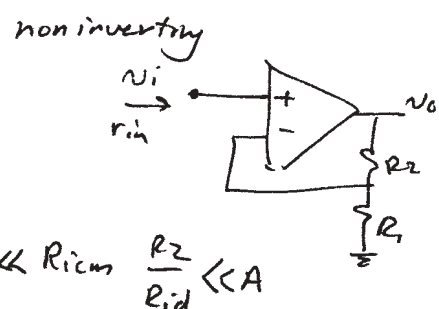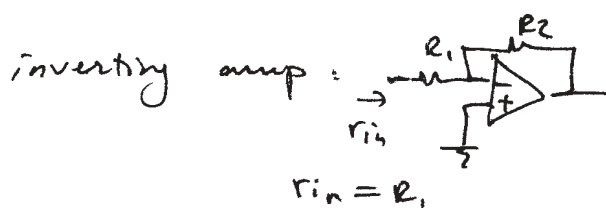
The input resistance of the closed-loop amplifier is important



Assuming
 $R_o \approx 0$ $R_1 \ll R_{icm}$ $\frac{R_2}{R_{id}} \ll A$

$$R_{in} \approx \{2R_{icm}\} \parallel \{(1 + A\beta)R_{id}\}, \quad \beta = \frac{R_1}{R_1 + R_2}$$

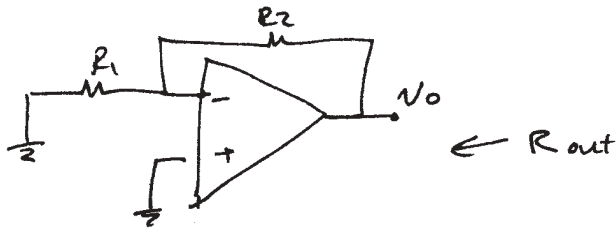Output resistance $R_o \rightarrow 75 - 100 \Omega$




ignoring the input resistances:

$$R_{out} = [R_1 + R_2] \parallel \left[\frac{R_o}{(1 + A\beta)} \right] \approx \frac{R_o}{A\beta}$$

↑ smaller than R_o .

DC Problems:

OFFSET VOLTAGE

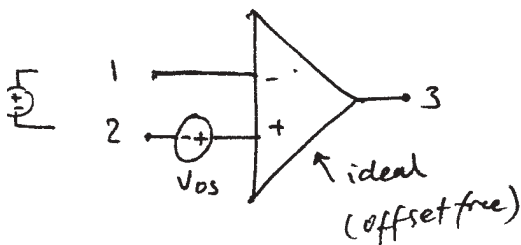


The inputs of the actual circuit is not exactly symmetrical $\rightarrow$ when both inputs are shorted, the output may not be zero.

Bias currents are needed. They may be different.



V_{os} - input offset voltage

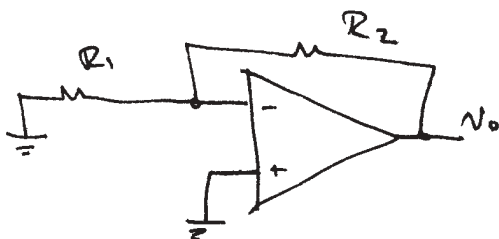


$$V_o = V_{os} \left(1 + \frac{R_2}{R_1} \right)$$

$$\frac{V_o}{1 + \frac{R_2}{R_1}} = V_{os}$$


V_o is measured
 V_{os} calculated.

To adjust for the input offset voltage

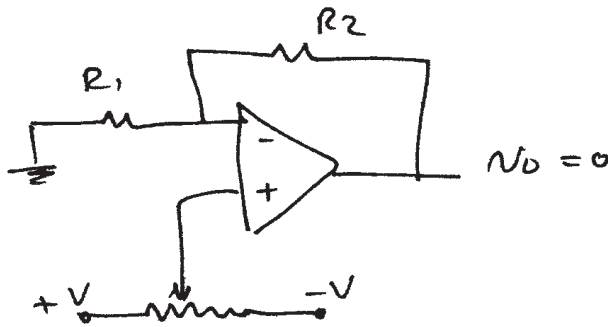

Special terminals of the opamp package may be used to cancel the effects of V_{OS} .

input offset currents:

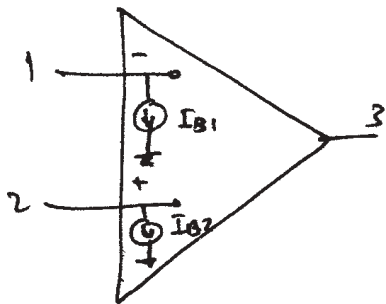


$$I_B = \frac{I_{B1} + I_{B2}}{2} \quad \text{input bias current}$$

$$I_{OS} = |I_{B1} - I_{B2}|$$

To . . . reduce the effects of input offset currents,

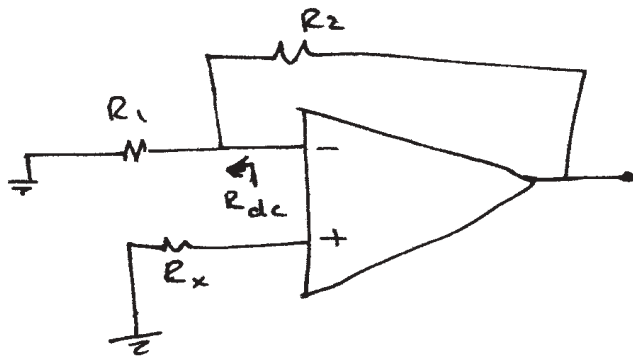Place a resistor in the noninverting lead:



R_{dc} the DC resistance seen by the inverting input.

Read about capacitive coupling and the rest of the chapter.

H.W.

2.16
2.17

2.22
2.23

2.32
2.33

2.40
2.41