
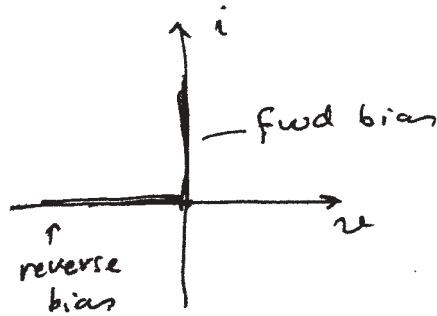


3. DIODES

3.1 IDEAL DIODE

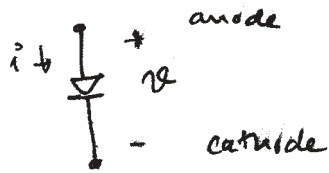



$v < 0 \Rightarrow$
 $i = 0$
 "cutoff"

$i > 0 \Rightarrow R = 0$
 "ON" short ckt.

nonlinear
 piecewise linear

The current is
 limited by the external
 circuit.

Rectifier

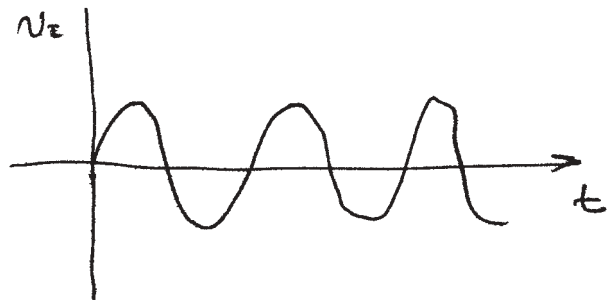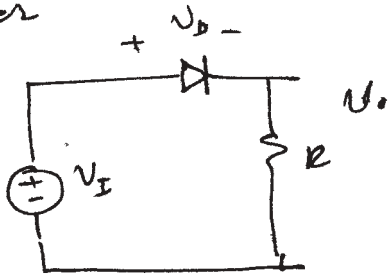



average values

$$\langle V_I \rangle = 0$$

$\langle V_O \rangle \neq 0$ and positive

\Rightarrow rectifier
 AC $\xrightarrow{\text{rectifier}}$ DC


Transfer characteristics
 V_O vs V_I

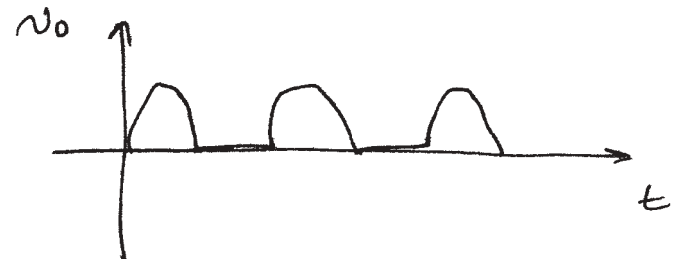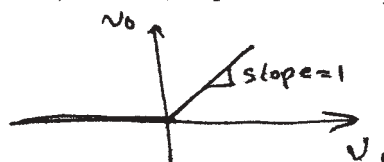


②

Diode logic gates

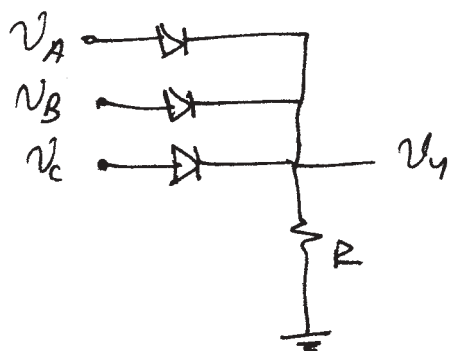Positive logic
 $0V \rightarrow "0"$ $5V \rightarrow "1"$



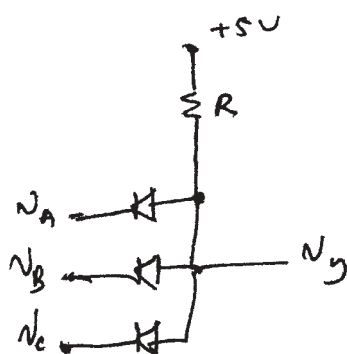
$$V_Y = V_A + V_B + V_C \quad \text{OR gate}$$



$$V_Y = V_A \cdot V_B \cdot V_C$$


AND gate

D is ON

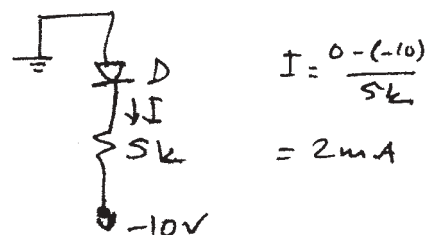

Example

Find I and V in the circuit below.

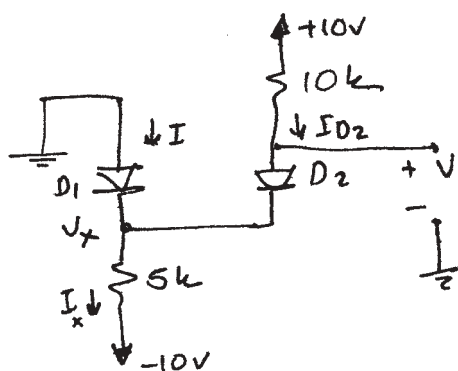

ARE THE DIODES ON OR OFF?

I

ASSUME D1 is OFF, D2 is ON $\rightarrow V_x = 0$

$V_x = ?$

$$I_{D2} = \frac{10 - (-10)}{10 + 5} = \frac{20}{15} \text{ mA}$$

$$V_x = -10 + 5 \times \frac{20}{15} = -10 + \frac{20}{3} = -3.33 \text{ V}$$


This would make $V_{D1} = 3.33 \text{ V} \rightarrow$ DIODE IS ON

$\Rightarrow V_x = 0 \text{ V} \Rightarrow$

$$I_x = \frac{0 - (-10)}{5k} = 2 \text{ mA}, \quad I_{D2} = \frac{10 - 0}{10} = 1 \text{ mA}$$

$$I = 2 - 1 = 1 \text{ mA}$$

Example

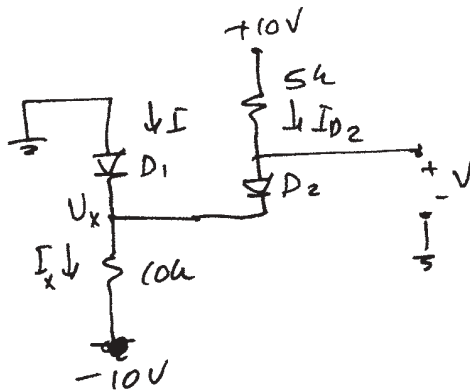Assume $D_1 : ON$ $D_2 : ON$ $D_1 : ON \rightarrow V_x = 0V$ $I_x = 1mA$

$$I + I_{D2} = I_x = 1mA$$

$$I_{D2} = \frac{10 - V}{5} = 2mA$$

$$I = I_x - I_{D2} = 1 - 2mA = -1mA$$

not possible $\rightarrow D_1 : OFF$

$$I_{D2} = \frac{10 - (-10)}{10 + 5} = \frac{20}{15} mA$$

$$\frac{10 - (-10)}{5 + 10} \times 10 - 10 = V$$



$$I = I_{D1} = 0$$

$$I_x = I_{D2}$$

$$\frac{200}{15} - 10 = V$$

$$3.33 = V$$

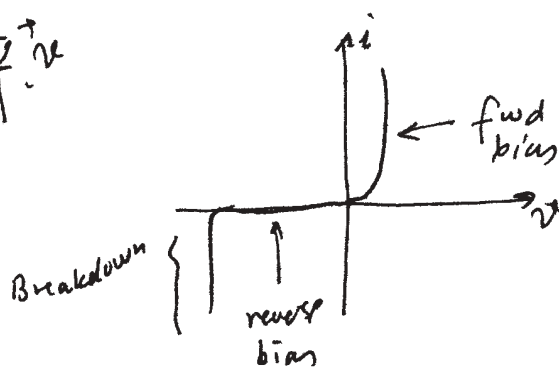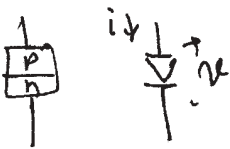Terminal characteristics of Junction Diodes



η = ideality factor
 $1 < \eta < 2$

Reverse and saturation region $\rightarrow i = I_s (e^{\frac{v}{\eta V_T}} - 1)$

(reverse)
 I_s = saturation current, $V_T = \frac{kT}{q}$ thermal voltage


$= 0.0258 V$ at Room Temp
 $300K$

$25 mV$ for practical purposes.

④

if $V \gg \eta V_T$ then $e^{\frac{V}{\eta V_T}} \gg 1 \Rightarrow I \approx I_S e^{\frac{V}{\eta V_T}}$

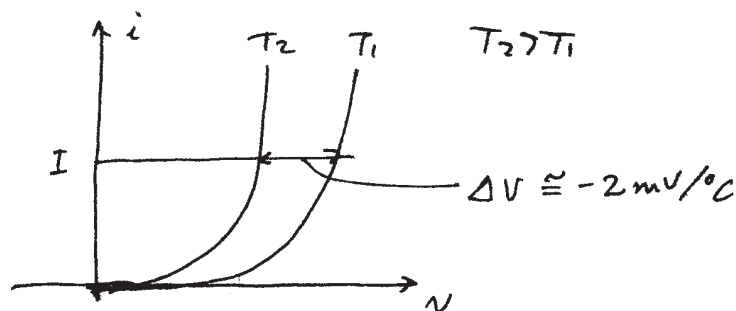
$$\Rightarrow V = \eta V_T \ln \frac{I}{I_S}$$



(I_S doubles for every 10° increase in temperature)

Suppose at 300 K $I_S = 10^{-9} \text{ A}$
 310 K $I_S = 2 \times 10^{-9} \text{ A}$
 320 K $I_S = 4 \times 10^{-9} \text{ A}$

Breakdown


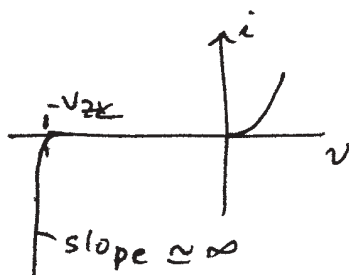


In breakdown, the voltage across the diode remains almost constant \rightarrow voltage reference or voltage regulator.


Analysis of Diode Ckts

graphical analysis

Valid for any nonlinear component

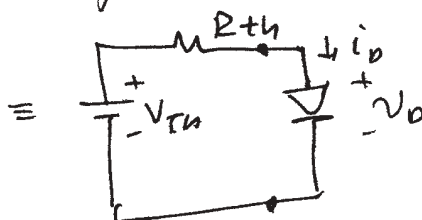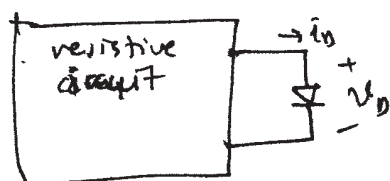

⑤

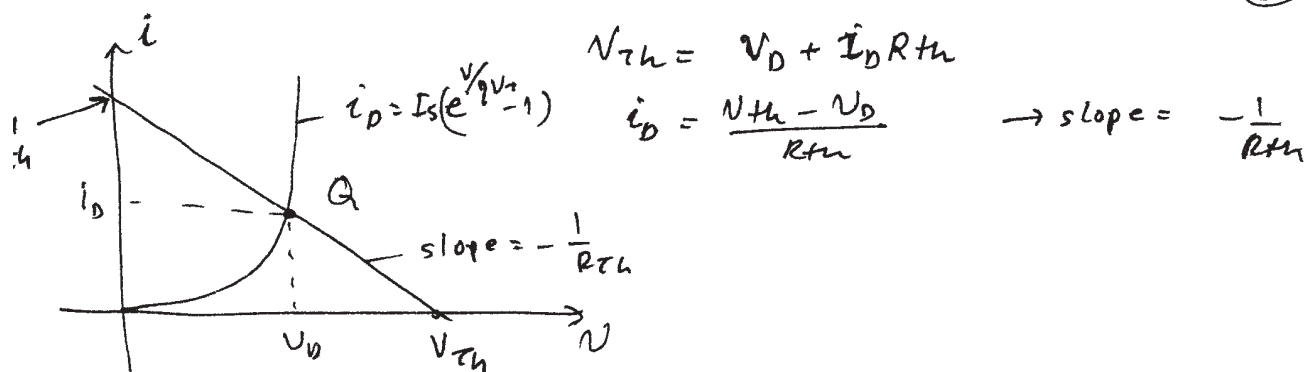

iterative analysis \rightarrow numerical analysis:


Assume $V_{D0} = 0 \Rightarrow I_{D0} = \frac{V_{TH} - V_{D0}}{R_{TH}}$

then find $V_{D1} = \eta V_T \ln \frac{I_{D0}}{I_S} = V_{D1}$

Then Recalculate $I_{D1} = \frac{V_{TH} - V_{D1}}{R_{TH}}$

find $V_{D2} = \eta V_T \ln \frac{I_{D1}}{I_S} \rightarrow$ calculate $I_{D2} = \frac{V_{TH} - V_{D2}}{R_{TH}}$





until V_D and I_D converge.

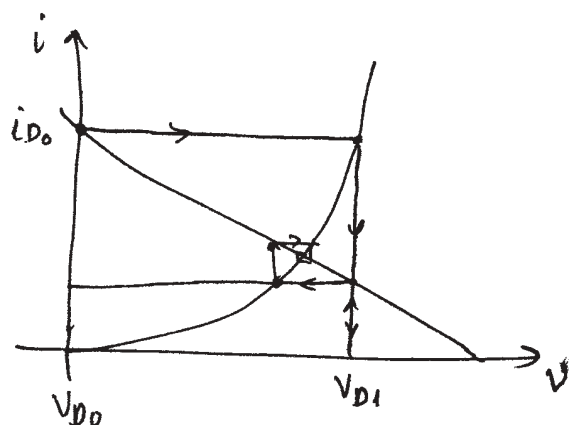

Piecewise linear models



Battery-plus-resistance model.

6

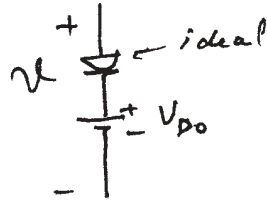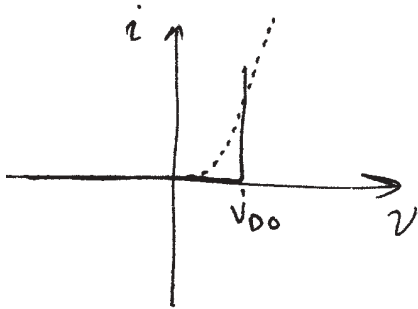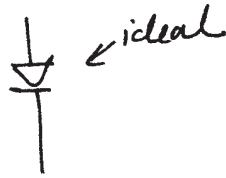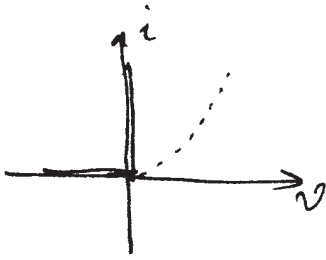

example:

V_D	i_D
0.63V	1 mA
0.72V	10 mA

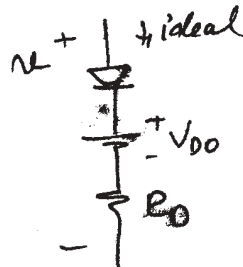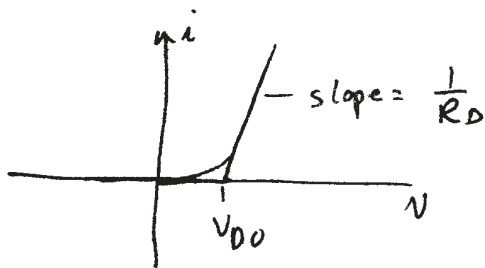

find


$$V_D$$

$$R_D$$


$$V_D = V_{D0} + I_D R_D$$

$$R_D = \frac{V_{D2} - V_{D1}}{I_{D2} - I_{D1}} = \frac{0.9V}{9mA} = 0.1 \Omega$$

Small signal model

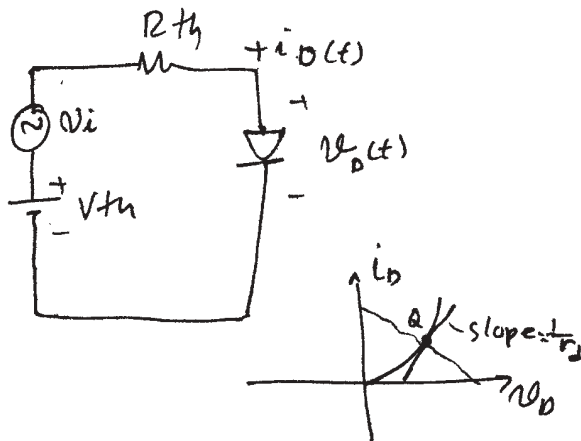


DC equivalent

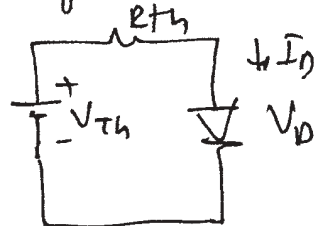

r_d is found from the slope of the characteristic curve at the operating point.

AC equivalent

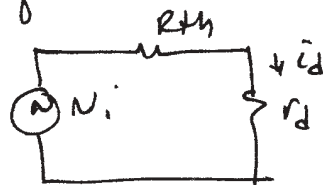


7

$$i_D \approx I_S e^{V_D / \eta V_T}, \quad \frac{di_D}{dV_D} = \frac{1}{\eta V_T} I_S e^{V_D / \eta V_T} = \frac{i_D}{\eta V_T}$$


$$\frac{1}{r_D} = \left. \frac{di_D}{dV_D} \right|_Q = \frac{I_{DQ}}{\eta V_T} \Rightarrow r_D = \frac{\eta V_T}{I_{DQ}}$$

Example:

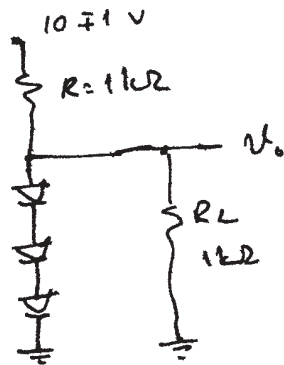

find V_O

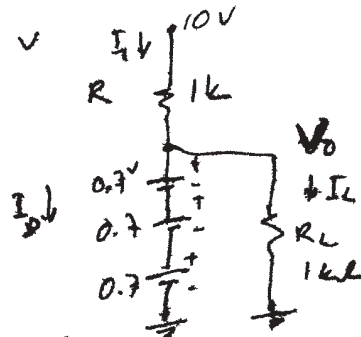DC model
 $V_{D0} \approx 0.7V$
 $\eta = 2$




$$V_O = 3 \times 0.7 = 2.1V$$

$$I_D = \frac{10 - 2.1}{1k} = 7.9mA$$

$$I_L = \frac{2.1V}{1k} = 2.1mA$$

$$I_D = I_D - I_L = 7.9 - 2.1 = 5.8mA$$

ac model

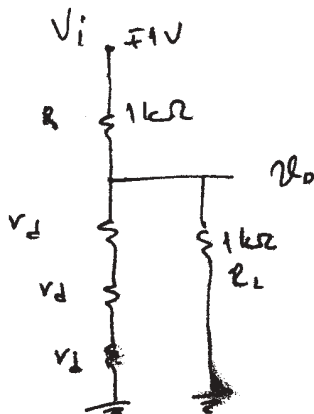

$$r_d = \frac{\eta V_T}{I_D} = \frac{2 \times 0.025V}{5.8mA} = \frac{50mV}{5.8mA} = 8.62\Omega$$

$$V_O = \frac{1000 \parallel 3 \times 8.62}{1000 + 1000 \parallel 3 \times 8.62} (1V) = \frac{25.21}{1025.21} = 0.0246V$$


$$V_O = 24.6mV$$

$$\frac{V_O}{V_i} = \frac{0.0246}{1} = 2.46\%$$

reduction: 97.54% reduction in ripple

8

Zener Diodes

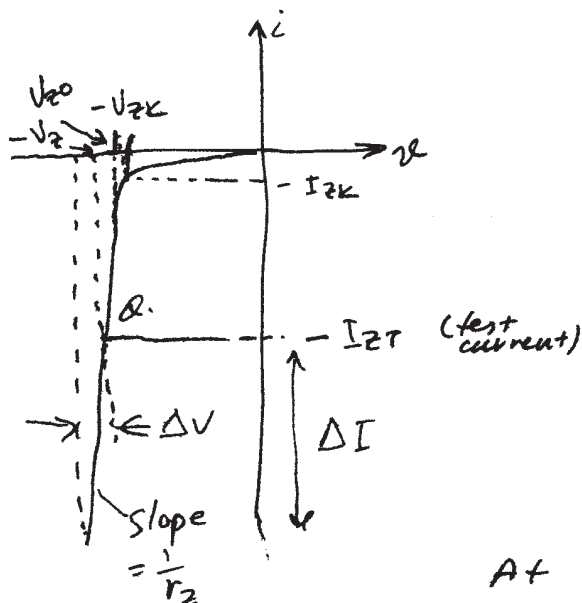


manufacturer specifies
 I_{zk} , $V_z @ I_{zT}$

Breakdown curve is almost linear below I_{zk} .

incremental resistance $\rightarrow r_z = \frac{1}{\text{slope}}$
dynamic resistance

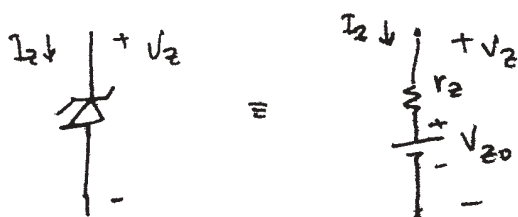
At the Q point the diode can be modeled as follows:



r_z is in Ω 's (small)
 \Rightarrow voltage source

NOT: If I_z falls below I_{zk} , this model becomes invalid!

Example

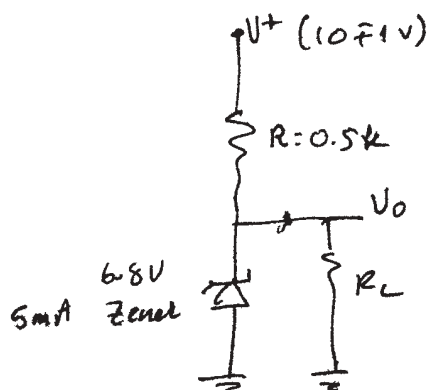


$$V_{z0} = V_z - I_{zT} r_z \\ = 6.8 - 5 \times 20 = 6.7V$$

$$V_z = 6.8V @ 5mA$$

$$r_z = 20\Omega, I_{zk} = 0.2mA$$

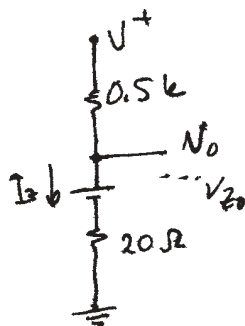a) find V_0 with $R_L \rightarrow \infty$



$$I_z = \frac{V^+ - V_z}{0.5 + 0.02} = \frac{10 - 6.8}{520}$$

$$= 6.35mA, 6.83$$

$$V_0 = 6.35 \times 20 + 6.8 = 7.97V$$

(9)

b) find $\frac{\Delta V_o}{\Delta V^+}$. $\frac{\Delta V_o}{\Delta V^+} = \frac{r_z}{R + r_z} = \frac{20}{520} = 0.0385$

$\Delta V^+ = \pm 1 \text{ V} \Rightarrow \Delta V_o = \pm 38.5 \text{ mV}$

c) When $R_L = 2 \text{ k}\Omega$, find ΔV_o .

$V_o \approx 6.8 \text{ V} \Rightarrow I_z = 6.35 - \frac{V_o}{R_L} = 6.35 - \frac{6.8}{2 \text{ k}} = (6.35 - 3.4) \text{ mA}$

change in $I_z \rightarrow \Delta I_z = 3.4 \text{ mA}$

$\Delta V_z = 3.4 \times 20 = 68 \text{ mV}$

d) Find V_o when $R_L = 0.5 \text{ k}\Omega$

expected value of V_o is 6.8 V

expected value of load current $6.8 / 0.5 = 13.6 \text{ mA}$


\Rightarrow This is not possible

initially $I_R \approx (10 - 6.8) / 0.5 \text{ k} = 6.4 \text{ mA}$

$I_R = I_L + I_z \quad I_z = I_R - I_L = 6.4 - 13.6 = -7.2 \text{ mA}$
not possible.

$\Rightarrow I_z \approx 0$ "blocking mode" (reverse bias w/o breakdown)

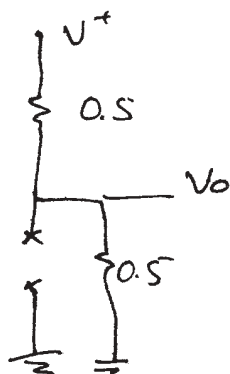\rightarrow Zener diode is almost an open circuit.



$V_o = V^+ \frac{0.5}{0.5 + 0.5} = \frac{V^+}{2} = 5 \text{ V} \pm 0.5 \text{ V}$




e) min value of $R_L = ?$ (To keep zener in breakdown)

$V_{\min}^+ = 10 - 1 = 9 \text{ V}$ $I_{R\min} = \frac{9 - 6.7}{0.5} = 4.6 \text{ mA}$

$V_z \approx V_{z0} = 6.7 \text{ V}$, $I_z = I_{zk} = 0.2 \text{ mA}$


$I_L = I_R - I_z = 4.6 - 0.2 = 4.4 \text{ mA}$, $R_L = V_o / I_L = \frac{6.7}{4.4} = 1.52 \text{ k}\Omega$

Design of Zener Shunt Regulator

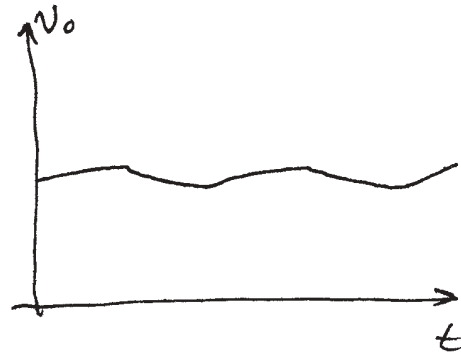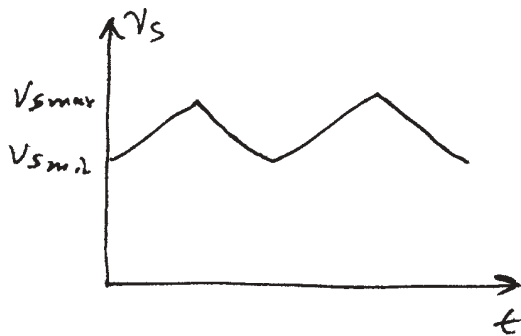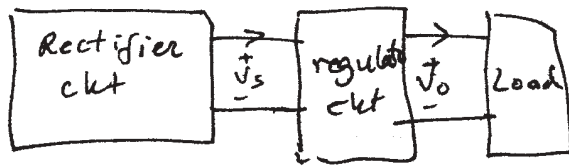

A zener diode that operates in breakdown can be used in the regulator.

Shunt Regulator

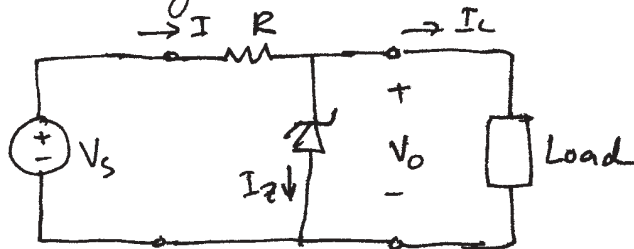


$$\text{Line regulation} = \frac{\Delta V_o}{\Delta V_s}$$

$$\frac{mV}{V}$$

$$\text{Load regulation} = \frac{\Delta V_o}{\Delta I_L}$$

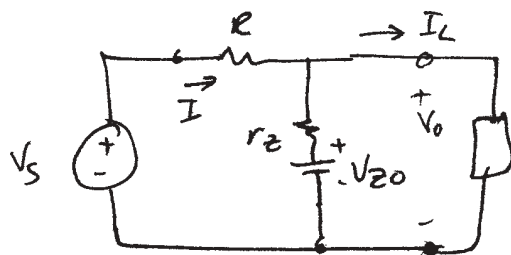Replace the zener diode with its equivalent



$$V_o = V_{z0} \frac{R}{R+r_z} + V_s \frac{r_z}{R+r_z} - I_L (R \parallel r_z)$$

$$\text{line regulation} = \frac{r_z}{R+r_z}$$

$$\text{load regulation} = - (r_z \parallel R_L)$$

$$R = \frac{V_{smin} - V_{z0} - r_z I_{zmin}}{I_{zmin} + I_{Lmax}}$$

(11)

In the design or analysis "the worst case scenario" technique is used.


For proper regulation, $I_Z \geq I_{Zmin} = I_{ZK}$ ($\sim 1 \text{ mA}$) consider V_S min, I_{Lmax}

for safety $I_{Zmax} \leq \frac{P_{Znominal}}{V_{ZK}}$ consider I_{Lmin} , V_S max

One has to consider the power dissipation in the series resistor R.

in the Most of the practical cases $R_2 \approx 0$.



Rectifier Circuits

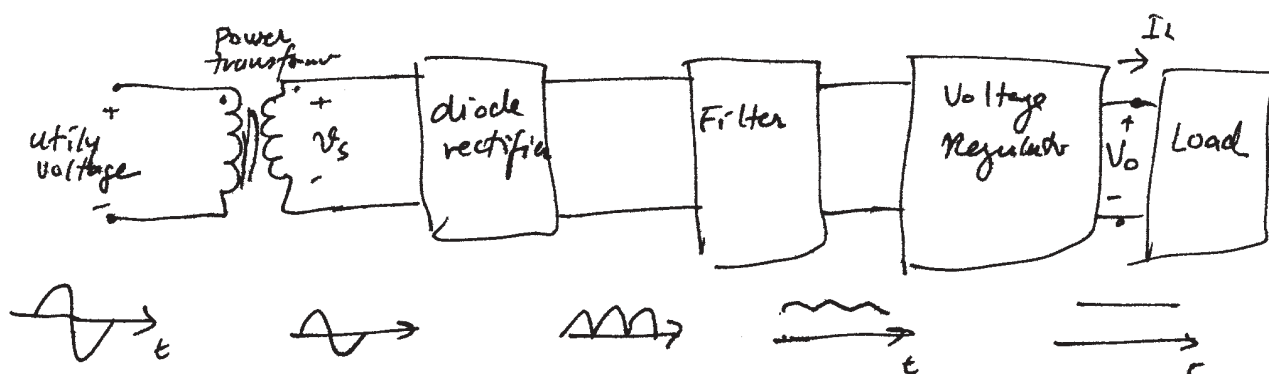

This is a block diagram of a dc power supply.





Power transformer \rightarrow steps down the voltage
 \rightarrow provides isolation

Diode rectifier Half-wave / Full wave

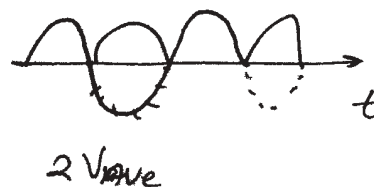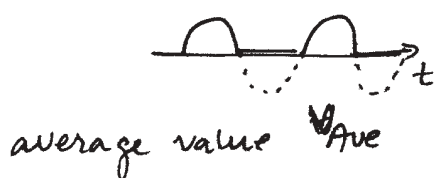

Half-wave rectifier

(12)

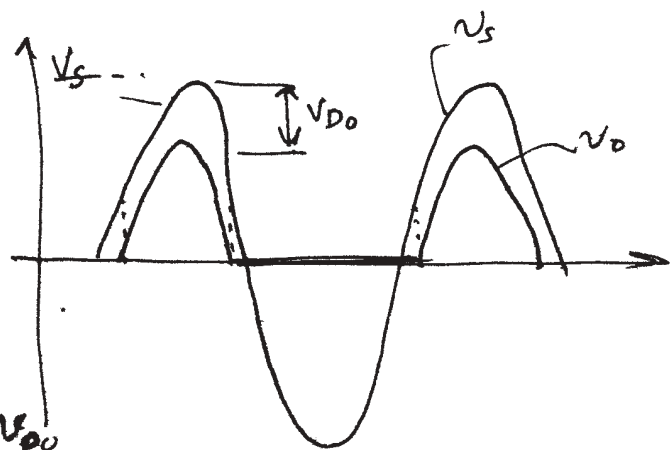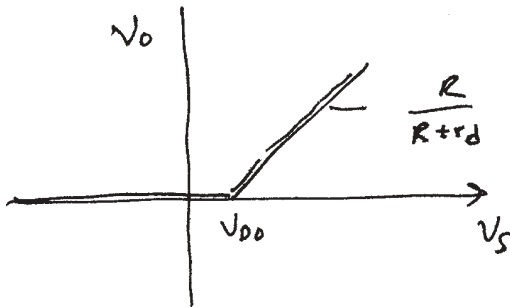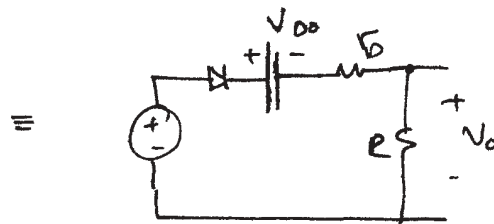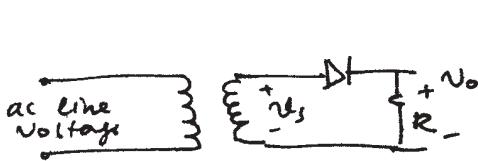

$$v_o \approx v_s - V_{D0} \text{ when } v_s > V_{D0}$$

in practice silicon diodes are used $\rightarrow V_{D0} \approx 0.7 \text{ V } 0.8 \text{ V}$

Peak inverse voltage PIV : max reverse biased voltage on the diode \rightarrow here $PIV = V_s$

Choose a diode such that $V_{ZK} \geq 1.5 V_s$

$$\text{Peak of } v_o \approx V_s - V_{D0}$$

$$\begin{aligned} \text{average of } v_o &= \frac{1}{T} \int_0^T v_o(t) dt \approx \frac{1}{T} \int_0^{T/2} V_m \sin \omega t dt \\ &= \frac{V_m}{\pi} \end{aligned}$$




$$V_o = \frac{V_s}{\pi} - \frac{V_{D0}}{2}$$

can be found from a more detailed analysis.

13

Full-wave rectifier

w/ center tapped transformer

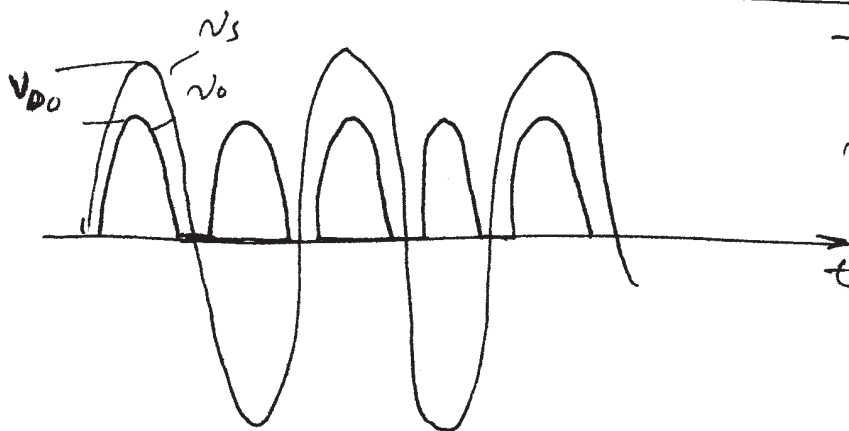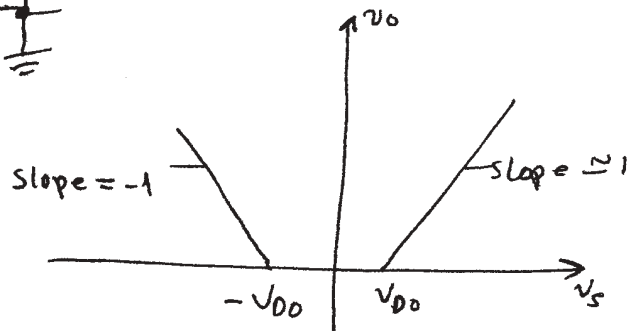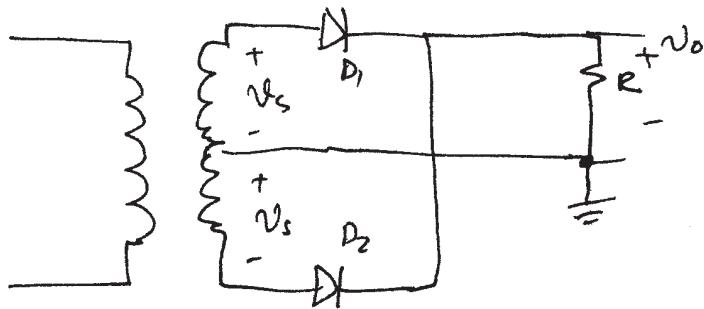

$v_s < 0 \rightarrow D_2 \text{ conducts}$
 $v_s > 0 \rightarrow D_1 \text{ conducts}$



$$PIV = 2V_s - V_{D0}$$

average

output =



$$V_{\text{oltage}} = \frac{2V_s}{\pi} - V_{D0}$$

Bridge Rectifier

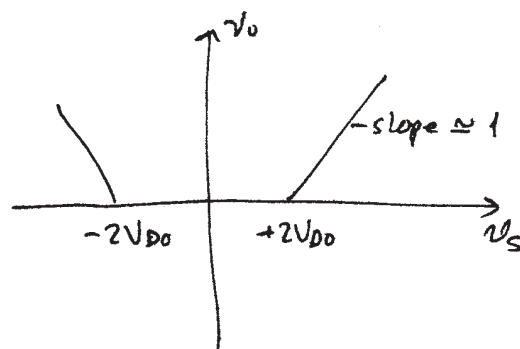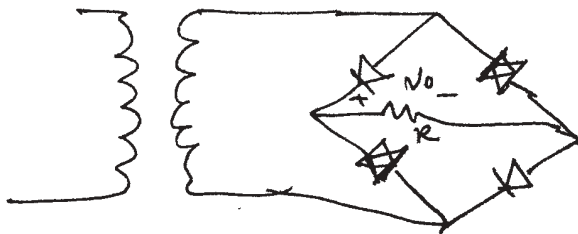

$$V_o \cong \frac{2V_s}{\pi} - 2V_{D0}$$

Peak rectifier ← ideal diode

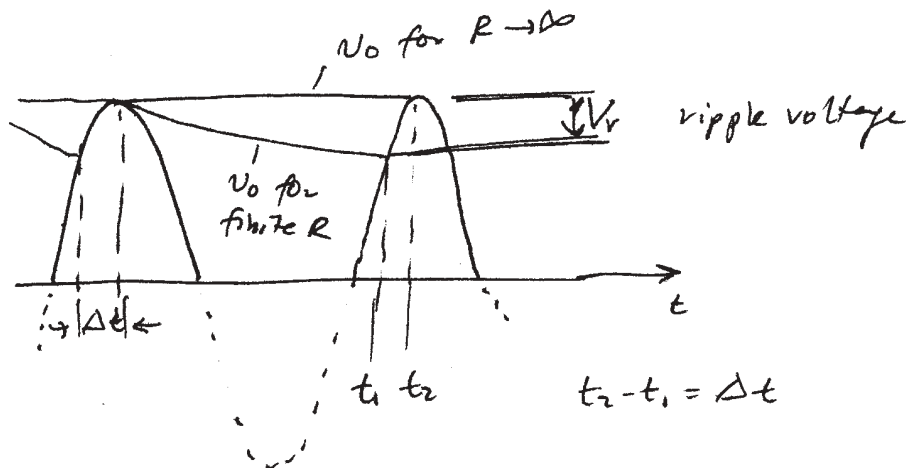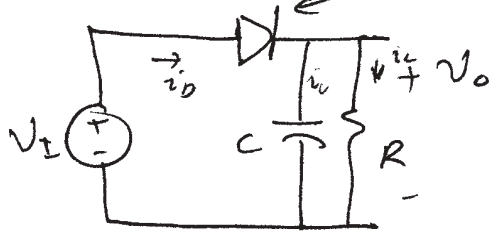

Diode conducts from t_1 to t_2 . → Capacitor is charged.
after t_2 , the capacitor discharges.

$$i_D = i_C + i_L$$

$$= C \frac{dV_1}{dt} + i_L$$

during the discharge $i_D = 0$

$$i_L = -C \frac{dV_1}{dt} \approx \text{constant}$$

$$\Delta t \ll T \Rightarrow i_L = -C \frac{\Delta V_1}{\Delta t} = -C \frac{V_r}{T} \Rightarrow |V_r| = \frac{T i_L}{C}$$

$$i_L \approx \frac{V_o}{R} \Rightarrow |V_r| \approx \frac{T V_o}{RC} = \frac{1}{f} \frac{V_o}{RC}$$

$$\Rightarrow V_o = V_p - \frac{1}{2} V_r$$

↑
peak voltage.

Example: input 50 Hz, 24 V rms
 $R = 10k\Omega$
 Find C so that $V_r = 2V$

Peak voltage $24\sqrt{2} = 33.94V$


$$C = \frac{1}{f} \frac{V_p}{V_r R} = \frac{1}{50} \frac{33.94}{2 \times 10^4 \times 10^{-3}} = 0.3394 \times 10^{-4} F = 33.94 \mu F.$$

Full wave rectifier \rightarrow charging + discharging freq $\rightarrow 2f$

$$V_r = \frac{V_p}{2fCR} \quad \text{has lower ripple.}$$


Read sections: Limiting and Clamping ccts.

DC restorer / clamped capacitor:

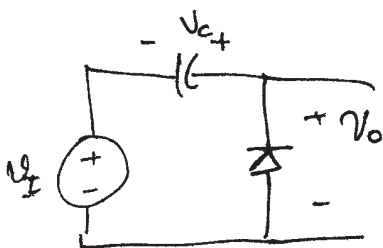

$$V_o = V_I + \max(V_I)$$

Voltage doubler:

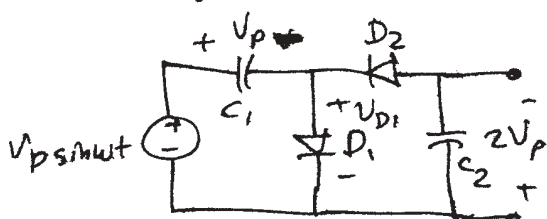

Also read

Physical Operation of
 Diodes — Basic
 Semiconductor Concepts

HW Problems:

3.32, 3.37, 3.45, 3.55