
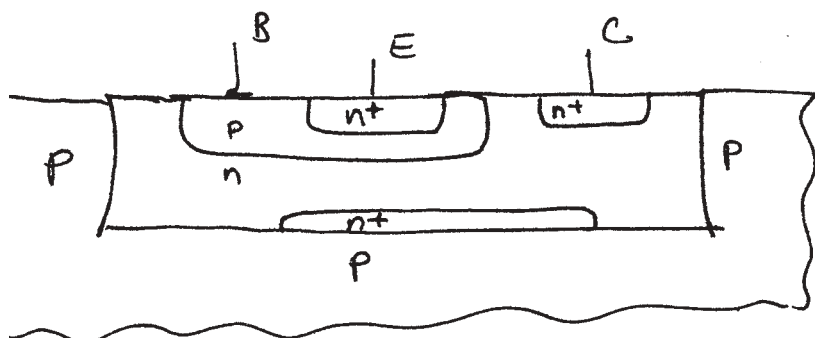


CHAPTER 4 — BIPOLAR JUNCTION TRANSISTORS

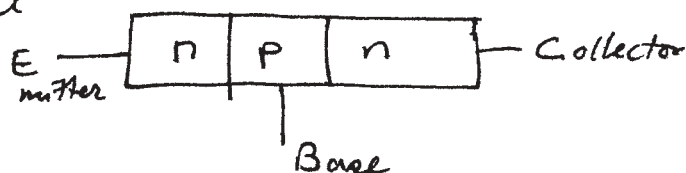Physical Structure NPN planar double diffused transistor



Text book model



Base region is very thin — the width is less than the diffusion length of minority carriers.


Transistor action: BE junction is fwd biased

- ⇒ injection of holes into the emitter (from base)
- " " electrons into the base (from the emitter)

BC junction is reverse biased

- ⇒ high electric field in the depletion region.

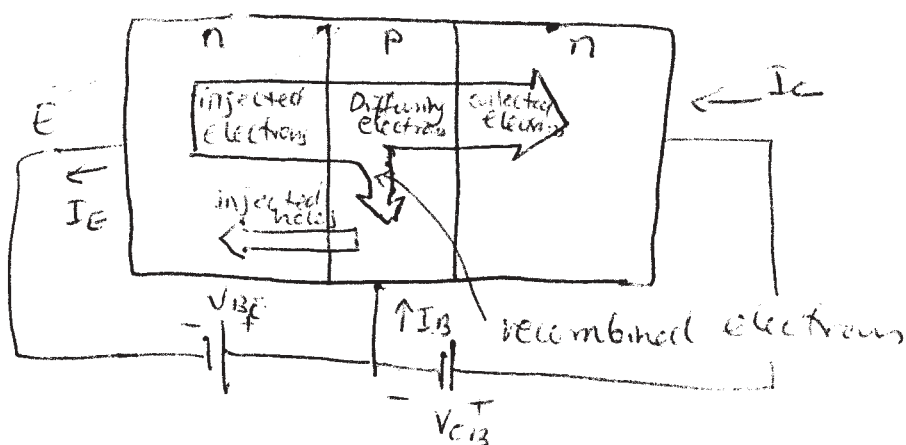Thin base → carriers injected into the base move to the collector side in no time → carriers get collected by the collector.



(2)

The collector current:

$$i_C = I_S e^{V_{BE}/V_T}$$

I_S : current scale factor

Base current: $i_B = \frac{i_C}{\beta} = \frac{I_S}{\beta} e^{V_{BE}/V_T}$ β = common emitter current gain

Emitter current $i_E = i_C + i_B$ 100 - 200 even higher

$$= i_C + \frac{i_C}{\beta} = i_C \left(1 + \frac{1}{\beta}\right) = i_C \frac{(\beta+1)}{\beta}$$

$$i_C = \alpha i_E = \frac{\beta}{\beta+1} i_E$$





$$\alpha = \frac{\beta}{\beta+1} = \text{Common base current gain}$$

$$i_E = \left(\frac{I_S}{\alpha}\right) e^{V_{BE}/V_T}$$


Practical purposes $i_C \approx i_E$
ignore base current

if $\beta \gg 100 \Rightarrow$

Equivalent circuit models:

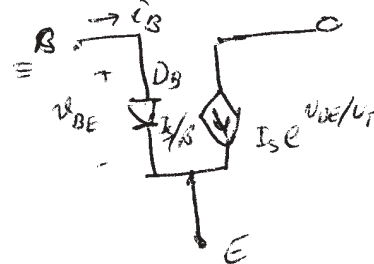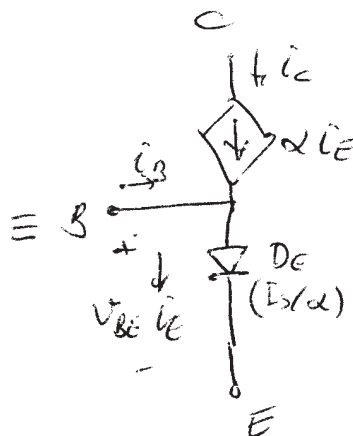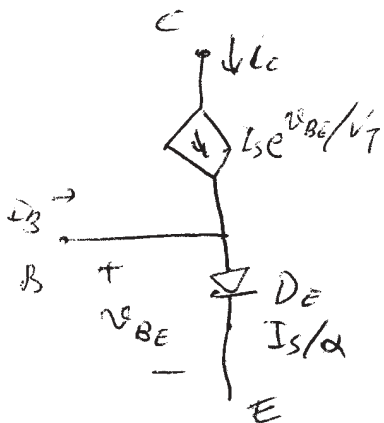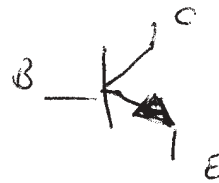

Common emitter



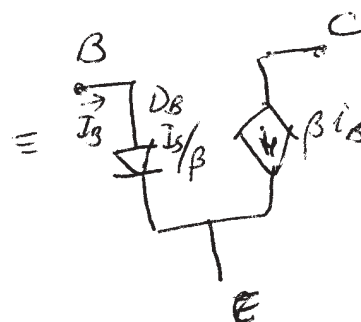


ideality factor ≈ 1



There is also I_{CBO} leakage current

3

PNP Transistor

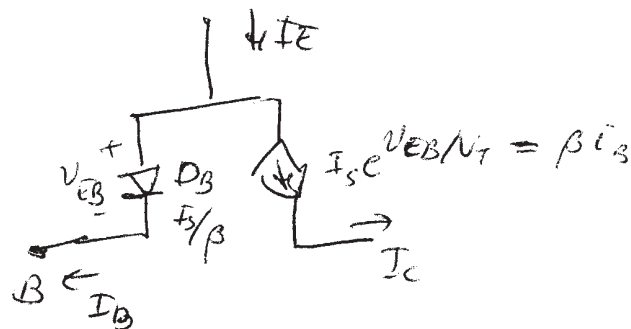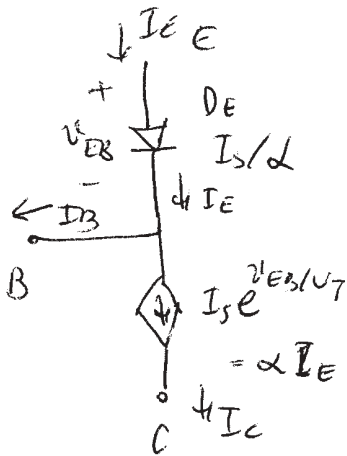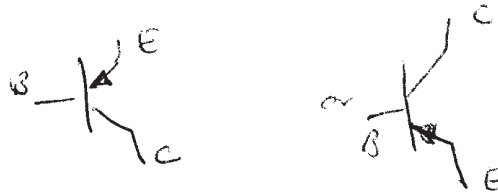

CONVENTIONS

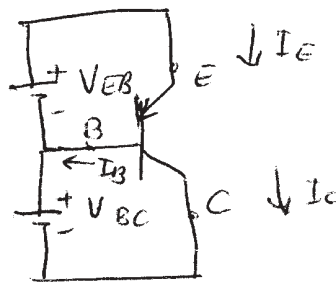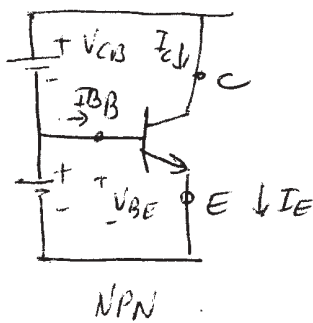

Practical:
approaches
 $|V_{BE}| \approx 0.7V$
for silicon
transistors.


(DESIGN EXAMPLE)

$$V_{BE} = 0.7 \text{ @ } I_C = 1 \text{ mA}$$

find R_C and R_E to have $I_C = 2 \text{ mA}$

$$\beta = 100$$

$$V_C = 5V$$

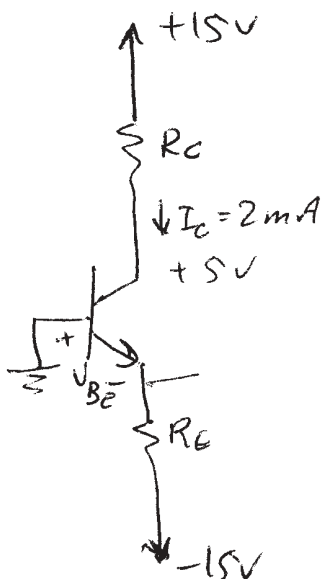

$$V_{BE} = V_T \ln \frac{I}{I_S} = V_T (\ln I - \ln I_S)$$

$$I_2 = 2 I_1 \Rightarrow$$

$$V_{BE} = V_T (\ln 2 I_1 - \ln I_S)$$

$$= V_T \ln 2 + V_T (\ln I_1 - \ln I_S)$$

$$= 0.025V \times 0.7V$$

$$= 0.717V$$

$$I_E = I_C + I_B = I_C + \frac{I_C}{100} = 2 + 0.02 \text{ mA} = 2.02 \text{ mA}$$

4


$$R_C = \frac{15-5}{2} = 5k\Omega, \quad R_E = \frac{-0.717 - (-15)}{2.02} = 7.07k\Omega$$

Q.D.H quick + Dirty analysis

$$I_C \approx I_E, \quad V_{BE} = 0.7V \Rightarrow$$

$$R_C = \frac{15-5}{2} = 5k\Omega, \quad R_E = \frac{-0.7 - (-15)}{2} = \frac{14.3}{2} = \underline{\underline{7.15k\Omega}}$$

example:

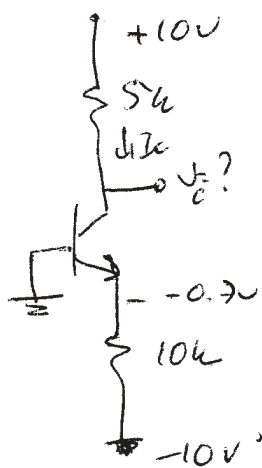

$$\begin{aligned} I_B &=? \\ I_E &=? \\ I_C &=? \\ V_{CE} &=? \\ V_{BE} &= 0.7V \\ \beta_F &= 50 \end{aligned}$$

$$I_E = \frac{-0.7 - (-10)}{10k} = 0.93mA$$


$$I_B = \frac{I_E}{\beta_F + 1} = \frac{0.93}{51} mA$$

$$I_C = \beta_F I_B = \frac{50}{51} \times 0.93 mA$$

$$V_C = 10 - I_C \times 5k = \quad V$$

$$V_{CE} = V_C - V_E = -(-0.7) = V$$

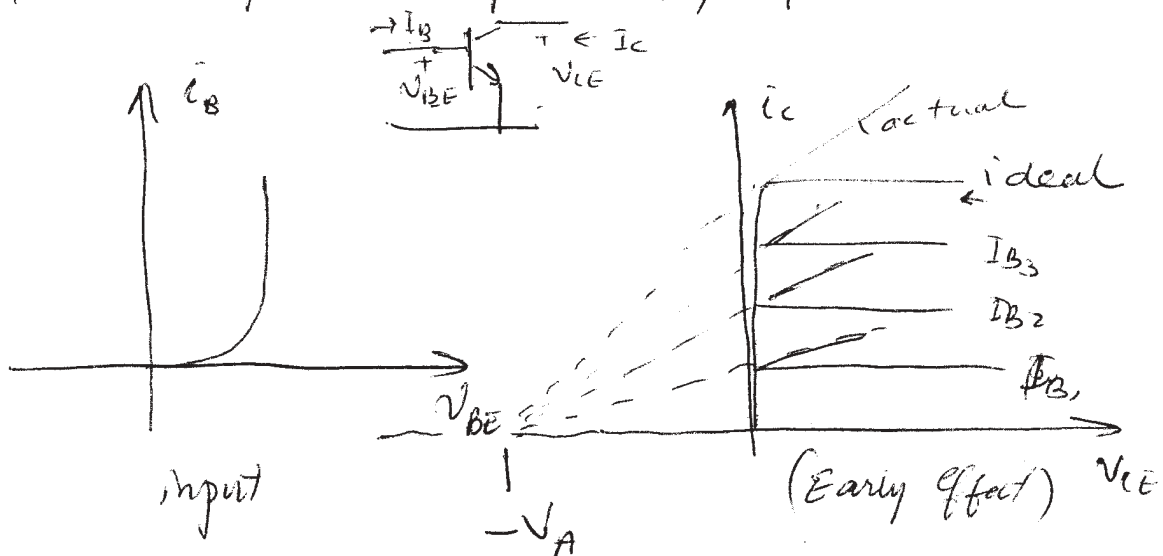4.5 Graphical Representation of IV relationship



$$I_C = I_S e^{V_{BE}/V_T} \left(1 + \frac{V_{CE}}{V_A}\right) \text{ include the Early effect}$$

(5)

Back to the modes of operation

(FWD) active mode

$$V_{BE} \approx 0.7V$$

β_F, α_F

$$V_{CE} > 0.2V$$

Saturation mode

$$\left. \begin{array}{l} V_{BE} \approx 0.7V \\ V_{BC} \approx 0.7V \end{array} \right\} V_{CE} \approx 0$$

if a $V_{CE} < 0$ is calculated for an NPN,
 $\Rightarrow$ saturation mode.


Cut off $V_{BE} < 0.5V$ (practical purposes)

Remove the transistor and measure ^{the voltage that would be} V_{BE} .


Reverse active (collector + emitter interchanged)

$$V_{BC} > 0, V_{BE} < 0 \rightarrow \beta_R, \alpha_R$$

Example w/ PNP

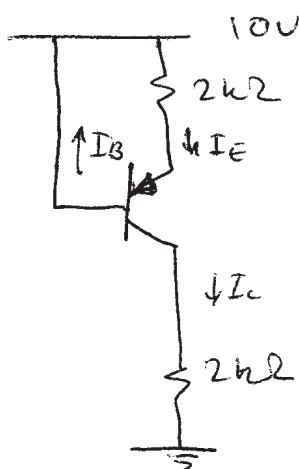

① remove the transistor

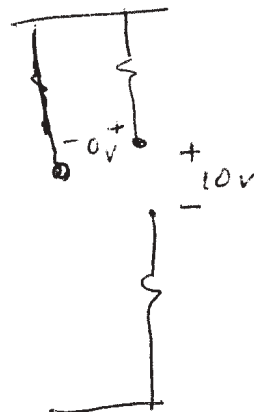


cut-off.

$$I_B \approx 0$$

$$I_C \approx 0$$

$$I_E \approx 0$$

6

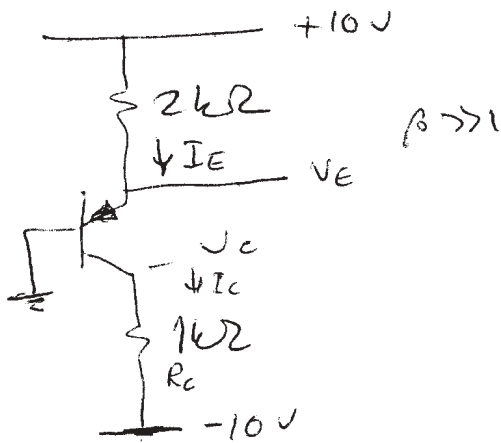

$$V_E = V_B + V_{BE} = 0 + 0.7 = 0.7 \text{ V}$$

$$I_E = \frac{10 - 0.7}{2} = \frac{9.3}{2} = 4.65 \text{ mA}$$



$$I_C \approx I_E = 4.65 \text{ mA}$$

$$V_C = I_C R_C + (-10) = 4.65 - 10 = -5.35 \text{ V}$$


Study examples 4.1, 4.2, 4.3, 4.4

4.5, 4.6, 4.7, 4.8

Graphical Determination of Currents

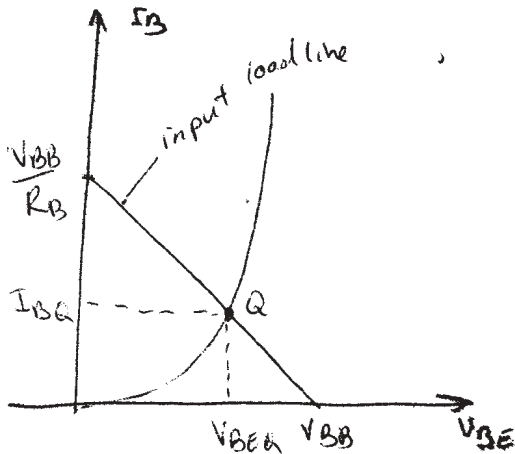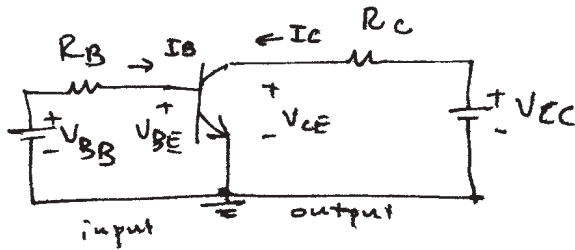


$$I_B = \frac{V_{BB} - V_{BE}}{R_B}$$

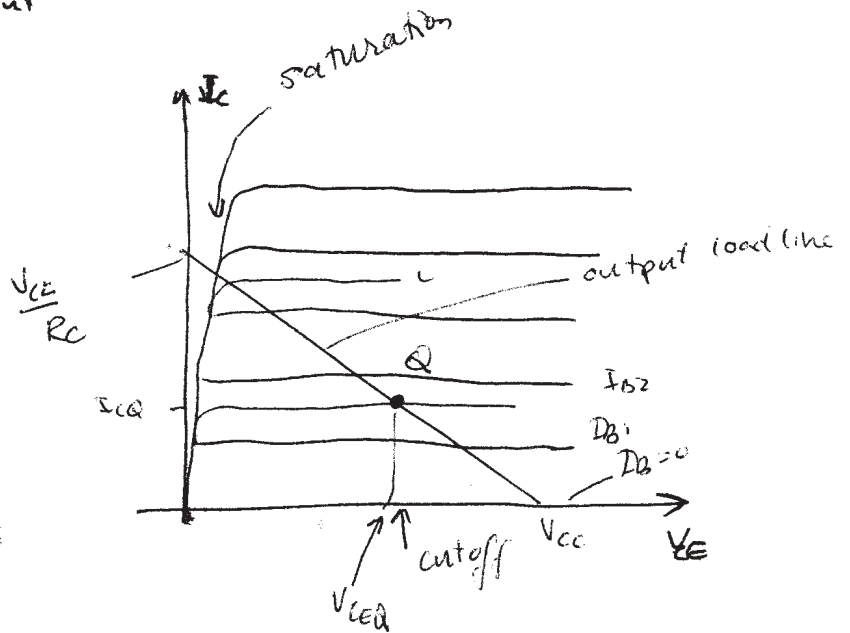

$$I_C = \beta I_B$$

$$V_{CE} = V_{CC} - I_C R_C$$

Example

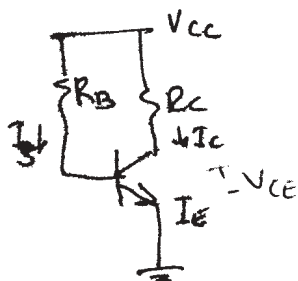


$$I_C = \beta I_B$$

$$I_E = (\beta + 1) I_B$$

$$I_B = (V_{CC} - V_{BE}) / R_B$$

$$V_{CE} = V_{CC} - I_C R_C$$

Example

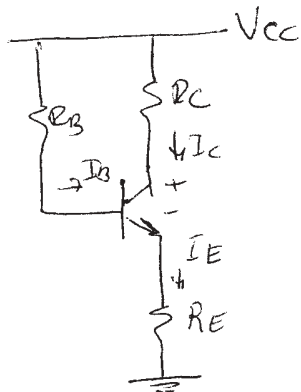

Two voltage equations can be written

$$I_E R_E + V_{BE} + I_B R_B = V_{CC}$$



$$I_E = (\beta_F + 1) I_B$$

$$(\beta_F + 1) R_E I_B + I_B R_B = V_{CC} - V_{BE}$$

$$I_B = \frac{V_{CC} - V_{BE}}{(\beta_F + 1) R_E + R_B}$$

$$I_C = \beta_F I_B, \quad V_{CE} = V_{CC} - I_C R_C - I_E R_E$$

Example:

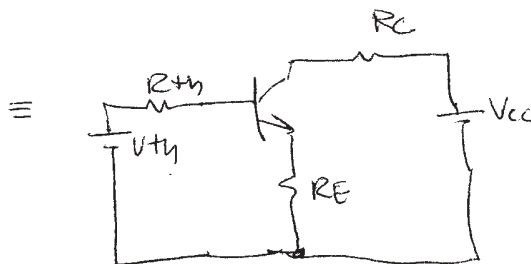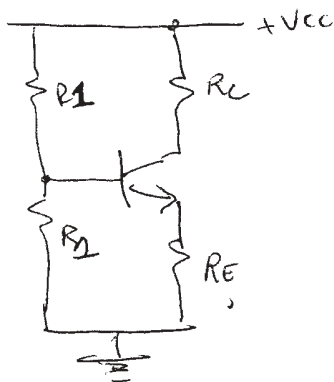

$$V_{TH} = V_{CC} \frac{R_2}{R_1 + R_2}$$


$$R_{TH} = R_1 || R_2$$

$$I_B = \frac{V_{TH} - V_{BE}}{R_{TH} + (\beta_F + 1) R_E}$$

$$I_C = \beta_F I_B$$

$$V_{CE} = V_{CC} - I_C R_C - I_E R_E$$

Example:

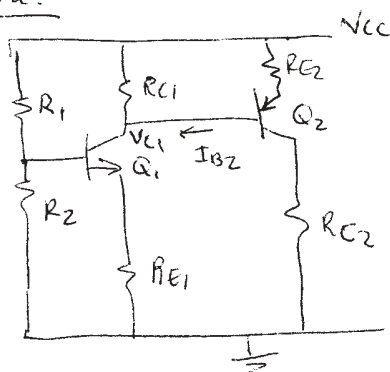


- ① ignore the effect of I_{B2}
- ② calculate V_{C1}
- ③ Determine I_{E2}
- ④ find I_{B2}
- ⑤ recalculate V_{C1}

see example 4.8

(8)


The Transistor as an amplifier

Consider the following ckt.

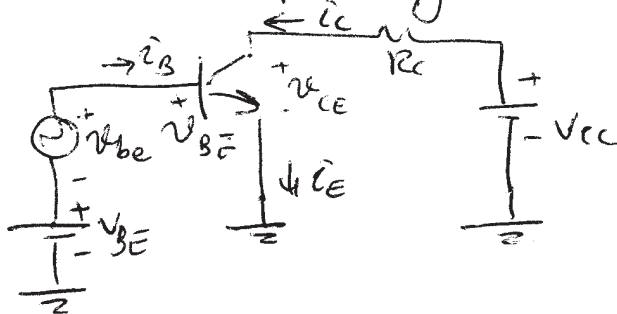

$|v_{be}| \ll |V_{BE}|$
"small signal"

The DC equivalent

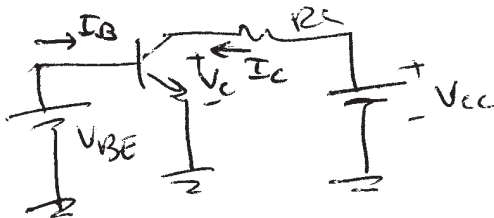

$$I_C = I_S e^{V_{BE}/V_T}$$

$$I_E = I_C / \alpha$$

$$I_B = I_C / \beta$$

$$V_C = V_{CE} = V_{CC} - I_C R_C$$

$$V_{CE} > V_{CESAT}$$

$V_{BE} > 0 \rightarrow$ (active mode)

Signal is applied $\rightarrow V_{BE} = v_{be} + V_{BE}$

collector current

$\uparrow$ signal $\uparrow$ bias

$$\begin{aligned} i_C &= I_S e^{V_{BE}/V_T} = I_S e^{(V_{BE} + v_{be})/V_T} \\ &= I_C e^{v_{be}/V_T} \end{aligned}$$

$\uparrow$ bias $\uparrow$ signal

$$e^x = 1 + x + \frac{x^2}{2!} + \frac{x^3}{3!} + \dots$$

if $x \ll 1 \Rightarrow e^x \simeq 1 + x$

$$|v_{be}| \ll V_T$$

$$e^{v_{be}/V_T} = 1 + \frac{v_{be}}{V_T}$$

$$i_C = I_C + I_C \frac{v_{be}}{V_T} = I_C + i_c$$

eq.


(9)

$$\frac{i_c}{\uparrow \text{signal}} = \frac{I_c}{V_T} \frac{v_{be}}{\uparrow \text{signal}} \equiv g_m v_{be}$$


$$\equiv g_m v_{be}$$

g_m - transconductance

$$g_m = \frac{I_c}{V_T}$$

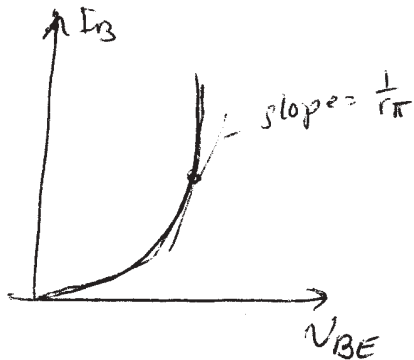

$$I_c = \beta I_B$$

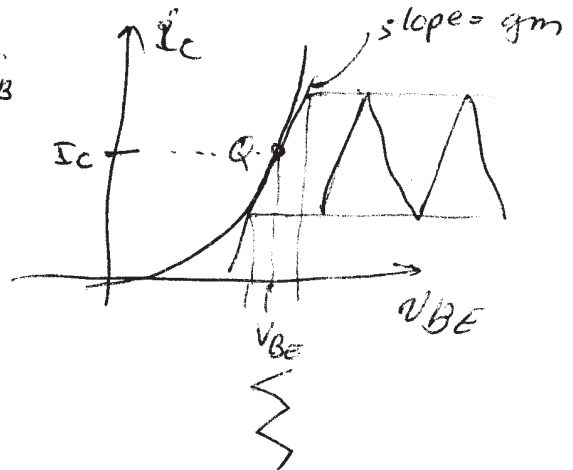

$$g_m = \left. \frac{\partial i_c}{\partial v_{BE}} \right|_Q$$


Base current

$$i_B = \frac{i_c}{\beta} = \frac{I_c}{\beta} + \frac{1}{\beta} \frac{I_c}{V_T} v_{be}$$

$$i_B = I_B + i_b \Rightarrow i_b = \frac{g_m}{\beta} v_{be} = \frac{1}{r_{\pi}} v_{be}$$

$$r_{\pi} = \frac{\beta}{g_m}$$

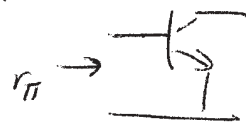small signal input resistance looking into the base.



Emitter current

$$i_E = \frac{i_c}{\alpha} = \frac{I_c}{\alpha} + \frac{i_c}{\alpha}$$

$\uparrow$ bias $\uparrow$ signal

$$i_e = \frac{i_c}{\alpha} = \frac{I_c}{\alpha V_T} v_{be} = \frac{I_E}{V_T} v_{be}$$

$$i_e = \frac{1}{r_e} v_{be}$$

Small signal resistance between base and emitter looking into the emitter.

$$r_e = \frac{V_T}{I_E}$$



$$r_e = \frac{\alpha}{g_m} \cong \frac{1}{g_m}$$

$$v_{be} = i_b r_{\pi} = i_e r_e$$

$$r_{\pi} = \frac{i_e}{i_b} r_e = (\beta + 1) r_e$$

$$g_m = \frac{I_c}{V_T}, \quad r_{\pi} = \frac{\beta}{g_m}, \quad r_e = \frac{1}{g_m}$$

Voltage gain:

$$v_c = V_{cc} - i_c R_c$$

$$= V_{cc} - (I_c + i_e) R_c$$

$$= (V_{cc} - R_c I_c) - i_e R_c$$

$$= V_c - i_e R_c = V_c + v_c$$

$\uparrow$ bias $\uparrow$ signal

where



$$v_c = -i_c R_c = -g_m v_{be} R_c$$

$$v_c = (-g_m R_c) v_{be}$$

Voltage gain (small signal, from the base to the collector)

$$\equiv \frac{v_c}{v_{be}} = -g_m R_c$$

Small Signal Equivalent Ckt models

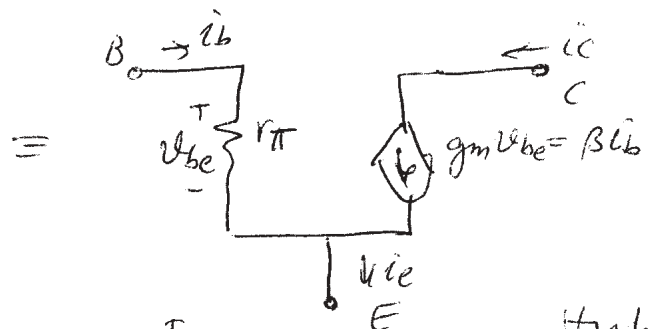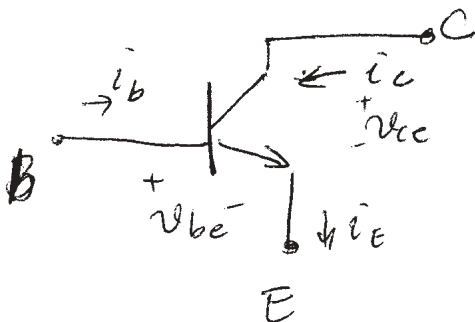


$$g_m = \frac{I_c}{V_T}$$

$$r_{\pi} = \frac{\beta}{g_m}$$

Hybrid
 π
model

(11)


T model

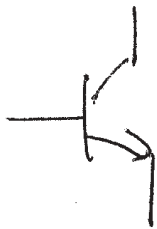

or



≡

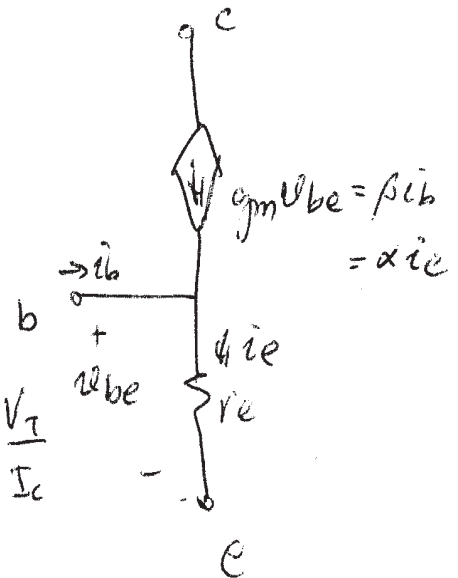


$$g_m = \frac{I_c}{V_T}$$

$$r_e = \frac{V_T}{I_E} = \frac{\alpha}{g_m} \approx \frac{1}{g_m} = \frac{V_T}{I_c}$$

$$v_{be} = (i_b + \beta i_b) r_e = (1 + \beta) i_b r_e = r_{\pi} i_b$$

$$\Rightarrow r_{\pi} = (1 + \beta) r_e$$

Example:

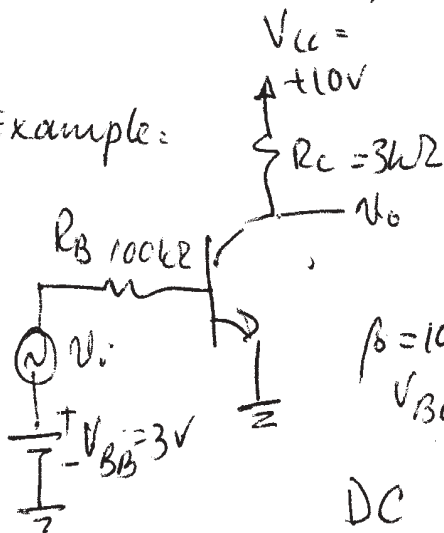

$$\beta = 100$$

$$V_{BE} = 0.7V$$

DC analysis

find $\frac{v_o}{v_i}$


AC Analysis

Transistor Biasing

- Why do we need biasing?
 I_c , V_{ce}



- Biasing from ~~two~~ sources
- Biasing from single source
- Feedback biasing
- Voltage Divider biasing
- Current source biasing
- Design for bias chgs.

example:

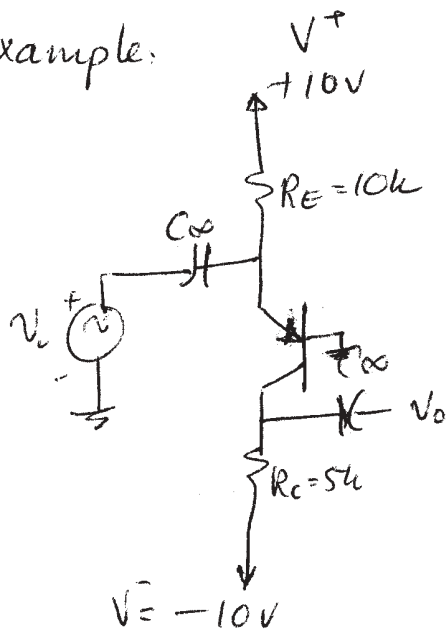


improving for the early voltage

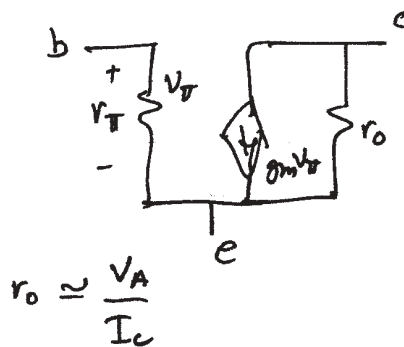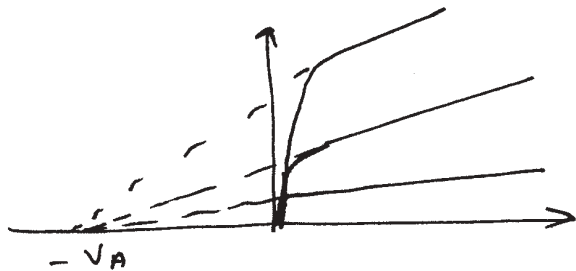the Early voltage
To take into account, a resistor is added
to the small signal models



$$r_o \approx \frac{V_A}{I_C}$$


Basic Single Stage BJT Amplifier

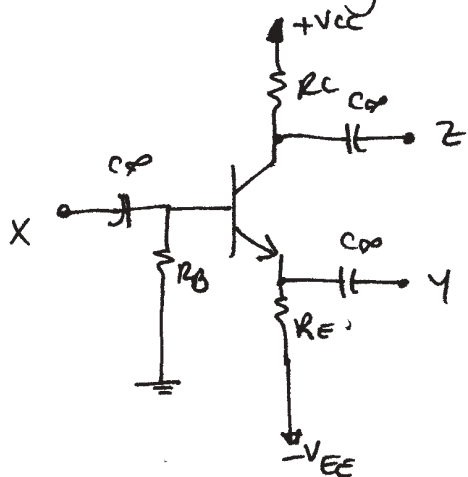

universal amplifier.


		input	output
Common Emitter	Y → ground	X	Z
Common Base	X → ground	Y	Z
Common Collector	Z → ground	X	Y

Mid frequency range

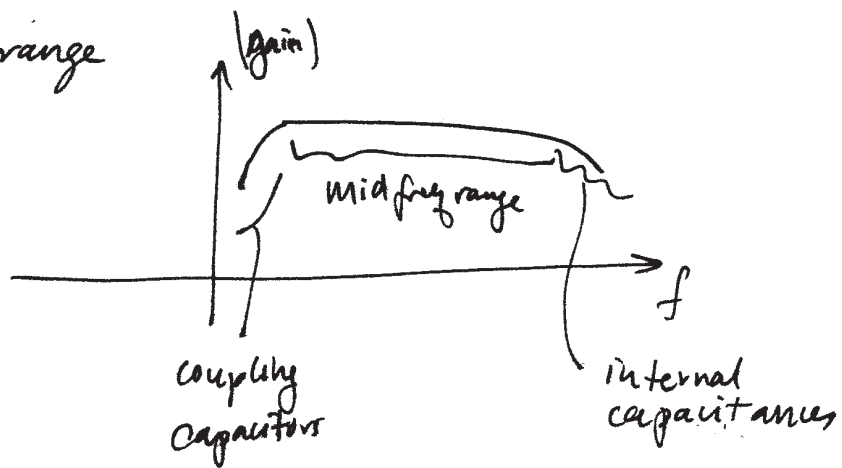


(15)

Common Emitter Amplifier

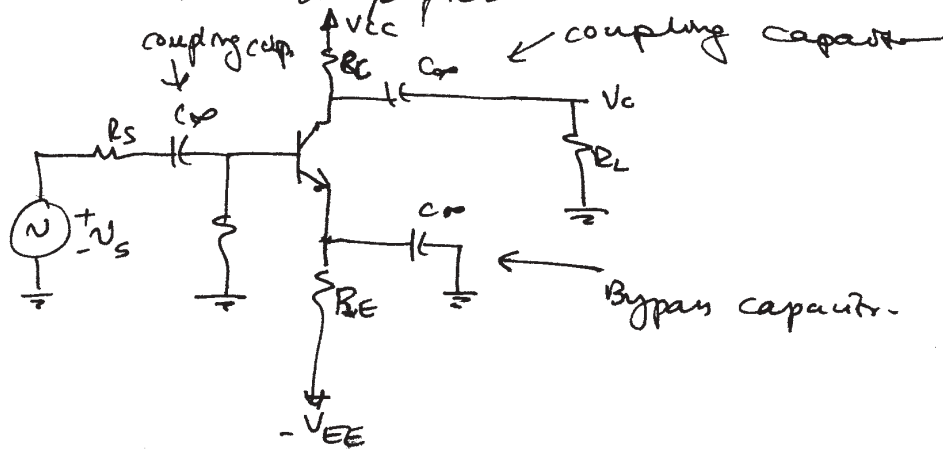

Small signal equivalent:

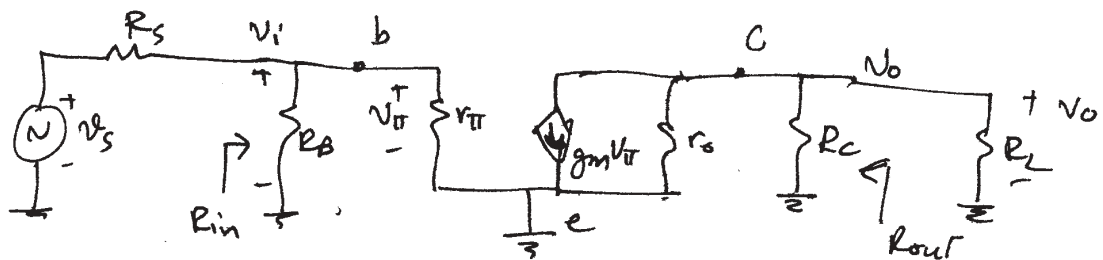

$$R_{in} = R_B || r_{\pi}$$

$$R_{out} = R_C || r_o$$

$$V_o = -(r_o || R_C || R_L) g_m V_i$$

$$V_i = V_{\pi}$$

$$\frac{V_o}{V_i} = -g_m (R_C || R_L || r_o)$$

$$\frac{V_o}{V_s} = A_v$$

#4

Homework: 4.10
4.20
4.30
4.40
4.50

#5

Homework: 4.60
4.70
4.75
4.80
4.90