


(1)

(5)

5. Field Effect Transistors

- Unipolar device - only electrons or only holes carry current.
- Smaller than BJTs in size
- Most digital ccts are made of FETs
- JFET, MOSFET, MESFET

MOSFET device structure:

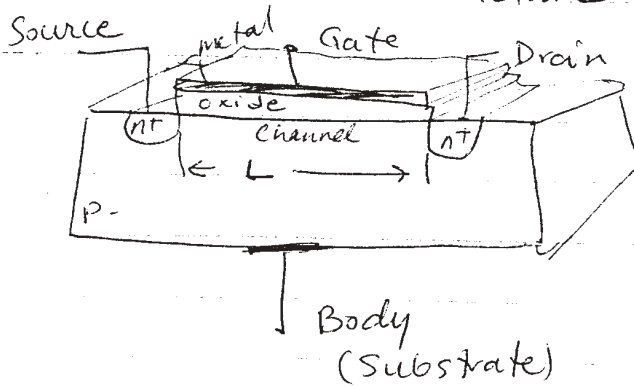


$$1 \mu\text{m} \leq L \leq 10 \mu\text{m}$$

Oxide Thickness $0.1 \mu\text{m}$
 $1000 \text{ \AA}$

IGFET Insulated gate
Field effect
transistor.

Operation w/ Gate open ckt

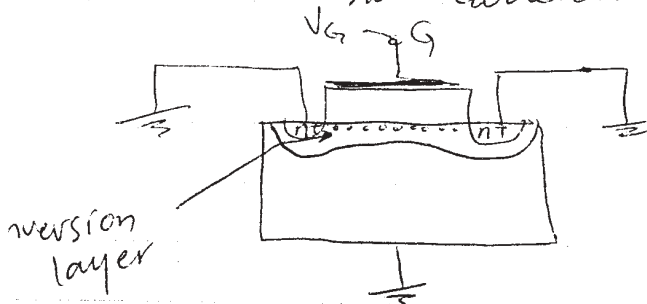→ Back to back two diode
no currents flow.



When $V_G = \text{Threshold voltage}$, a channel is formed between the two n^+ regions

V_t


Why is it called "field effect" transistor?

Threshold voltage = V_t , V_T , V_{TR}

Thermal voltage = $V_T = \frac{kT}{q}$


2

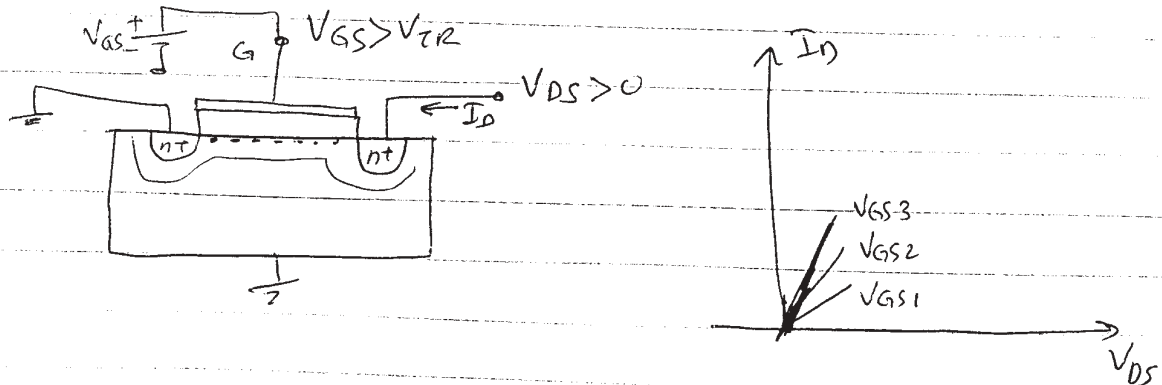Now apply a voltage to the drain terminal



for small V_{DS} , I_D is proportional to the gate excess voltage $(V_{GS} - V_t) V_D$

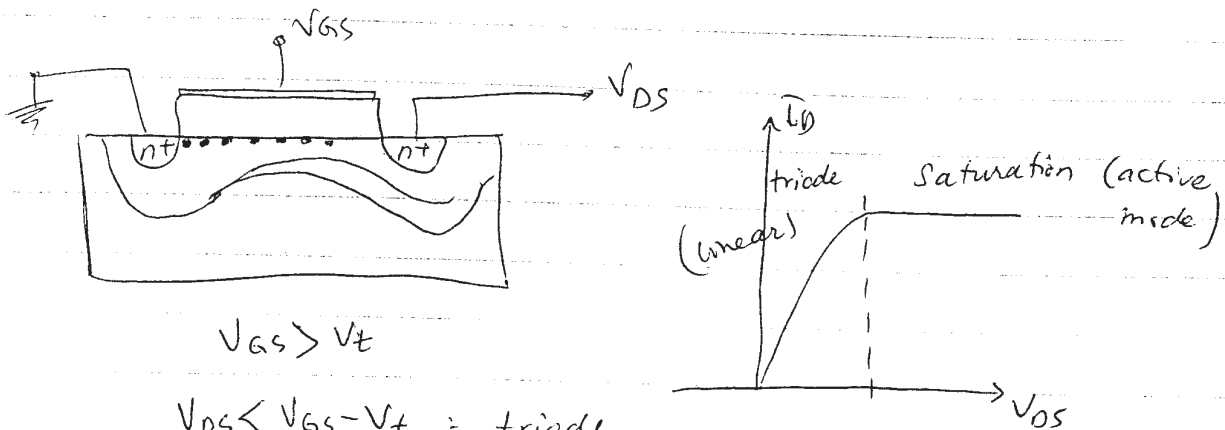
For larger V_{DS} , the voltage along the channel varies, and electron density varies too.




$V_{DS} < V_{GS} - V_t$: triode

$V_{DS} > V_{GS} - V_t$: saturation

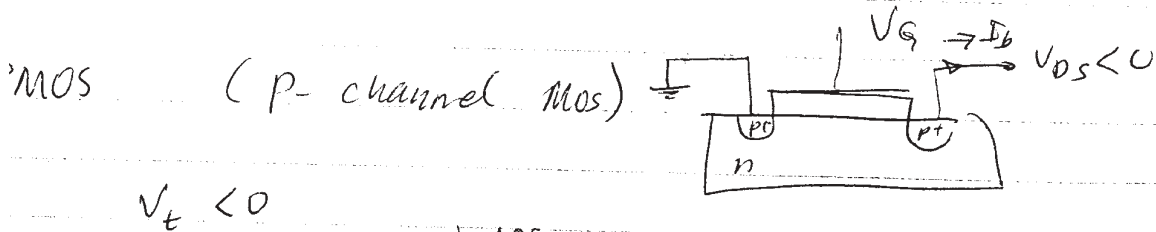channel is pinched off at saturation $\rightarrow$ constant current.



CMOS


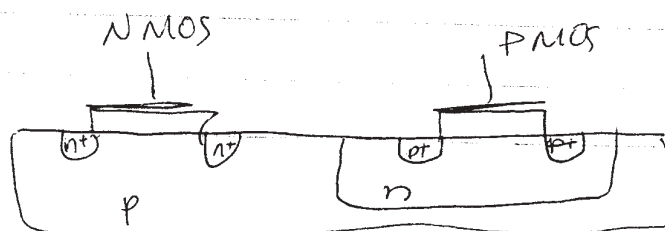


(3)


Current Voltage Characteristics of MOSFET

n-channel $V_t > 0 \Rightarrow$ enhancement mode
 $V_t < 0 \Rightarrow$ depletion mode

enhancement mode

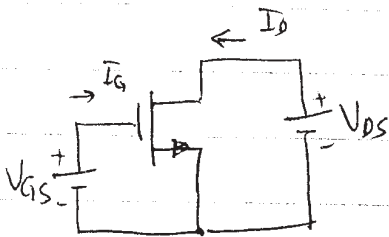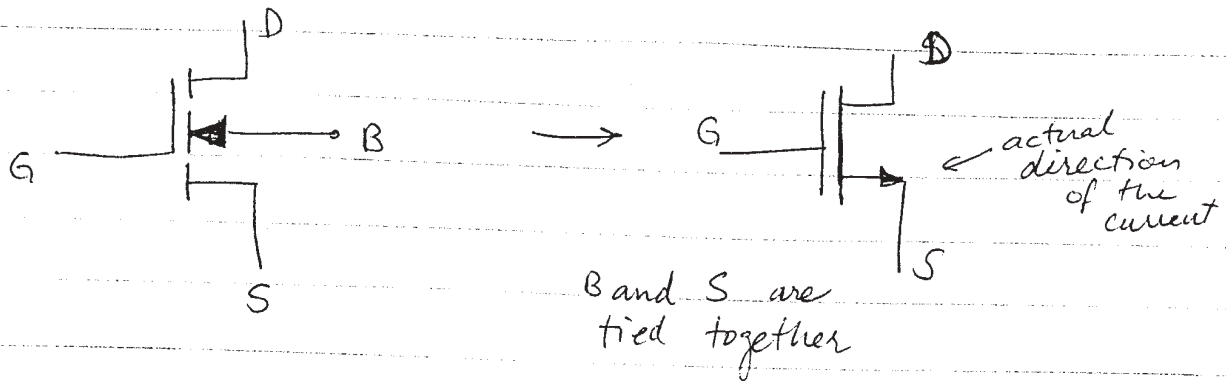

$I_G = 0$

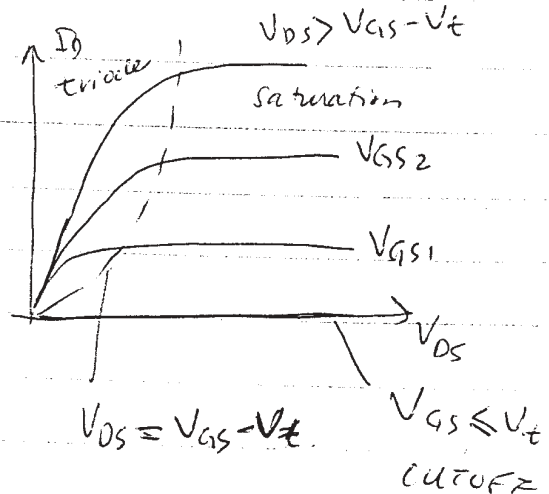

Three modes of Operation:

CUTOFF $\rightarrow V_{GS} \leq V_t \rightarrow I_D = 0$

Triode Mode (linear mode): $V_{GS} > V_t$
 $V_{DS} < V_{GS} - V_t$

$$I_D = K [2(V_{GS} - V_t) V_{DS} - V_{DS}^2] \quad \text{for small } V_{DS}$$

$$I_D \approx 2K(V_{GS} - V_t) V_{DS}$$

SATURATION MODE $V_{GS} > V_t$, $V_{DS} > V_{GS} - V_t$

$$I_D = K (V_{GS} - V_t)^2$$

(4)

K: Conductance parameter - related to the physical properties of the device


$$K = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L} \right)$$

μ_n : electron mobility C_{ox} : oxide capacitance $\frac{W}{L}$: aspect ratio


$$C_{ox} = \frac{\epsilon_{ox}}{t_{ox}}$$

$$\frac{W}{L} : \text{aspect ratio}$$


Large
signal
eq.
for
SATURATION
MODE

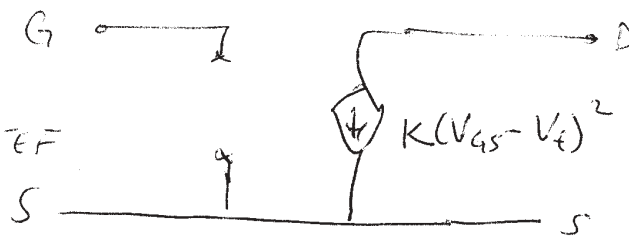

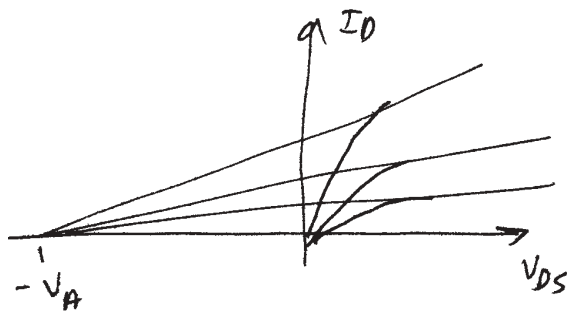Finite output resistance - channel length modulation


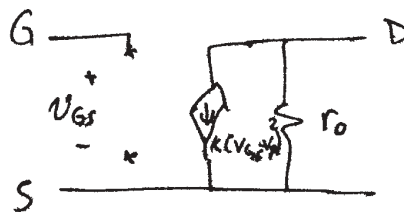
$$i_D = K(V_{GS} - V_t)^2 (1 + \lambda V_{DS})$$



$$r_o \approx \frac{1}{\lambda I_D}$$

$$\frac{1}{\lambda} = V_A$$

$$30 < V_A < 200$$

$$\text{ideal} \rightarrow V_A \rightarrow \infty$$

P-channel MOSFET

$$V_{GS} > V_t \rightarrow \text{cutoff}$$

$$V_{GS} \leq V_t, \quad V_{DS} \geq V_{GS} - V_t \rightarrow \text{triode}$$

$$i_D = K(V_{GS} - V_t)V_{DS} - V_{DS}^2$$

$$V_{GS} \leq V_t, \quad V_{DS} \leq V_{GS} - V_t \rightarrow \text{saturation}$$

$$i_D = K(V_{GS} - V_t)^2 (1 + \lambda V_{DS})$$

(5)

Both K and V_t are temperature dependent
 $|V_t|$ decreases $2\text{mV}/^\circ\text{C}$ with temperature
 K decreases w/ Temp.


Overall effect I_D decreases as $T \uparrow$.

Depletion mode device (n-channel)

$V_t > 0 \Rightarrow$ no channel when $V_{GS} = 0$

Enhancement mode

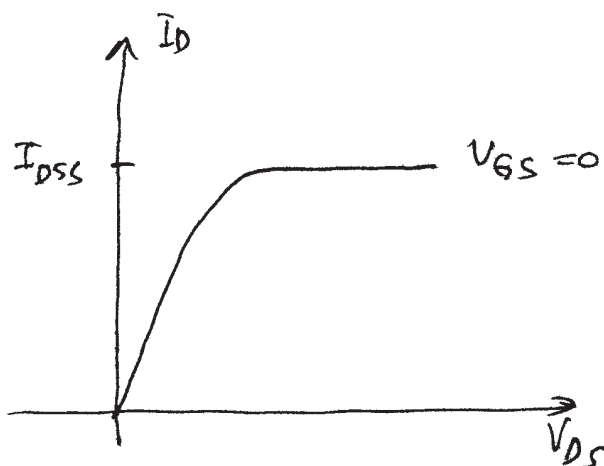
$V_t < 0 \Rightarrow$ there is a channel when $V_{GS} = 0$
 $\Rightarrow$ depletion mode.



$$I_{DSS} = I_D \Big|_{V_{GS}=0} = K (V_{GS} - V_t)^2 \Big|_{V_{GS}=0} = K V_t^2$$



P-channel : $V_t < 0$ enhancement
 $V_t > 0$ depletion mode

Transconductance curves (saturation)

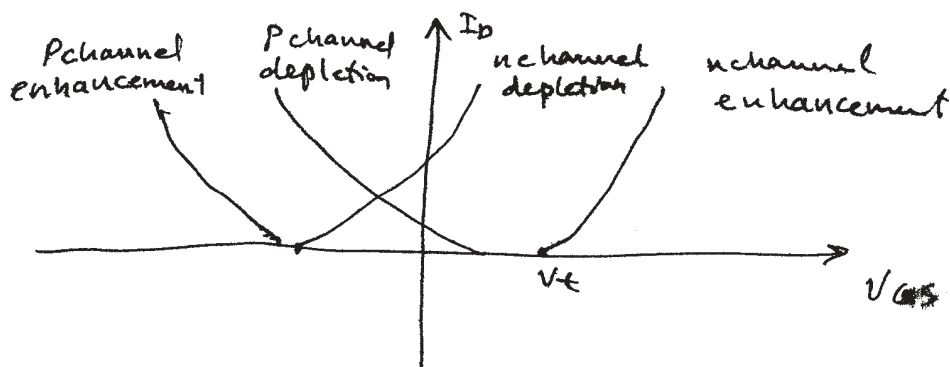


(6)

1 JFET

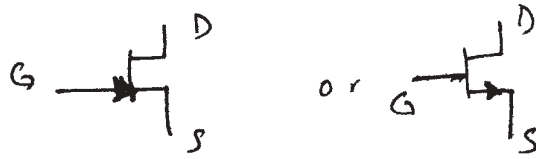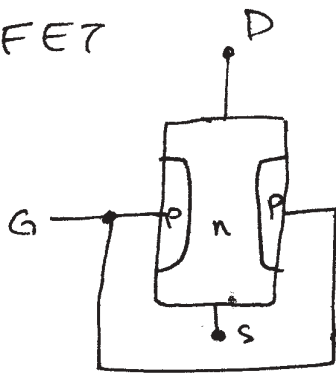

n channel

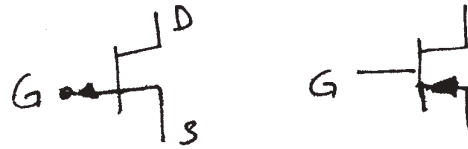


p-channel


Operation:

- 1 a channel exists between Drain and Source.
if a voltage is applied to the drain, current flows.

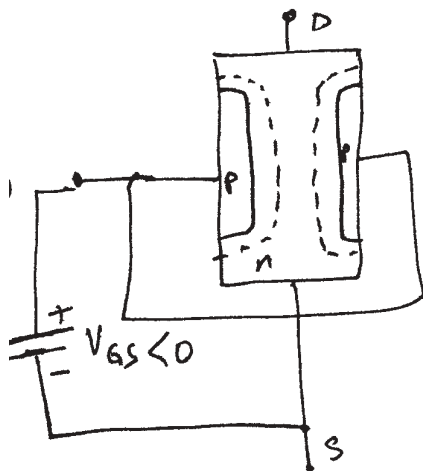A reverse voltage between G and S would increase the depletion region — channel resistance increases $\rightarrow$ less current



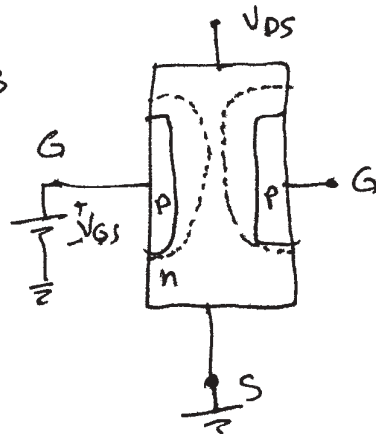Larger $V_{DS} \rightarrow$ voltage gradient along the channel
nonuniform (gradual) depletion width $\rightarrow$ nonuniform channel cross section



when $V_{DS} = 0$,
 $V_{GS} = V_p$ would deplete the entire channel $\rightarrow$ ~~no~~

when $V_{DS} \geq V_{GS} - V_p$
~~entire channel was~~

the channel is pinched off at the drain end.

(7)

Modes of operation:

$$V_{GS} < V_p \rightarrow \text{cutoff } I_D = 0$$

$$V_{GS} \geq V_p \quad + \quad V_{DS} < V_{GS} - V_p \quad \text{Triode mode}$$

$$i_D = K [2(V_{GS} - V_p) V_{DS} - V_{DS}^2]$$

$$V_{GS} > V_p \quad + \quad V_{DS} > V_{GS} - V_p \quad \text{constant current mode}$$

$$i_D = K (V_{GS} - V_p)^2$$

$V_p \rightarrow$ ~~the~~ same as V_t for a MOSFET


$$K = ?$$

$$V_{GS} = 0 \Rightarrow i_D = K V_p^2 = I_{DSS}$$

$$\Rightarrow \boxed{K = \frac{I_{DSS}}{V_p^2}}$$

$$\boxed{V_t = V_p}$$

EXAMPLES

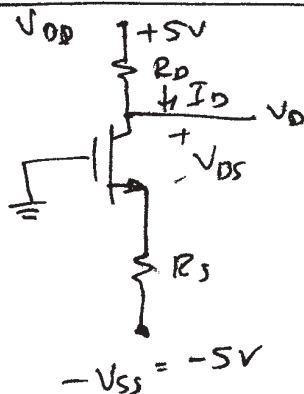

Determine R_D and R_S
so that $I_D = 0.4 \text{ mA}$
 $V_D = 1.0 \text{ V}$

$$V_t = 2 \text{ V}$$

$$\mu_n C_{ox} = \frac{20 \mu\text{A}}{\text{V}^2}, \quad L = 10 \mu\text{m}, \quad W = 400 \mu\text{m}$$

$$\lambda = 0$$

$$K = \frac{\mu_n C_{ox}}{2} \left(\frac{W}{L} \right) = \frac{20}{2} \times \frac{400}{10} = \frac{800}{2} \mu\text{A/V} = 0.4 \text{ mA/V}$$


$$\text{Constant current mode} \rightarrow I_D = K (V_{GS} - V_t)^2$$

(8)

$$0.4 \text{ mA} = 0.4 (V_{GS} - V_t)^2$$

$$\Rightarrow V_{GS} - V_t = 1$$
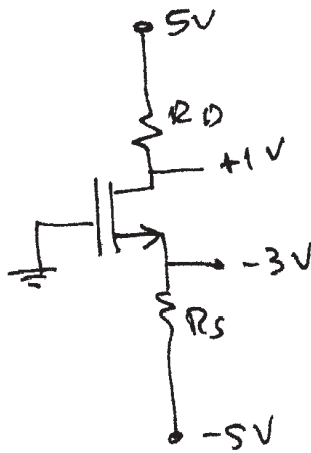
$$V_{GS} = V_t + 1 = 2 + 1 = 3 \text{ V.}$$



$$V_G = 0, \quad V_S = V_G - V_{GS} = 0 - 3 = -3 \text{ V}$$


$$R_S I_D = -3 - (-5) = 2 \text{ V}$$

$$R_S = \frac{2 \text{ V}}{0.4 \text{ mA}} = 5 \text{ k}\Omega$$

$$I_D R_D = 5 - 1 = 4 \text{ V}$$

$$R_D = \frac{4 \text{ V}}{0.4 \text{ mA}} = 10 \text{ k}\Omega$$

— 0 —

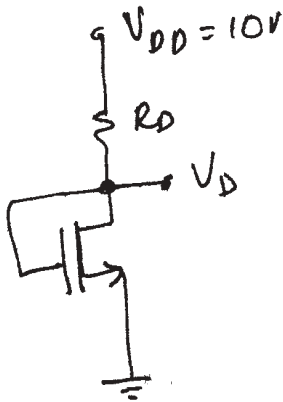Find R_D so that $I_D = 0.4 \text{ mA}$

$$\left. \begin{array}{l} \mu_n C_{ox} = 20 \text{ mA/V}^2 \\ W = 100 \text{ }\mu\text{m} \\ L = 10 \text{ }\mu\text{m} \end{array} \right\}$$

$$K = \frac{1}{2} 20 \times \frac{100}{10} = 0.1 \text{ mA/V}^2$$

$$V_t = 2 \text{ V}$$

$$V_{DS} = V_{GS}$$

$$V_t > 0 \Rightarrow V_{DS} > V_{GS} - V_t$$

 $\Rightarrow$ Constant current mode $V_{DS} > V_{tr}$

$$0.4 = 0.1 (V_{GS} - V_t)^2 \Rightarrow (V_{GS} - V_t)^2 = 4$$


$$V_{GS} - V_t = 2$$

$$V_{GS} = V_t + 2 = 4 \text{ V.}$$

$$V_D = 4 \text{ V}, \quad R_D = \frac{10 - 4}{0.4} = \frac{6}{0.4} = 15 \text{ k}\Omega$$

9

Example

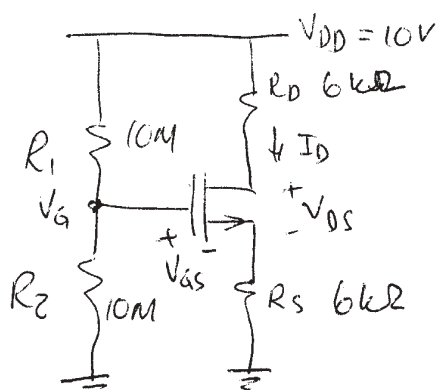

$$\lambda = 0$$

$$K = 0.5 \text{ mA/V}^2$$

$$V_T = 1 \text{ V}$$

find I_D and V_{DS}

Assume constant current mode


$$I_D = K (V_{GS} - V_T)^2$$

$$V_{DS} \geq V_{GS} - V_{TR}$$

$$V_G = 5 \text{ V}$$

$$V_G = I_D R_S + V_{GS} \Rightarrow V_{GS} = V_G - I_D R_S$$
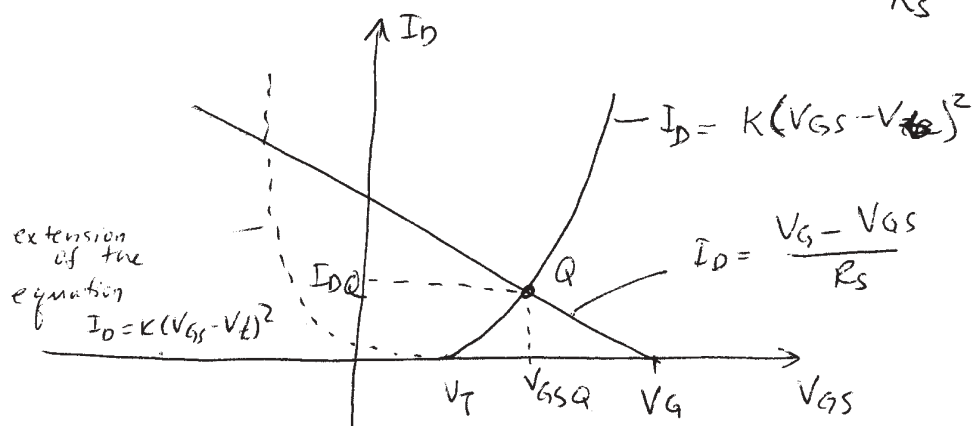
$$\Rightarrow I_D = \frac{V_G - V_{GS}}{R_S}$$



Analytical solution of these equations would yield two V_{GS} values — only one is valid.

$$\left. \begin{aligned} I_D &= \frac{V_G - V_{GS}}{R_S} \\ I_D &= K (V_{GS} - V_T)^2 \end{aligned} \right\} \begin{aligned} V_G - V_{GS} &= K R_S (V_{GS}^2 - 2 V_{GS} V_{TR} + V_{TR}^2) \\ 0 &= K R_S V_{GS}^2 + (1 - 2 V_{TR} K R_S) V_{GS} - V_G + V_{TR} K R_S \\ 0 &= V_{GS}^2 + \left(\frac{1}{K R_S} - 2 V_{TR} \right) V_{GS} + \frac{V_{TR}^2}{K R_S} - \frac{V_G}{K R_S} \end{aligned}$$

Solve for V_{GS1} and V_{GS2}

$V_{GS} > V_T \rightarrow$ is the solution

(10)

$$V_{GS} = 5 - 6 I_D$$

$$I_D = k(V_{GS} - V_t)^2$$

$$= 0.5(5 - 6 I_D - 1)^2 \Rightarrow 18 I_D^2 - 25 I_D + 8 = 0$$

$$I_{D1} = 0.89 \text{ mA}$$

$$I_{D2} = 0.5 \text{ mA}$$

I_{D1} is not acceptable:

because $6 \times 0.89 = 5.34 \text{ V}$

$5.34 > V_G$ not possible

$$I_D = 0.5 \text{ mA} \rightarrow$$


$$V_S = 0.5 \times 6 = 3 \text{ V}$$

$$V_D = 10 - 6 \times 0.5 = 7 \text{ V}$$

$$\left. \begin{array}{l} V_S = 0.5 \times 6 = 3 \text{ V} \\ V_D = 10 - 6 \times 0.5 = 7 \text{ V} \end{array} \right\} V_{DS} = 7 - 3 = 4 \text{ V.}$$

(9)

Example

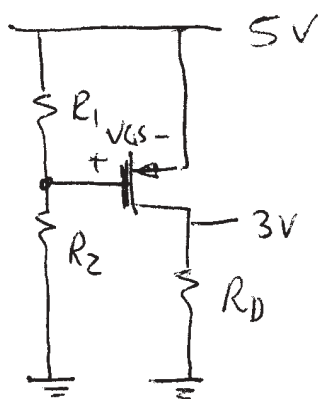Design for $I_D = 0.5 \text{ mA}$

$$V_D = +3 \text{ V}$$

$$V_t = -1 \text{ V}$$

$$K = 0.5 \text{ mA/V}^2$$

$$\lambda = 0$$

$$I_D = K(V_{GS} - V_t)^2$$

$$V_{GS} = -2 \text{ V}$$

$$V_G = 5 - 2 = 3 \text{ V}$$

$$\text{Let } R_2 = 3 \text{ M}\Omega$$

$$R_1 = 2 \text{ M}\Omega$$

$$R_D = \frac{3}{0.5} = 6 \text{ k}\Omega$$

$$0.5 = 0.5(V_{GS} + 1)^2$$

$$(V_{GS} + 1)^2 = 1$$

$$V_{GS} + 1 = 1 \quad \text{or} \quad V_{GS} + 1 = -1$$

$$V_{GS} = 0$$

$$\underline{V_{GS} = -2}$$

↑ not acceptable


$$V_{DS} = -2 \text{ V}$$

What is the largest value of R_D that would still keep the MOSFET in saturation mode?

$$V_{DS} \leq V_{GS} - V_t = -1$$

That means V_D can be as large as 4V.

$$R_{D\text{max}} = \frac{4}{0.5} = 8 \text{ k}\Omega$$

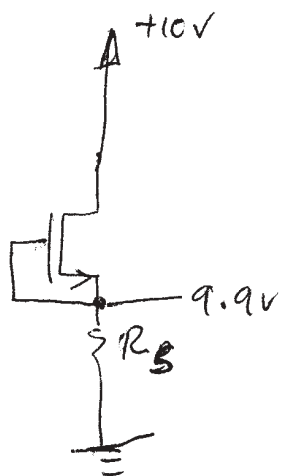Example

Design a circuit so that $V_S = 9.9V$
What would be the effective resistance between the drain and the source?

$$V_t = -1V$$

$$K = 0.5 \text{ mA/V}^2$$

$$V_{DS} = 0.1V < V_G - V_t = 0 + 1$$


$\Rightarrow$ triode mode

$$I_D = K [2(V_{GS} - V_t)V_{DS} - V_{DS}^2]$$

$$= 0.5 [2(0 + 1)0.1 - 0.01] \approx 0.1 \text{ mA}$$

$$R_S = \frac{9.9}{0.1} = 99 \text{ k}\Omega \approx 100 \text{ k}\Omega$$
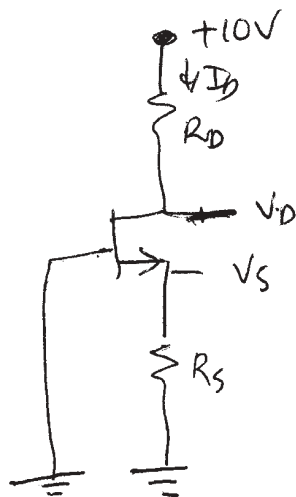
$$r_{ds} = \frac{V_{DS}}{I_D} = \frac{0.1V}{0.1 \text{ mA}} = 1 \text{ k}\Omega$$



$$I_D = 4 \text{ mA}$$

$$V_D = 6V$$

$$V_P = -4V$$

$$I_{DSS} = 16 \text{ mA}$$

$$\lambda = 0$$

$$K = \frac{I_{DSS}}{V_P^2} = \frac{16}{16} = 1 \text{ mA/V}^2$$

Determine R_S and R_D

1) Find V_{GS} to have $I_D = 4 \text{ mA}$.

$$I_D = K(V_{GS} - V_t)^2$$

$$V_{GS1} = \sqrt{\frac{I_D}{K}} + V_t = 2 - 4 = -2V$$

$$V_{GS2} = -\sqrt{\frac{I_D}{K}} + V_t = -(2 + 4) = -6V$$


$$V_{GS} = -2V, V_G = 0, V_S = 2V, V_{DS} = 6 - 2 = 4V > V_{GS} - V_t \text{ not acceptable}$$

$= -2 + 4 = 2V$

$$R_S = \frac{2}{4} = 0.5 \text{ k}\Omega$$

$$R_D = \frac{10 - 6}{4} = 1 \text{ k}\Omega$$

THE FET AS AN AMPLIFIER

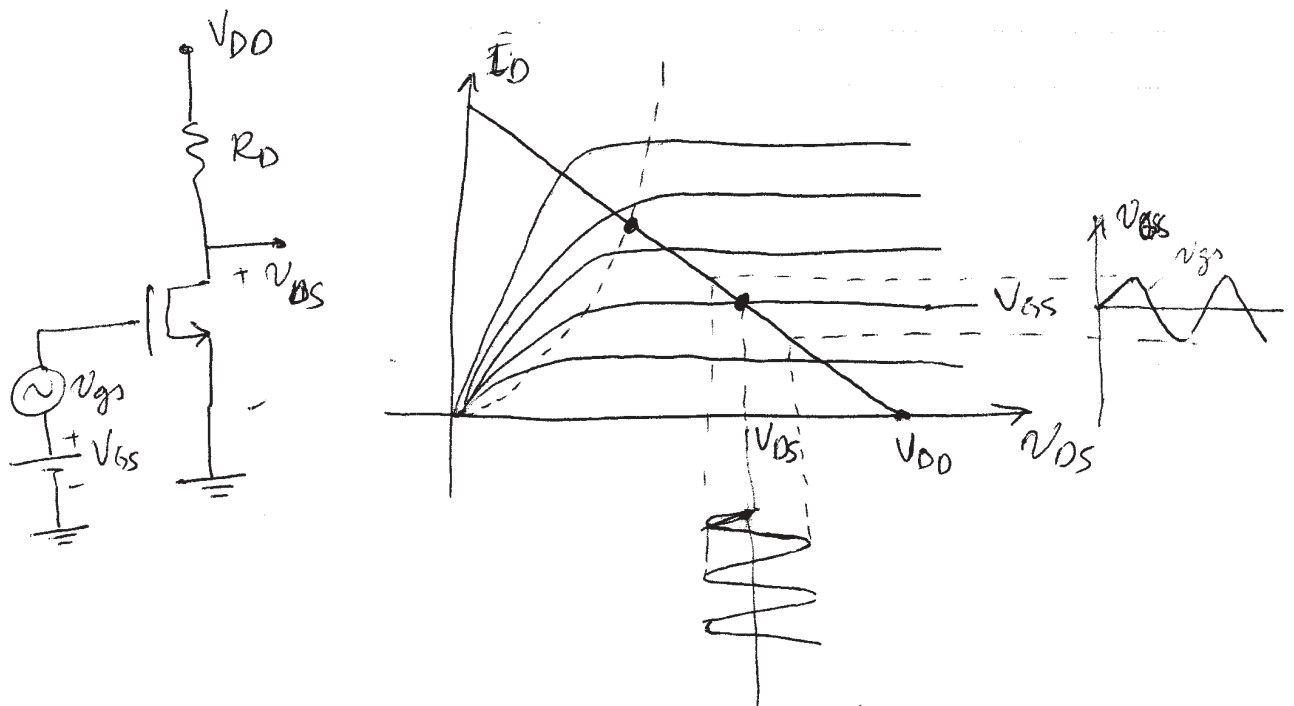

Suppose that V_{GS} and V_{DS} are large enough to keep the MOSFET in saturation mode

$$I_D = K(V_{GS} - V_t)^2$$

When $V_{GS} = 0$

$$V_{DS} = V_{DD} - I_D R_D$$

With signal,

$$v_{GS} = V_{GS} + v_{gs}$$

$$i_D = K(v_{GS} - V_t)^2 = K(V_{GS} + v_{gs} - V_t)^2$$

$$= \underbrace{K(V_{GS} - V_t)^2}_{I_D} + \underbrace{2K(V_{GS} - V_t)v_{gs}}_{i_d} + K v_{gs}^2$$

$$i_d = \underbrace{2K(V_{GS} - V_t)v_{gs}}_{\text{linear}} + \underbrace{K v_{gs}^2}_{\text{quadratic}}$$

↑
undesirable

$v_{gs} \ll 2(V_{GS} - V_t)$ then nonlinear term is negligible

(14)

$$\hat{i}_d \approx 2K(V_{GS} - V_t) v_{gs} = g_m v_{gs}$$

define transconductance : $g_m \equiv \frac{\hat{i}_d}{v_{gs}} = 2K(V_{GS} - V_t)$

$$g_m = \left. \frac{\partial \hat{i}_d}{\partial V_{GS}} \right|_{V_{GS} = V_{GS}}$$


Remember $I_D = K(V_{GS} - V_t)^2$

$$\sqrt{I_D} = \sqrt{K} (V_{GS} - V_t)$$

$$\sqrt{\frac{I_D}{K}} = (V_{GS} - V_t)$$

$$g_m = 2K(V_{GS} - V_t) = 2K\sqrt{\frac{I_D}{K}} = 2\sqrt{\frac{K^2 I_D}{K}} = 2\sqrt{K I_D}$$
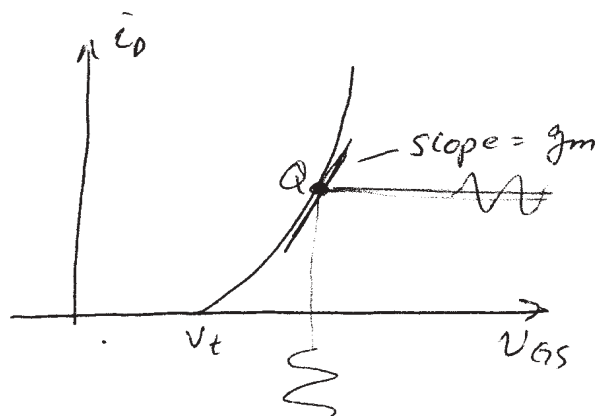
$$g_m = \sqrt{2\mu_n C_{ox}} \sqrt{\frac{W}{L}} \sqrt{I_D}$$



in the ckt, $v_D = V_{DD} - R_D i_D$

$$v_D = \underbrace{V_{DD} - R_D I_D}_{\text{bias} = V_D} - \underbrace{R_D \hat{i}_d}_{\text{signal} = v_d}$$

$$v_d = -\hat{i}_d R_D = -g_m v_{gs} R_D$$

Voltage gain $\frac{v_d}{v_{gs}} = -g_m R_D$

These expressions are valid as long as the device remains in constant current mode and the input signal small.

Small signal model for a FET (saturation mode)
(low and medium frequencies)



r_o is ignored most of the time.


$$r_o = \frac{|V_A|}{I_D}$$

$$g_m = 2\sqrt{K I_D}$$


For a JFET

$$g_m = \frac{2I_{DSS}}{|V_P|} \sqrt{\frac{I_D}{I_{DSS}}}$$

Example

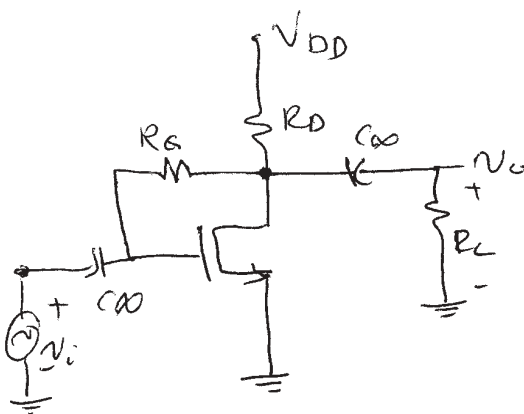

small signal eq. ckt:

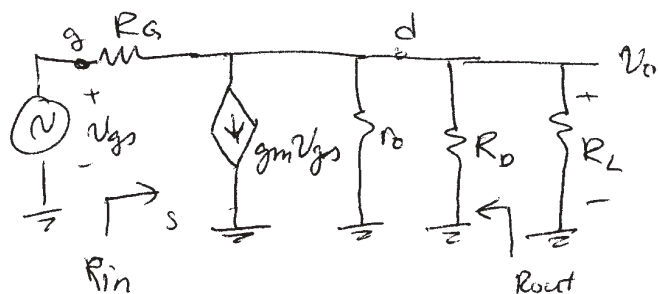

$$\left. \begin{aligned} V_t &= 1.5 \text{ V} \\ K &= 0.175 \text{ mA/V}^2 \\ V_A &= 50 \text{ V} \\ R_G &= 10 \text{ M}\Omega \\ R_D &= 10 \text{ k}\Omega \\ R_L &= 10 \text{ k}\Omega \\ V_{DD} &= 15 \text{ V} \\ \lambda &= 0 \end{aligned} \right\}$$

$$\begin{aligned} V_{GS} &= 4.4 \text{ V} = V_D \\ I_D &= 1.06 \text{ mA} \end{aligned}$$

$$g_m = 2\sqrt{K I_D} = 0.725 \text{ mA/V}$$


$$r_o = \frac{50}{1.06} = 47 \text{ k}\Omega$$

$$\begin{aligned} \frac{v_o}{v_i} &\approx -g_m (R_D \parallel r_o \parallel R_L) \\ &= -3.3 \end{aligned}$$

Current in R_G can be ignored since R_G is large
(Compared to the current $g_m v_{gs}$)


$$R_{in} = \frac{v_{gs}}{i_{in}} = \frac{v_{gs}}{(v_{gs} - v_o)/R_G} = R_G \frac{1}{1 - \frac{v_o}{v_{gs}}} = \frac{R_G}{4.3} = 2.33 \text{ M}\Omega$$

T equivalent circuit

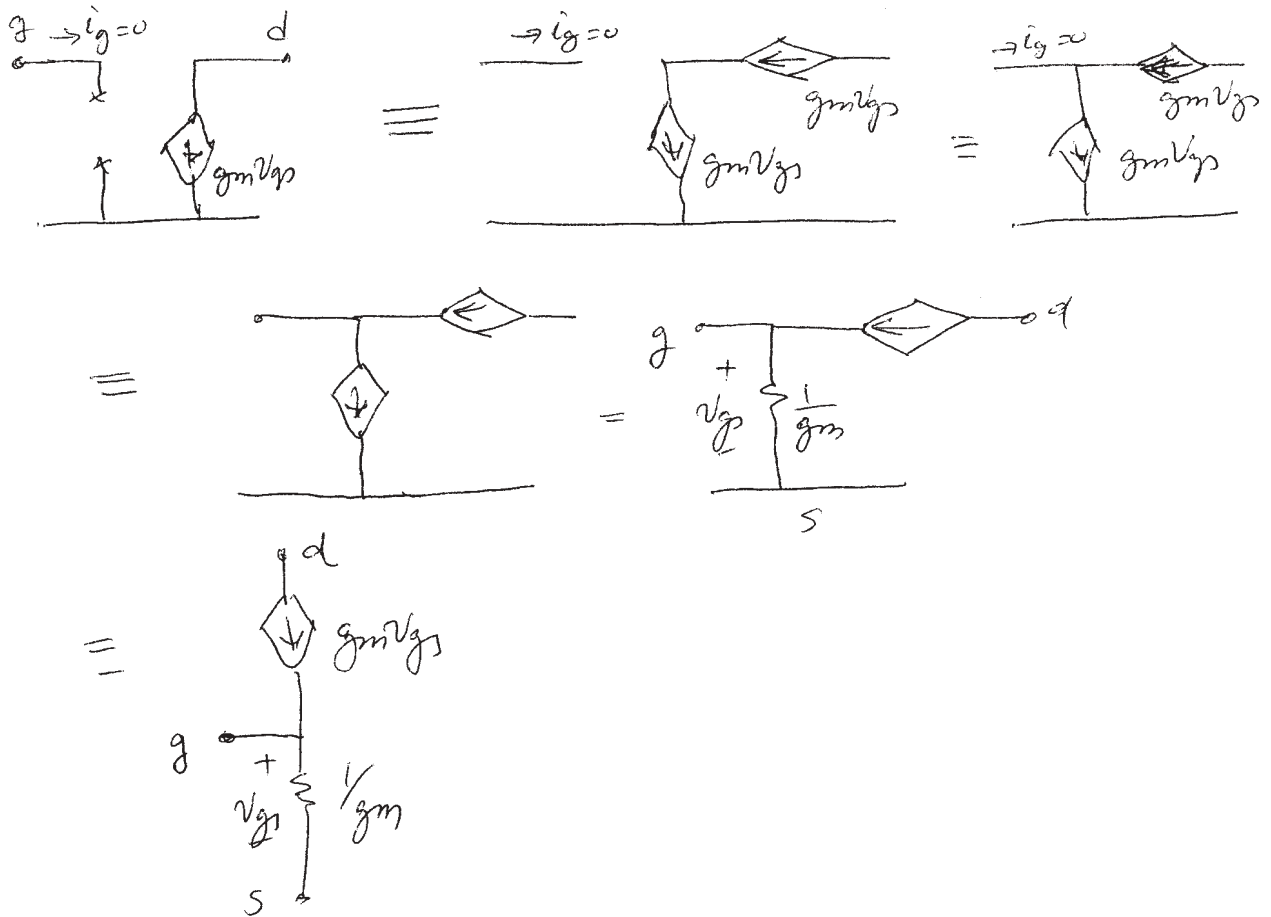


FET BIAS CIRCUITS

direct bias

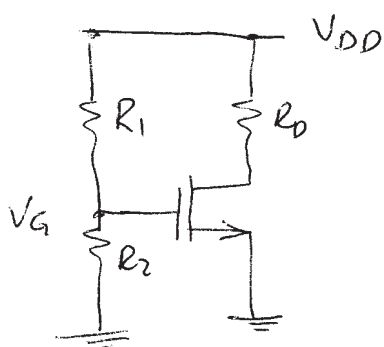


$$V_G = V_{DD} \frac{R_2}{R_1 + R_2} \quad (\text{constant})$$

$$V_{GS} = V_G = \text{constant}$$

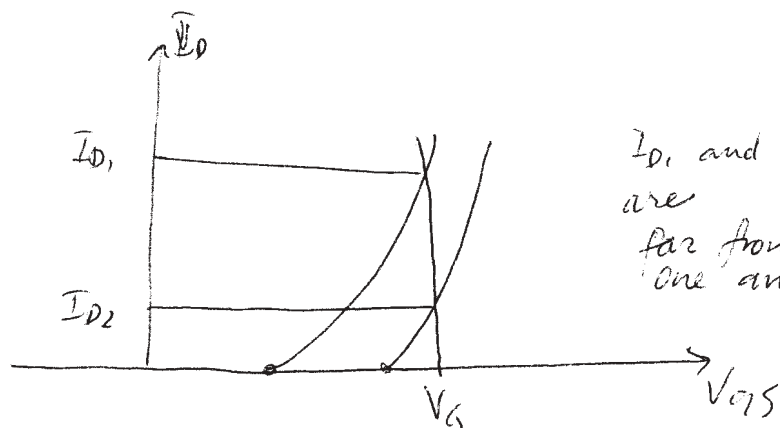

I_{D1} and I_{D2} are far from one another.


Integrated ch MOS Amplifiers

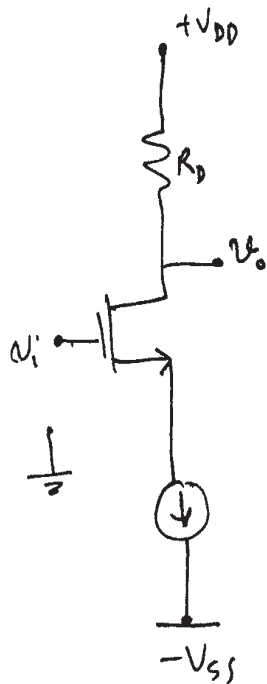

R_D takes more space than a MOSFET

is it possible to replace R_D w/ a MOSFET?

Consider the following ch:

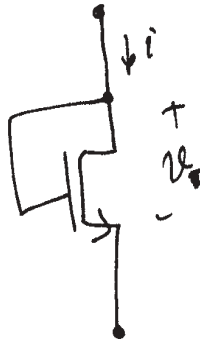


$$V_T > 0$$



$\Rightarrow$ always in Saturation mode.

$$V_{gs} = V_{ds}; \quad i = K(V - V_t)^2$$

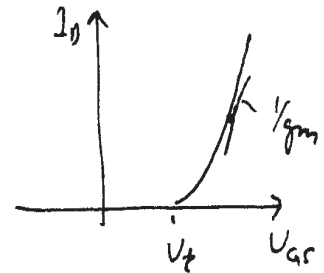its small signal resistance is $\frac{1}{g_m}$



Another one

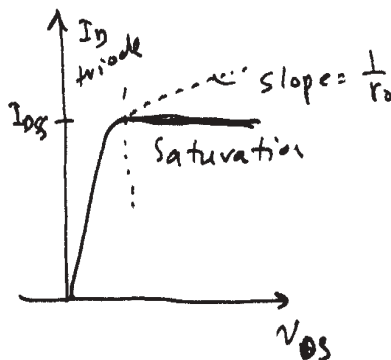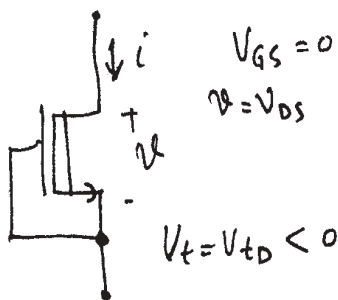

triode region:

$$i = K(-2V_{t0}v - v^2)$$

onset of saturation




$$i = KV_{t0}^2 = I_{DSS}$$

Channel length mod.

$$i \approx KV_{t0}^2 \left(1 + \frac{v}{V_A}\right)$$

In triode mode the device would act like a low-valued resistor r_{DS}

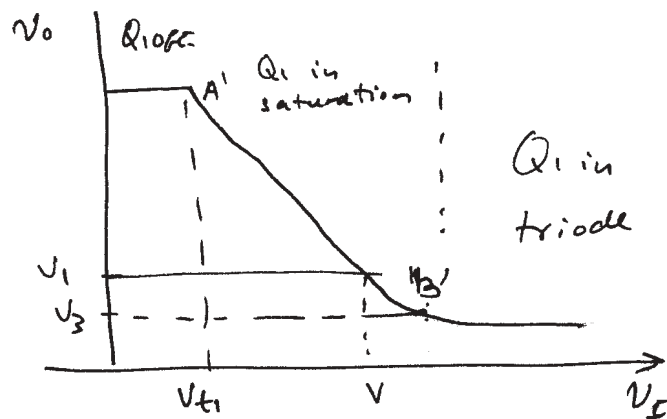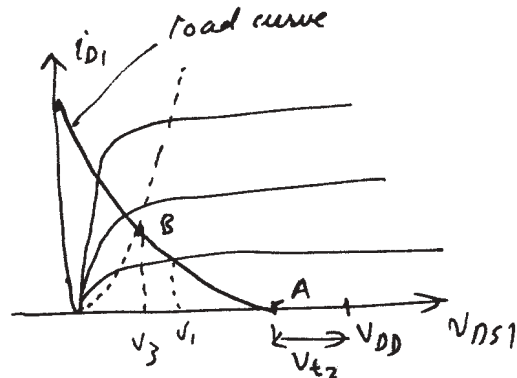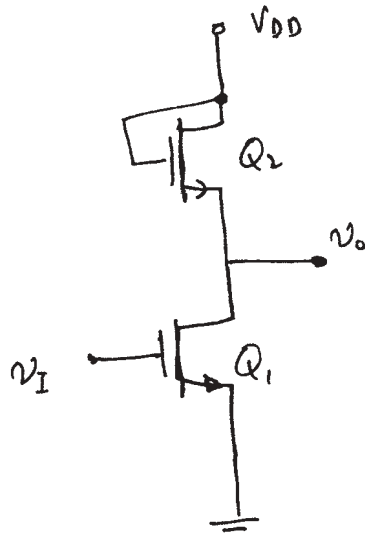in the sat mode $\rightarrow$ large valued resistor $\rightarrow r_o$.



$$i_{D1} = K_1 (V_{GS1} - V_t)^2$$

$$V_{GS1} = V_I$$


$$i_{D1} = i_{D2} = K_2 (V_{GS2} - V_t)^2 = i_D$$

$$V_{GS2} = V_{DD} - v_O \Rightarrow i_D = K_2 (V_{DD} - v_O - V_t)^2$$

$$v_O = (V_{DD} - V_t + \sqrt{\frac{K_1}{K_2}} V_t) - \sqrt{\frac{K_1}{K_2}} V_I$$

voltage gain $\frac{\Delta v_O}{\Delta v_I} = -\sqrt{\frac{K_1}{K_2}}$

using the small signal models

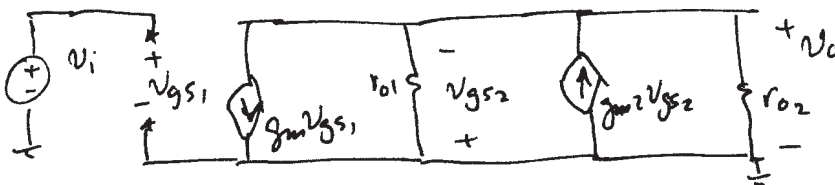


$$g_m = 2\sqrt{K I_D}$$

$$\frac{v_O}{v_i} = \frac{-g_{m1}}{g_{m2} + \frac{1}{r_{o1}} + \frac{1}{r_{o2}}}$$

$$\approx \frac{-g_{m1}}{g_{m2}}$$
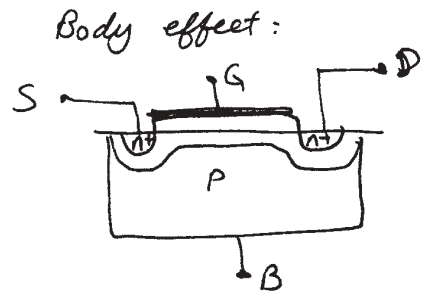
$$\frac{g_{m1}}{g_{m2}} = \frac{\sqrt{K_1}}{\sqrt{K_2}}$$



If B is not tied to S, there will be "body effect"


The "body" voltage affects V_t hence it affects I_D .

body trans conductance $\rightarrow g_{mb} = \frac{\partial I_D}{\partial V_{BS}} \bigg|_Q$



$$g_{mb} = \chi g_m$$

$$\chi = \frac{\partial V_t}{\partial V_{BS}} = \frac{\gamma}{2\sqrt{2\phi_f + V_{BS}}} \quad 0.1 < \chi < 0.3$$

Modified Mosfet model:



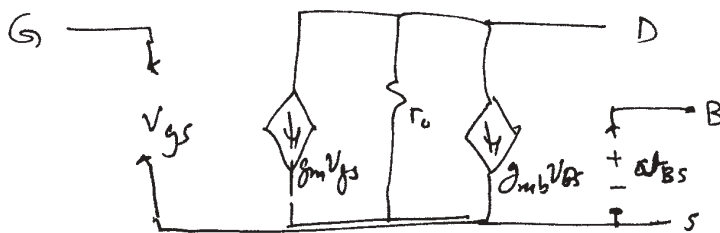


Small signal model

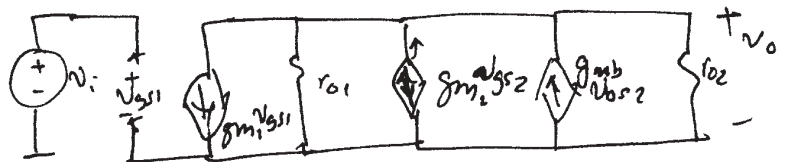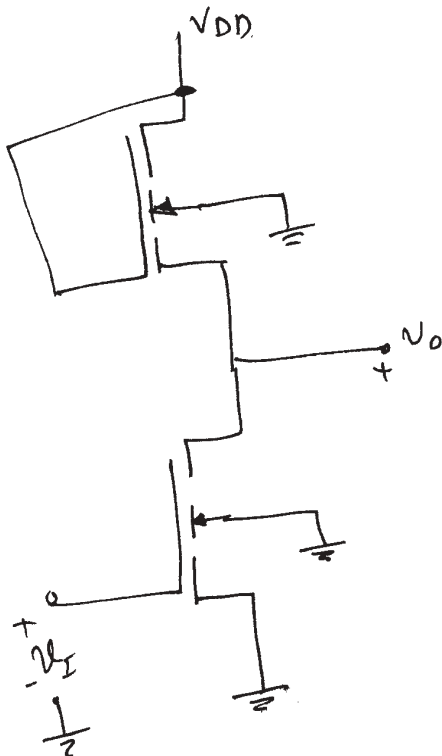

$$\begin{aligned} \frac{V_o}{V_i} &= - \frac{g_{m1}}{g_{m2} + g_{mb2} + \frac{1}{r_{o1}} + \frac{1}{r_{o2}}} \approx \frac{-g_{m1}}{g_{m2} + g_{mb2}} \\ &= \frac{-g_{m1}}{g_{m2}} \frac{1}{1 + \chi} \end{aligned}$$

NMOS Amplifier w/ depletion load

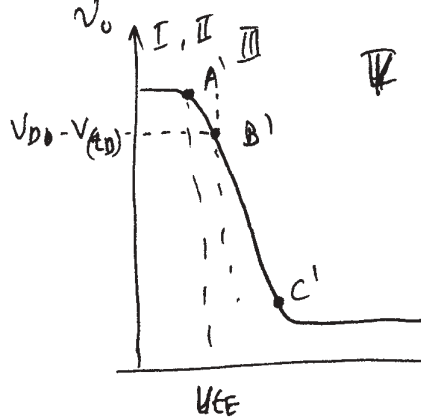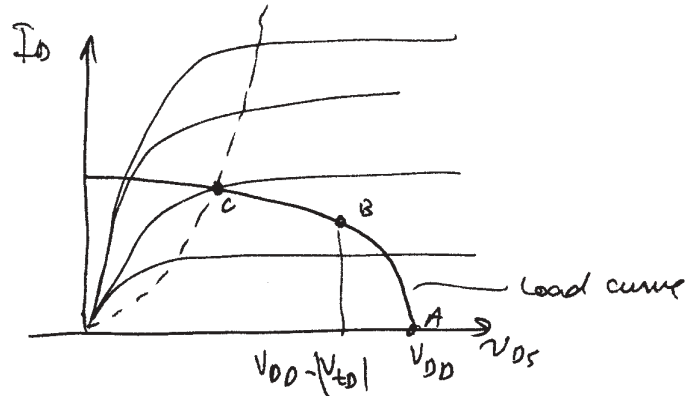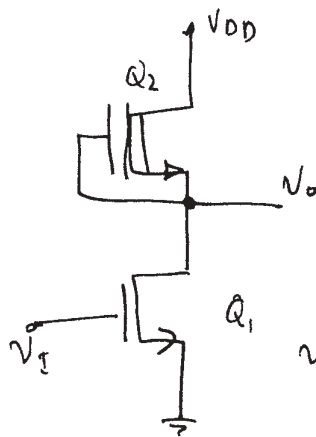

I : Q_1 OFF
 Q_2 TRIODE

II : Q_1 SAT
 Q_2 TRI

III : Q_1 SAT
 Q_2 SAT

IV : Q_1 TRI
 Q_2 SAT

if the operation is in region III, $A_v = \frac{V_o}{V_i} = -g_{m1}(r_{o1} || r_{o2})$


including the body effect:

$$A_v = -g_{m1} \left[\frac{1}{g_{mb2}} || r_{o1} || r_{o2} \right] \approx -\frac{g_{m1}}{g_{mb2}} = -\frac{g_{m1}}{g_{m2}} \frac{1}{\chi}$$

Bias current $\approx I_{DSS}$

DON'T WE NEED RESISTORS TO BIAS THE MOSFET?

One can use MOSFETS as voltage dividers

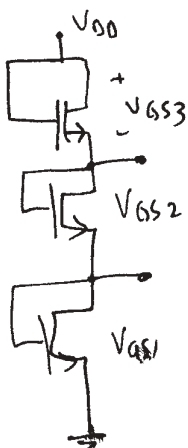

$$V_{GS1} + V_{GS2} + V_{GS3} = V_{DD}$$


if $K_1 = K_2 = K_3$

$V_t \rightarrow$ same $\rightarrow I_D =$ equal

$$V_{GS1} = V_{GS2} = V_{GS3} = \frac{V_{DD}}{3}$$

By making K different
one can adjust the voltages.

Current mirror:

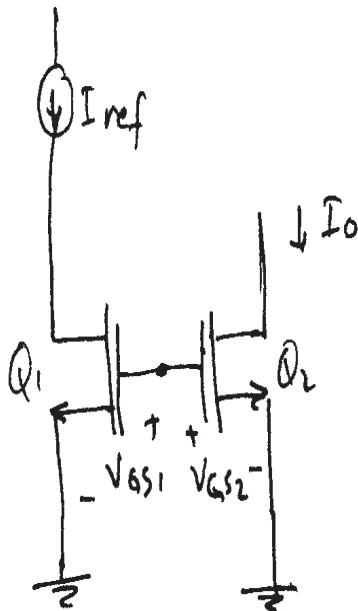


if Q_1 and Q_2 are identical
and they both in saturation mode
then $I_o = I_{ref}$.

if the two transistors are not
identical but both in saturation
mode $\rightarrow I_o$ and I_{ref} are
related because $V_{GS1} = V_{GS2}$

$$\left. \begin{aligned} I_{ref} &= k_1 (V_{GS1} - V_t)^2 \\ I_o &= k_2 (V_{GS2} - V_t)^2 \end{aligned} \right\} \frac{I_o}{I_{ref}} = \frac{k_2}{k_1}$$

w/ BJT

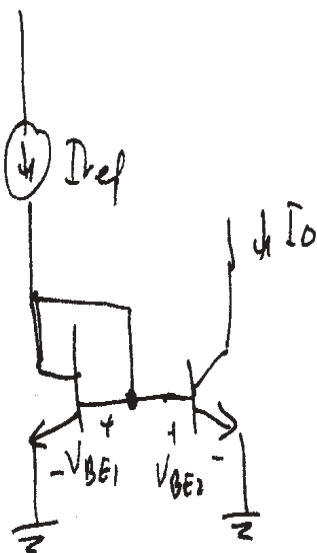

Read the sections

- FET switches
- GaAs Device