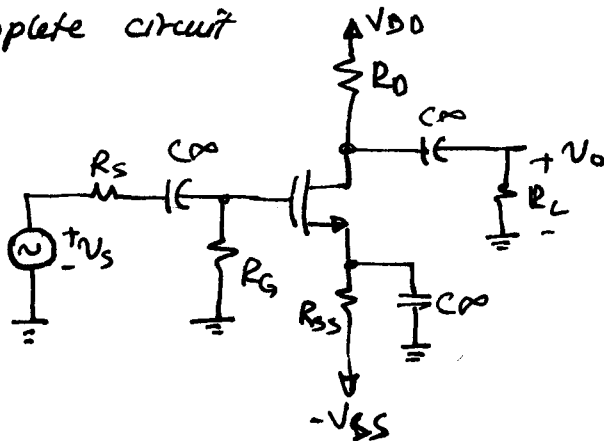


FET AMPLIFIERS (H.H. Erkaya)


①

FETs are operated in constant current mode when they are used as amplifiers. (similar to the active mode)
The configuration is named after the terminal that is common to input and output ports

Common Source Amplifier Complete circuit




or

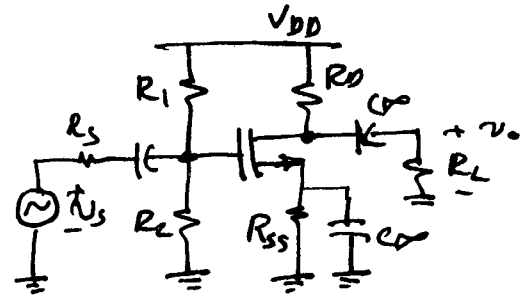

The small-signal equivalent circuit:

$$g_m = 2\sqrt{K I_D}$$

$$r_o \approx \frac{V_A}{I_D}$$

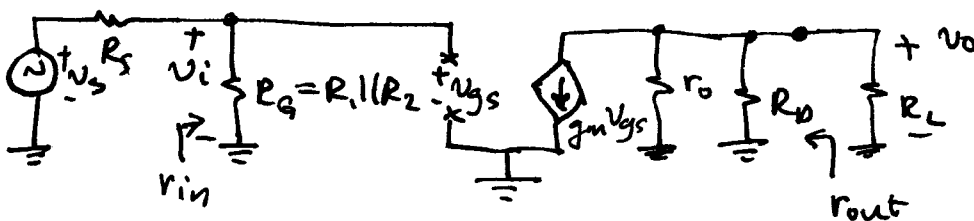

$$r_{in} = R_G = R_1 \parallel R_2$$

$$v_o = -g_m v_{gs} (r_o \parallel R_D \parallel R_L)$$

$$v_i = v_{gs}$$

$$r_{out} = r_o \parallel R_D$$

hence $\frac{v_o}{v_i} = -g_m (r_o \parallel R_D \parallel R_L)$



$$\frac{v_i}{v_s} = \frac{r_{in}}{R_s + r_{in}}$$

$$\frac{v_o}{v_s} = -g_m v_{gs} (r_o \parallel R_D \parallel R_L) \frac{r_{in}}{R_s + r_{in}}$$

Note: r_o is often ignored due to its large value

Common Gate Amplifier


complete circuit:

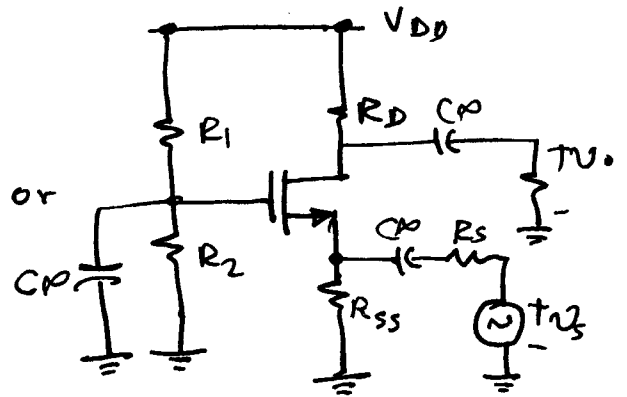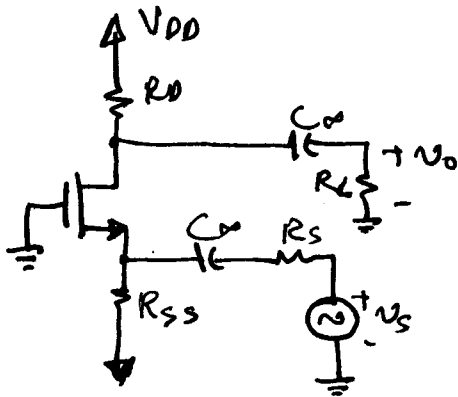

Small signal equivalent circuit

(r_o is ignored)

$$g_m = 2\sqrt{k_n I_{DQ}}$$

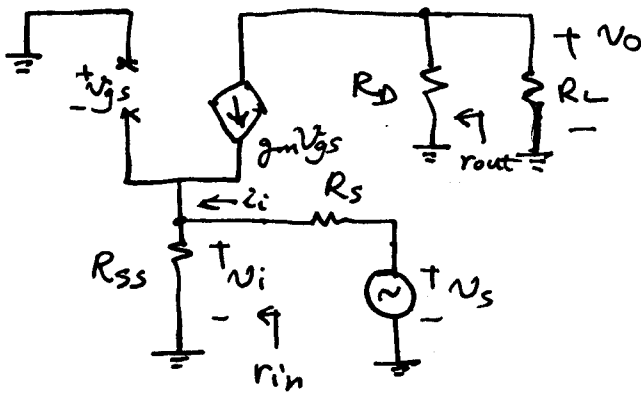

$$r_{out} = R_D$$

$$r_{in} = R_{ss} \parallel \frac{1}{g_m}$$

$$v_o = -g_m v_{gs} (R_D \parallel R_L)$$

$$v_i + v_{gs} = 0$$

$$v_i = -v_{gs}$$

$$\frac{v_o}{v_s} = g_m (R_D \parallel R_L) \frac{r_{in}}{R_{ss} + r_{in}}$$

To find r_{in} :

By definition, $r_{in} = \frac{v_i}{i_i}$

$$i_i = \frac{v_i}{R_{ss}} - g_m v_{gs} = \frac{v_i}{R_{ss}} + g_m v_i$$


$$r_{in} = \frac{v_i}{\frac{v_i}{R_{ss}} + \frac{v_i}{\frac{1}{g_m}}} = \frac{1}{\frac{1}{R_{ss}} + \frac{1}{\frac{1}{g_m}}} = R_{ss} \parallel \frac{1}{g_m}$$

$$r_{out} = \left. \frac{v_{oc}}{i_{sc}} \right|_{R_L \rightarrow \infty} = \frac{-g_m v_{gs} R_D}{-g_m v_{gs}} = R_D$$


Common Drain Amplifier (source follower)

(3)


Complete circuit:

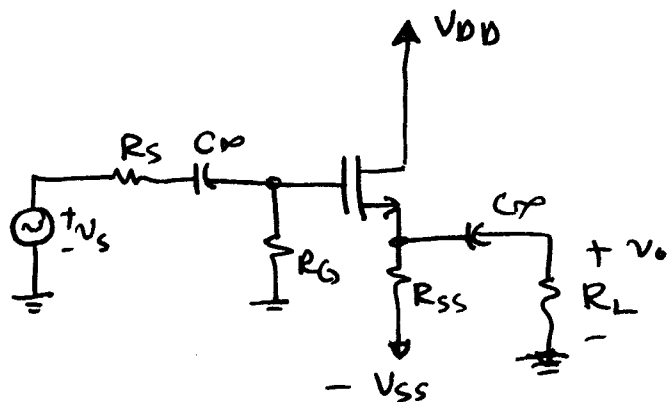

or

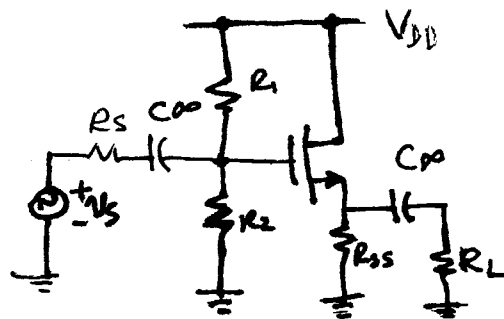

The small signal eq. ckt:

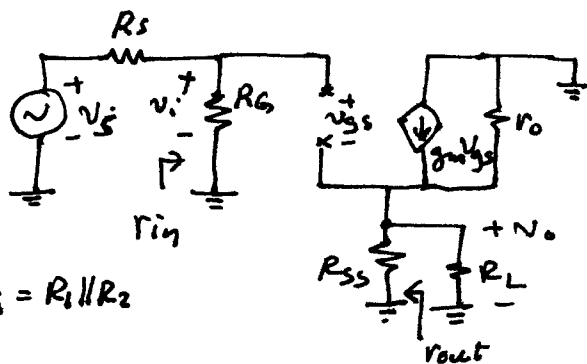

$$R_G = R_1 \parallel R_2$$

please note: r_o becomes parallel to R_{ss} if $R_{ss} \ll r_o$, ignore r_o ; else, $R_{ss} \leftarrow R_{ss} \parallel r_o$

$$r_{in} = R_G = R_1 \parallel R_2$$

$$r_{out} = R_{ss} \parallel r_o \parallel \frac{1}{g_m}$$

$$\left. \begin{aligned} V_o &= g_m V_{gs} (R_{ss} \parallel r_o \parallel R_L) \\ V_i &= V_o + V_{gs} \\ \frac{V_i}{V_s} &= \frac{R_{in}}{R_s + r_{in}} \end{aligned} \right\}$$

$$\frac{V_o}{V_s} = \frac{g_m (R_{ss} \parallel r_o \parallel R_L)}{1 + g_m (R_{ss} \parallel r_o \parallel R_L)} \frac{r_{in}}{R_s + r_{in}}$$