

①

6. Differential and Multistage Amplifiers

"The most widely used circuit building block"


OPAMP input stage, ECL input stage

BJT, MOSFET, JFET, MESFET

"Biasing" is important - to be discussed here

6.1 The BJT Differential Amplifier

Topology:

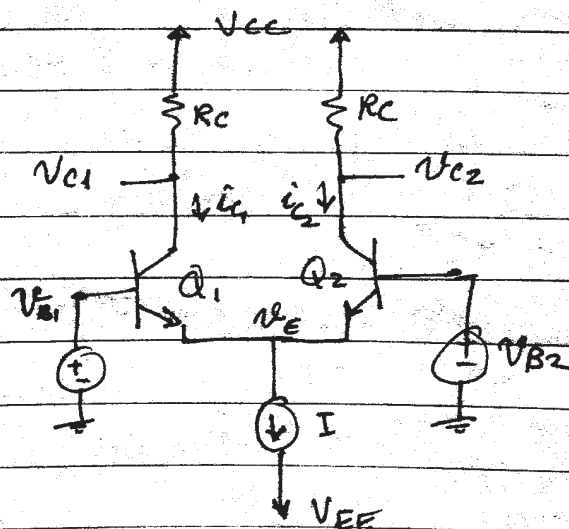

Keep in mind:

- 1) Q_1 and Q_2 may not go into saturation mode
- 2) Q_1 and Q_2 are "identical."

The current I is shared between the two emitters: $I = i_{E1} + i_{E2}$

if $V_{B1} = V_{B2}$, then $i_{E1} = i_{E2} = \frac{I}{2}$

This is called common-mode.

Then, $i_{C1} = i_{C2} = \alpha i_{E1} = \alpha \frac{I}{2} \approx \frac{I}{2}$ since $\alpha \approx 1$ for practical BJTs.

Common mode $\rightarrow V_{B1} = V_{B2} = V_{cm}$, $V_E = V_{cm} - V_{BE}$

$$V_{C1} = V_{C2}$$

$$= V_{CC} - \frac{1}{2} \alpha I R_C \quad \leftarrow \text{independent of } V_{B1} \text{ or } V_{B2} \text{ (in common mode)}$$

The amplifier rejects the common-mode signals.

Now make $V_{B1} \neq V_{B2}$ for example: $V_{B1} = +1V$, $V_{B2} = 0V$

Q_1 will have more current $\rightarrow V_E = V_{B1} - V_{BE} = 1 - 0.7 = 0.3V$

(2)

$$V_{BE2} = V_{B2} - V_E = 0 - 0.3V = -0.3V < 0.7 \rightarrow Q_2 \text{ is OFF}$$

$$i_{E1} = \alpha I, \quad V_{C1} = V_{CC} - \alpha I R_C, \quad V_{C2} = V_{CC}$$

If you make $V_{B1} = -1$, $V_{B2} = 0$ then

$$Q_1: \text{OFF}, \quad Q_2: \text{ON} \quad V_{C1} = V_{CC} \quad V_{C2} = V_{CC} - \alpha I R_C$$

Small differences between V_{B1} and V_{B2} causes large changes in i_{E1} and i_{E2} .

$$i_c = \frac{I}{2} \mp \Delta I$$

$$\Delta V_i \rightarrow \Delta I \rightarrow \Delta V_o = \alpha \Delta I R_C$$

$$\text{differential output} \rightarrow \Delta V_o = 2 \Delta I R_C$$

Large Signal Model

$$i_{E1} = \frac{I_s}{\alpha} e^{(V_{B1} - V_E)/V_T}$$


$$i_{E2} = \frac{I_s}{\alpha} e^{(V_{B2} - V_E)/V_T}$$

$$\frac{i_{E1}}{i_{E2}} = e^{(V_{B1} - V_{B2})/V_T}$$

$$i_{E1} + i_{E2} = I$$


$$i_{E1} = \frac{I}{1 + e^{(V_{B2} - V_{B1})/V_T}}$$
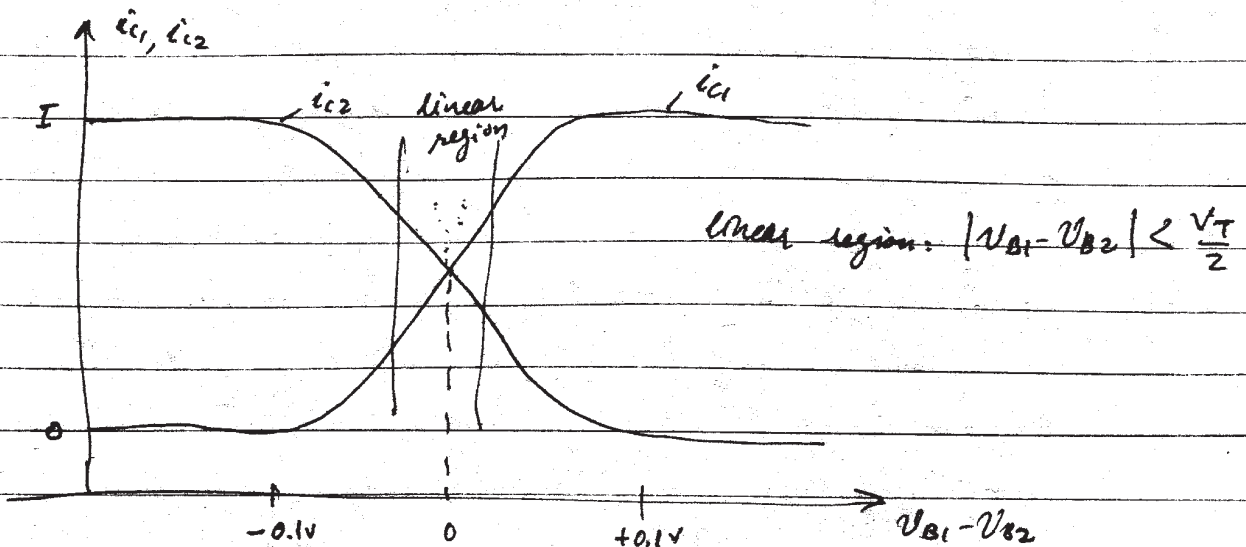
$$i_{E2} = \frac{I}{1 + e^{(V_{B1} - V_{B2})/V_T}}$$



(3)

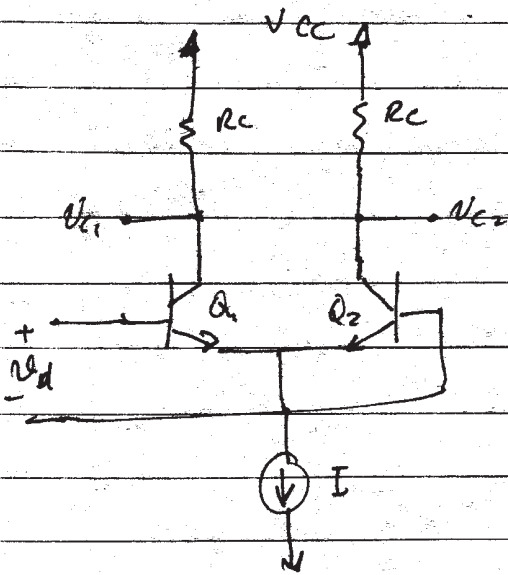6.2 Small Signal Operation of BJT Diff. Amp.



differential mode

$$v_{b1} = -v_{b2}$$

$$v_{b1} - v_{b2} = 2v_{b1} = v_d$$

$$v_d \ll V_T$$

$$i_{c1} = \frac{\alpha I}{1 + e^{-v_d/V_T}}, \quad i_{c2} = \frac{\alpha I}{1 + e^{v_d/V_T}}$$

multiplying the numerator and the denominator by $e^{v_d/2V_T}$

$$i_{c1} = \frac{\alpha I e^{(v_d/2V_T)}}{e^{(v_d/2V_T)} + e^{(-v_d/2V_T)}}$$

$$v_d \ll V_T \Rightarrow e^{\pm v_d/2V_T} \approx 1 \pm \frac{v_d}{2V_T}$$

$$i_{c1} \approx \frac{\alpha I \left(1 + \frac{v_d}{2V_T}\right)}{1 + \frac{v_d}{2V_T} + 1 - \frac{v_d}{2V_T}} = \frac{\alpha I}{2} + \frac{\alpha I}{2V_T} \frac{v_d}{2}$$

likewise, $i_{c2} \approx \frac{\alpha I}{2} - \frac{\alpha I}{2V_T} \frac{v_d}{2}$

~~~~~  
bias                  signal


$$i_c = -\frac{\alpha I}{2V_T} \frac{v_d}{2}$$

The transconductance  $g_m = \frac{I_c}{V_T} = \frac{\alpha I/2}{V_T} = \frac{\alpha I}{2V_T}$

That means  $i_{c1} = g_m \frac{v_d}{2}$ ,  $i_{c2} = -g_m \frac{v_d}{2}$

(4)
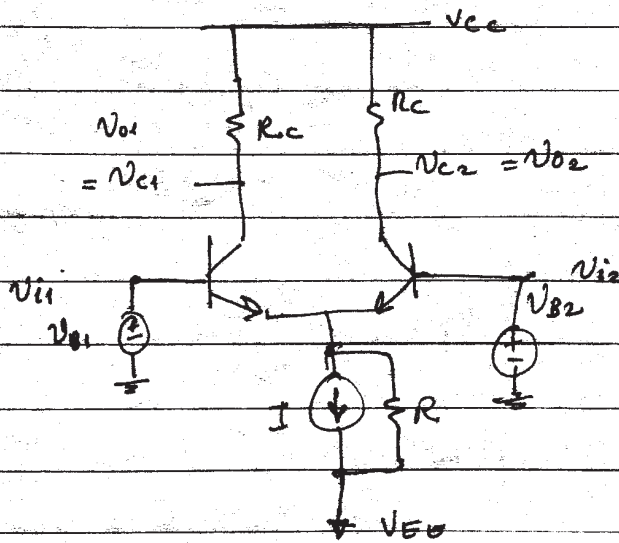
## SMALL SIGNAL MODEL FOR A BJT DIFF. AMP



Purely differential mode  $\rightarrow V_{i1} = -V_{i2}$

Purely common mode  $\rightarrow V_{i1} = V_{i2}$


for any combination:  $V_{idm} = \frac{V_{i1} - V_{i2}}{2}$  diff. mode of inputs  
 $V_{icm} = \frac{V_{i1} + V_{i2}}{2}$  common mode of input.

$V_{i1}$  and  $V_{i2}$  can be reconstructed:

$$V_{i1} = V_{icm} + \frac{V_{idm}}{2}$$

$$V_{i2} = V_{icm} - \frac{V_{idm}}{2}$$

Small signal model:

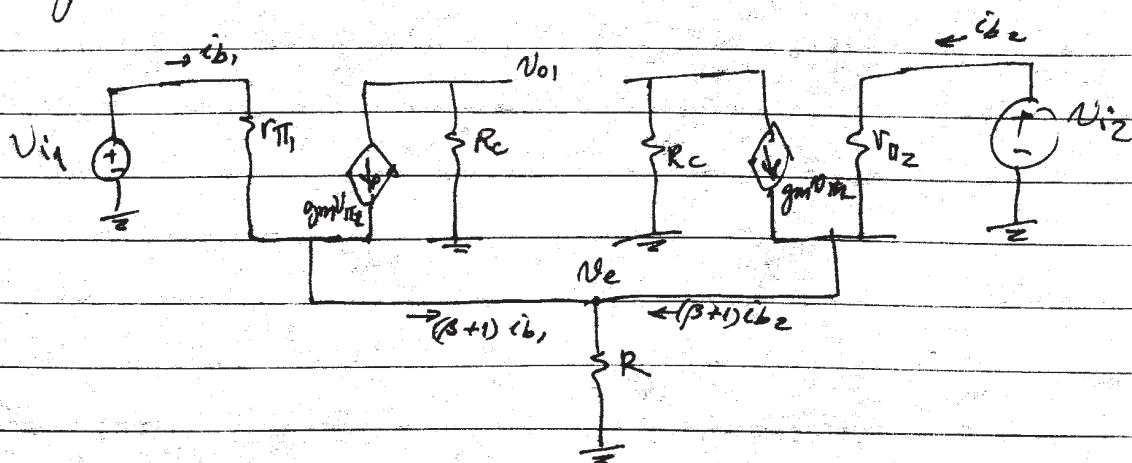

$$V_{o1} = -g_m V_{\pi 1} R_C$$

$$V_{o2} = -g_m V_{\pi 2} R_C$$

(5)

Purely differential mode:  $V_{i1} = -V_{i2}$ ,  $i_{b1} = -i_{b2}$ ,  $V_{i1} = -V_{i2}$   
 since the current in  $R$  equals zero,  $V_e = 0$   
 virtual ground.

$$V_{i1} = V_{idm} \quad V_{o1} = -g_m R_c V_{i1} = -g_m R_c \frac{V_{idm}}{2}$$

Single-ended, diff mode gain:  $A_{dm-se1} = \frac{V_{o1}}{V_{idm}} = -\frac{g_m R_c}{2}$

$$A_{dm-se2} = \frac{V_{o2}}{V_{idm}} = +\frac{g_m R_c}{2}$$

The diff mode input resistance:  $r_{indm} = \frac{V_{idm}}{i_{b1}}$

$$r_{in-dm} = \frac{2V_{i1}}{i_{b1}} = 2r_{\pi}$$

$$r_{out-se} = R_c$$

Differential mode of the output is possible:

$$A_{dm-diff} = \frac{V_{o1} - V_{o2}}{V_{idm}} = -g_m R_c$$

$$r_{out-diff} = 2R_c$$

Common mode analysis:  $V_{i1} = V_{i2} = V_{icm}$   
 in this case,  $V_e \neq 0$

$$V_e = R(i_{e1} + i_{e2})$$

$$V_e = R(\beta+1)(i_{b1} + i_{b2})$$

$$V_e = 2R(\beta+1)i_{b1}$$

$$V_{i1} = V_e + i_{b1} r_{\pi}$$

$$V_{i1} = [r_{\pi} + 2R(\beta+1)] i_{b1}$$

$$V_{o1} = -g_m V_{i1} R_c$$

$$= -\beta i_{b1} R_c$$

$$A_{cm-se1} = \frac{V_{o1}}{V_{icm}} = \frac{-\beta R_c}{r_{\pi} + 2(\beta+1)R}$$

$$A_{cm-se2} = \frac{V_{o2}}{V_{icm}} = \frac{\beta R_c}{r_{\pi} + 2(\beta+1)R}$$

(6)

ideal current source  $\rightarrow R = \infty \Rightarrow A_{cm-set} = 0$

Common mode

input resistance:  $r_{in,cm} = \frac{v_{icm}}{i_{b1}} = \frac{v_{i1}}{i_{b1}} = r_{\pi} + 2(\beta+1)R$

output resistance  $r_{out-se} = R_c$

Common mode rejection ratio:  $CMRR = \left| \frac{A_{dm}}{A_{cm}} \right|$   
 Sometimes in dB:  $20 \log \left| \frac{A_{dm}}{A_{cm}} \right|$


For our alet:  $CMRR = \frac{g_m R_c / 2}{\beta R_c / (r_{\pi} + 2(\beta+1)R)}$

$g_m = \frac{\beta}{r_{\pi}} \Rightarrow CMRR = \frac{r_{\pi} + 2(\beta+1)R}{2r_{\pi}} \approx \frac{(\beta+1)R}{r_{\pi}}$

Read section 6.2 for details.

### 6.3 Non-ideal Characteristics of The Diff. Amp.

input offset voltage

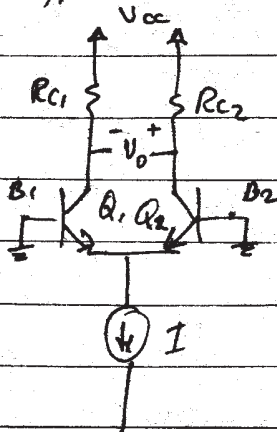

Since no two things are absolutely identical

$\rightarrow i_{c1} \neq i_{c2} \quad R_{c1} \neq R_{c2}$


$\rightarrow V_o$  is nonzero when both inputs are zero.

input offset voltage:  $V_{os} = V_o / A_{dm}$

$V_o$ : output offset voltage

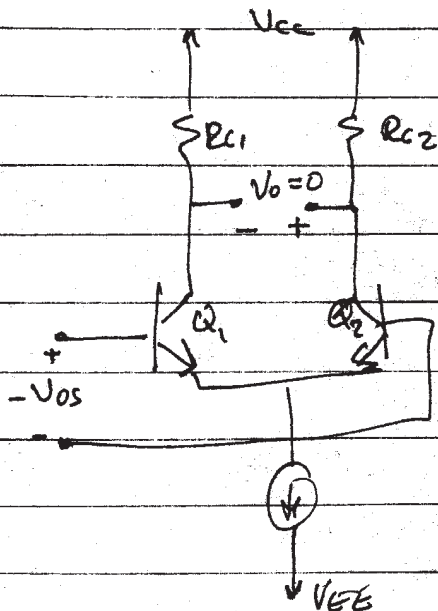(7)

if one applies  $-V_{os}$  between the input terminals, the output voltage  $= 0$ .



Read section 6.3 for a detailed analysis

$V_{os}$  can be due to mismatches between  $R_{C1}$  and  $R_{C2}$  or between  $I_{S1}$  and  $I_{S2}$  of  $Q_1$  and  $Q_2$ .

$$V_{os} = V_T \sqrt{\left(\frac{\Delta R_C}{R_C}\right)^2 + \left(\frac{\Delta I_S}{I_S}\right)^2}$$

$R_C, I_S$  : average values

Input bias and offset currents

$$I_{os} = |I_{B1} - I_{B2}| = I_B \left( \frac{\Delta \beta}{\beta} \right)$$

↑  
average

Input common mode range

The range is determined from the condition that  $Q_1$  and  $Q_2$  must stay in active mode.


An additional condition comes from the current source.

8

## BIASING THE BJT INTEGRATED CKTS

Resistors and capacitors take too much space on an integrated ckt  $\rightarrow$  they are avoided in IC design.

### The current mirror

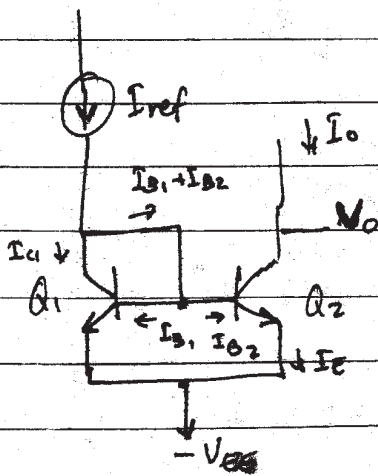

$Q_1$  and  $Q_2$  are identical

$$V_{BE1} = V_{BE2}$$

$$\Rightarrow I_{C1} = I_{C2} = I_O$$

$$I_{ref} = I_{C1} + I_{B1} + I_{B2} = I_O + 2I_{B1}$$

if  $\beta \gg 1$  then the base currents can be neglected

$$\rightarrow I_O \approx I_{ref}$$


To be more precise:

$$\frac{I_O}{I_{ref}} = \frac{\beta}{\beta+2} = \frac{1}{1+\frac{2}{\beta}}$$

$$I_O = \frac{\beta}{\beta+1} I_E, \quad I_{ref} = \frac{\beta+2}{\beta+1} I_E$$

this (ignores the Early effect)

### Example

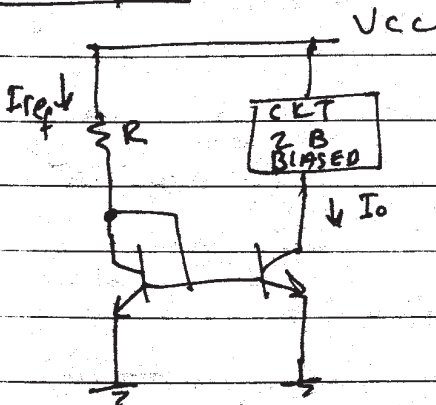


$$I_{ref} = \frac{V_{cc} - V_{BE}}{R}$$

$$\left. \begin{array}{l} I_O = 1 \text{ mA} \\ V_{cc} = 5 \text{ V} \end{array} \right\} \Rightarrow R = \frac{5 - 0.7}{1} = 4.3 \text{ k}\Omega$$

(9)

## Current Steering Circuits

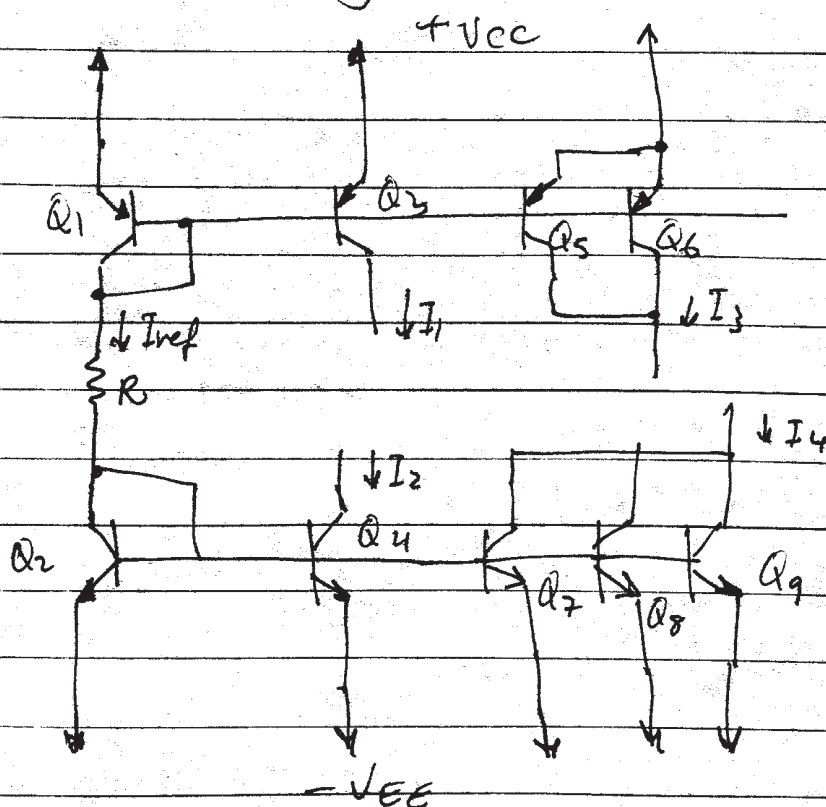


$I_{ref}$  provides the base currents for all transistors.

Read details in section 6.4 including Wilson + Widlar sources.

Study Example 6.2 on p. 438
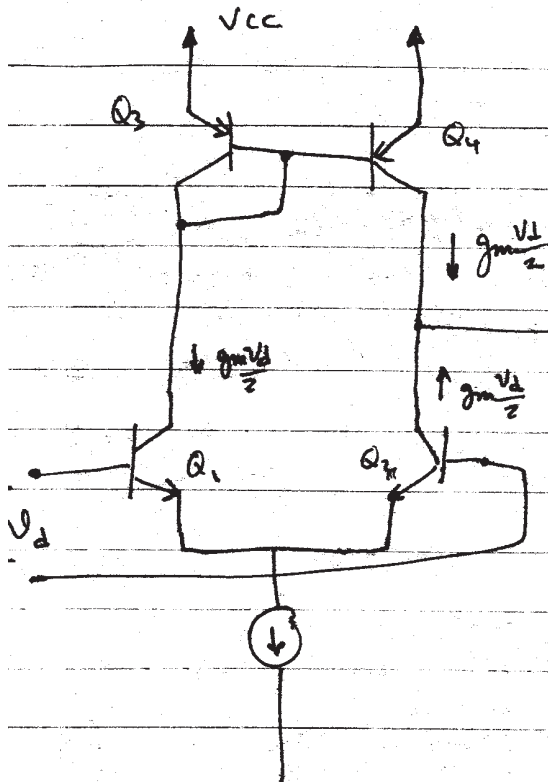
## 6.5 The BJT Differential Amplifier w/ Active Load

A transistor operated as a current source has a large small signal resistance  $\rightarrow$  it may be utilized as a high-value resistor.



$$V_o = g_m V_d R_o$$


$$R_o = r_{o2} \parallel r_{o4} \approx$$

$$r_{o2} = r_{o4} = r_o \Rightarrow V_o = g_m V_d r_o$$

$$g_m = \frac{I_c}{V_T}, \quad r_o = \frac{V_A}{I_c}, \quad I_c = \frac{I}{2}$$

$$g_m r_o = \frac{V_A}{V_T}$$

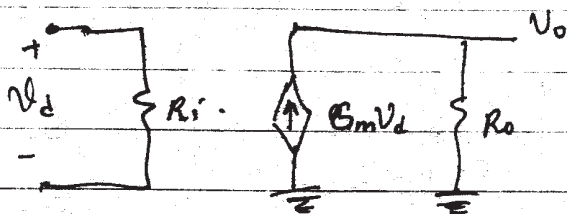
$$V_A = 100V \rightarrow g_m r_o = 4000, \quad \text{gain} \approx 2000$$



$$R_i = 2R$$

$$G_m = g_m = \frac{I/2}{V_T}$$

### The Cascode configuration

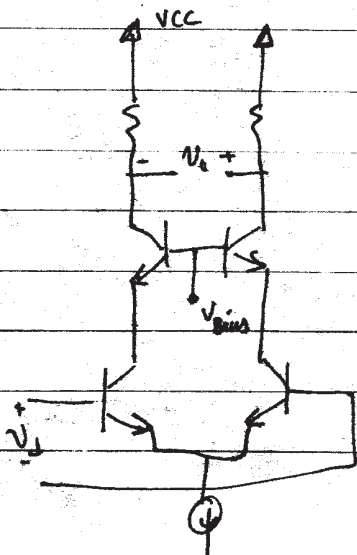


However, voltage gain does not change much.  
freq. response is improved.

# JFET and MOSFET DIFF. PAIRS

— high input resistance —

$$V_{G1} - V_{G2} = V_{id}$$

identical JFETs

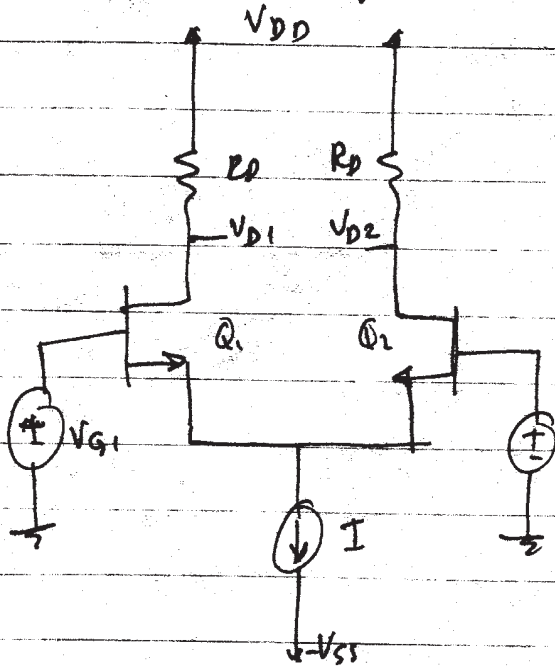

$$i_{D1} = \frac{I}{2} + V_{id} \frac{1}{-2V_p} \sqrt{2 \frac{I_{DSS}}{I} - \left( \frac{V_{id}}{V_p} \right)^2 \left( \frac{I_{DSS}}{I} \right)^2}$$

$$i_{D2} = \frac{I}{2} - V_{id} \frac{1}{-2V_p} \sqrt{2 \frac{I_{DSS}}{I} - \left( \frac{V_{id}}{V_p} \right)^2 \left( \frac{I_{DSS}}{I} \right)^2}$$

Small signal operation:

$$i_D = I_{DSS} \left( 1 - \frac{V_{GS}}{V_p} \right)^2$$

$$V_{d1} = -g_m \frac{V_{id}}{2} R_D$$

$$V_{d2} = +g_m \frac{V_{id}}{2} R_D$$

MOSFET  $i_D = k(V_{GS} - V_t)^2$

$$i_{D1} = \frac{I}{2} + \left( \frac{I}{V_{GS} - V_t} \right) \left( \frac{V_{id}}{2} \right) \sqrt{1 - \left( \frac{V_{id}/2}{V_{GS} - V_t} \right)^2}$$

$$i_{D2} = \frac{I}{2} - \left( \frac{I}{V_{GS} - V_t} \right) \left( \frac{V_{id}}{2} \right) \sqrt{1 - \left( \frac{V_{id}/2}{V_{GS} - V_t} \right)^2}$$

$$g_m = \frac{2I_D}{V_{GS} - V_t} = \frac{I}{V_{GS} - V_t}$$

Read the rest of the section