


I have neither given nor received unauthorized help with this exam.

ID: _____ Name: SOLUTIONS Signature: _____ Grade: _____

- 6:49 1) (25 pts) Two identical diodes are connected in a circuit as shown below.
($I_S = 1 \text{ nA}$, $\eta = 1$, $V_T = 25 \text{ mV}$)

a) **Estimate** the current in the circuit. D_2 Reverse biased $I = I_S$

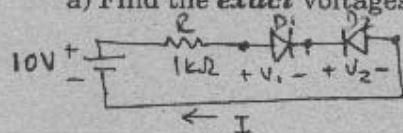a) Find the **exact** voltages across the diodes within tenths of mV.



$$I = I_S \left(e^{V_D / \eta V_T} - 1 \right)$$

$$V_D = \eta V_T \ln \left(\frac{I}{I_S} + 1 \right), \quad V_{D1} = 0.025 \ln \left(\frac{I_S}{I_S} + 1 \right) = 17.3 \text{ mV}$$


$$10 \text{ V} = IR + V_1 + V_2$$

$$V_2 = 10 - V_1 - IR = 10000 - 17.3 - 1000 \times 10^{-9} \times 10^3 =$$

$$= 10000 - 17.3 - 10^{-3} = 9982.699 \text{ mV}$$

$$\approx 9982.7 \text{ mV}$$

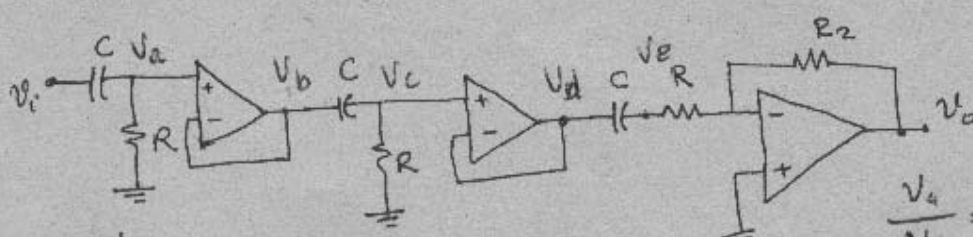- 6:55 2) (20 pts) Find the frequency domain transfer function for the circuit given below.



$$\frac{V_b}{V_a} = \frac{V_d}{V_c} = 1$$

$$\frac{V_o}{V_i} = \frac{V_o}{V_e} \cdot \frac{V_e}{V_d} \cdot \frac{V_d}{V_c} \cdot \frac{V_c}{V_b} \cdot \frac{V_b}{V_a} \cdot \frac{V_a}{V_i}$$

$$\frac{V_d}{V_i} = \frac{R}{\frac{1}{j\omega C} + R} = \frac{j\omega RC}{1 + j\omega RC}$$

$$= \left(\frac{j\omega RC}{1 + j\omega RC} \right)^3 \left(-\frac{R_2}{R} \right)$$


$$\frac{V_c}{V_b} = \frac{V_e}{V_d} = \frac{V_a}{V_i}$$

$$\frac{V_o}{V_e} = -\frac{R_2}{R}$$

6:58

58

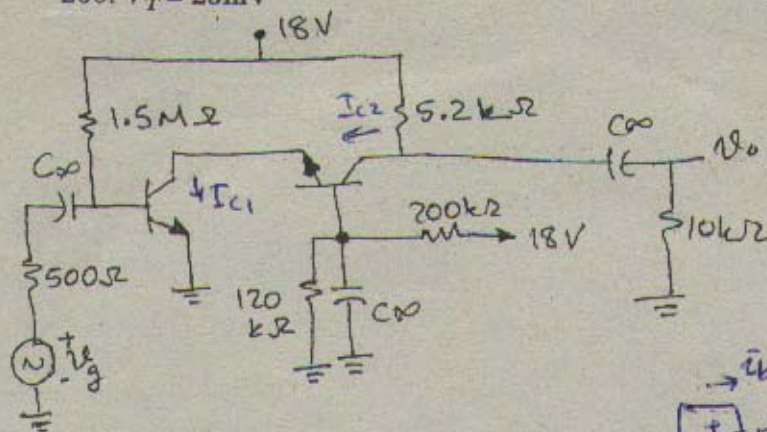3) (25 pts) a) Find the small signal voltage gain in the circuit below. Assume $V_{BE} = 0.7 \text{ V}$, $h_{FE} = 200$, $V_T = 25 \text{ mV}$




$$\frac{v_o}{v_g} = \underline{\hspace{2cm}}$$

$$I_{C1} \approx I_{C2}$$

$$I_{B1} = \frac{18 - 0.7}{1500} = 0.0115 \text{ mA}$$

$$I_{C1} = h_{FE} I_{B1} = 200 \times 0.0115 = 2.3067 \text{ mA}$$
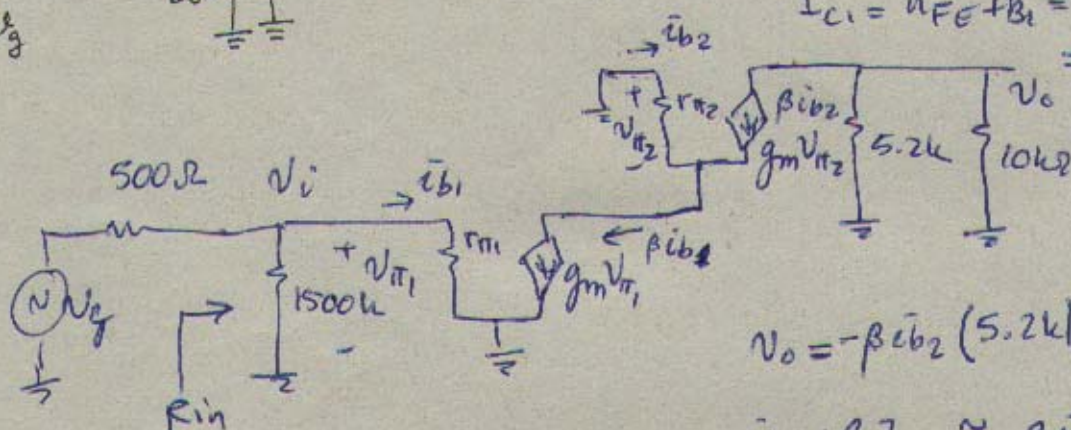
$$g_m = \frac{2.3}{0.025} = 92 \text{ mA/V}$$



$$v_o = -\beta i_{b2} (5.2 \text{ k} \parallel 10 \text{ k})$$

$$g_m v_{\pi 1} = i_{b2} + \beta i_{b2} \approx \beta i_{b2} \quad \text{since } \beta \gg 1$$

$$\Rightarrow v_o \approx -g_m v_{\pi 1} (5.2 \text{ k} \parallel 10 \text{ k})$$

$$R_{in} = 1500 \text{ k} \parallel r_{\pi 1} = 1500 \text{ k} \parallel \frac{200}{92} = 2.17 \text{ k}\Omega$$


$$v_{\pi 1} = v_i = v_g \frac{R_{in}}{0.5 + R_{in}} = v_g \frac{2.17}{2.67} = 0.81 v_g$$

$$\frac{v_o}{v_g} = \frac{v_o}{v_{\pi 1}} \cdot \frac{v_{\pi 1}}{v_i} \cdot \frac{v_i}{v_g} = -92 (5.2 \parallel 10) (1) (0.81) = \underline{\underline{-254.9}}$$

7:10

7:10

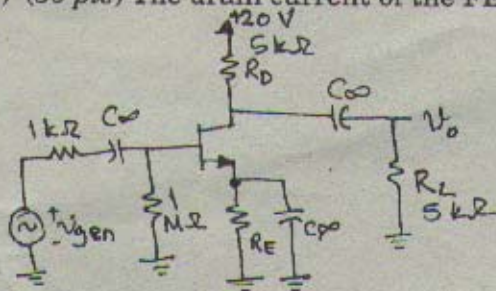- 4) (30 pts) The drain current of the FET in the circuit below is desired to be 2 mA. $V_p = -3V$, $I_{DSS} = 8mA$



$$I_D = K(V_{GS} - V_P)^2$$

$$K = \frac{I_{DSS}}{V_P^2} = \frac{8}{9} \text{ mA/V}^2$$

$$I_G = 0, V_{GS} = -I_D R_E \Rightarrow R_E = \frac{-V_{GS}}{I_D}$$

$$R_E = \frac{1.5}{2} = 0.75 \text{ k}\Omega$$


- a) Find the value of R_E

$$2 = \frac{8}{9}(V_{GS} + 3)^2 \Rightarrow (V_{GS} + 3) = \sqrt{\frac{18}{8}}, V_{GS} = \sqrt{\frac{18}{8}} - 3 = -1.5 \text{ V}$$

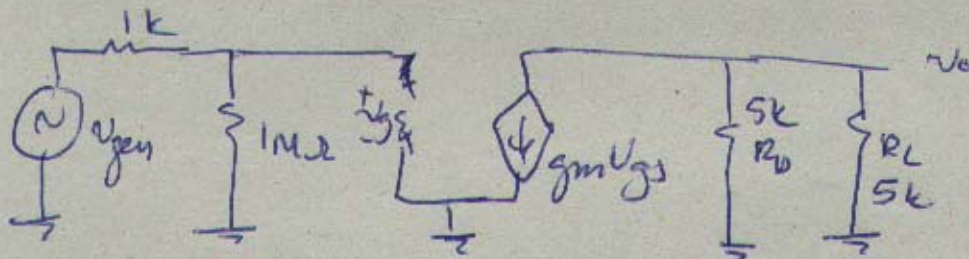- b) Find the small signal voltage gain.

$$\frac{v_O}{v_{gen}} = -6.66$$

$$g_m = 2\sqrt{KI_D} = 2\sqrt{\frac{8}{9} \times 2} = 2\sqrt{\frac{16}{9}} = 2 \frac{4}{3} = \frac{8}{3} \text{ mA/V}$$



$$\frac{V_{GS}}{V_{gen}} = \frac{1000}{1001} \approx 1$$

$$v_O = -g_m v_{gs} (R_D \parallel R_L) = -v_{gs} \left(\frac{8}{3} \times 2.5 \right)$$


$$\frac{v_O}{v_{gen}} = \frac{v_O}{v_{gs}} \cdot \frac{v_{gs}}{v_{gen}} \approx -\frac{8}{3} \times 2.5 = -6.66$$

7:17

17
11

28 min. x 3 ≈ 90 min

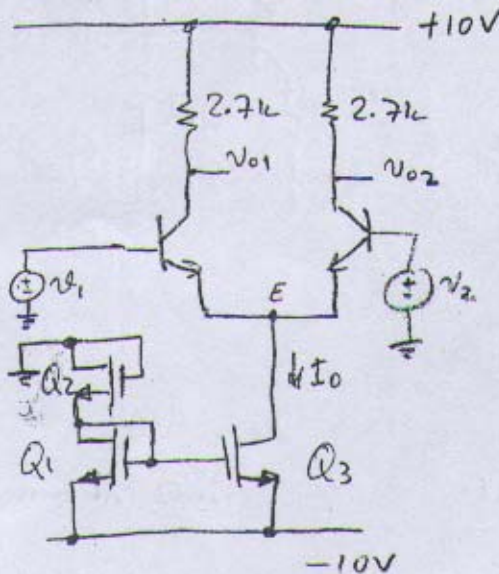3) Analyze the differential amplifier given below. Find the diff. and common mode gains, input resistances and single-ended output resistance. Also, find the amplitude of V_{idm} for the max output signal w/o distortion. What are the max and min common mode input voltages?



$$\beta = 250$$

$$V_{BE} = 0.7V$$

$$V_T = 0.025V$$

$$MOSFETS: K = 0.75 \text{ mA/V}^2$$

$$V_{TN} = 3V$$

$$V_A = 150V$$

$$A_{dm-se1} = -81$$

$$A_{cm-se1} = -0.027$$

$$r_{in-dm} = 8.34k$$

$$r_{in-cm} = 25104k$$

$$r_{out-se1} = 2.7k$$

$$|V_{idm}|_{max} = 0.05V$$

$$V_{icm-min} = -12.3V$$

$$V_{icm-max} = 6.45V$$

$$I_{D1} = I_{D2} \rightarrow V_{GS1} = V_{GS2}$$

$$V_{GS1} + V_{GS2} = 10V$$

$$V_{GS1} = V_{GS2} = V_{GS3} = 5V$$

$$I_0 = K(V_{GS} - V_{TN})^2 = 0.75(5-3)^2 = 3 \text{ mA}$$


$$V_{DSmin} = V_{GS} - V_{TN} = 5-3 = 2V$$

$$I_{C1} = I_{C2} = \frac{I_0}{2} = 1.5 \text{ mA}$$

$$r_{o3} = \frac{150}{3} = 50k\Omega$$

$$g_m = \frac{1.5}{0.025} = 60 \text{ mA/V}$$

$$r_{\pi} = \frac{250}{60} = 4.17k$$

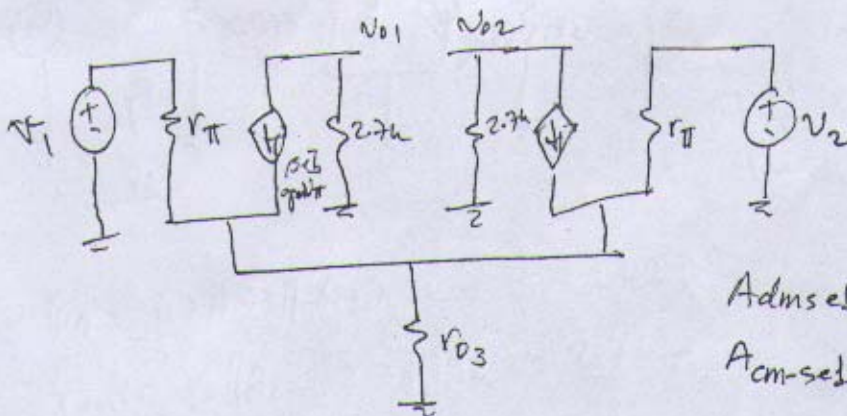

$$A_{dm-se1} = -\frac{g_m R_c}{2} = -\frac{60 \times 2.7}{2} = -81$$

$$A_{cm-se1} = \frac{-\beta R_c}{r_{\pi} + 2(\beta+1)r_{o3}} = \frac{-250 \times 2.7}{4.17 + 502 \times 50} = -0.027$$

$$r_{in-dm} = 2r_{\pi} = 8.34k\Omega, \quad r_{in-cm} = r_{\pi} + 2(\beta+1)r_{o3} = 4.17 + 502 \times 50 = 25104k\Omega$$


$$r_{out-se} = 2.7k$$

Each collector current: $0 - 3 \text{ mA}$, DC output voltage: $10 - 2.7 \times 1.5 = 5.95V$.

Saturation limit $\rightarrow V_{ominSAT} = -0.7 + 0.2 = -0.5V$.

Current source limit $V_{omin} = 10 - 3 \times 2.7 = 1.9V$.

diff mode

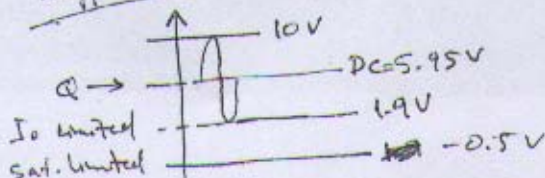

w/o distortion max output signal ampl. $\frac{2.7 \times 15V}{81} = 4.05V$

$$|V_{idm}|_{max} = \frac{4.05}{81} = 0.05V$$


common mode: $V_0 = \text{constant}$

$$V_{icm-min} = V_0 - V_{CESAT} + V_{BE} = 5.95 - 0.2 + 0.7 = 6.45V$$

$$V_{icm-max} = 15 - 2.7 + 0.2 = -12.3V$$

ID Number: _____ Name: Solutions Signature: _____ Grade: _____

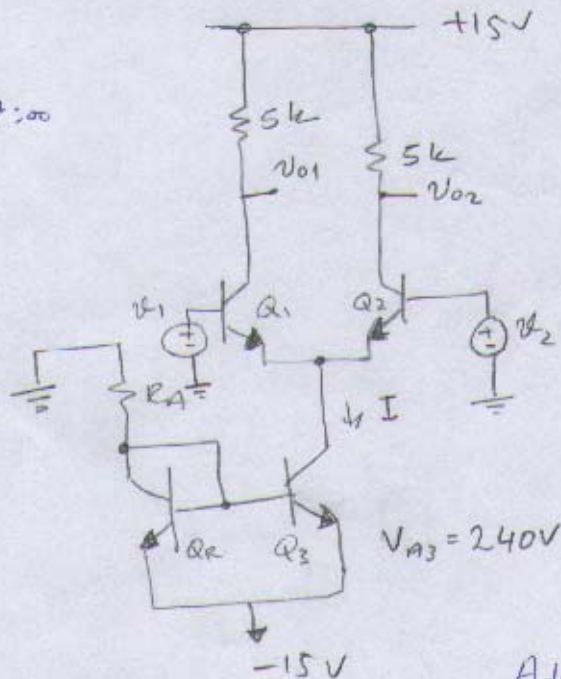For the amplifier below, $I = 3 \text{ mA}$, and the BJTs have a beta of 200. Find the differential and common mode single-ended voltage gain and input resistance.



$$A_{dmse1} = \underline{\hspace{2cm}}$$

$$A_{cmse1} = \underline{\hspace{2cm}}$$

$$R_{in-dm} = \underline{\hspace{2cm}}$$

$$R_{in-cm} = \underline{\hspace{2cm}}$$

$$I_{C1} = I_{C2} = \frac{3}{2} = 1.5 \text{ mA}$$

$$g_{m1} = g_{m2} = \frac{1.5}{0.025} = 60 \text{ mA/V}$$

$$r_{\pi 1} = r_{\pi 2} = \frac{200}{60} = 3.33 \text{ k}\Omega$$

$$r_{o3} \approx \frac{V_{A3}}{I} = \frac{240 \text{ V}}{3 \text{ mA}} = 80 \text{ k}\Omega$$


$$A_{dm-se1} = -\frac{g_m R_C}{2} = -\frac{60 \times 5}{2} = -150$$

$$A_{cm-se1} = \frac{-\beta R_C}{2r_o(\beta+1) + r_{\pi}} = \frac{-200 \times 5}{402 \times 80 + 3.33} = \frac{-1000}{32163.33} = -0.0311$$

$$R_{in-dm} = 2r_{\pi} = 6.66 \text{ k}\Omega$$

$$R_{in-cm} = r_{\pi} + 2(\beta+1)r_o = 32163.33 \text{ k}\Omega$$

Small signal eq. det:

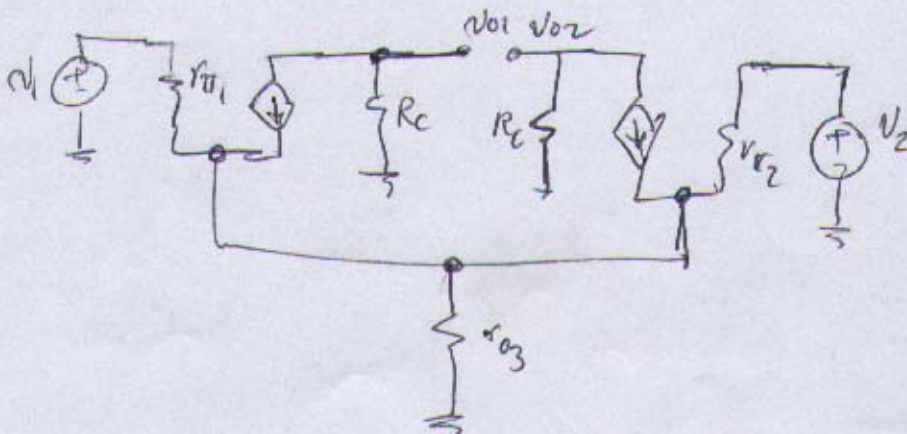

3) The circuit below is to be used as a battery charger. Assume $\beta = 400$, $V_{BE} = 0.7$ V.

a) What would be the battery voltage when it is completely charged?


$$V_{\text{battery max}} = \underline{5.3 \text{ V}}$$

b) What would be the maximum charging current when the battery is completely drained to 0 V?



$$I_{\text{battery max}} = \underline{193 \text{ mA}}$$

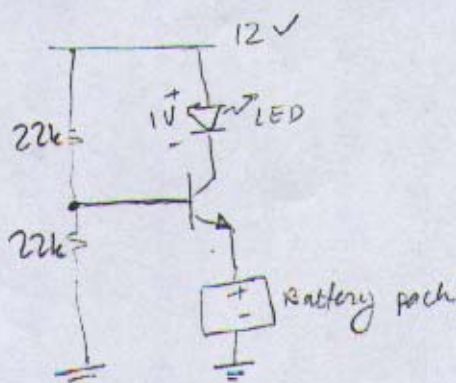c) What must be the minimum power rating of the transistor?

$$P_{\text{min}} = \underline{2.12 \text{ W}}$$


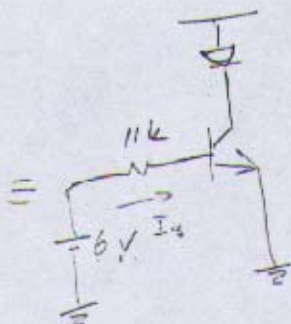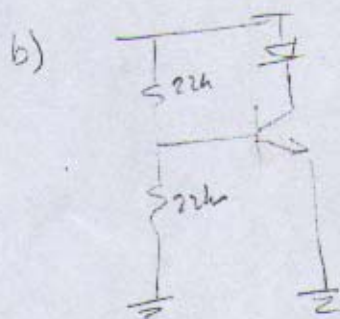
$$\begin{aligned} V_{\text{battery max}} &= V_B - V_{BE} \\ V_B &= 12 \frac{22}{22+22} = 6.0 \text{ V} \end{aligned} \quad \left. \begin{array}{l} \\ \end{array} \right\} V_{\text{battery max}} = 6 - 0.7 = \underline{5.3 \text{ V}}$$



$$I_B = \frac{6 - 0.7}{11 \text{ k}} = \frac{5.3 \text{ V}}{11 \text{ k}} = 0.4818 \text{ mA}$$

$$I_E = (\beta + 1) I_B = 401 \times 0.482 = 193 \text{ mA}$$

c) max possible power dissipation in the transistor.

$$V_{CE \text{ max}} I_{C \text{ max}} = (12 - 1) 0.193 = 2.12 \text{ W}$$

$$\text{min power rating} = \underline{2.12 \text{ W}}$$

$$I_D = 2 \text{ mA}$$

2) For the FET in the circuit below, assume $K = 10 \text{ mA/V}^2$.

a) Find V_p and a small signal equivalent of the amplifier circuit.

b) Find the input resistance of the amplifier.

c) Find the output resistance of the amplifier.

d) Find $\frac{v_o}{v_s}$ voltage gain

$$V_p = -2.44 \text{ V}$$


$$r_{in} = 0.1 \text{ k}\Omega$$

$$r_{out} = 5 \text{ k}\Omega$$

$$\frac{v_o}{v_s} = 14.90$$

S=39

S=47

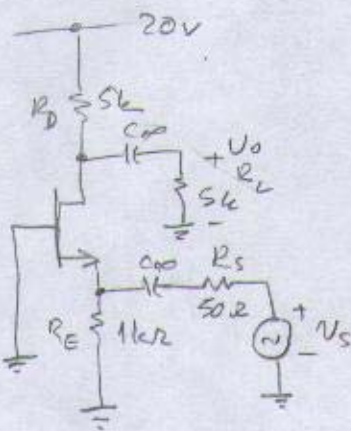

$$a) I_D = 2 \text{ mA}, R_E I_D = 2 \text{ V} \rightarrow$$


$$V_G = 0, V_S = R_E I_D = 2 \text{ V} \rightarrow V_{GS} = -2 \text{ V}$$

$$\text{Constant current mode} \rightarrow I_D = K (V_{GS} - V_p)^2$$

$$2 = 10 (V_{GS} - V_p)^2$$

$$\sqrt{\frac{2}{10}} = V_{GS} - V_p$$
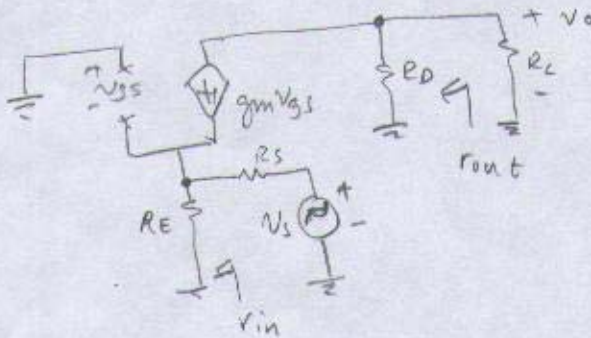
$$V_p = V_{GS} - \sqrt{\frac{2}{10}} = -2 - \sqrt{\frac{2}{10}} = -2.44 \text{ V}$$



$$g_m = 2\sqrt{KI_D} = 2\sqrt{2 \times 10} = 8.94 \text{ mA/V}$$

$$b) r_{in} = R_E \parallel \frac{1}{g_m} = 1 \parallel \frac{1}{8.94} = 0.1 \text{ k}\Omega$$


$$c) r_{out} = R_D = 5 \text{ k}\Omega$$

$$d) \frac{v_o}{v_i} = +g_m R_D \parallel R_L = 8.94 \times 5 \parallel 5 = 22.35$$

$$\frac{v_o}{v_s} = \frac{v_o}{v_i} \frac{r_{in}}{R_S + r_{in}} = 22.35 \frac{100}{50 + 100} = 14.90$$

ID number SOLUTIONS Name: ERRAYA Signature: _____

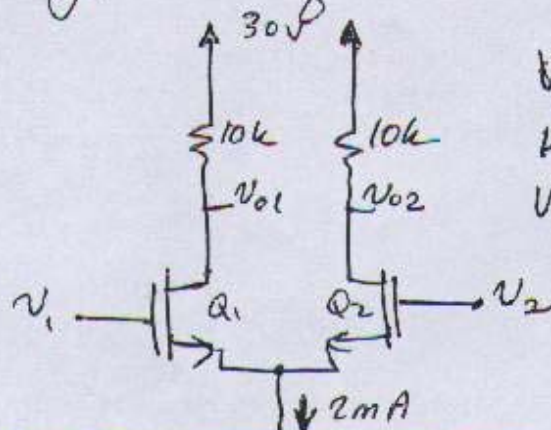- 1) Design a bias circuit for the differential amplifier given below.
- 2) Calculate the diff. and common mode single ended gain using an equivalent circuit. Also find the input resistance.



$$V_{th} = 2V$$

$$K = 10 \text{ mA/V}$$

$$V_A = 500V$$

$$I_D = 1 \text{ mA}$$

$$g_m = 2\sqrt{1 \times 10} = 6.32 \text{ mA/V}$$



Small signal eq. ch

$$A_{dm-se1} = -31.6$$

$$A_{cm-se1} = -0.02$$

$$r_{in-dm} = \infty$$

$$r_{in-cm} = \infty$$

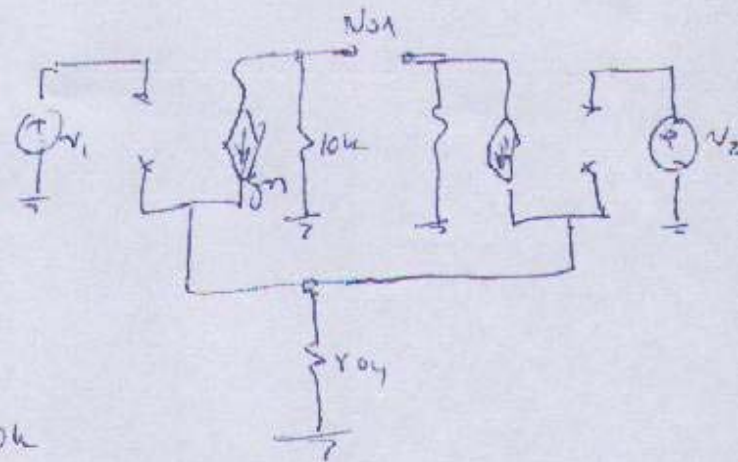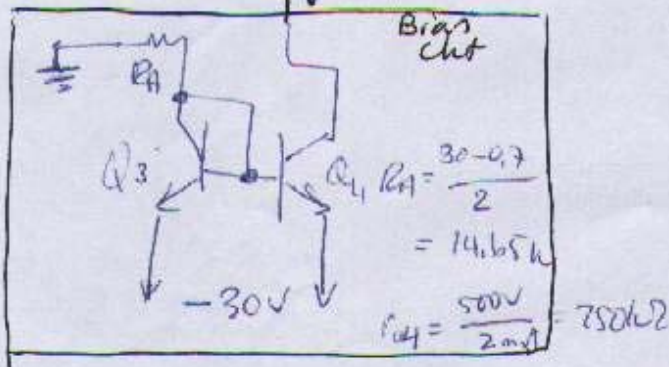

diff mode : gain

$$A_{dm-se1} = -\frac{g_m 10k}{2}$$

$$= -\frac{63.2}{2} = -31.6$$

Common mode gain

$$\frac{-g_m 10k}{(2r_{04} g_m + 1)} = \frac{-63.2}{250 \times 6.32 + 1} = -0.02$$

Since the input current = 0, the input resistance $\rightarrow \infty$



Electronics I * Final Exam * February 1, 2005 * 90 minutes

I have never received or given any unauthorized help with this exam, nor do I have reason to believe that anybody else has.

ID Number: ERIKAYA Name: SOLUTIONS Signature: _____

- 1) The diodes in the circuit below are identical with a reverse saturation current of 10 nA and an ideality factor of 1.4. The input voltage is as shown below. Sketch the output voltage and calculate the peak values.

15 pts

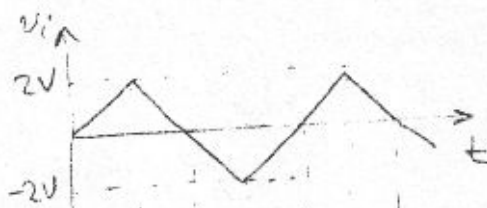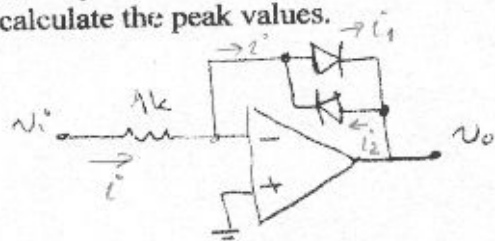

$V_{max} =$ _____
 $V_{min} =$ _____

$$v_i > 0 \rightarrow i_1 = i_2 = I_s (e^{v_o / \eta V_T} - 1) = \frac{v_i}{1k}$$


$$v_o = -\eta V_T \ln\left(\frac{i}{I_s} + 1\right)$$

$$v_i < 0 \rightarrow i = -i_2 = -I_s (e^{v_o / \eta V_T} - 1)$$

$$v_o = \eta V_T \ln\left(\frac{-i}{I_s} + 1\right)$$

$$\eta = 1.4$$


$$I_s = 10 \times 10^{-9} \text{ A}$$

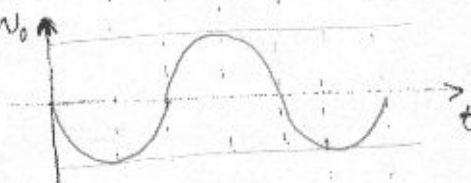

v_i	i	v_o
0	0	0 V
1V	1mA	0.42 V
2V	2mA	0.427 V

- 2) In the circuit below assume R is selected to bias the BJT in active mode. Find the operating point for the transistor. Also find the minimum and maximum values for R to keep the transistor at the same operating point without any damage to any components in the circuit.

15 pts

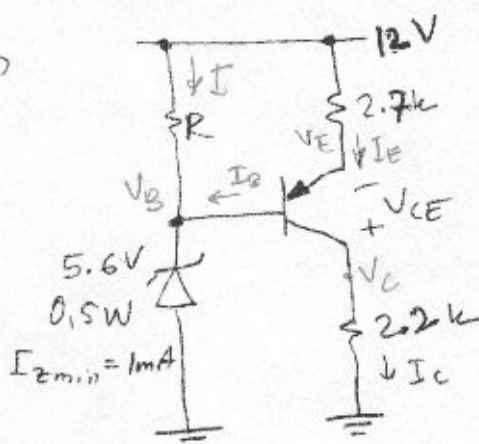

Silicon $V_B = 5.6V$
 $\beta = 300$
 $V_E = 5.6 + 0.7 = 6.3V$
 $I_E = \frac{12 - 6.3}{2.7} = 2.11 \text{ mA}$
 $I_C \approx I_E = 2.11 \text{ mA}$

$$V_{CE} = 12 - 2.2 \times 2.11 = 4.64V$$

$$V_{CE} = V_C - V_E = 4.64 - 6.30 = -1.66V$$

$$I = I_Z - I_B$$

$$I_{Zmin} = 1 \text{ mA}$$

$$I_{Zmax} = \frac{500 \text{ mW}}{5.6 \text{ V}} = 89.285 \text{ mA}$$


$$I_B = \frac{2.11}{300} = 0.007 \text{ mA}$$

$$I_{min} = I_{Zmin} - I_B = 1 - 0.007 = 0.993 \text{ mA} \rightarrow R_{max} = \frac{12 - 5.6}{0.993} = 6.445 \text{ k}\Omega$$

$$I_{max} = I_{Zmax} - I_B = 89.285 - 0.007 = 89.278 \text{ mA}$$

$$R_{min} = \frac{12 - 5.6}{89.278} = 0.0717 \text{ k}\Omega = 71.7 \Omega$$

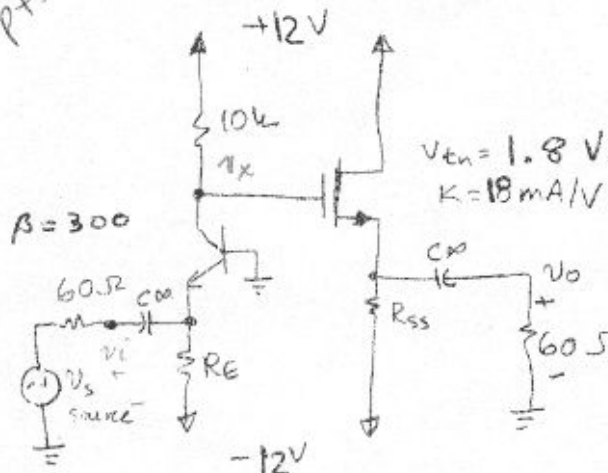- 3) The circuit below is to be used as an impedance matching amplifier. Determine R_E and R_{SS} so that the input resistance as well as the output resistance of the amplifier is 60 ohms. With your design values, what is the voltage gain when this amplifier is placed between a 60-ohm output signal source and a 60 ohm load?



$$r_{in} = R_E \parallel \frac{r_{\pi}}{\beta + 1} \approx \frac{1}{g_{m1}}$$

$$R_E = 27k\Omega$$

$$r_{out} = R_{SS} \parallel \frac{1}{g_{m2}} \approx \frac{1}{g_{m2}}$$

$$R_{SS} = 4.56k\Omega$$

$$v_o/v_s = 41.65$$

$$g_{m1} = g_{m2} = \frac{1}{60\Omega} = \frac{1}{0.06k\Omega} = 16.66 \text{ mA/V}$$

$$g_{m1} = \frac{I_C}{V_T} \rightarrow I_C = g_{m1} V_T = 16.66 \times 0.025 = 0.417 \text{ mA}$$

$$g_{m2} = 2\sqrt{K I_D} \rightarrow g_{m2}^2 = 4K I_D$$

$$I_D = \frac{g_{m2}^2}{4K} = \frac{(16.66)^2}{4 \times 18} = 3.85 \text{ mA}$$

$$I_C \approx I_E = \frac{12 - 0.7}{R_E} \Rightarrow \frac{11.3}{R_E} = 0.417$$

$$R_E = \frac{11.3}{0.417} = 27k\Omega$$

$$V_{GS} = 12 - 10 I_C = 12 - 10 \times 0.417 = 7.83 \text{ V}$$

$$I_D = K (V_{GS} - V_{tn})^2$$

$$V_{GS} = V_{tn} + \sqrt{\frac{I_D}{K}} = 1.8 + \sqrt{\frac{3.85}{18}} = 2.26 \text{ V}$$

$$\frac{v_o}{v_s} = \frac{v_o}{v_x} \cdot \frac{v_x}{v_i} \cdot \frac{v_i}{v_s}$$

$$\frac{v_o}{v_x} = \frac{(R_{SS} \parallel R_L) g_{m2} v_{gs}}{v_{gs} + (R_{SS} \parallel R_L) g_{m2} v_{gs}} \approx$$

$$\frac{0.06 \times 16.66}{1 + 0.06 \times 16.66} = 0.5$$

$$V_S = V_{GS} - V_{GS} = 7.83 - 2.26 = 5.57 \text{ V}$$

$$-12 + R_{SS} I_D = 5.57$$

$$R_{SS} = \frac{5.57 + 12}{I_D} = \frac{17.57}{3.85}$$


$$R_{SS} = 4.56k\Omega$$

$$\frac{v_x}{v_i} = g_{m1} R_C = 16.66 \times 10 = 166.6$$

$$\frac{v_i}{v_s} = \frac{r_{in}}{R_S + r_{in}} = \frac{60}{60 + 60} = \frac{1}{2}$$

$$\frac{v_o}{v_s} = 0.5 \times 166.6 \times 0.5 = 41.65 \text{ V/V}$$

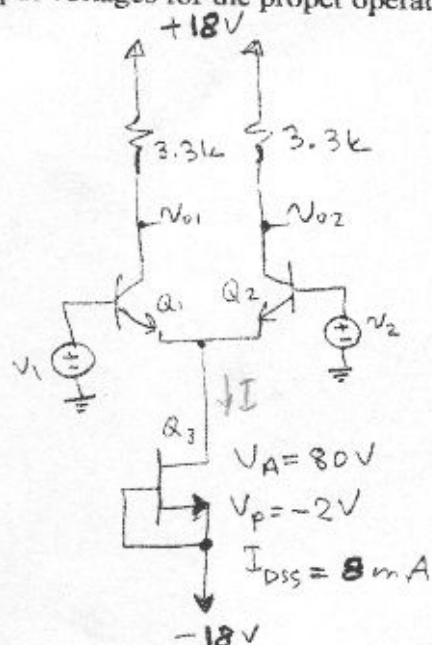4) Draw a small-signal equivalent circuit for the differential amplifier given below. Find the gain, input resistance and output resistance for differential and common modes. Also, find the maximum differential mode input signal amplitude, maximum and minimum common mode input voltages for the proper operation of the circuit.



$$\beta = 250 \text{ for } Q_1, Q_2$$

Silicon BJT:

$$I = 8 \text{ mA} = I_{DSS}$$

$$r_{03} = \frac{80 \text{ V}}{8 \text{ mA}} = 10 \text{ k}\Omega$$

$$I_{C1} = I_{C2} = \frac{I}{2} = 4 \text{ mA}$$

$$g_{m1} = g_{m2} = \frac{4}{0.025} = 160 \text{ mA/V}$$

$$V_{01} = 18 - 4 \times 3.3 = 4.8 \text{ V}$$

$$V_{02} = 4.8 \text{ V (no signal)}$$

$$r_{\pi} = \frac{250}{160} = 1.56 \text{ k}\Omega$$

$$r_{in-dm} = 3.12 \text{ k}\Omega$$

$$r_{in-cm} = 5021 \text{ k}\Omega$$

$$r_{out-se} = 3.3 \text{ k}\Omega$$

$$A_{dm-se} = -264$$

$$A_{cm-se} = 0.164$$

$$\max |v_{idm}| = 0.0163 \text{ V}$$

$$\max(v_{icm}) = 5.3 \text{ V}$$

$$\min(v_{icm}) = -15.3 \text{ V}$$

$$r_{out-se} = 3.3 \text{ k}\Omega$$



differential mode

$$r_{in-dm} = 2r_{\pi} = 2 \times 1.56 = 3.12 \text{ k}\Omega$$

$$A_{dm-se} = -\frac{g_m R_c}{2} = -\frac{160 \times 3.3}{2} = -264$$

max signal amplitude w/o distortion

$$\max |v_{icm}| = \frac{4.3}{264} = 0.0163 \text{ V}$$

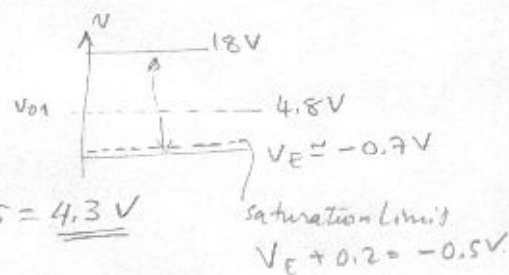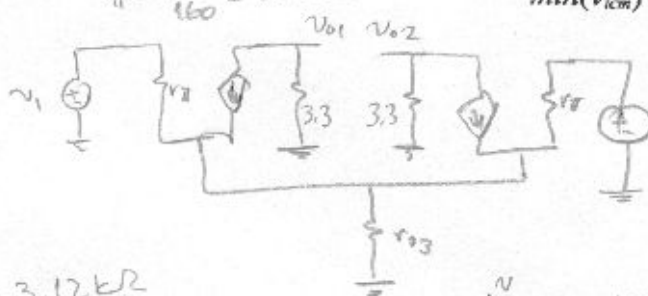

Common mode

$$r_{in-cm} = r_{\pi} + 2(\beta+1)r_{03} = 1.56 + 2 \times 251 \times 10 = 5021.56 \text{ k}\Omega$$

$$A_{cm-se} = \frac{-\beta R_c}{r_{\pi} + 2(\beta+1)r_{03}} = \frac{-250 \times 3.3}{5021.56} = 0.164$$

$$\max(v_{icm}) = V_{01} - V_{CESAT} + V_{BE} = 4.8 - 0.2 + 0.7 = 5.3 \text{ V}$$

$$\min(v_{icm}) = -18 \text{ V} + V_{DSmin} + V_{BE} = -18 + 2 + 0.7 = -15.3 \text{ V}$$

$$V_{DSmin} = V_{GS} - V_{th} = 0 - (-2) = 2 \text{ V}$$