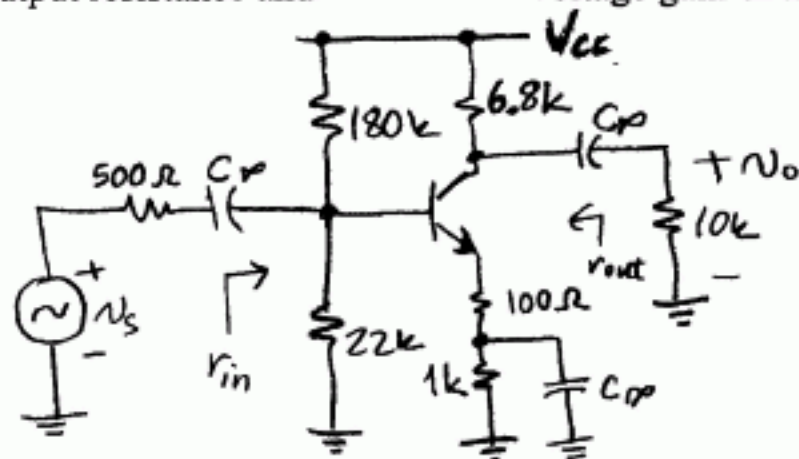


I have never given nor received any unauthorized help with this exam, nor do I have reason to believe that anybody else has.

ID number: SOLUTIONS Name: ERKAYA Signature: _____

- 1) Obtain a small-signal equivalent circuit for the amplifier given below. Then find the input resistance, output resistance and voltage gain of the amplifier.



$$I_C = 1.5 \text{ mA}$$

$$\beta = 240$$


$$g_m = \frac{I_C}{V_T} = \frac{1.5}{0.025} = 60 \text{ mA/V}$$

$$r_{\pi} = \frac{\beta}{g_m} = \frac{240}{60} = 4 \text{ k}\Omega$$

$$r_{in} = 11.54 \text{ k}\Omega$$

$$r_{out} = 6.8 \text{ k}\Omega$$

$$v_o/v_s = -33.13$$

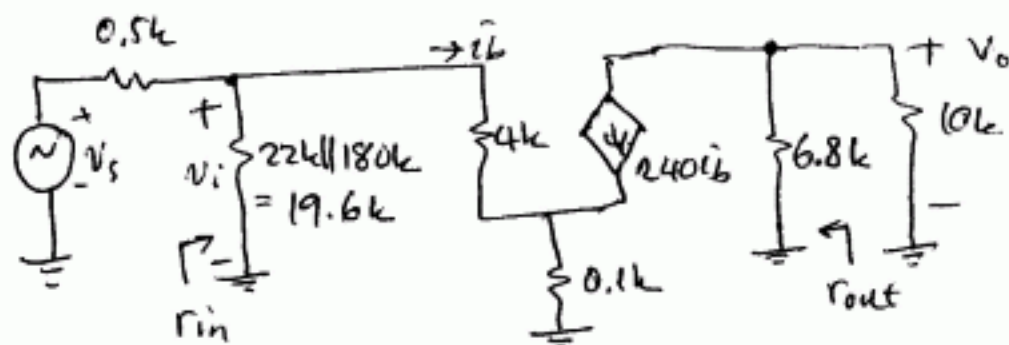

$$r_{in} = 19.6 \text{ k} \parallel [4 \text{ k} + 0.1(240+1)] = 19.6 \text{ k} \parallel 28.1 \text{ k} = 11.54 \text{ k}$$


$$r_{out} = 6.8 \text{ k}$$

$$\left. \begin{aligned} v_o &= -240 i_b (6.8 \parallel 10) \\ v_i &= [4 \text{ k} + 0.1(240+1)] i_b \end{aligned} \right\} \frac{v_o}{v_i} = \frac{-240 (6.8 \parallel 10)}{28.1} = -34.57$$

$$\frac{v_o}{v_s} = -34.57 \frac{11.54}{0.5 + 11.54} = -33.13$$

2) Find the operating points of the bipolar junction transistors in the circuits given below:

$$\beta = 250, V_{BE} = 0.7V$$

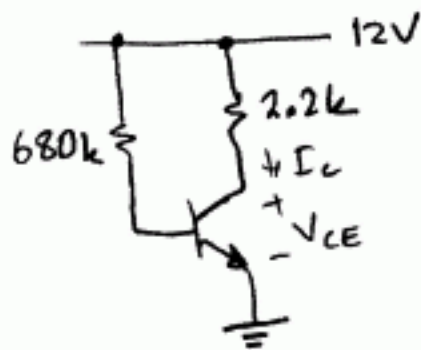


$$I_c = \frac{4.154 \text{ mA}}{V_{CE} = 2.86}$$

$$I_B = \frac{12 - 0.7}{680k} = 0.0166 \text{ mA}$$

$$I_c = \beta I_B = 4.154 \text{ mA}$$
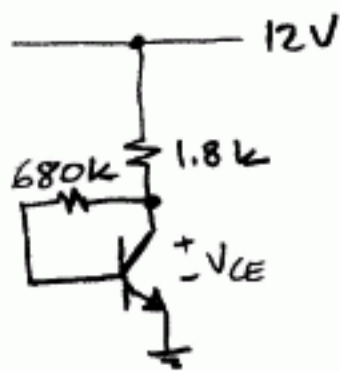
$$V_{CE} = 12 - 2.2 \times 4.154 = 2.86 \text{ V}$$




$$I_c = 2.5 \text{ mA}$$

$$V_{CE} = 7.5 \text{ V}$$

$$I_B = \frac{12 - 0.7}{680 + 251 \times 1.8} = 0.01 \text{ mA}$$

$$I_c = 250 \times I_B = 2.5 \text{ mA}$$
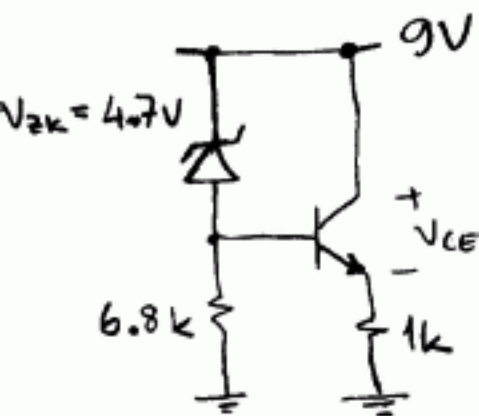
$$V_{CE} = 12 - 1.8 \times 2.5 = 7.5 \text{ V}$$



$$I_c = 3.6 \text{ mA}$$


$$V_{CE} = 5.4 \text{ V}$$

$$V_B = 9 - 4.7 = 4.3 \text{ V}$$

$$V_E = V_B - V_{BE} = 4.3 - 0.7 = 3.6 \text{ V}$$

$$I_E = \frac{3.6 \text{ V}}{1k} = 3.6 \text{ mA}, I_c \approx I_E$$

$$V_{CE} = 9 - 3.6 = 5.4 \text{ V}$$

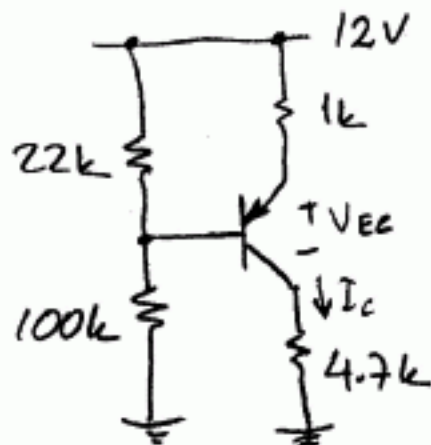

$$I_c = 1.47 \text{ mA}$$

$$V_{CE} = 3.65 \text{ V}$$

$$V_B = 12 \times \frac{100}{100 + 22} = 9.83 \text{ V}$$

$$V_E = V_B - 0.7 = 10.53 \text{ V}$$


$$I_E = \frac{12 - 10.53}{1k} = 1.47 \text{ mA}$$

$$I_c \approx I_E$$

$$V_{EC} = 12 - 1 \times 1.47 - 4.7 \times 1.47$$

$$V_{EC} = 3.65 \text{ V}$$

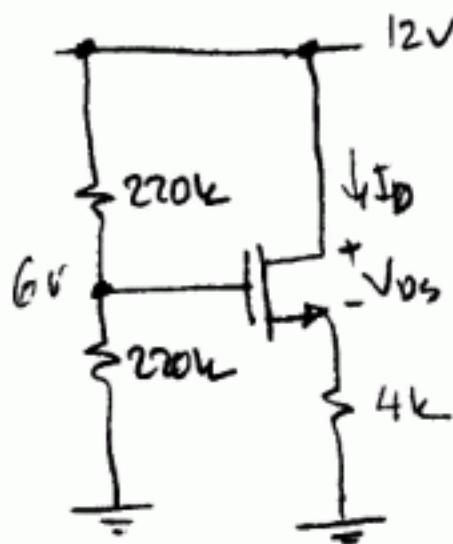3) Find the operating points of the field effect transistors in the circuits given below:



$$K = 1 \text{ mA/V}^2$$

$$V_t = 1 \text{ V}$$

$$I_D = 1 \text{ mA}$$

$$V_{DS} = 8 \text{ V}$$

$$V_G = 12 \frac{220}{220+220} = 6 \text{ V}$$

$$4I_D + V_{GS} = 6$$

$$4 \times 1 (V_{GS} - V_t)^2 + V_{GS} - 6 = 0$$

$$4(V_{GS}^2 - 2V_{GS}V_t + V_t^2) + V_{GS} - 6 = 0$$

$$4V_{GS}^2 - 7V_{GS} + 4 - 6 = 0$$


$$V_{GS1} = \frac{7 + \sqrt{49 - 32}}{8} = 2 \text{ valid}$$

$$V_{GS2} = \frac{7 - \sqrt{49 - 32}}{8} = -\frac{2}{8} < V_t$$

not valid

$$I_D = 1(2 - 1)^2 = 1 \text{ mA}$$

$$V_{DS} = 12 - 4 = 8 \text{ V}$$

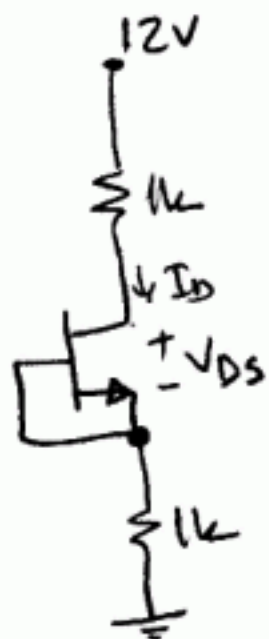

$$I_{DSS} = 2 \text{ mA}$$

$$V_p = -2 \text{ V}$$


$$I_D = 2 \text{ mA}$$

$$V_{DS} = 8 \text{ V}$$

$$V_{GS} = 0$$

By definition of I_{DSS} , $I_{D0} = I_{DSS} = 2 \text{ mA}$

$$V_{DS} = 12 - 2(1 + 1) = 8 \text{ V}$$

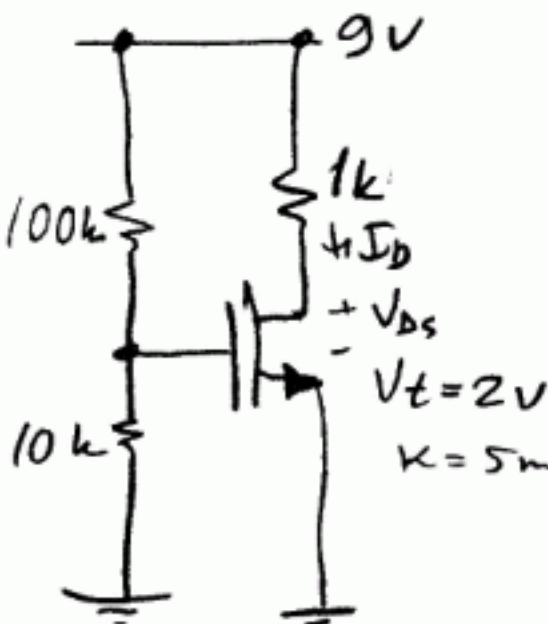

$$I_D = 0$$

$$V_{DS} = 9 \text{ V}$$

$$V_{GS} = 9 \frac{10}{10+100} = 0.82 \text{ V} < V_t = 2 \text{ V}$$

$$\text{CUTOFF} \rightarrow I_D = 0$$

$$V_{DS} = 9 - I_D \times 1 = 9 \text{ V}$$

Dec 13, 2005

Electronics I - Midterm 2


60 minutes

Name: ERIKAYAID number: SOLUTIONS

Signature: _____

- 1) The circuit below is to be used as a constant current battery charger. The positions of the switch S corresponds to the following current values:

Position	Current
1	100 mA
2	200 mA
3	300 mA
4	400 mA

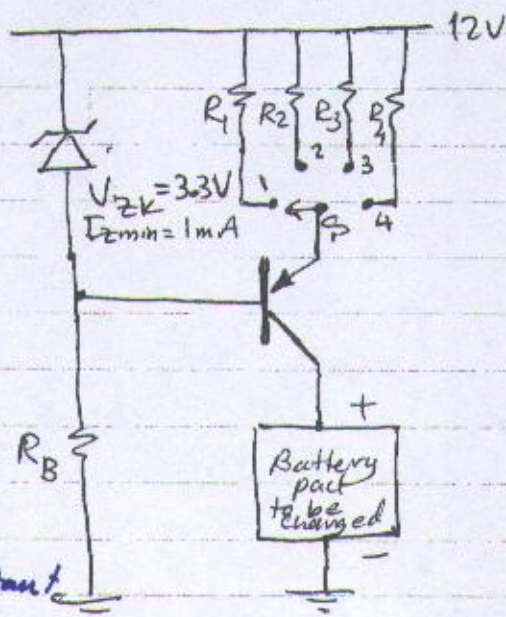Silicon BJT
 $\beta = 70$

$$R_{Bmax} = \frac{1.29 \text{ k}\Omega}{\beta} = 1.29 \text{ k}\Omega$$

$$R_1 = 26 \Omega$$

$$R_2 = 13 \Omega$$

$$R_3 = 8.66 \Omega$$

$$R_4 = 6.5 \Omega$$

- a) What could be the max value for R_B ?

The current in R_B is constant
It must be at least

$$I_{Zmin} + I_{Bmax} = 1 + \frac{400}{70} = 6.71 \text{ mA}, \quad R_{Bmax} = \frac{12 - 3.3}{6.71} = 1.29 \text{ k}\Omega$$

- b) What should be the resistor values R_1, R_2, R_3, R_4 ?

The voltage across R_1, R_2, R_3, R_4 is $3.3 - 0.7 = 2.6 \text{ V}$

$$R_1 = \frac{2.6}{0.1} = 26 \Omega, \quad R_2 = \frac{2.6}{0.2} = 13 \Omega, \quad R_3 = \frac{2.6}{0.3} = 8.66 \Omega, \quad R_4 = \frac{2.6}{0.4} = 6.5 \Omega$$

- c) What is the maximum voltage that the rechargeable battery pack may have?

$$V_{Cmax} = V_E - V_{CESAT} = 12 - 2.6 - 0.2 = 9.2 \text{ V}, \quad V_{battery max} = 9.2 \text{ V}$$

- d) What must be the power rating of the BJT?

$$P_{max} = |I_{Cmax} V_{CEmax}| = 0.4 \times (12 - 2.6) = \underline{\underline{3.76 \text{ W}}}$$

2) Find the operating point of the transistor given in the circuit below. Also find a small signal equivalent circuit, input resistance, output resistance and voltage gain for the amplifier.

$$V_{BE} = 0.7V, \beta = 250, V_T = 0.025V$$

$$I_C = 1.13mA$$

$$r_{in} = 22\Omega$$



$$I_C \approx I_E = \frac{-0.7 - (-12)}{10} = 1.13mA$$

$$r_{out} = 5k$$

$$\frac{V_o}{V_s} = 75$$

$$g_m = \frac{I_C}{V_T} = \frac{1.13}{0.025} = 45.2mA/V$$
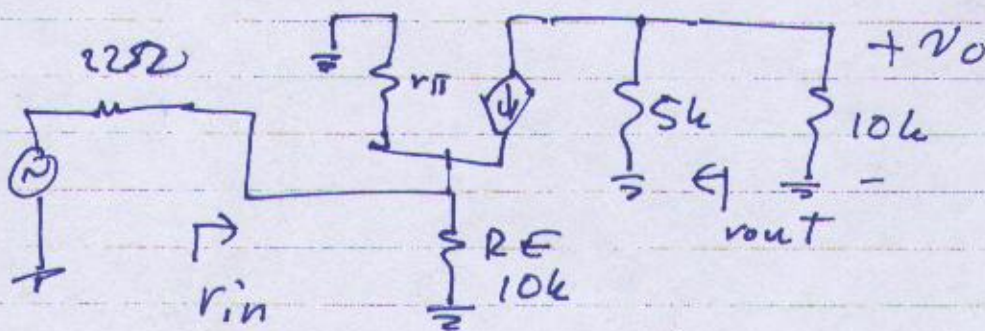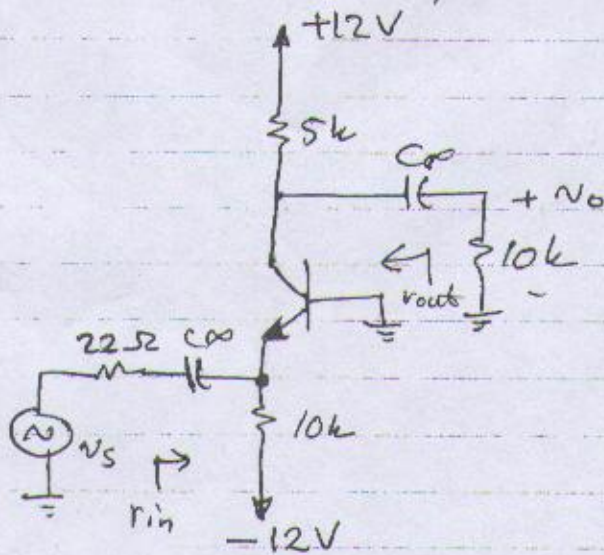
$$r_{\pi} = \frac{\beta}{g_m} = \frac{250}{45.2} = 5.53k\Omega$$



$$r_{in} = 10k \parallel \frac{r_{\pi}}{\beta + 1} = 10k \parallel \frac{5.53k}{251} = 0.022\Omega$$

$$r_{out} = 5k$$


$$\frac{V_o}{V_i} = g_m (R_C \parallel R_L) = 45.2 \times 5 \parallel 10 = 150$$

$$\frac{V_o}{V_s} = \frac{r_{in}}{R_s + r_{in}} = \frac{22}{22 + 22} = \frac{1}{2}$$

$$\frac{V_o}{V_s} = 150 \times \frac{1}{2} = 75$$

3) Find the operating points for the FETs given below:


a)

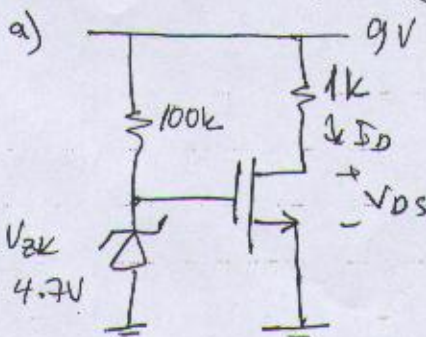

$V_t = 2.5V$
 $K = 0.5 \text{ mA/V}^2$
 $V_{GS} = 4.7V$
 $I_D = \underline{2.42 \text{ mA}}$
 $V_{DS} = \underline{6.58V}$
 $I_D = 0.5 (4.7 - 2.5)^2 = 2.42 \text{ mA}$
 $V_{GS} = 9 - 1 \times 2.42 = 6.58V$


Verification $V_{DS} \geq V_{GS} - V_t = 2.2V$
 $6.58 > 2.2$ assumption is valid.

b)

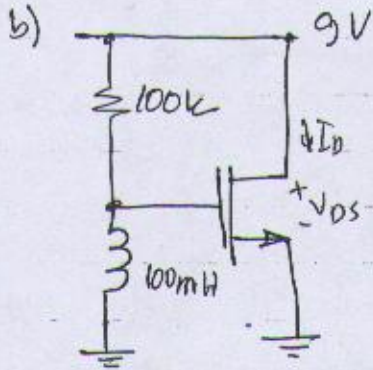

$V_t = 2.5V$
 $K = 0.5 \text{ mA/V}^2$
 $I_D = \underline{0}$
 $V_{DS} = \underline{9V}$

$V_{GS} = 0, < V_t \rightarrow I_D = 0$

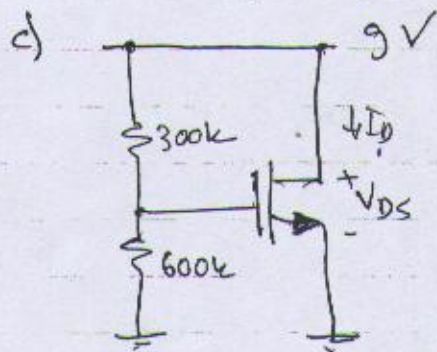


$V_t = 2.5V$
 $K = 0.5 \text{ mA/V}^2$

$I_D = \underline{6.12 \text{ mA}}$
 $V_{DS} = \underline{9V}$

$V_{GS} = 9 \frac{600}{300 + 600} = 6V$

$I_D = 0.5 (6 - 2.5)^2 = 6.12 \text{ mA}$

$V_{DS} = 9V > 6 - 2.5 = 3.5$ ✓

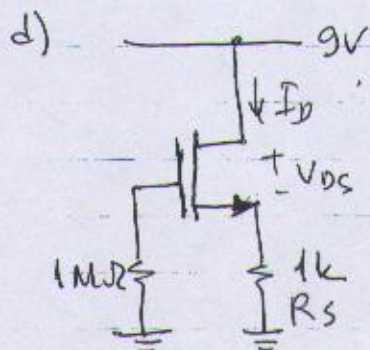

$V_t = -1V$
 $K = 0.5 \text{ mA/V}^2$

$I_D = \underline{0.27 \text{ mA}}$
 $V_{DS} = \underline{8.73V}$

$V_G = 0, V_S = I_D R_S$

$V_{GS} = V_G - V_S = -I_D R_S$

$V_{GS} = -K (V_{GS} - V_t)^2 R_S$

$V_{GS} + K R_S (V_{GS}^2 - 2 V_{GS} V_t + V_t^2) = 0$

$2 V_{GS} + V_{GS}^2 + 2 V_{GS} + 1 = 0$

$V_{GS1,2} = \frac{-4 \pm \sqrt{16 - 4}}{2} = -2 \pm \sqrt{3}$

$V_{GS}^2 + 4 V_{GS} + 1 = 0$

$I_D = \frac{+0.27}{1k} = 0.27 \text{ mA}$

$-2 - \sqrt{3} < V_t = -1$ not valid

$-2 + \sqrt{3} = 0.27V$