

ERKAYA


I have neither given nor received unauthorized help with this exam.

ID: _____ Name: SOLUTIONS Signature: _____ Grade: _____

1) (25 pts) A BJT amplifier circuit is given below. ($h_{FE} = 499$, $|V_{EB}| = 0.7V$, $V_T = 25mV$)

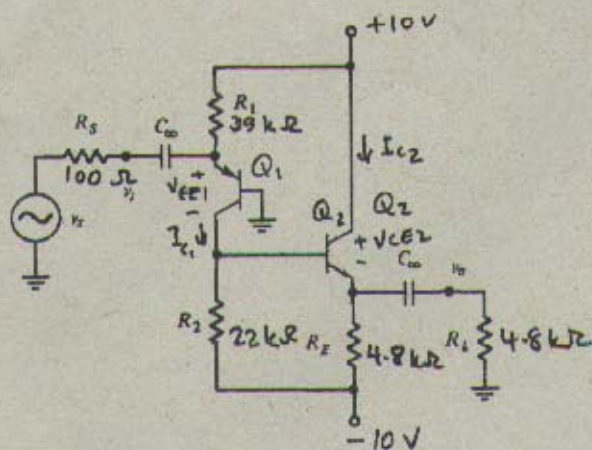a) Draw the DC equivalent circuit and find the operating points of the transistors.

$I_{C1} = 0.238 \text{ mA}$ $I_{C2} = 0.946 \text{ mA}$ $V_{EC1} = 5.46 \text{ V}$ $V_{CE2} = 15.46 \text{ V}$



$V_{E1} = 0.7V$

$I_{E1} = \frac{10 - 0.7}{39k} = 0.2385 \text{ mA}$

$I_{C1} \approx I_{E1} = 0.238 \text{ mA}$

ignoring I_{B2} , $V_{C1} = -10 + I_{C1} \cdot 22k$
 $= -10 + 0.238 \times 22k$
 $= -4.76 \text{ V}$

$V_{EC1} = V_{E1} - V_{C1}$
 $= 0.7 - (-4.76) = 5.46 \text{ V}$


$V_{E2} = V_{C1} - 0.7 = -4.76 - 0.7 = -5.46 \text{ V}$

$I_{E2} = \frac{-5.46 - (-10)}{4.8} = 0.946 \text{ mA}$


$I_{B2} = \frac{0.946}{499} = 0.0019 \text{ mA}$

$I_{C2} \approx I_{E2} = 0.946 \text{ mA}$

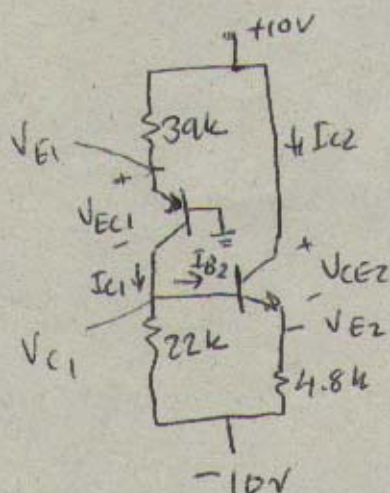$V_{CE2} = 10 - V_{E2} = 10 - (-5.46) = 15.46 \text{ V}$



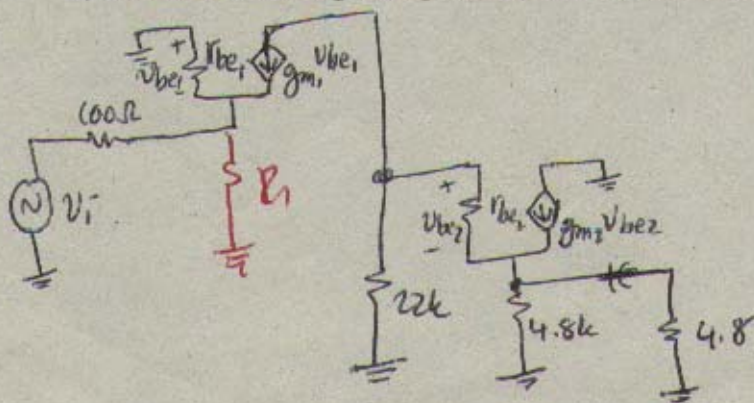b) Obtain a small-signal equivalent of the circuit (including small signal models of the transistors).




$g_{m1} = \frac{I_{C1}}{V_T} = \frac{0.238}{0.025} = 9.52 \text{ mA/V}$

$r_{be1} = \frac{\beta}{g_m} = \frac{499}{9.52} = 52.42 \text{ k}\Omega$

$g_{m2} = \frac{I_{C2}}{V_T} = \frac{0.946}{0.025} = 37.84 \text{ mA/V}$

$r_{be2} = \frac{499}{37.84} = 13.18 \text{ k}\Omega$

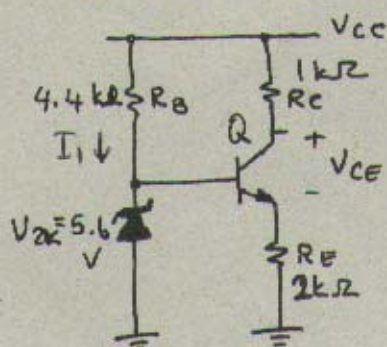2) (25 pts) a) Find the operating point of the bipolar transistor in the circuit below. Assume $V_{CC} = 10\text{ V}$, $V_{BE} = 0.7\text{ V}$, $h_{FE} = 100$.



Expected operation

$$I_C = 2.4\text{ mA} \quad V_{CE} = 2.7\text{ V}$$

$$V_B = V_{ZK} = 5.6\text{ V}$$

$$V_E = 5.6 - 0.7 = 4.9\text{ V} \rightarrow I_E = \frac{4.9}{2\text{ k}} = 2.45\text{ mA}$$

$$I_C \approx \frac{100}{101} 2.45 = 2.40\text{ mA}, \quad I_B = 0.04\text{ mA}$$

$I_B \ll I_1 \Rightarrow$ Zener diode is in breakdown
expected operation is valid

$$I_1 = \frac{10 - 5.6}{4.4\text{ k}} = 1\text{ mA}$$

$$V_{CE} = 10 - 1\text{ k} \cdot 2.4 - 2\text{ k} \cdot 2.45 = 2.7\text{ V}$$

b) What will be the values of I_C and V_{CE} if the supply voltage V_{CC} is doubled?

$$I_C = 2.4\text{ mA} \quad V_{CE} = 12.7\text{ V}$$

$$V_B = V_{ZK} = 5.6\text{ V} \rightarrow V_E = 4.9\text{ V} \rightarrow I_E = 2.45\text{ mA}$$

the same I_C as above

$$V_{CE} = 20 - 2.4 - 4.9 = 12.7\text{ V}$$

c) What will be the values of I_C and V_{CE} if the supply voltage V_{CC} is halved? ($V_{CC} = 5\text{ V}$)

$V_{CC} = 5\text{ V} \Rightarrow$ Zener open ckt

$$I_C = 1.45\text{ mA} \quad V_{CE} = 0.2\text{ V}$$

assume active mode: $I_B = \frac{5 - 0.7}{2(101) + 4.4} = 0.0208\text{ mA}, \quad I_C = 2.08\text{ mA}$

$$V_E \approx V_{CC} - I_C R_C - I_E R_E = 5 - 1 \times 2.08 - 2 \times 2.08 = -1.24\text{ V} < 0$$

saturation $\rightarrow V_{CE} = V_{CE\text{SAT}} = 0.2\text{ V}, \quad I_C \neq 2.08\text{ mA}$

$$(I_C + I_B)2 + 0.7 + 4.4 I_B = 5\text{ V}, \quad (I_C + I_B)2 + 0.2 + I_C = 5\text{ V}$$

d) What will be the values of I_C and V_{CE} if $h_{FE} = 500$? ($V_{CC} = 15\text{ V}$)

$$I_C = 2.45\text{ mA} \quad V_{CE} = 7.65\text{ V}$$

$$d) \quad V_B = V_{ZK} \rightarrow V_E = 4.9$$

$$I_E = 2.45\text{ mA}$$

$$I_C = 2.45\text{ mA} \quad \text{Same as in (a)}$$

$$V_{CE} \leq 15 - 2.45(1+2) = 7.65\text{ V}$$

$$(6.4 I_B + 2 I_C = 4.3\text{ V}) \quad (3)$$

$$(2 I_B + 3 I_C = 4.8\text{ V}) \quad (2)$$

$$15.2 I_B = 3.3$$


$$I_B = \frac{3.3}{15.2} = 0.2171\text{ mA}$$

$$V_E = 5 - 4.4 \times 0.2171 - 0.7 = 3.34\text{ V}$$

$$I_C = \frac{5 - (V_E + 0.2)}{1} = \frac{5 - 3.54}{1} = 1.45\text{ mA}$$

3) (25 pts) Design a bias circuit to have the operating point of a PNP bipolar transistor to be $V_{EC} = 5\text{ V}$, $I_C = 2\text{ mA}$. Any circuit that works is acceptable. (Assume $\beta = 200$, $V_{EB} = 0.7\text{ V}$)

7-29

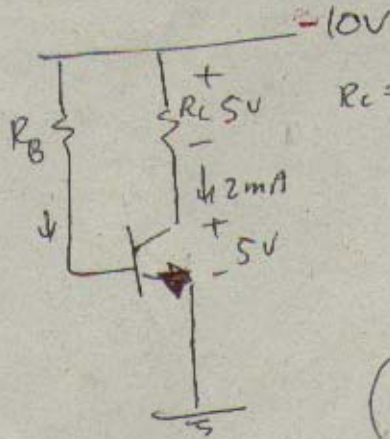

$$R_C = \frac{5}{2} = 2.5\text{ k}\Omega$$

$$I_B = \frac{2}{200} = \frac{1}{100}\text{ mA}$$



$$R_B = \frac{10 - 0.7}{I_B} = \frac{9.3}{\frac{1}{100}} = 930\text{ k}\Omega$$

(no unique solution)

7-31

2

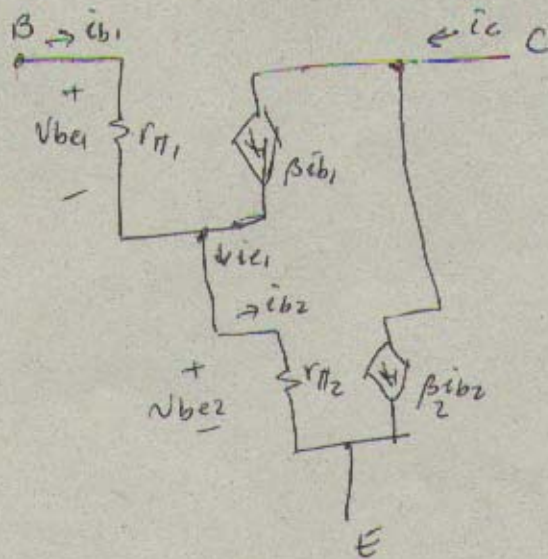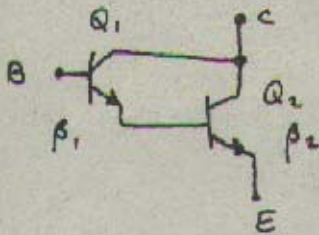4. (25 pts) Sometimes, a high- β transistor is needed for applications. Two transistors are connected as shown below and used as a single transistor. This is also known as Darlington pair. Obtain a small signal model for the Darlington pair. (Reduce it to a resistor and a current source)



$$V_{be1} = i_{b1} r_{\pi 1}$$


$$V_{be2} = i_{b2} r_{\pi 2}$$

$$i_{b2} = (\beta_1 + 1) i_{b1}$$

$$V_{be2} = r_{\pi 2} (\beta_1 + 1) i_{b1}$$

$$V_{be} = V_{be1} + V_{be2} = i_{b1} [r_{\pi 1} + (\beta_1 + 1) r_{\pi 2}]$$
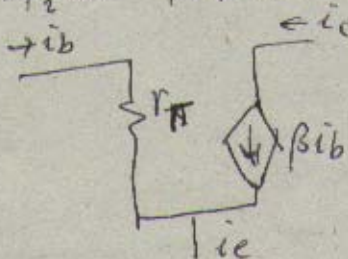
$$i_c = \beta_1 i_{b1} + \beta_2 i_{b2} = \beta_1 i_{b1} + (\beta_1 + 1) i_{b1} \beta_2 = i_{b1} (\beta_1 + \beta_1 \beta_2 + \beta_2)$$



$$r_{\pi} = (\beta_1 + 1) r_{\pi 2} + r_{\pi 1}$$

$$\beta = (\beta_1 + \beta_1 \beta_2 + \beta_2)$$

$$r_{\pi 1} = \frac{V_T}{I_{B1}}$$

$$r_{\pi 2} = \frac{V_T}{I_{B2}} = \frac{V_T}{(\beta_1 + 1) I_{B1}}$$

$$r_{\pi 2} = \frac{r_{\pi 1}}{(\beta_1 + 1)}$$


$$r_{\pi} = \frac{(\beta_1 + 1) r_{\pi 1}}{(\beta_1 + 1)} = r_{\pi 1} = 2 r_{\pi 1} = 2 \frac{V_T}{I_{B1}}$$

7-37

6

ID Number: _____ Name: SOLUTIONS Signature: _____

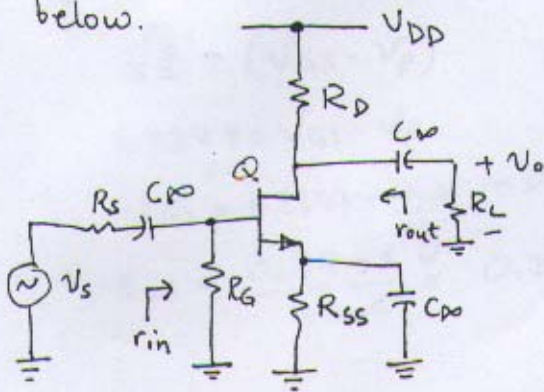- 1) Find the operating point of the FET in the circuit below.



Assume the following

$$V_{DD} = 12\text{ V}$$

$$V_p = -2\text{ V}$$

$$K = 2\text{ mA/V}^2$$

$$R_{ss} = 0.5\text{ k}\Omega$$

$$R_s = 1\text{ k}\Omega$$

$$R_g = 1\text{ M}\Omega$$

$$R_D = 3.8\text{ k}\Omega$$

$$R_L = 10\text{ k}\Omega$$

$$I_D = 2\text{ mA}$$

$$V_{DS} = 3.4\text{ V}$$

from the cut

$$I_D R_{ss} + V_{GS} = 0 \Rightarrow I_D = -\frac{V_{GS}}{R_{ss}}$$

also assume

$$I_D = K(V_{GS} - V_p)^2$$

$$K(V_{GS}^2 - 2V_p V_{GS} + V_p^2) = -\frac{V_{GS}}{R_{ss}}$$

$$K R_{ss} (V_{GS}^2 - 2V_p V_{GS} + V_p^2) + V_{GS} = 0$$

Substitute the numerical values $\rightarrow$

$$K R_{ss} = 1$$

$$V_p^2 = 4$$

$$V_{GS}^2 + 5V_{GS} + 4 = 0 \quad \frac{-b \pm \sqrt{b^2 - 4ac}}{2a} = \frac{-5 \pm \sqrt{25 - 16}}{2} = \frac{-5 \pm 3}{2}$$

$$V_{GS1} = -4, \quad V_{GS2} = -1$$

 $\uparrow$ not valid

because

it is less than V_p $\leftarrow$ valid.

$$I_D = 2(-1 + 2)^2 = 2\text{ mA}$$

$$V_{DS} = V_{DD} - I_D(R_D + R_{ss}) = 12 - 2(3.8 + 0.5) = 3.4\text{ V}$$

verify assumption $\rightarrow V_{DS} > V_{GS} - V_p = -1 + 2 = +1$
 $3.4 > +1 \quad \checkmark$ Cut-off: $V_{GS} < V_p, \quad I_D = 0$ Linear mode: $V_{GS} > V_p, \quad V_{DS} < V_{GS} - V_p$ constant current mode: $V_{GS} > V_p, \quad V_{DS} > V_{GS} - V_p$

$$I_D = K(V_{GS} - V_p)^2$$

$$I_D = K[2(V_{GS} - V_p)V_{DS} - V_{DS}^2]$$

2) In the amplifier circuit of question 1, V_{DD} and R_{SS} are changed (40pts) to have $I_D = 3\text{mA}$ and $V_{DS} = 5\text{V}$.

a) What must be the new values of R_{SS} and V_{DD}

$$I_D = 3\text{mA} = 2(V_{GS} - V_P)^2$$

$$\sqrt{\frac{3}{2}} = (V_{GS} - V_P)$$

$$1.2247 = V_{GS} - V_P$$

$$V_{GS} = 1.2247 - 2 = -0.7753\text{V}$$

$$R_{SS} = \frac{0.7753\text{V}}{3\text{mA}} = 0.258\text{k}\Omega$$


$$R_{SS} = 0.258\text{k}\Omega$$

$$V_{DD} = 17.17\text{V}$$

$$V_{DD} = 0.7753 + 5 + 3 \times 3.8 = 17.17\text{V}$$

b) Draw a small-signal equivalent ckt for the amplifier

$$g_m = 4.899\text{mA/V}$$

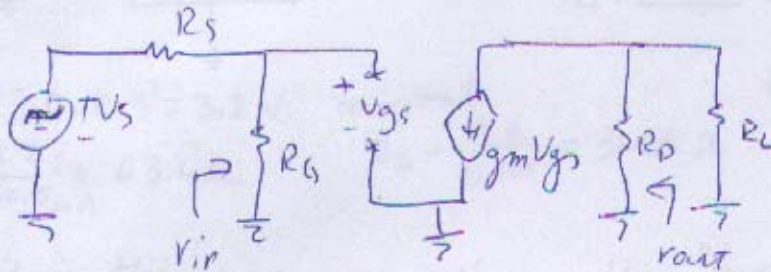

$$g_m = 2\sqrt{K I_D} = 2\sqrt{2 \times 3} = 4.899\text{mA/V}$$

c) Find the input resistance, output resistance and the gain v_o/v_s of the amplifier circuit.

$$r_{in} = R_G = 1\text{M}\Omega$$

$$r_{out} = R_D = 3.8\text{k}\Omega$$

$$\frac{v_o}{v_s} = -g_m (R_D || R_L) \frac{r_{in}}{R_s + r_{in}}$$

$$= -4.89 (3.8 || 10) \frac{1000}{1 + 1000} = -13.47$$


$$r_{in} = 1\text{M}\Omega$$

$$r_{out} = 3.8\text{k}\Omega$$

$$\frac{v_o}{v_s} = -13.47$$

- 3) The following ckt is to be used as a constant-current battery charger. The positions of the switch S corresponds to the following current values:

Position	1	2	3	4
Current	50mA	100mA	200mA	400mA

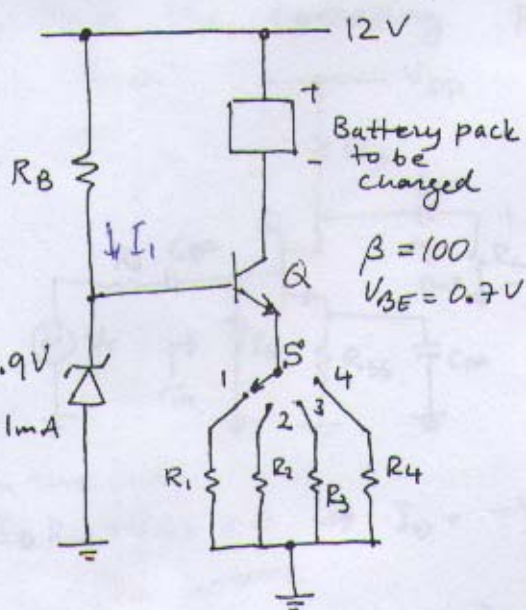

- a) Determine the max value for R_B

$$R_{B_{max}} = \underline{1.62 k\Omega}$$

$$I_{B_{max}} = \frac{I_{C_{max}}}{\beta} = \frac{400}{100} = 4 \text{ mA}$$

$$I_1 = I_B + I_Z = 4 + 1 = 5 \text{ mA}$$

$$R_{B_{max}} = \frac{12 - 3.9}{5 \text{ mA}} = 1.62 k\Omega$$

- b) Determine the resistor values:

$$R_1 = \underline{63.4 \Omega} \quad R_2 = \underline{31.68 \Omega} \quad R_3 = \underline{15.84 \Omega} \quad R_4 = \underline{7.92 \Omega}$$

$$R_3 = \frac{3.2}{0.202} = 15.84 \Omega$$

$$R_4 = \frac{3.2}{0.404} = 7.92 \Omega$$

$$V_E = 3.9 - 0.7 = 3.2 \text{ V constant}$$

$$R_1 = \frac{3.2 \text{ V}}{50.5 \text{ mA}} = 63.4 \Omega$$

$$R_2 = \frac{3.2}{0.101} = 31.68 \Omega$$

- c) What is the maximum voltage the "rechargeable battery pack" may have?

$$V_{\text{Battery max}} = \underline{8.6}$$

Q must be in active mode at all times $\rightarrow V_{CE} \geq V_{CE_{sat}} \approx 0.2 \text{ V}$

$$V_{\text{battery pack}} \leq V_{DD} - V_E - V_{CE_{sat}} = 12 - 3.2 - 0.2 = 8.6 \text{ V}$$

- d) What must be the power rating of the BJT.

$$P_{Q_{max}} \equiv V_{CE_{max}} I_{C_{max}} = 8.8 \times 0.4 = 3.52 \text{ W.}$$

possible

$$V_{CE_{max}} = 12 - 3.2 = 8.8 \text{ V}$$

$$I_{C_{max}} = 400 \text{ mA}$$

The power rating must be greater than 3.52 W

$$I_D = 2 \text{ mA}$$

2) For the FET in the circuit below, assume $K = 10 \text{ mA/V}^2$.

a) Find V_P and a small signal equivalent of the amplifier circuit.

b) Find the input resistance of the amplifier.

c) Find the output resistance of the amplifier.

d) Find $\frac{v_o}{v_s}$ voltage gain

$$V_P = -2.44 \text{ V}$$


$$r_{in} = 0.1 \text{ k}\Omega$$

$$r_{out} = 5 \text{ k}\Omega$$

$$\frac{v_o}{v_s} = 14.90$$

S=39

S=47

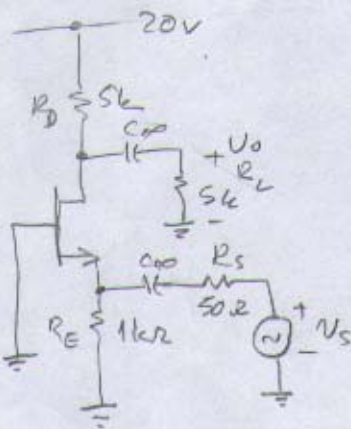

$$a) I_D = 2 \text{ mA}, R_E I_D = 2 \text{ V} \Rightarrow$$


$$V_G = 0, V_S = R_E I_D = 2 \text{ V} \rightarrow V_{GS} = -2 \text{ V}$$

$$\text{Constant current mode} \rightarrow I_D = K (V_{GS} - V_P)^2$$

$$2 = 10 (V_{GS} - V_P)^2$$

$$\sqrt{\frac{2}{10}} = V_{GS} - V_P$$
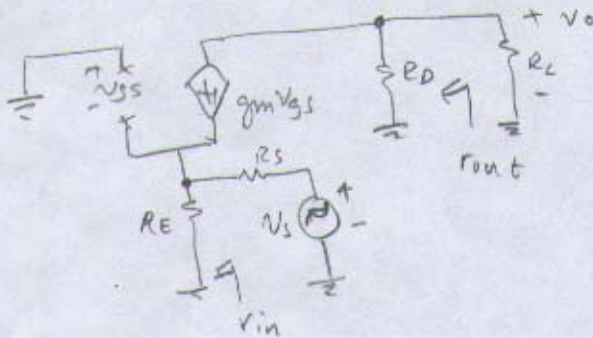
$$V_P = V_{GS} - \sqrt{\frac{2}{10}} = -2 - \sqrt{\frac{2}{10}} = -2.44 \text{ V}$$



$$g_m = 2\sqrt{KI_D} = 2\sqrt{2 \times 10} = 8.94 \text{ mA/V}$$


$$b) r_{in} = R_E \parallel \frac{1}{g_m} = 1 \parallel \frac{1}{8.94} = 0.1 \text{ k}\Omega$$

$$c) r_{out} = R_D = 5 \text{ k}\Omega$$

$$d) \frac{v_o}{v_i} = +g_m R_D \parallel R_L = 8.94 \times 5 \parallel 5 = 22.35$$

$$\frac{v_o}{v_s} = \frac{v_o}{v_i} \frac{r_{in}}{R_s + r_{in}} = 22.35 \frac{100}{50 + 100} = 14.90$$

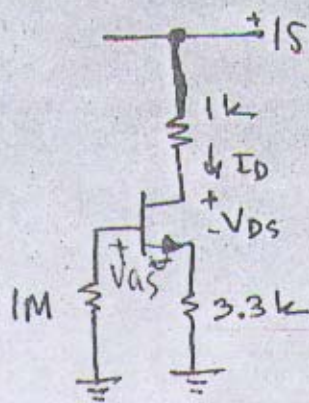3. Find the operating point for the JFET in the circuit below.



$$V_p = -3V$$

$$I_{DSS} = 18mA$$

$$K = \frac{I_{DSS}}{V_p^2} = \frac{18}{9} = 2mA/V^2$$

$$I_D = K(V_{GS} - V_p)^2$$

$$3.3 I_D + V_{GS} = 0$$

$$3.3 \times K(V_{GS} - V_p)^2 + V_{GS} = 0$$

$$3.3 \times 2(V_{GS} + 3)^2 + V_{GS} = 0$$

$$6.6(V_{GS}^2 + 6V_{GS} + 9) + V_{GS} = 0$$

$$6.6V_{GS}^2 + 40.6V_{GS} + 59.4 = 0$$

$$V_{GS} = \frac{-b \pm \sqrt{b^2 - 4ac}}{2a}$$

$$V_{GS1} = \frac{-40.6 - \sqrt{(40.6)^2 - 4 \times 6.6 \times 59.4}}{2 \times 6.6}$$

$$= \frac{-40.6 - 8.955}{2 \times 6.6} = -3.75V$$

Since V_{GS} must be greater than V_p ,

Valid solution $\rightarrow V_{GS} = -2.397V$

$$V_{GS2} = \frac{-40.6 + 8.955}{2 \times 6.6} = -2.397V$$

$$I_D = 2(-2.397 + 3)^2 = 0.726mA$$

$$V_S = 0.726 \times 3.3 = 2.39V \quad \left. \vphantom{V_S} \right\} V_{DS} = 11.88V$$

$$V_D = 15 - 1 \times 0.726 = 14.27V$$


$$I_D = 0.726mA$$

$$V_{DS} = 11.88V$$

ID No: ERIGAYA Name: SOLUTIONS Signature: _____

- 1) For the rectifier circuit below, the peak-to-peak ripple is required to be less than 5% of the peak voltage. Determine the minimum C value for a load current of 500 mA.

$$C = \underline{12300 \mu F}$$

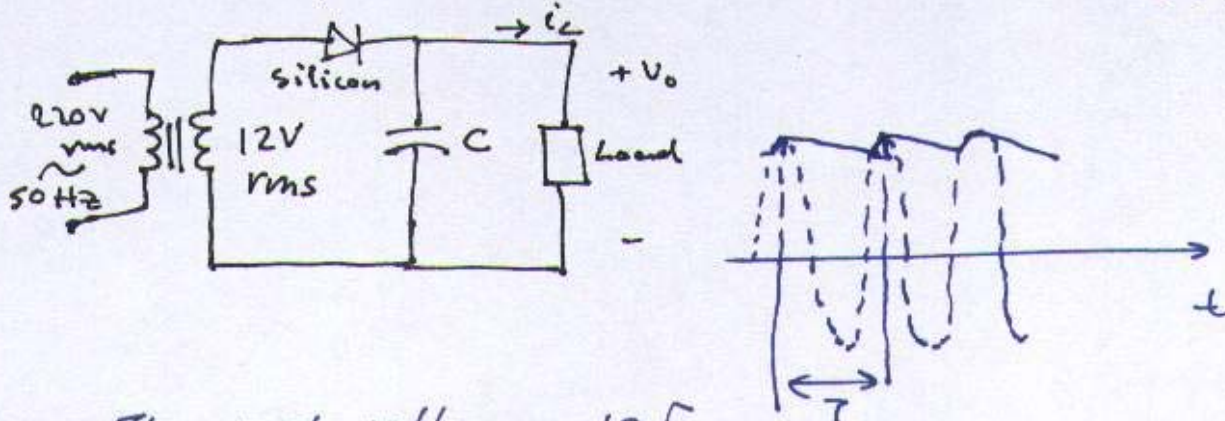


$$\text{The peak voltage} = 12\sqrt{2} - 0.7 = 16.27 \text{ V}$$

$$5\% \text{ ripple} \rightarrow 0.81 \text{ V} = \Delta V$$

$$\Delta Q = I_L T = 0.5 \times \frac{1}{50} = 0.01 \text{ C}$$

$$C = \frac{\Delta Q}{\Delta V} = \frac{0.01}{0.81} = 0.0123 \text{ F} = 12300 \mu\text{F}$$

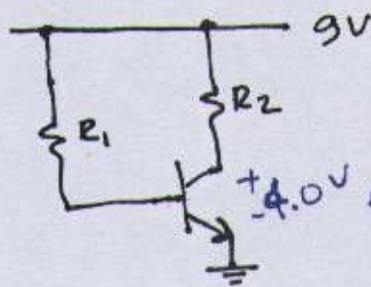- 2) The transistor in the cts below has the operating point of $I_c = 1\text{mA}$, $V_{CE} = 4\text{V}$; it is made of silicon and has a β of 300. Find R_1 and R_2 in each bias circuit. ($V_{BE} = 0.7\text{V}$)




$$I_E \cong I_C = 1\text{mA}$$

$$R_2 = \frac{9 - 4}{1} = 5\text{k}\Omega$$

$$R_1 = \frac{9 - 0.7}{\frac{1}{300}} = 2.49\text{M}\Omega$$

$$R_1 = \underline{2.49\text{M}\Omega}$$

$$R_2 = \underline{5\text{k}\Omega}$$

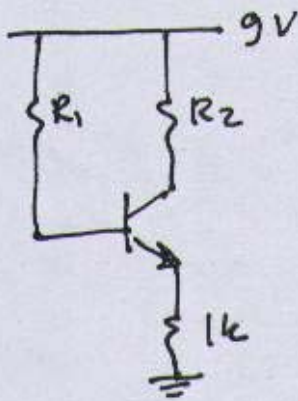


$$R_2 = \frac{9 - 4 - 1 \times 1}{1} = 4\text{k}\Omega$$

$$R_1 = \frac{9 - (4 + 0.7)}{\frac{1}{300}} = 2.19\text{M}\Omega$$

$$R_1 = \underline{2.19\text{M}\Omega}$$

$$R_2 = \underline{4\text{k}\Omega}$$

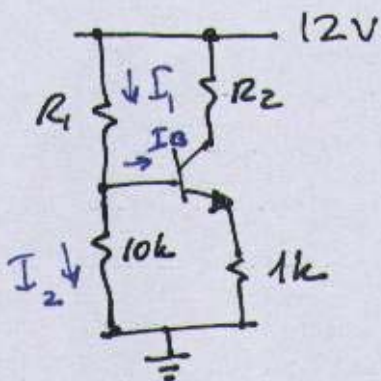

$$V_B = 1 \times 1 + 0.7 = 1.7\text{V}$$

$$I_2 = \frac{1.7}{10\text{k}} = 0.17\text{mA}$$

$$I_1 = I_2 + I_B = 0.17 + \frac{1}{300} = 0.1733\text{mA}$$

$$R_1 = \frac{12 - V_B}{I_1} = \frac{12 - 1.7}{0.1733} = 59.43\text{k}\Omega$$


$$R_1 = \underline{59.43\text{k}\Omega}$$

$$R_2 = \underline{7\text{k}\Omega}$$

$$R_2 = \frac{12 - 4 - 1 \times 1}{1} = 7\text{k}\Omega$$

ID number ERKAYIA Name: SOLUTIONS Signature: _____

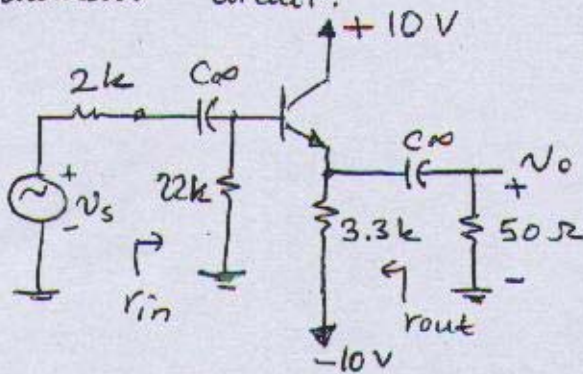Find the DC operating point for the transistor in the amplifier circuit below. Also find the voltage gain, input resistance and output resistance of the amplifier using a small-signal equivalent circuit.



$$\beta = 250$$

$$V_{BE} = 0.7V$$

$$V_{CE} = 10.97V$$

$$I_C = 2.73mA$$

$$\frac{V_o}{V_s} = 0.6874$$

$$r_{in} = 8.795k\Omega$$

$$r_{out} = 16.4\Omega$$

DC analysis: KVL

$$-10 + 3.3I_E + 0.7 + 22I_B = 0$$

$$(3.3 \times 251 + 22) I_B = 9.3$$


$$I_B = \frac{9.3}{3.3 \times 251 + 22} = 0.0109mA$$

$$I_C = 250 I_B = 2.73mA$$

$$I_E \approx I_C \text{ since } \beta \gg 1$$

KVL

$$-10 + 3.3 \times 2.73 + V_{CE} = 10V, \quad V_{CE} = 20 - 3.3 \times 2.73 = 10.97V$$

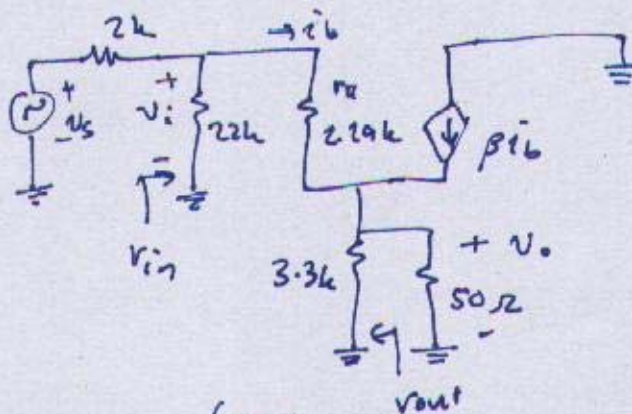SS. eq. ckt

$$g_m = \frac{I_C}{V_T} = \frac{2.73}{0.025} = 109.2 \text{ mA/V}$$

$$r_{\pi} = \frac{250}{109.2} = 2.29k\Omega$$

$$r_{in} = 22k \parallel [2.29 + 251 \times (3.3 \parallel 0.05)]$$

$$= 8.795k\Omega$$

$$r_{out} = 3.3k \parallel \frac{2.29k + 22 \parallel 2k}{251} = 16.4\Omega$$

$$\frac{V_o}{V_i} = \frac{251 (3.3 \parallel 0.05)}{2.29 + 251 (3.3 \parallel 0.05)} = \frac{12.36}{14.65} = 0.8437$$


$$\frac{V_i}{V_s} = \frac{r_{in}}{R_s + r_{in}} = \frac{8.795}{10.795} = 0.8147$$

$$\frac{V_o}{V_s} = 0.8437 \times 0.8147 = 0.6874$$

I have never given nor received any unauthorized help with this exam, nor do I have reason to believe that anybody else has.

ID number: SOLUTIONS Name: ERKAYA Signature: _____

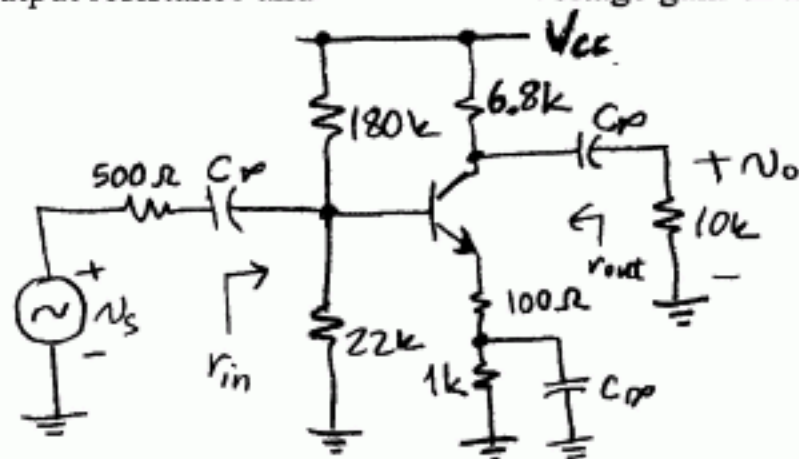- 1) Obtain a small-signal equivalent circuit for the amplifier given below. Then find the input resistance, output resistance and voltage gain of the amplifier.



$$I_c = 1.5 \text{ mA}$$

$$\beta = 240$$


$$g_m = \frac{I_c}{V_T} = \frac{1.5}{0.025} = 60 \text{ mA/V}$$

$$r_{\pi} = \frac{\beta}{g_m} = \frac{240}{60} = 4 \text{ k}\Omega$$

$$r_{in} = 11.54 \text{ k}\Omega$$

$$r_{out} = 6.8 \text{ k}\Omega$$

$$v_o/v_s = -33.13$$

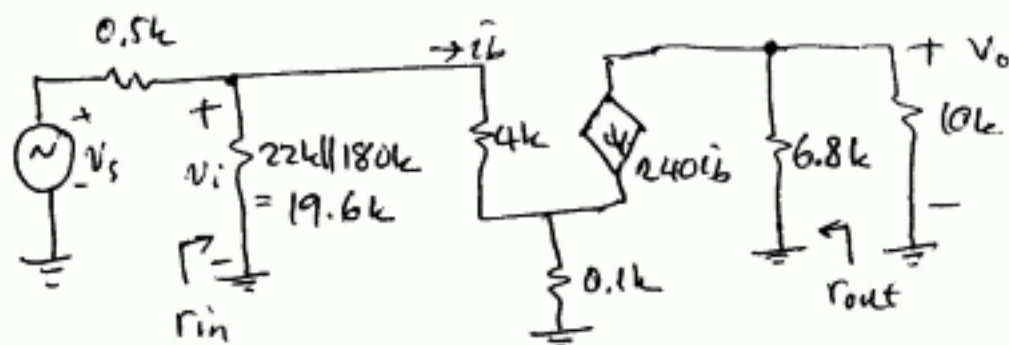

$$r_{in} = 19.6 \text{ k} \parallel [4 \text{ k} + 0.1(240+1)] = 19.6 \text{ k} \parallel 28.1 \text{ k} = 11.54 \text{ k}$$


$$r_{out} = 6.8 \text{ k}$$

$$\left. \begin{aligned} v_o &= -240 i_b (6.8 \parallel 10) \\ v_i &= [4 \text{ k} + 0.1(240+1)] i_b \end{aligned} \right\} \frac{v_o}{v_i} = \frac{-240 (6.8 \parallel 10)}{28.1} = -34.57$$

$$\frac{v_o}{v_s} = -34.57 \frac{11.54}{0.5 + 11.54} = -33.13$$

2) Find the operating points of the bipolar junction transistors in the circuits given below:

$$\beta = 250, V_{BE} = 0.7V$$

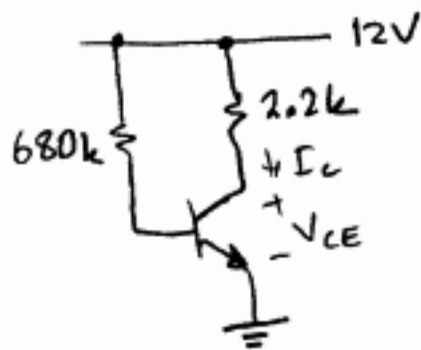


$$I_c = \frac{4.154 \text{ mA}}{V_{CE} = 2.86}$$

$$I_B = \frac{12 - 0.7}{680k} = 0.0166 \text{ mA}$$

$$I_c = \beta I_B = 4.154 \text{ mA}$$
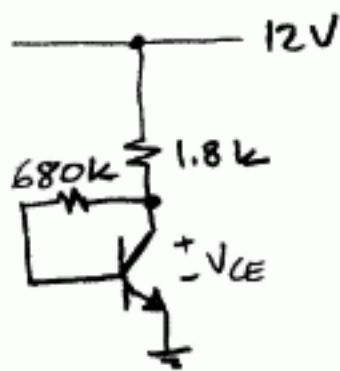
$$V_{CE} = 12 - 2.2 \times 4.154 = 2.86 \text{ V}$$




$$I_c = 2.5 \text{ mA}$$

$$V_{CE} = 7.5 \text{ V}$$

$$I_B = \frac{12 - 0.7}{680 + 251 \times 1.8} = 0.01 \text{ mA}$$

$$I_c = 250 \times I_B = 2.5 \text{ mA}$$
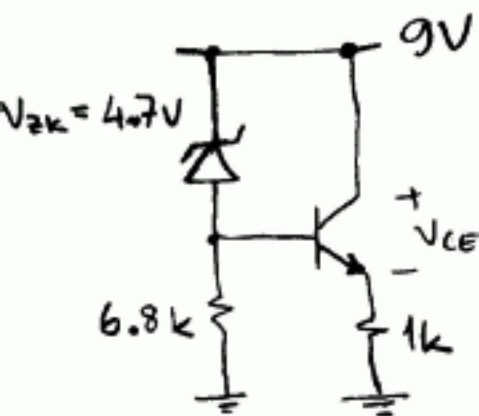
$$V_{CE} = 12 - 1.8 \times 2.5 = 7.5 \text{ V}$$



$$I_c = 3.6 \text{ mA}$$


$$V_{CE} = 5.4 \text{ V}$$

$$V_B = 9 - 4.7 = 4.3 \text{ V}$$

$$V_E = V_B - V_{BE} = 4.3 - 0.7 = 3.6 \text{ V}$$

$$I_E = \frac{3.6 \text{ V}}{1k} = 3.6 \text{ mA}, I_c \approx I_E$$

$$V_{CE} = 9 - 3.6 = 5.4 \text{ V}$$

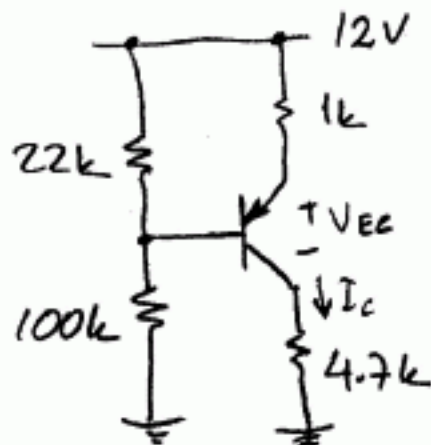

$$I_c = 1.47 \text{ mA}$$

$$V_{CE} = 3.65 \text{ V}$$

$$V_B = 12 \times \frac{100}{100 + 22} = 9.83 \text{ V}$$

$$V_E = V_B - 0.7 = 10.53 \text{ V}$$


$$I_E = \frac{12 - 10.53}{1k} = 1.47 \text{ mA}$$

$$I_c \approx I_E$$

$$V_{EC} = 12 - 1 \times 1.47 - 4.7 \times 1.47$$

$$V_{EC} = 3.65 \text{ V}$$

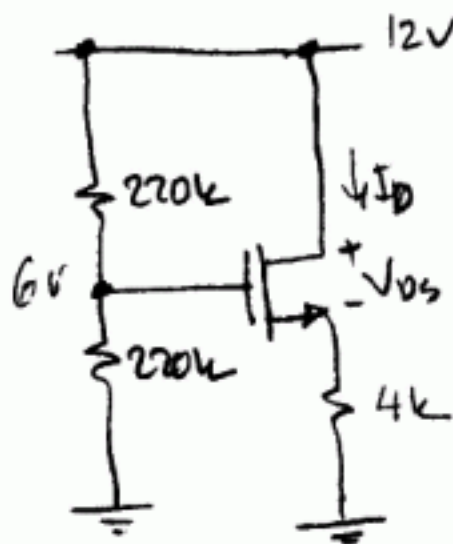3) Find the operating points of the field effect transistors in the circuits given below:



$$K = 1 \text{ mA/V}^2$$

$$V_t = 1 \text{ V}$$

$$I_D = 1 \text{ mA}$$

$$V_{DS} = 8 \text{ V}$$

$$V_G = 12 \frac{220}{220+220} = 6 \text{ V}$$

$$4I_D + V_{GS} = 6$$

$$4 \times 1 (V_{GS} - V_t)^2 + V_{GS} - 6 = 0$$

$$4(V_{GS}^2 - 2V_{GS}V_t + V_t^2) + V_{GS} - 6 = 0$$

$$4V_{GS}^2 - 7V_{GS} + 4 - 6 = 0$$


$$V_{GS1} = \frac{7 + \sqrt{49 - 32}}{8} = 2 \text{ valid}$$

$$V_{GS2} = \frac{7 - \sqrt{49 - 32}}{8} = -\frac{2}{8} < V_t$$

not valid

$$I_D = 1(2 - 1)^2 = 1 \text{ mA}$$

$$V_{DS} = 12 - 4 = 8 \text{ V}$$

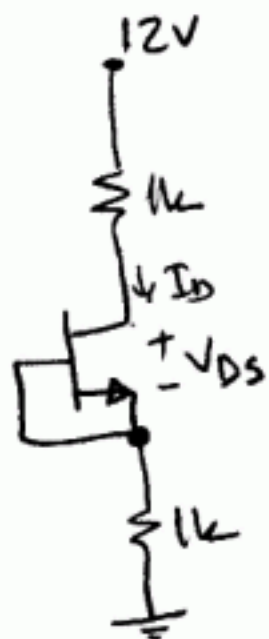

$$I_{DSS} = 2 \text{ mA}$$

$$V_p = -2 \text{ V}$$


$$I_D = 2 \text{ mA}$$

$$V_{DS} = 8 \text{ V}$$

$$V_{GS} = 0$$

By definition of I_{DSS} , $I_{D0} = I_{DSS} = 2 \text{ mA}$

$$V_{DS} = 12 - 2(1 + 1) = 8 \text{ V}$$

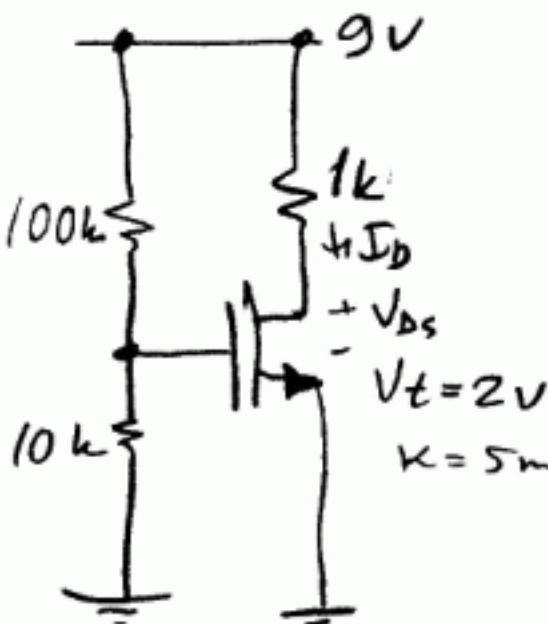

$$I_D = 0$$

$$V_{DS} = 9 \text{ V}$$

$$V_{GS} = 9 \frac{10}{10+100} = 0.82 \text{ V} < V_t = 2 \text{ V}$$

$$\text{CUTOFF} \rightarrow I_D = 0$$

$$V_{DS} = 9 - I_D \times 1 = 9 \text{ V}$$

Dec 13, 2005


Electronics I - Midterm 2

60 minutes

Name: ERIKAYA ID number: SOLUTIONS Signature: _____

- 1) The circuit below is to be used as a constant current battery charger. The positions of the switch S corresponds to the following current values:

Position	Current
1	100 mA
2	200 mA
3	300 mA
4	400 mA

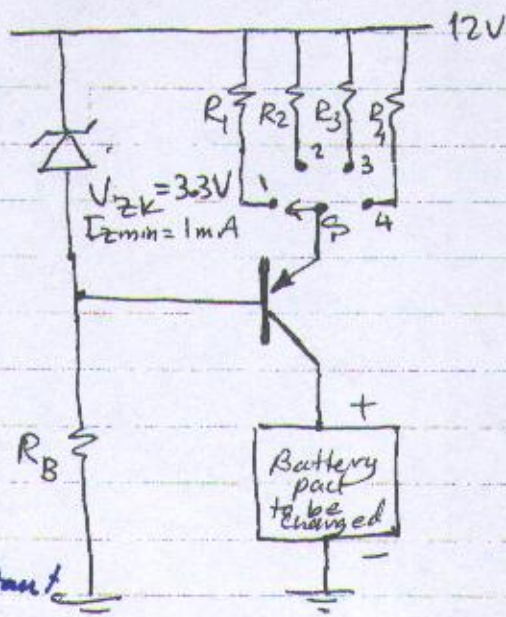Silicon BJT
 $\beta = 70$

$$R_{Bmax} = \frac{1.29 \text{ k}\Omega}{\beta} = \frac{1.29 \text{ k}\Omega}{70} = 18.4 \text{ }\Omega$$

$$R_1 = \frac{2.6 \text{ V}}{0.1 \text{ A}} = 26 \text{ }\Omega$$

$$R_2 = \frac{2.6 \text{ V}}{0.2 \text{ A}} = 13 \text{ }\Omega$$

$$R_3 = \frac{2.6 \text{ V}}{0.3 \text{ A}} = 8.66 \text{ }\Omega$$

$$R_4 = \frac{2.6 \text{ V}}{0.4 \text{ A}} = 6.5 \text{ }\Omega$$

- a) What could be the max value for R_B ?

The current in R_B is constant
It must be at least

$$I_{Zmin} + I_{Bmax} = 1 + \frac{400}{70} = 6.71 \text{ mA}, \quad R_{Bmax} = \frac{12 - 3.3}{6.71} = 1.29 \text{ k}\Omega$$

- b) What should be the resistor values R_1, R_2, R_3, R_4 ?

The voltage across R_1, R_2, R_3, R_4 is $3.3 - 0.7 = 2.6 \text{ V}$

$$R_1 = \frac{2.6}{0.1} = 26 \text{ }\Omega, \quad R_2 = \frac{2.6}{0.2} = 13 \text{ }\Omega, \quad R_3 = \frac{2.6}{0.3} = 8.66 \text{ }\Omega, \quad R_4 = \frac{2.6}{0.4} = 6.5 \text{ }\Omega$$

- c) What is the maximum voltage that the rechargeable battery pack may have?

$$V_{Cmax} = V_E - V_{CESAT} = 12 - 2.6 - 0.2 = 9.2 \text{ V}, \quad V_{battery max} = 9.2 \text{ V}$$

- d) What must be the power rating of the BJT?

$$P_{max} = |I_{Cmax} V_{CEmax}| = 0.4 \times (12 - 2.6) = \underline{\underline{3.76 \text{ W}}}$$

2) Find the operating point of the transistor given in the circuit below. Also find a small signal equivalent circuit, input resistance, output resistance and voltage gain for the amplifier.

$$V_{BE} = 0.7V, \beta = 250, V_T = 0.025V$$

$$I_C = 1.13mA$$

$$r_{in} = 22\Omega$$



$$I_C \approx I_E = \frac{-0.7 - (-12)}{10} = 1.13mA$$

$$r_{out} = 5k$$

$$\frac{V_o}{V_s} = 75$$

$$g_m = \frac{I_C}{V_T} = \frac{1.13}{0.025} = 45.2mA/V$$
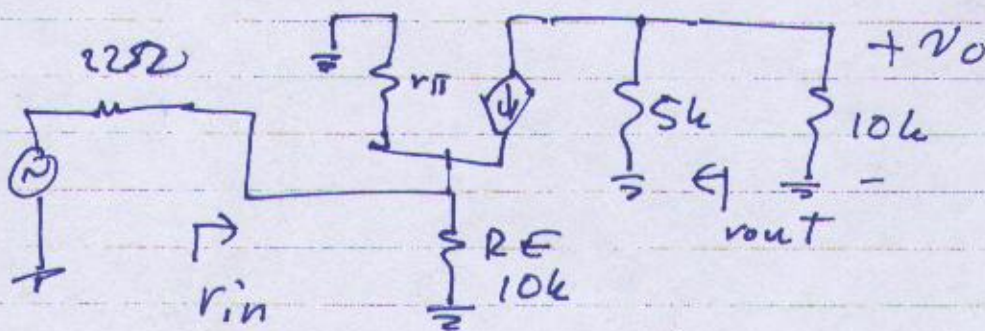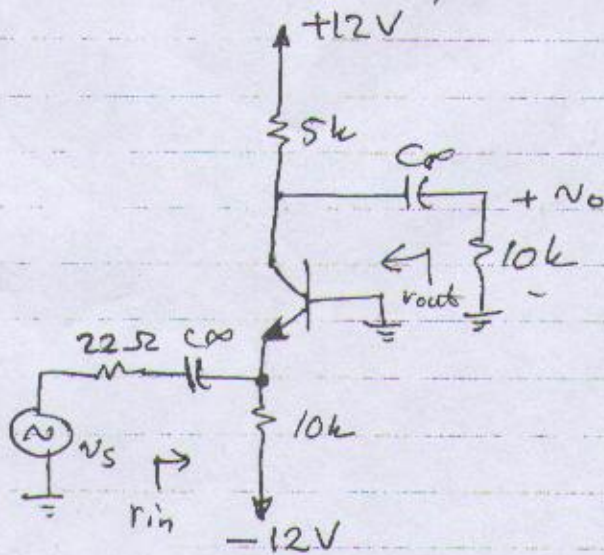
$$r_{\pi} = \frac{\beta}{g_m} = \frac{250}{45.2} = 5.53k\Omega$$



$$r_{in} = 10k \parallel \frac{r_{\pi}}{\beta + 1} = 10k \parallel \frac{5.53k}{251} = 0.022\Omega$$

$$r_{out} = 5k$$


$$\frac{V_o}{V_i} = g_m (R_C \parallel R_E) = 45.2 \times 5 \parallel 10 = 150$$

$$\frac{V_o}{V_s} = \frac{r_{in}}{R_s + r_{in}} = \frac{22}{22 + 22} = \frac{1}{2}$$

$$\frac{V_o}{V_s} = 150 \times \frac{1}{2} = 75$$

3) Find the operating points for the FETs given below:


a)

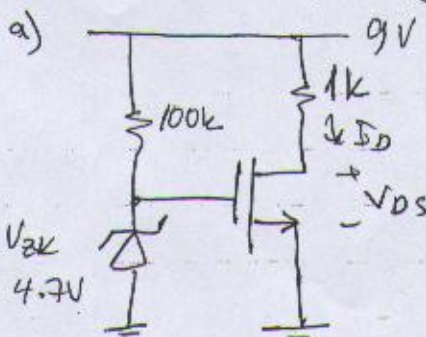

$V_t = 2.5V$
 $K = 0.5 \text{ mA/V}^2$
 $V_{GS} = 4.7V$
 $I_D = \underline{2.42 \text{ mA}}$
 $V_{DS} = \underline{6.58V}$
 $I_D = 0.5 (4.7 - 2.5)^2 = 2.42 \text{ mA}$
 $V_{GS} = 9 - 1 \times 2.42 = 6.58V$


Verification $V_{DS} \geq V_{GS} - V_t = 2.2V$
 $6.58 > 2.2$ assumption is valid.

b)

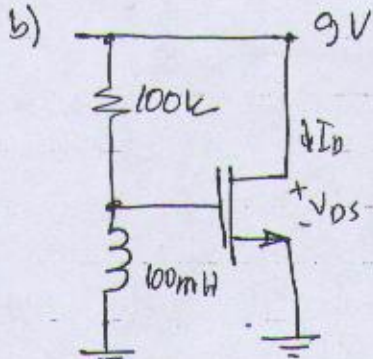

$V_t = 2.5V$
 $K = 0.5 \text{ mA/V}^2$
 $I_D = \underline{0}$
 $V_{DS} = \underline{9V}$

$V_{GS} = 0, < V_t \rightarrow I_D = 0$

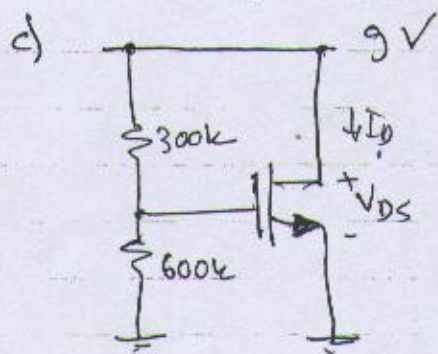


$V_t = 2.5V$
 $K = 0.5 \text{ mA/V}^2$

$I_D = \underline{6.12 \text{ mA}}$
 $V_{DS} = \underline{9V}$

$V_{GS} = 9 \frac{600}{300 + 600} = 6V$

$I_D = 0.5 (6 - 2.5)^2 = 6.12 \text{ mA}$

$V_{DS} = 9V > 6 - 2.5 = 3.5$ ✓

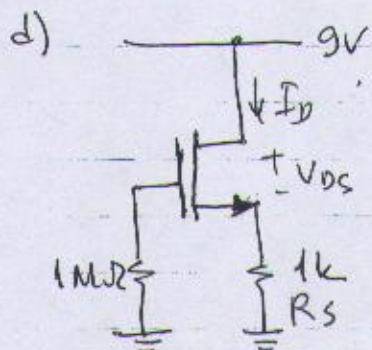

$V_t = -1V$
 $K = 0.5 \text{ mA/V}^2$

$I_D = \underline{0.27 \text{ mA}}$
 $V_{DS} = \underline{8.73V}$

$V_G = 0, V_S = I_D R_S$

$V_{GS} = V_G - V_S = -I_D R_S$

$V_{GS} = -K (V_{GS} - V_t)^2 R_S$

$V_{GS} + K R_S (V_{GS}^2 - 2 V_{GS} V_t + V_t^2) = 0$

$2 V_{GS} + V_{GS}^2 + 2 V_{GS} + 1 = 0$

$V_{GS1,2} = \frac{-4 \pm \sqrt{16 - 4}}{2} = -2 \pm \sqrt{3}$

$V_{GS}^2 + 4 V_{GS} + 1 = 0$

$I_D = \frac{+0.27}{1k} = 0.27 \text{ mA}$

$-2 - \sqrt{3} < V_t = -1$ not valid

$-2 + \sqrt{3} = 0.27V$