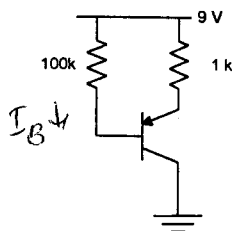


Find the operating points for the transistors in the circuits given below. (Assume  $\beta=200$ )

$I_C =$  \_\_\_\_\_

$V_{EC} =$  \_\_\_\_\_



**Cut-off**  
 $I_C \approx 0$   
 $V_{EC} = 9V$


Actually  
 It would be  
 reverse active  
 mode.  
 $\beta_R \approx \frac{1}{\beta_F} = \frac{1}{200}$

$$I_B = \frac{9 - 0.7}{100}$$

$$\beta_R I_B = \frac{8.3}{20000} \text{ mA} \approx 0$$


$I_C =$  \_\_\_\_\_

$V_{CE} =$  \_\_\_\_\_

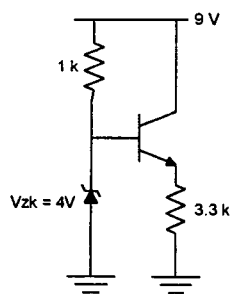


$$I_C \approx I_E = \frac{9 - 0.7}{3.3} = 1 \text{ mA}$$
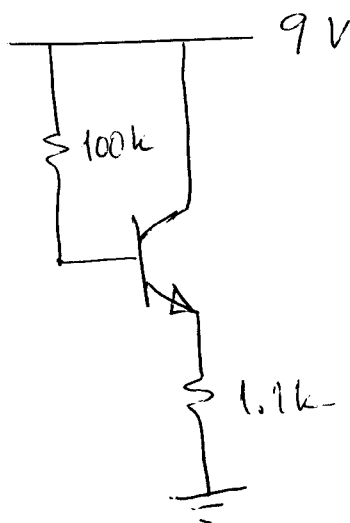
$$V_{CE} = 9 - 3.3 \times 1 = 5.7 \text{ V}$$



$$I_C = \frac{200(9 - 0.7)}{201 \times 1.1 + 100} = 5.16 \text{ mA}$$
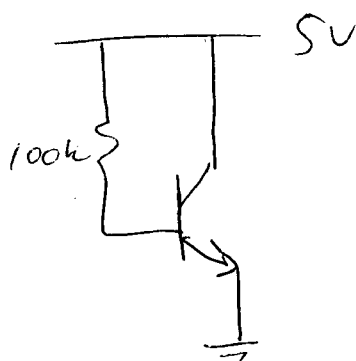
$$V_{CE} = 9 - 5.16 \times 1.1 = 3.31 \text{ V}$$



$$V_{CE} = 5 \text{ V}$$

$$I_C = 200 \frac{5 - 0.7}{100} = 8.6 \text{ mA}$$