

Electronics I * Midterm 1 * November 3, 2009 * 60 minutes


I have neither given nor received any unauthorized help with this exam, nor do I have any reason to believe that anybody else has.

30pts ID number: ERYAYA Name: SOLUTIONS Signature: _____

1. The amplifier in the circuit below is made of two identical cascaded (one is placed after the other) stages. Each stage has $10\text{ k}\Omega$ input resistance, $1\text{ k}\Omega$ output resistance, 40 open-circuit voltage gain. Also, each stage draws 5 mA DC current from a 9 V power supply. If the signal at the load is $3\text{ sin}\omega t\text{ V}$, what would be the voltage gain and efficiency of the amplifier?

$$\eta = \underline{5\%}$$

$$\frac{V_o}{V_s} = \underline{661}$$

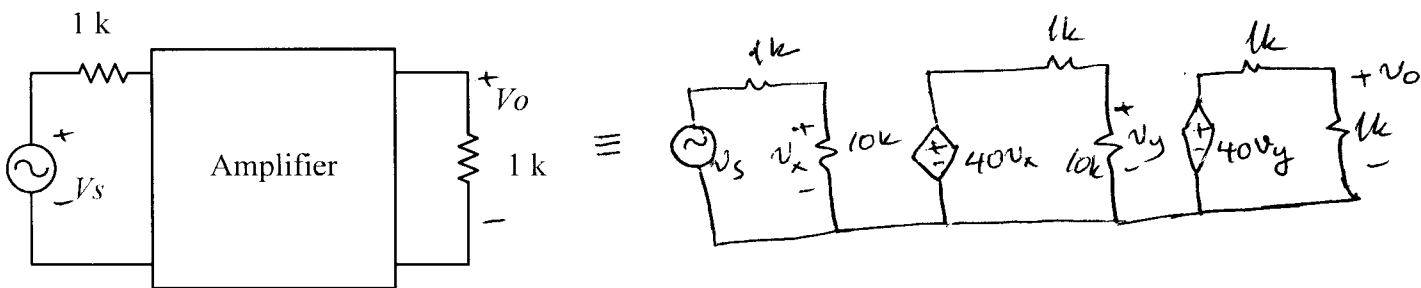

$$\frac{V_o}{V_s} = 40 \times 40 \times \frac{10}{10+1} \times \frac{10}{10+1} \times \frac{1}{1+1} = 1600 \times \frac{100}{242} \approx 661$$


$$P_L = V_{\text{rms}} I_{\text{rms}} \cos \varphi = \frac{3}{\sqrt{2}} \times \frac{3/1k}{\sqrt{2}} = 4.5\text{ mW}$$

$$P_{DC} = 2 \times 5\text{ m} \times 9 = 90\text{ mW}$$

$$\eta = \frac{P_L}{P_{DC}} = \frac{4.5}{90} = \frac{5}{100} = 5\%$$

2. The OPAMP in the circuit below has $f_t = 2 \text{ MHz}$, $SR = 1 \text{ V}/\mu\text{s}$, and $V_{omax} = 10 \text{ V}$. The signal source has a sine-wave with peak amplitude V_i .

40 pts

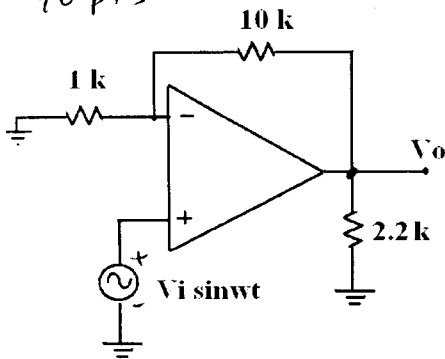

(a) If $V_i = 0.4 \text{ V}$, what is the maximum frequency before the output distorts?
 $f_{max} = \underline{36.2 \text{ kHz}}$

(b) If $f = 20 \text{ kHz}$, what is the maximum value of V_i before the output distorts?
 $V_{i \max} = \underline{0.72 \text{ V}}$

(c) If $V_i = 50 \text{ mV}$, what is the useful frequency range of operation?
 $f_{range} = \underline{0 - 181.8}$

(d) If $f = 5 \text{ kHz}$, what is the useful input voltage range?
 $V_i \text{ range: } \underline{0 - 0.9 \text{ V}}$

This is a non-inverting amplifier. $gain = 1 + \frac{10}{1} = 11$

$V_o = 11 \times V_i \sin \omega t$. Gain-bandwidth product $11 \cdot f_\beta = 2 \text{ MHz}$
 useful frequency range: $0 - \frac{2}{11} \text{ MHz} = \underline{0 - 181.8 \text{ kHz}}$

a) $|V_o| = 0.4 \times 11 = 4.4 \text{ V}$
 due to SR limitation $f_{max} \leq \frac{SR}{2\pi|V_o|} = \frac{1 \times 10^6}{2\pi \times 4.4} = 36.2 \text{ kHz}$

b) $f = 20 \text{ kHz}$, $|V_o| \leq \frac{1 \times 10^6}{2\pi \times 20 \times 10^3} = 7.95 \text{ V}$
 $V_i \leq \frac{7.95}{11} = 0.72 \text{ V}$

c) $V_i = 50 \text{ mV}$ expected $|V_o| = 0.55 \text{ V}$ expected $f_{max} = \frac{1 \times 10^6}{2\pi \times 0.55} \text{ Hz}$
 $= 289 \text{ kHz}$

Since $289 > f_\beta$, the gain falls before SR limitation occurs.

hence $f_{max} = f_\beta = 181.8 \text{ kHz}$

d) $f = 5 \text{ kHz}$, $|V_o| \leq \frac{SR}{2\pi f} = \frac{10^6}{2\pi \times 5 \times 10^3} = 31.83 \text{ V}$


not possible because $V_{omax} = 10 \text{ V}$

hence $V_{i \max} = \frac{10}{11} = 0.9 \text{ V}$


3. Assuming that the diodes in the circuit are made of silicon, find V and I in each circuit below:

30 P.


a)

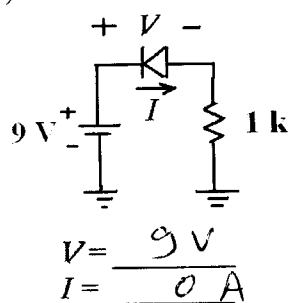


b)

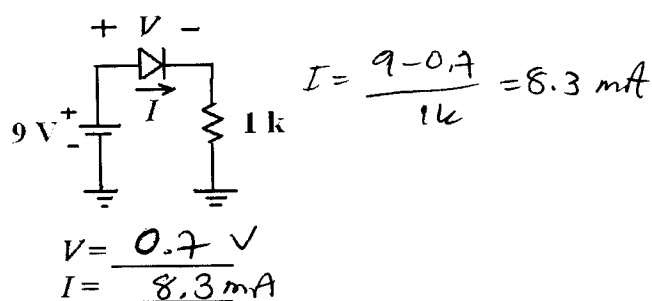

c)

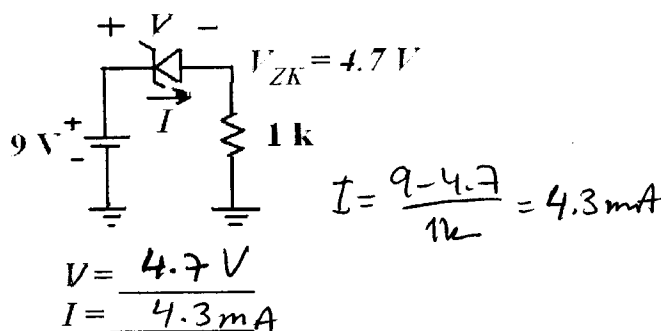

d)

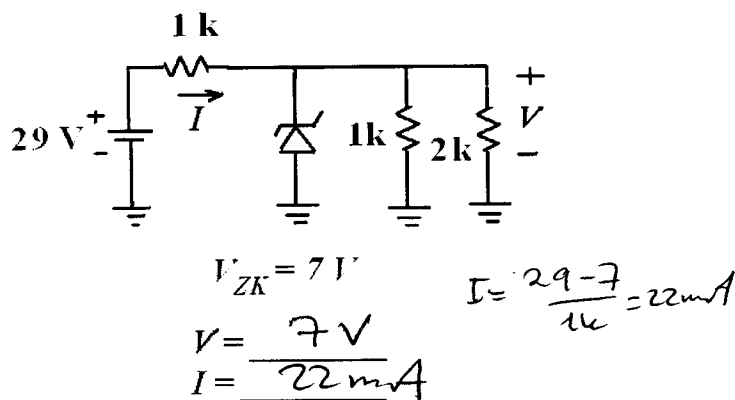

e)

