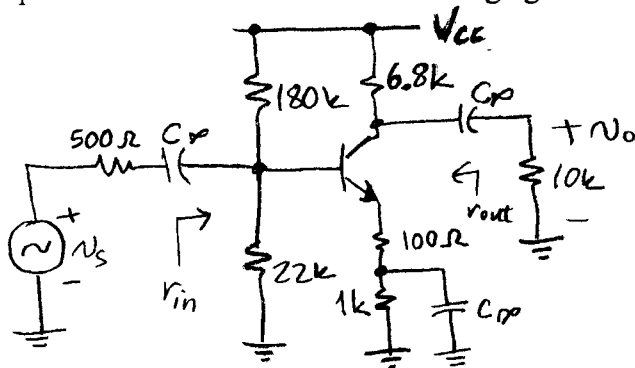


I have never given nor received any unauthorized help with this exam, nor do I have reason to believe that anybody else has.

ID number: SOLUTIONS Name: ERKAYA Signature: _____

- 1) Obtain a small-signal equivalent circuit for the amplifier given below. Then find the input resistance, output resistance and voltage gain of the amplifier.



$$I_c = 1.5 \text{ mA}$$

$$\beta = 240$$


$$g_m = \frac{I_c}{V_T} = \frac{1.5}{0.025} = 60 \text{ mA/V}$$

$$r_{\pi} = \frac{\beta}{g_m} = \frac{240}{60} = 4 \text{ k}\Omega$$

$$r_{in} = 11.54 \text{ k}\Omega$$

$$r_{out} = 6.8 \text{ k}\Omega$$

$$v_o/v_s = -33.13$$

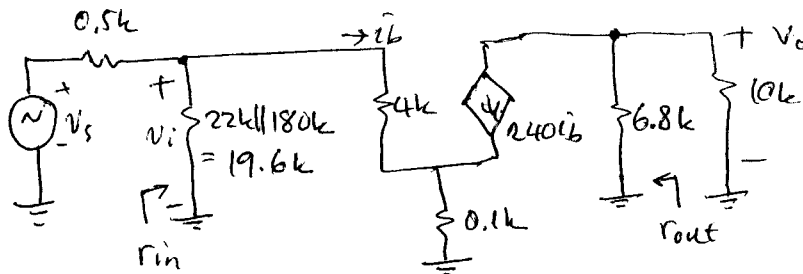

$$r_{in} = 19.6 \text{ k}\Omega \parallel [4 \text{ k}\Omega + 0.1(240 + 1)] = 19.6 \text{ k}\Omega \parallel 28.1 \text{ k}\Omega = 11.54 \text{ k}\Omega$$


$$r_{out} = 6.8 \text{ k}\Omega$$

$$\left. \begin{aligned} v_o &= -240 i_b (6.8 \parallel 10) \\ v_i &= [4 \text{ k}\Omega + 0.1(240 + 1)] i_b \end{aligned} \right\} \frac{v_o}{v_i} = \frac{-240 (6.8 \parallel 10)}{28.1} = -34.57$$

$$\frac{v_o}{v_s} = -34.57 \frac{11.54}{0.5 + 11.54} = -33.13$$

2) Find the operating points of the bipolar junction transistors in the circuits given below:

$$\beta = 250, V_{BE} = 0.7 \text{ V}$$

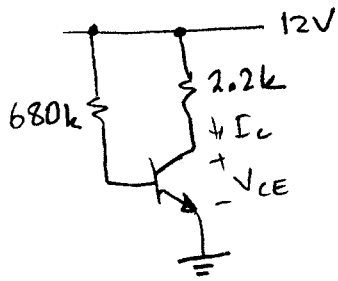


$$I_c = \frac{4.154 \text{ mA}}{4} = 1.0385 \text{ mA}$$

$$V_{CE} = 2.86 \text{ V}$$

$$I_B = \frac{12 - 0.7}{680 \text{ k}} = 0.0166 \text{ mA}$$

$$I_c = \beta I_B = 4.154 \text{ mA}$$
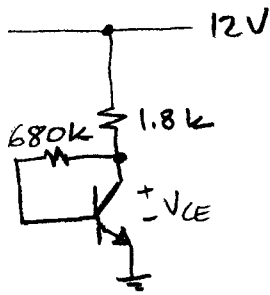
$$V_{CE} = 12 - 2.2 \times 4.154 = 2.86 \text{ V}$$




$$I_c = 2.5 \text{ mA}$$

$$V_{CE} = 7.5 \text{ V}$$

$$I_B = \frac{12 - 0.7}{680 + 251 \times 1.8} = 0.01 \text{ mA}$$

$$I_c = 250 \times I_B = 2.5 \text{ mA}$$
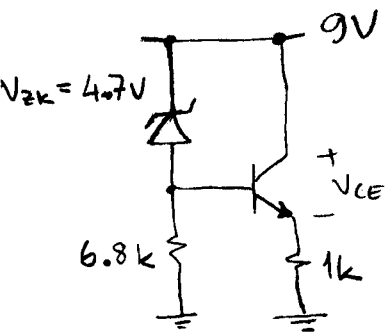
$$V_{CE} = 12 - 1.8 \times 2.5 = 7.5 \text{ V}$$



$$I_c = 3.6 \text{ mA}$$


$$V_{CE} = 5.4 \text{ V}$$

$$V_B = 9 - 4.7 = 4.3 \text{ V}$$

$$V_E = V_B - V_{BE} = 4.3 - 0.7 = 3.6 \text{ V}$$

$$I_E = \frac{3.6 \text{ V}}{1 \text{ k}} = 3.6 \text{ mA}, I_c \approx I_E$$

$$V_{CE} = 9 - 3.6 = 5.4 \text{ V}$$

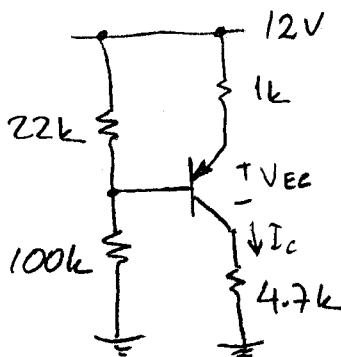

$$I_c = 1.47 \text{ mA}$$

$$V_{EC} = 3.65 \text{ V}$$

$$V_B = 12 \times \frac{100}{100 + 22} = 9.83 \text{ V}$$

$$V_E = V_B + 0.7 = 10.53 \text{ V}$$


$$I_E = \frac{12 - 10.53}{1 \text{ k}} = 1.47 \text{ mA}$$

$$I_c \approx I_E$$

$$V_{EC} = 12 - 1 \times 1.47 - 4.7 \times 1.47$$

$$V_{EC} = 3.65 \text{ V}$$

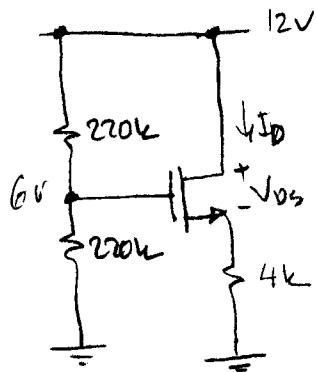3) Find the operating points of the field effect transistors in the circuits given below:



$$K = 1 \text{ mA/V}^2$$

$$V_t = 1 \text{ V}$$

$$I_D = 1 \text{ mA}$$

$$V_{DS} = 8 \text{ V}$$

$$V_G = 12 \times \frac{220}{220+220} = 6 \text{ V}$$

$$4I_D + V_{GS} = 6$$

$$4 \times 1 (V_{GS} - V_t)^2 + V_{GS} - 6 = 0$$

$$4(V_{GS}^2 - 2V_{GS}V_t + V_t^2) + V_{GS} - 6 = 0$$

$$4V_{GS}^2 - 7V_{GS} + 4 - 6 = 0$$


$$V_{GS1} = \frac{7 + \sqrt{49 - 32}}{8} = 2 \text{ valid}$$

$$V_{GS2} = \frac{7 - \sqrt{49 - 32}}{8} = -\frac{2}{8} < V_t$$

not valid

$$I_D = 1(2 - 1)^2 = 1 \text{ mA}$$

$$V_{DS} = 12 - 4 = 8 \text{ V}$$

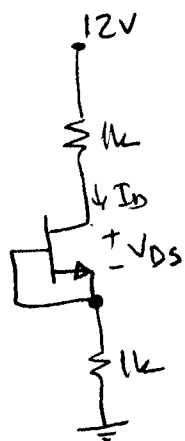

$$I_{DSS} = 2 \text{ mA}$$

$$V_p = -2 \text{ V}$$


$$I_D = 2 \text{ mA}$$

$$V_{DS} = 8 \text{ V}$$

$$V_{GS} = 0$$

By definition of I_{DSS} , $I_{D0} = I_{DSS} = 2 \text{ mA}$

$$V_{DS} = 12 - 2(1+1) = 8 \text{ V}$$

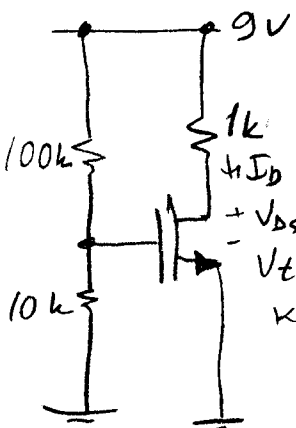

$$I_D = 0$$

$$V_{DS} = 9 \text{ V}$$

$$V_{GS} = 9 \times \frac{10}{10+100} = 0.82 \text{ V} < V_t = 2 \text{ V}$$

CUTOFF $\rightarrow I_D = 0$

$$V_{DS} = 9 - I_D \times 1 = 9 \text{ V}$$