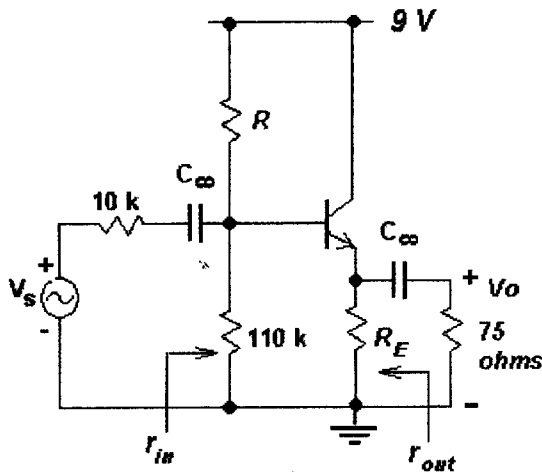


ID no: SOLUTIONS

Name: ERKAYA

Signature: _____

1. Find R_E and R in the BJT amplifier such that the BJT has 1.5 mA collector current, 4.5 V collector-emitter voltage. Find its voltage gain, input resistance and output resistance when it is operated with a signal source whose output resistance is 10 kohm and a load of 75 ohms. (Assume silicon NPN BJT, $\beta=300$, and any value of resistor is available)



$$V_E = 9 - 4.5 = 4.5V$$

$$R_E = 3k\Omega$$

$$R_E = \frac{V_E}{I_E} \approx \frac{V_E}{I_C} = \frac{4.5}{1.5} = 3k\Omega$$

$$R = 80k$$

$$V_B = V_E + V_{BE} = 4.5 + 0.7 = 5.2V \quad v_o/v_s = 0.51$$

ignoring the base current

$$r_{in} = 17.06k$$

$$r_{out} = 43\Omega$$

$$\frac{5.2}{110k} = I_2 \approx I_1 = 0.047mA$$


$$R = \frac{9 - 5.2}{0.047} \approx 80k\Omega$$

$$R_B = 80k \parallel 110k = 46.3k$$

$$g_m = \frac{I_C}{V_T} = \frac{1.5}{0.025} = 60mA/V$$

$$r_{\pi} = \frac{\beta}{g_m} = \frac{300}{60} = 5k\Omega$$

S.S. eq. ckt

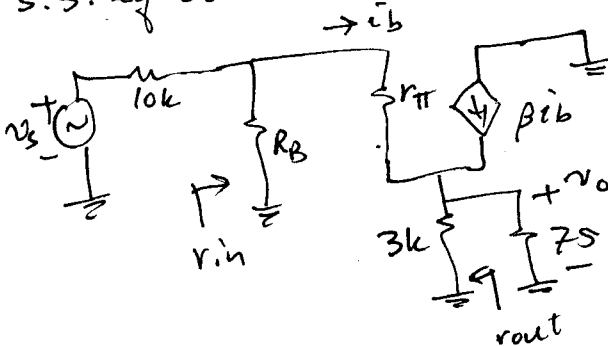

$$r_{in} = R_B \parallel [r_{\pi} + (\beta + 1)(R_E \parallel R_L)]$$

$$= 46.3 \parallel [5 + 301(3k \parallel 0.075)]$$

$$= 17.06k\Omega$$

$$r_{out} = 3k \parallel \frac{r_{\pi} + (10k \parallel R_B)}{\beta + 1}$$


$$= 3k \parallel \frac{5 + 10k \parallel 46.3}{301} \approx 0.043k$$

$$\frac{v_o}{v_s} = \frac{(\beta + 1)(R_L \parallel R_E)}{r_{\pi} + (\beta + 1)(R_L \parallel R_E)} \cdot \frac{r_{in}}{R_s + r_{in}} \approx \frac{301 \times 73}{5000 + 301 \times 73} \cdot \frac{17.06}{10 + 17.06} \approx 0.51$$

q:26

2. Find the operating points of the silicon bipolar transistors given below ($\beta=100$).

q:27

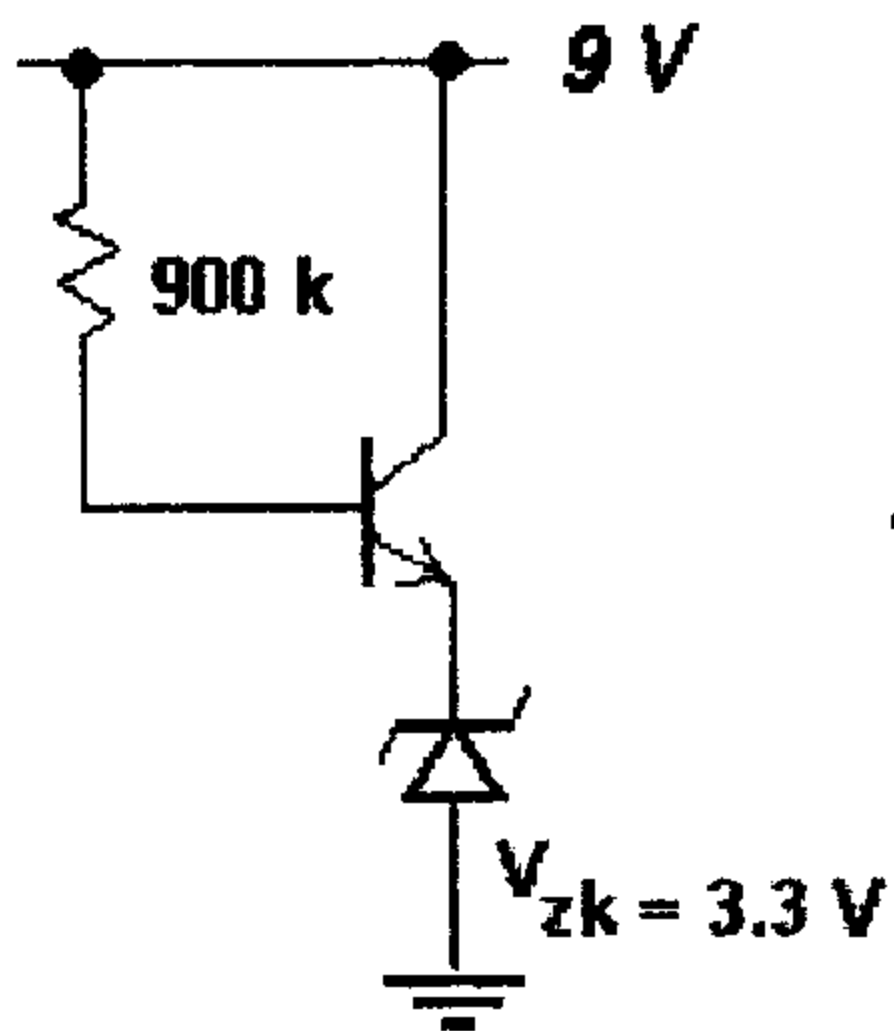

$$I_B = \frac{9 - 3.3 - 0.7}{900k} = \frac{5}{900} \text{ mA}$$


$$I_C = \beta I_B = \frac{100 \times 5}{900} = \frac{5}{9} = 0.555 \text{ mA}$$

$$V_{CE} = 9 - 3.3 = 5.7 \text{ V}$$

$$I_C = \underline{0.555 \text{ mA}}$$

$$V_{CE} = \underline{5.7 \text{ V}}$$

q:28

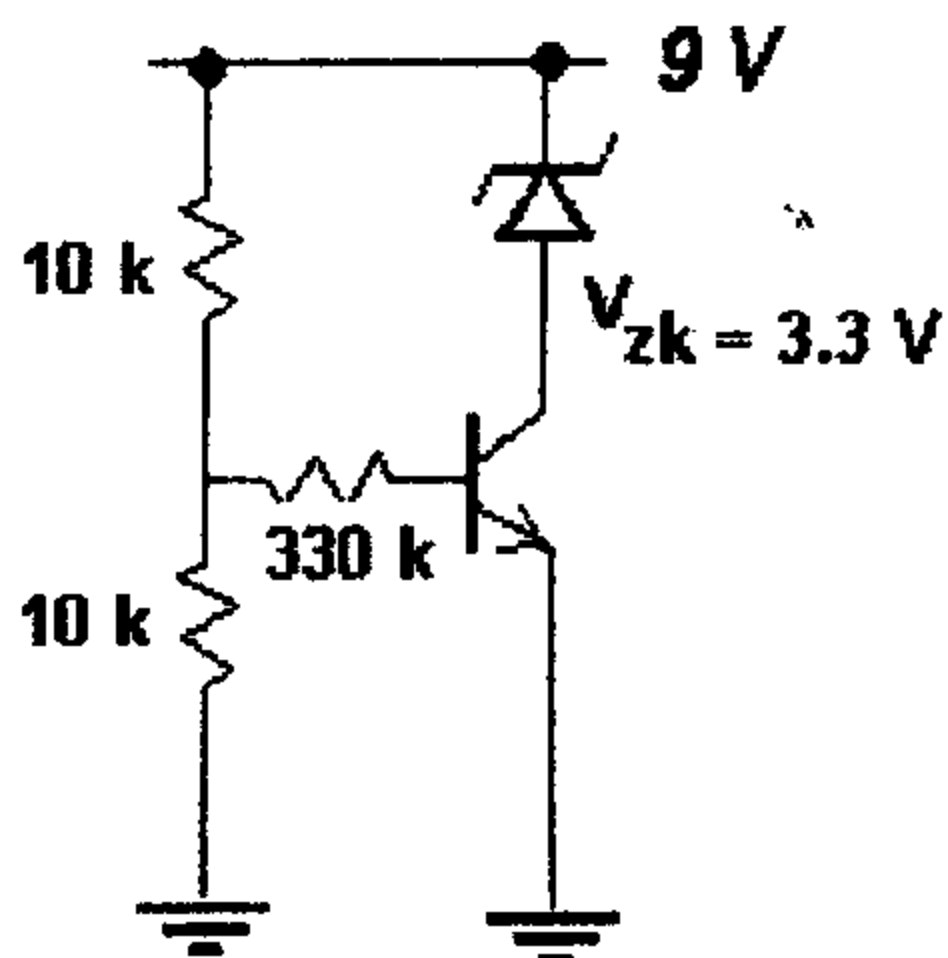


$$V_B = 4.5 \text{ V} = V_{TH}$$

$$R_{TH} = 10k || 10k = 5k$$

$$I_B = \frac{4.5 - 0.7}{335k} = 0.0113 \text{ mA}$$

$$I_C = \underline{1.13 \text{ mA}}$$


$$V_{CE} = \underline{5.7 \text{ V}}$$

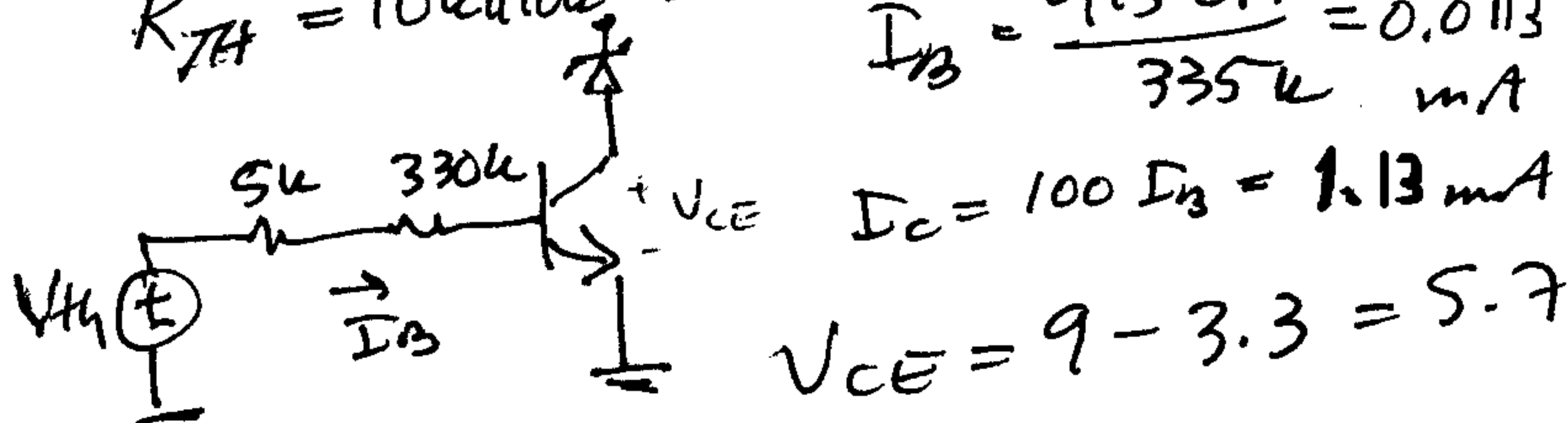


$$I_C = 100 I_B = 1.13 \text{ mA}$$

$$V_{CE} = 9 - 3.3 = 5.7$$

q:30

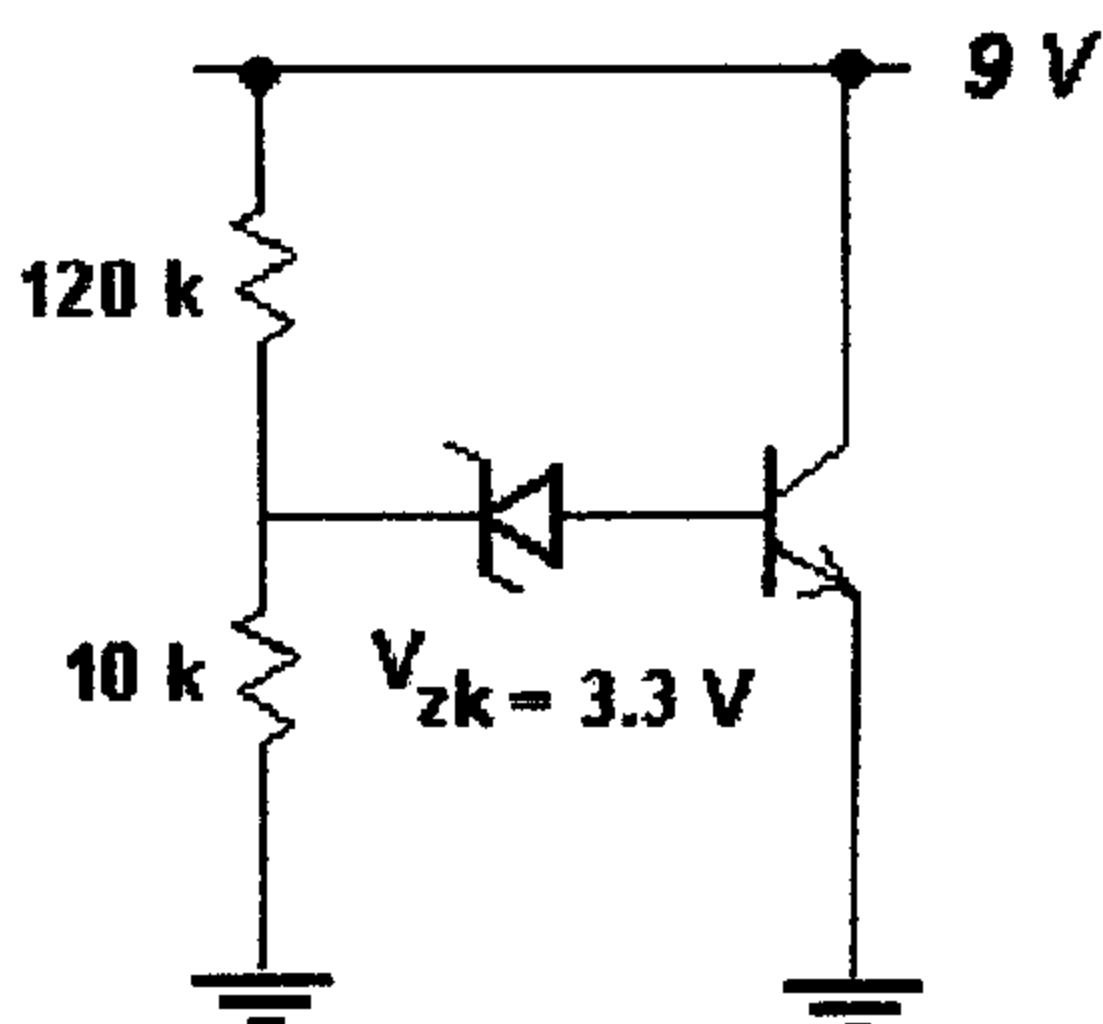
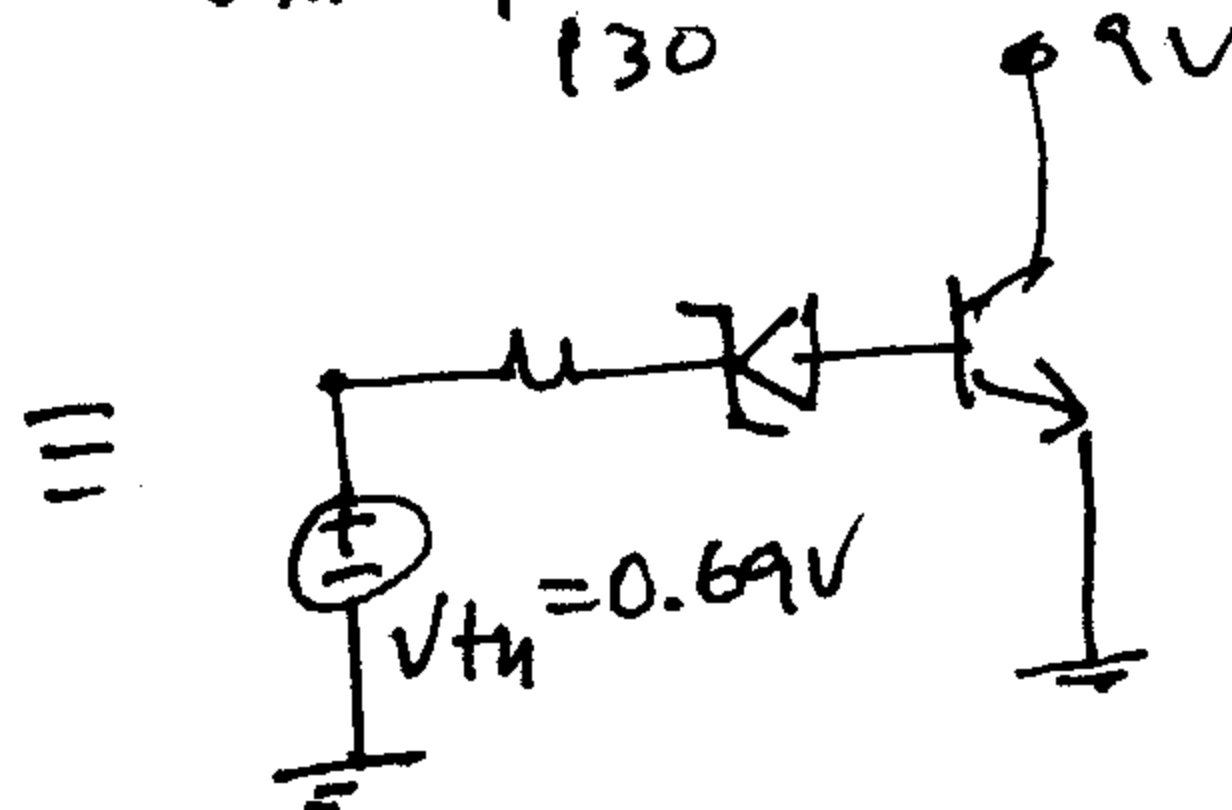
$$V_{TH} = 9 \times \frac{10}{130} = 0.69$$




Q: cut-off

$$I_C = 0$$

$$V_{CE} = 9 \text{ V}$$

$$I_C = \underline{0}$$

$$V_{CE} = \underline{9 \text{ V}}$$

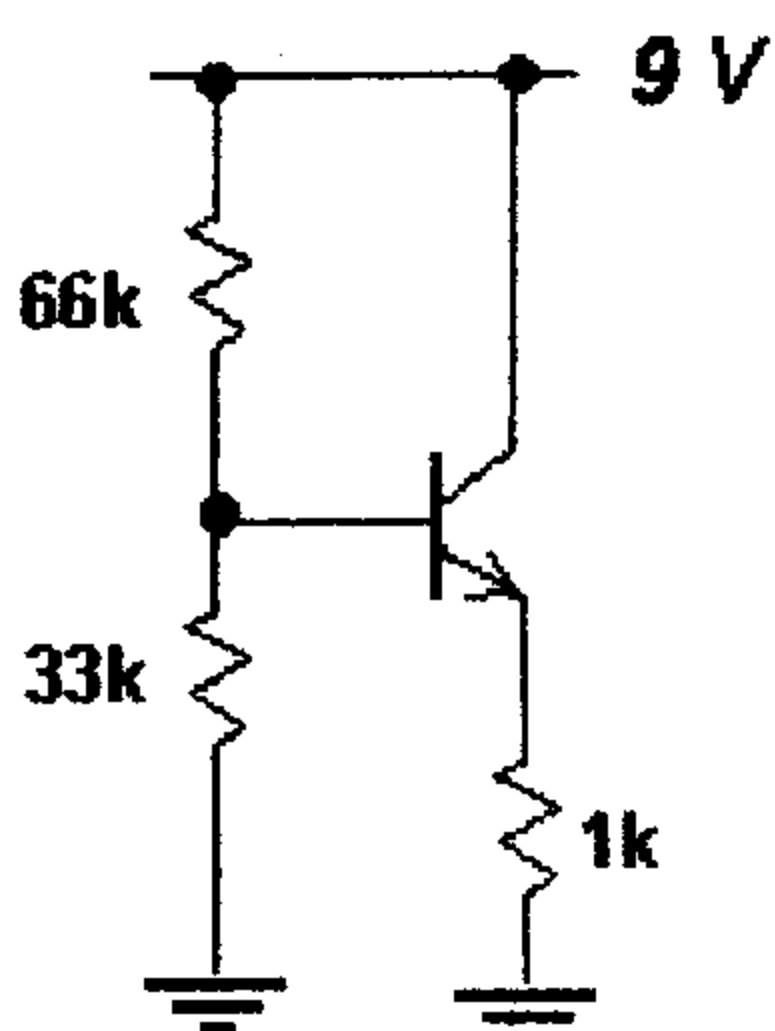

$$V_B \approx 9 \frac{33}{33+66} = 3 \text{ V}$$

$$V_E = 3 - 0.7 = 2.3 \text{ V}$$

$$I_E = \frac{2.3}{1k} = 2.3 \text{ mA} \approx I_C$$

$$V_{CE} = 9 - 2.3 = 6.7 \text{ V}$$


$$I_C = \underline{2.3 \text{ mA}}$$

$$V_{CE} = \underline{6.7 \text{ V}}$$

q:32

3. Find the currents as indicated in the circuit below. Assume the opamp to be ideal, and $\beta=50$ for the BJT.

9:32

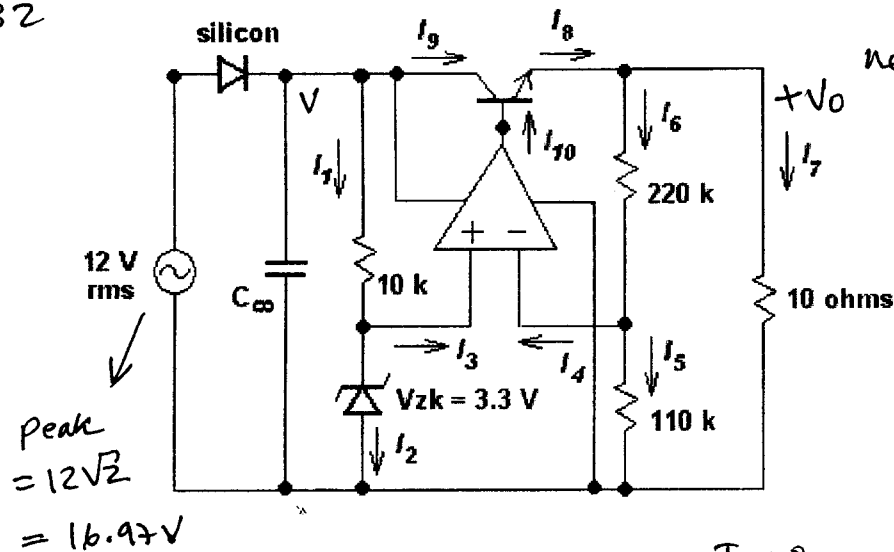

negative fb

$$V_+ = V_-$$

$$V_+ = 3.3V$$

$$I_1 = 1.29mA$$

$$I_2 = 1.29mA$$

$$I_3 = 0$$

$$I_4 = 0$$

$$I_5 = 0.03mA$$

$$I_6 = 0.03mA$$

$$I_7 = 0.99A$$

$$I_8 = 0.99A$$

$$I_9 = 0.97A$$

$$I_{10} = 19.4mA$$

$$V = 16.97 - 0.7 = 16.27V$$

$$I_3 = 0$$

$$I_4 = 0$$

$$I_1 = \frac{V - V_{zk}}{10k} = \frac{16.27 - 3.3}{10k} = 1.29mA$$

$$I_2 = I_1 \text{ because } I_3 = 0$$

$$I_5 = \frac{3.3}{110k} = 0.03mA$$

$$I_6 = I_5 = 0.03mA$$

$$V_0 = 110 \times I_5 + 220 \times I_6 = 9.9V$$

$$I_7 = \frac{9.9V}{10} = 0.99A$$

$$I_8 = I_6 + I_7 = 0.99A + 0.03mA \approx 0.99A$$

$$I_9 \approx \frac{\beta}{\beta+1} I_8 = \frac{50}{51} \times 0.99 = 0.97A$$

$$I_{10} = \frac{I_8}{51} = \frac{0.99}{51} = 0.0194A = 19.4mA$$

9:38