


I have neither given nor received unauthorized help with this exam, nor do I have reason to believe that anybody else has.

ID No: ERKAYA Name: SOLUTIONS Signature: _____

1) The BJT in the amplifier circuit below has $I_C = 1.5 \text{ mA}$ and $V_{CE} = 2.5 \text{ V}$. What should be the values of R and R_E ? Calculate the input resistance, output resistance and voltage gain of the amplifier circuit.

(Assume silicon BJT with $\beta = 200$) $V_A = 750 \text{ V}$

5:30

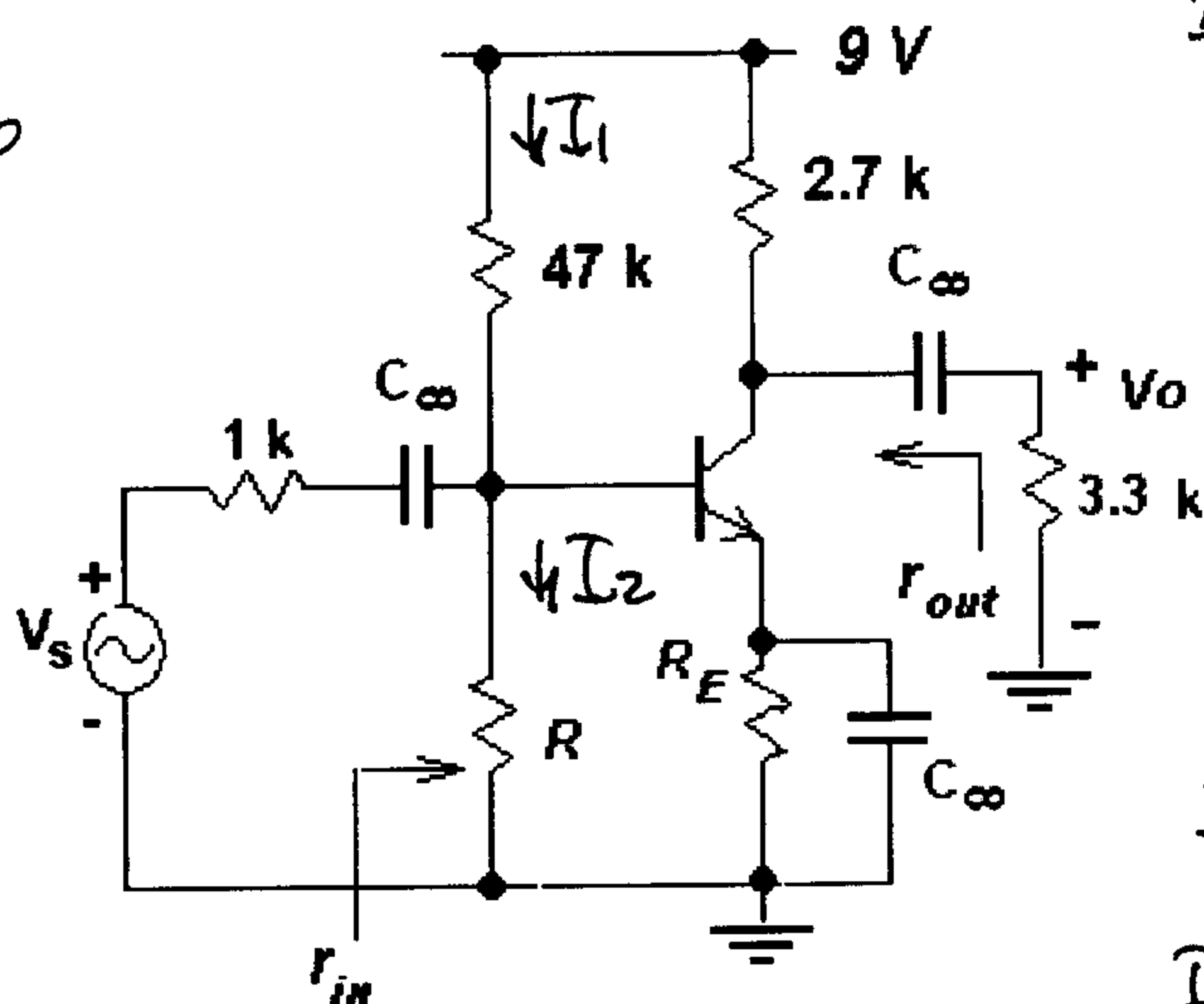

$$I_C \approx I_E \quad (R_E + R_C)I_C + V_{CE} = 9 \text{ V}$$

$$R_E = \frac{9 - V_{CE}}{I_C} - R_C = \frac{9 - 2.5}{1.5} - 2.7 = 1.63 \text{ k}\Omega$$

$$V_B = I_E R_E + V_{BE} = 1.5 \times 1.63 + 0.7 = 3.15 \text{ V}$$

$$I_1 = \frac{9 - 3.15}{47} = 0.1245 \text{ mA}$$

$$I_B = \frac{I_C}{\beta} = \frac{1.5}{200} = 0.0075 \text{ mA}$$

$$I_2 = I_1 - I_B = 0.1170 \text{ mA}$$

R	26.93k
R_E	1.63k
r_{in}	2.78k
r_{out}	2.7k
V_o/V_s	-65.52

$$R = \frac{V_B}{I_2} = \frac{3.15}{0.117} = 26.93 \text{ k}\Omega$$

Small signal Eq. ch: $r_o \approx \frac{V_A}{I_C} = \frac{750}{1.5} = 500 \text{ k}\Omega \gg R_C \rightarrow \text{ignore } r_o$

$$g_m = \frac{I_C}{V_T} = \frac{1.5}{0.025} = 60 \text{ mA/V}$$

$$r_{\pi} = \frac{\beta}{g_m} = \frac{200}{60} = 3.33 \text{ k}\Omega$$

$$R_B = R \parallel 47 \text{ k} = 26.93 \parallel 47 = 17.12 \text{ k}\Omega$$

$$r_{in} = r_{\pi} \parallel R_B = 3.33 \parallel 17.12 = 2.78 \text{ k}\Omega$$

$$r_{out} = 2.7 \text{ k}\Omega$$


$$\frac{V_o}{V_s} = \frac{V_o}{V_i} \cdot \frac{V_i}{V_s} = -89.1 \times 0.735 = -65.52$$

$$\frac{V_o}{V_i} = -g_m (2.7 \parallel 3.3) = -60 (2.7 \parallel 3.3) = -89.1$$

$$\frac{V_i}{V_s} = \frac{r_{in}}{R_s + r_{in}} = \frac{2.78}{1 + 2.78} = 0.735$$

5:40

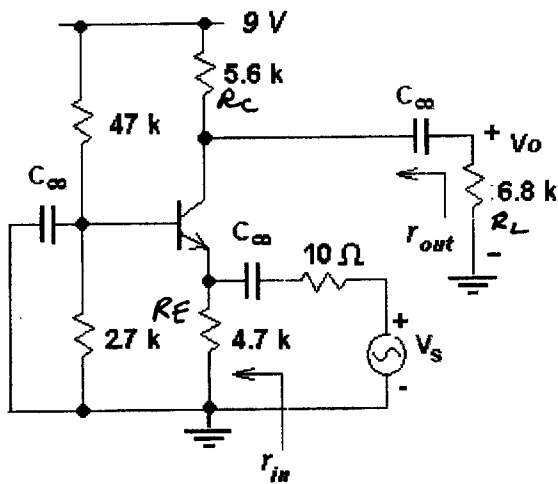2) Find the operating point for the silicon BJT in the amplifier circuit below. Calculate the input resistance, output resistance and voltage gain of the amplifier circuit. (Assume $\beta=200$, $V_A = 500$ V)



$$V_{TH} = 9 \frac{27}{47+27} = 3.28 \text{ V}$$

$$R_{TH} = (47 \parallel 27) \text{ k}\Omega = 17.15 \text{ k}\Omega$$

$$I_c = \frac{\beta (V_{TH} - V_{BE})}{(\beta+1) R_E + R_{TH}}$$


$$= \frac{200 (3.28 - 0.7)}{201 \times 4.7 + 17.15} = 0.54 \text{ mA}$$

$$I_c \approx I_E,$$

$$V_{CE} = 9 - 0.54 (5.6 + 4.7) = 3.47 \text{ V}$$

I_c	0.54 mA
V_{CE}	3.47
r_{in}	46.1 Ω
r_{out}	5.6 k Ω
$\frac{v_o}{v_s}$	54.39

Small Signal Eq. Ckt:

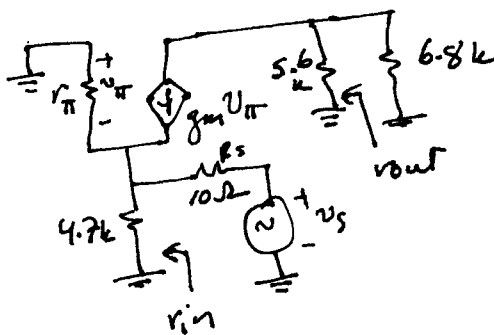

$$r_o \approx \frac{V_A}{I_c} = \frac{500}{0.54} = 926 \text{ k}\Omega$$

$$r_o \gg R_c \rightarrow \text{ignore } r_o$$

$$r_{in} = 4.7 \parallel \frac{9.26}{201} \text{ k}\Omega$$

$$= 46.1 \Omega$$

$$r_{out} \approx R_c = 5.6 \text{ k}\Omega$$

$$g_m = \frac{I_c}{V_T} = \frac{0.54}{0.025} = 21.6 \text{ mA/V}$$

$$r_{\pi} = \frac{\beta}{g_m} = \frac{200}{21.6} = 9.26 \text{ k}\Omega$$

$$\frac{v_o}{v_s} = \frac{v_o}{v_i} \frac{v_i}{v_s}$$

$$\frac{v_i}{v_s} = \frac{r_{in}}{R_s + r_{in}} = \frac{46.1}{10 + 46.1} = 0.82$$

$$\frac{v_o}{v_i} = g_m (R_c \parallel R_L) = 21.6 (5.6 \parallel 6.8) = 66.33$$

$$\frac{v_o}{v_s} = 66.33 \times 0.82 = 54.39$$