

I have neither given nor received any unauthorized help with this exam.

ID number: _____ Name: ERKAYA Signature: _____

30p 1) A sinusoidal signal source which has a 1-kohm output resistance is connected to an amplifier set which is made of a pre amplifier and a power amplifier cascade as shown below. The preamplifier has 2.5 kohm input resistance, 10 kohm output resistance and an open-circuit voltage gain of 400 whereas the power amplifier has 10 kohm input resistance, 4 ohm output resistance and an open-circuit voltage gain of 1. An 8-ohm load is connected to the output of the power amplifier. The output voltage across the load is 10 *sin* ωt V.



- Find the signal amplitude when the source is open-circuit.
- Find the power delivered to the load.
- Find the total power dissipated in the amplifiers
- Find the overall efficiency of the system

$$V_s = 0.105 \text{ V}$$

$$P_L = 6.25 \text{ W}$$

$$P_{diss} = 18.95 \text{ W}$$

$$\eta = 24.8\%$$

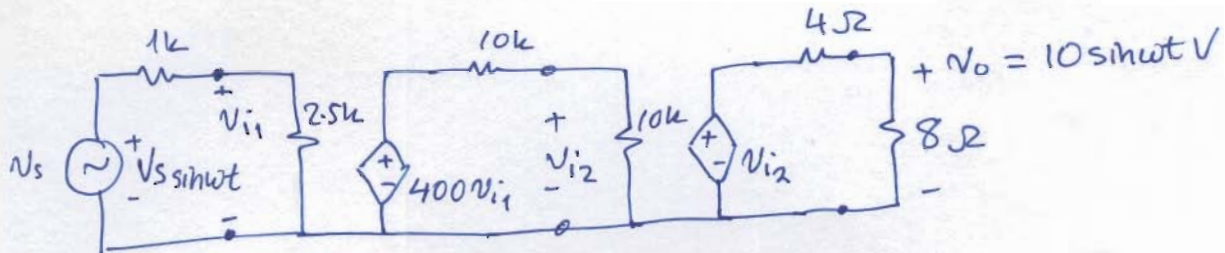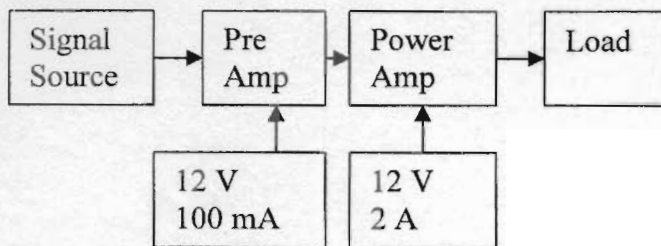

$$\frac{V_o}{V_s} = (400)(1) \frac{2.5}{1+2.5} \frac{10}{10+10} \frac{8}{4+8} = 95.24$$

a) $V_s = \frac{10}{95.24} = 0.105 \text{ V}$

b) $P_L = \frac{V_{o,rms}^2}{R_L} = \frac{(10/\sqrt{2})^2}{8} = \frac{100}{16} = 6.25 \text{ W}$

c) The power supplied to the amplifiers $P_{DC} = 12(2 + 0.1) = 25.20 \text{ W}$
 Out of this power 6.25W is supplied to the load. The rest
 is dissipated in the amplifiers $P_{diss} = P_{DC} - P_L = 25.20 - 6.25$
 (The signal power at the input is ignored) $= 18.95 \text{ W}$

d) $\eta = \frac{P_L}{P_{DC}} = \frac{6.25}{25.20} = 0.248 = 24.8\%$

30p



2) A full-wave rectifier circuit operates at 50 Hz and rectifies the ac voltage at the output of a transformer. The rectifier produces a peak voltage of 12 V at a constant load current of 2A. The ripple voltage at the output is desired to be less than 0.2 V. Each diode in the circuit has a voltage drop of 0.7 V when it is on.

- Draw a circuit diagram for such a rectifier circuit
- Find the minimum value of the filter capacitor
- Estimate the average power dissipation in each diode
- If the transformer has 80% efficiency, what should be the power-rating of the transformer. (Explain briefly)

$$\min C = \frac{0.1 F}{}$$

$$P_{\text{diode}} = \frac{0.7 W}{}$$

$$\min 33.25 W$$

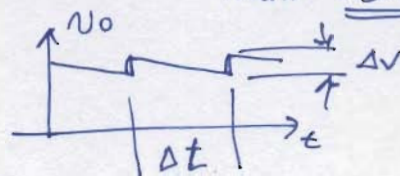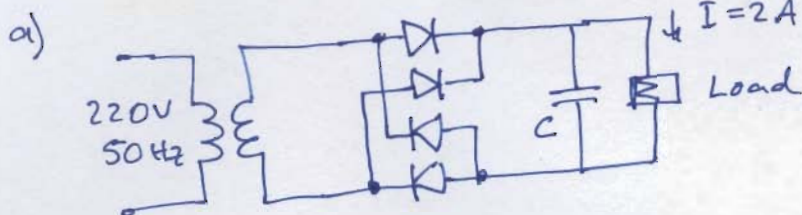

- b) The current in the capacitor equals the load current (in amplitude)
- $$i_c = C \frac{dV_c}{dt} = C \frac{\Delta V}{\Delta t}$$
- $$\Delta V = \text{ripple voltage} = 0.2 V$$
- $$\Delta T = \frac{T}{2} = \frac{1}{100} s$$
- $$C = I \frac{\Delta t}{\Delta V} = 2 \frac{\frac{1}{100}}{0.2} = 0.1 F$$

- c) Two diodes are on over half the period. The diodes are on over a very short time. The voltage of the diodes are constant when the diodes are on.

$$P_{\text{diode}} = \frac{1}{T} \int_0^{T/2} V_d i_d dt = V_d \frac{1}{T} \int_0^{T/2} i_d dt = V_d \frac{1}{2} \underbrace{\frac{1}{T/2} \int_0^{T/2} i_d dt}_{I \text{ average load current}}$$

$$P_{\text{diode}} = \frac{V_d I}{2} = 0.7 \times \frac{2}{2} = 0.7 W$$

- d) The transformer must provide power for the load and for the dissipation on diodes.

$$P_{\text{out}} = 4 \times P_{\text{diode}} + P_L = 4 \times 0.7 + 2 \times (12 - 0.1) = 26.60 W$$

$$\eta = \frac{P_{\text{out}}}{P_{\text{in}}} = 0.8$$

$$P_{\text{in}} = \frac{P_{\text{out}}}{\eta} = \frac{26.60}{0.8} = \underline{\underline{33.25 W}}$$

Note: The transformer output voltage (rms) may be found as follows:


$$\frac{V_{\text{peak}} + 2 \times 0.7}{\sqrt{2}} = \frac{12 + 1.4}{\sqrt{2}} = 9.48 V_{\text{rms}}$$

40p

3) Find I and V in the circuits below. Assume silicon BJTs with a common emitter current gain of 300.

$$I = 0.99 \text{ mA}$$

$$V = 2.82 \text{ V}$$

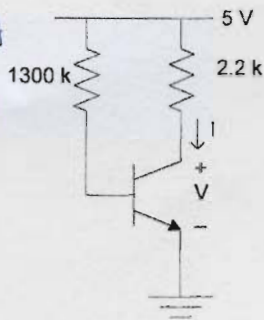


$$I_B = \frac{5 - 0.7}{1300 \text{ k}} = 0.0033 \text{ mA}$$

$$I_C = 300 \times 0.0033 = 0.99 \text{ mA}$$

$$V = 5 - 2.2 \times 0.99 = 2.82 \text{ V}$$

$$I = 2.18 \text{ mA}$$

$$V = 0.2 \text{ V}$$

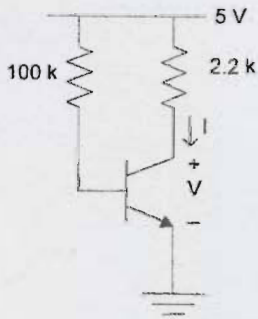

$$I_B = \frac{5 - 0.7}{100} = 0.43 \text{ mA}$$

$$I_C = 300 \times 0.43 = 129 \text{ mA (expected)}$$


$$V = 5 - 129 \times 2.2 = -278.8 \text{ V (not possible)}$$

Saturation $\rightarrow V = 0.2 \text{ V}$

$$I = \frac{5 - 0.2}{2.2} = 2.18 \text{ mA}$$

$$I = 1.7 \text{ mA}$$

$$V = 6.39 \text{ V}$$

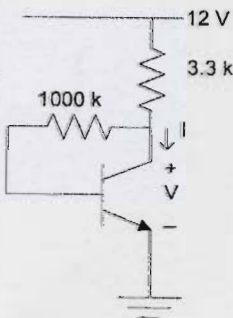

$$V_{BE} + I_B(1000 + 3.3(\beta + 1)) = 12$$


$$I_B = \frac{12 - 0.7}{1000 + 301 \times 3.3} = 0.0057 \text{ mA}$$

$$I_C = 300 \times 0.0057 = 1.7 \text{ mA}$$

$$V \approx 12 - 3.3 \times 1.7 = 6.39 \text{ V}$$

$$I = 5.7 \text{ mA}$$

$$V = 6.3 \text{ V}$$

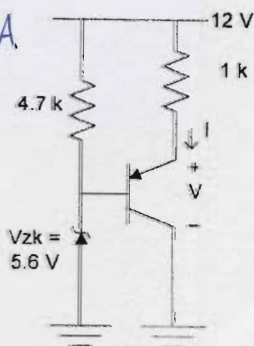

$$V = 5.6 + 0.7 = 6.3 \text{ V}$$

$$I = \frac{12 - 6.3}{1} = 5.7 \text{ mA}$$