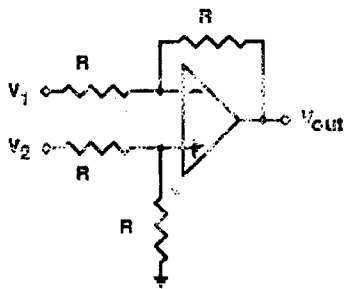


ELECTRONICS I * Midterm 1 * 60 minutes * closed books and notes

I have neither given nor received unauthorized help with this exam, nor do I have reason that anybody else has

ID no : _____ Name: _____ Signature: _____

1) For the circuit given below, express v_{out} as a function of v_1 and v_2 . What is the input resistance seen by v_1 alone (i.e., the other source is zero)? By v_2 alone? By a source connected between two input terminals? By a source connected to both input terminals simultaneously?



use superposition

$$v_1 = 0 \rightarrow v_{out} = \left(\frac{R+R}{R} \right) v_+ \quad (\text{noninv. amp})$$

$$v_+ = v_2 \frac{R}{R+R}$$

$$v_o = v_2$$

$$v_2 = 0 \rightarrow \text{non-inverting amp } v_{out} = -\frac{R}{R} v_1 = -v_1$$


Superposition $v_{out} = v_2 - v_1$

$$r_{in1} = \frac{v_1 - 0}{I_1} = \frac{v_1}{\frac{v_1}{R}} = R$$

$$r_{in2} = R + R = 2R$$

$$r_{indiff} = \frac{V}{I}$$

where

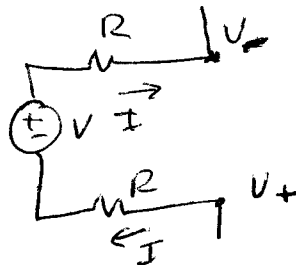

$$v_- = v_+ \quad (\text{neg. f.b.})$$


$$v_- + IR - v_+ + IR = v_+$$

$$2IR = V$$

$$2R = \frac{V}{I}$$

$$r_{incom} = \frac{V}{I}$$

where

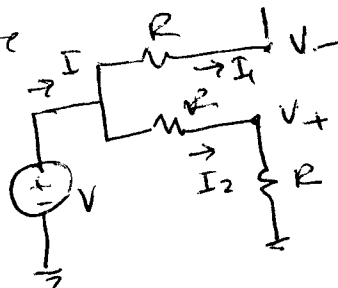

$$v_+ = v_-$$

$$v_+ = \frac{V}{2}$$

$$I = I_1 + I_2$$

$$I_1 = I_2 = \frac{v_+ - \frac{V}{2}}{R} = \frac{V}{2R}$$


$$I = 2 \frac{V}{2R} = \frac{V}{R}$$

hence $\frac{V}{I} = R$

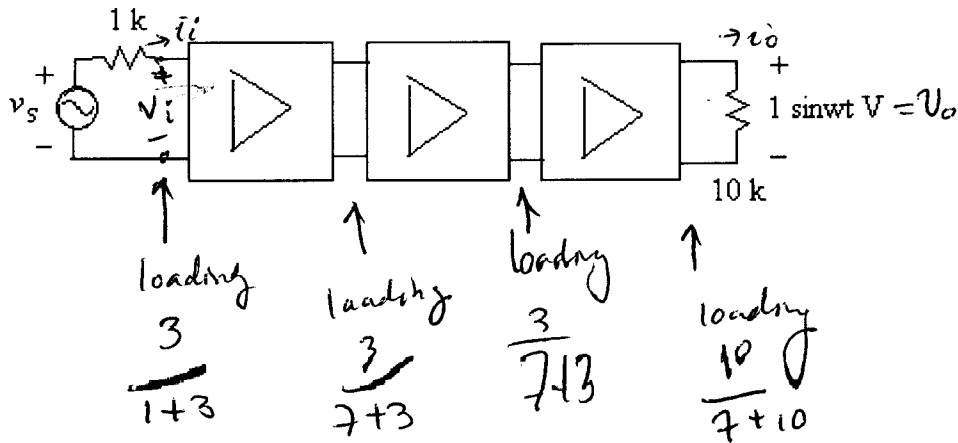2) The amplifiers used in the circuit are identical with $r_{in} = 3 \text{ k}\Omega$, $r_{out} = 7 \text{ k}\Omega$, open-circuit voltage gain $= -80 \text{ v/v}$, and each amplifiers draw 100 mA from a 9V power supply regardless of the signal amplitude.

- Find the overall voltage gain
- Find the overall power gain
- Find the overall current gain
- Find the efficiency of the amplifier circuit

$$\begin{aligned} v_o/v_s &= -20329 \\ p_o/p_i &= 220411482 \\ i_o/i_s &= -8131 \\ \eta &= 1.85 \times 10^{-3} \% \end{aligned}$$



$$\frac{v_o}{v_i} = (-80)(-80)(-80) \frac{3}{10} \frac{3}{10} \frac{10}{17} = -27105$$

$$\frac{v_o}{v_s} = \frac{v_o}{v_i} \cdot \frac{3}{1+3} = -20329$$


$$A_i = \frac{i_o}{i_s} = \frac{v_o/10k}{v_s/(1+3)} = -20329 \frac{4}{10} = -8131$$

$$\frac{p_o}{p_i} = \frac{v_o \cdot i_o}{v_i \cdot i_i} = -27105 \times (-8131) = 220411482$$

$$\begin{aligned} \text{efficiency} = \eta &= \frac{p_o}{p_{DC}} = \frac{\left(\frac{1}{\sqrt{2}}\right)^2 \frac{1}{10k}}{3 \times 100 \times 9} = \frac{0.05 \text{ mW}}{2700 \text{ mW}} \\ &= 1.85 \times 10^{-5} \\ &= 1.85 \times 10^{-3} \% \end{aligned}$$

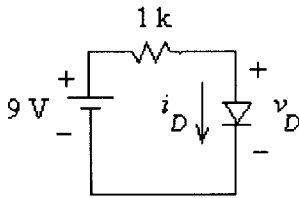3) Use the non-linear diode model to find the voltage and current of the diode in the circuit below. ($I_s = 1 \text{ nA}$, $V_T = 0.025 \text{ V}$, $\eta = 1$) Calculate the voltage with an accuracy of 1 mV; current, 1 μA .

$$v_D = \underline{0.3992 \text{ V}} \quad i_D = \underline{8.6008 \text{ mA}}$$



$q = 40$

$$\eta = 1, \quad I_s = 10^{-9} \text{ A}$$

$$I_D = I_s (e^{v_D / \eta V_T} - 1)$$

$$v_D = \eta V_T \ln \left(\frac{I_D}{I_s} + 1 \right)$$

$$v_D + i_D \cdot 1k = 9$$

$$i_D = \frac{9 - v_D}{1k}$$

$$\text{initial guess: } v_{D0} = 0 \rightarrow i_{D0} = 9 \text{ mA} = 9000 \mu\text{A}$$

$$v_{D1} = 0.025 \ln \left(\frac{9 \times 10^{-3}}{10^{-9}} + 1 \right) = 0.4003 \text{ V}$$

$$i_{D1} = \frac{9 - 0.4003}{1k} = 8.5997 \text{ mA}$$

$$v_{D2} = 0.025 \ln \left(\frac{8.5997 \times 10^{-3}}{10^{-9}} + 1 \right) = 0.3992 \text{ V}$$

$$i_{D2} = \frac{9 - 0.3992}{1k} = 8.6008 \text{ mA}$$

$$v_{D3} = 0.025 \ln \left(\frac{8.6008 \times 10^{-3}}{10^{-9}} + 1 \right) = 0.3992 \text{ V}$$

$$i_{D3} = \frac{9 - 0.3992}{1k} = 8.6008 \text{ mA}$$

$q = 49$