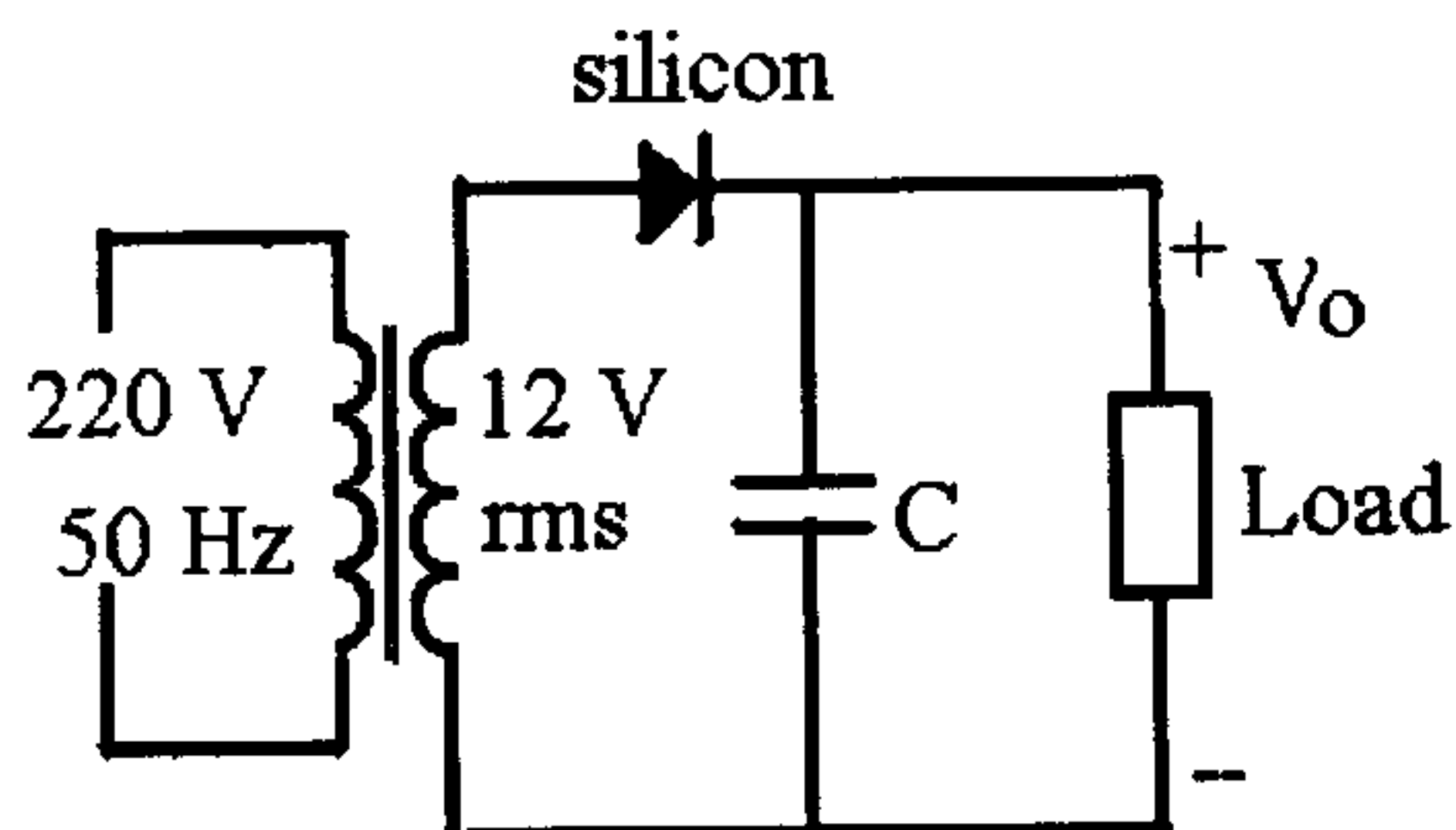


I have neither given nor received unauthorized help with this exam, nor do I believe anyone else has.

ID number: ERKAYH Name: SOLUTIONS Signature: _____

3) For the rectifier circuit below, the peak-to-peak ripple is required to be less than 4 % of the peak voltage. Find the minimum value of C for a load current of 400 mA. min C = _____



$$\text{peak output voltage} = 12\sqrt{2} - 0.7 = 16.27 \text{ V}$$

$$4\% \rightarrow 0.65 \text{ V}$$

$$I = C \frac{\Delta V}{\Delta T} \rightarrow C = \frac{I}{\frac{\Delta V}{\Delta T}} = \frac{0.4}{\frac{0.65}{\frac{1}{50}}} = 0.0123 \text{ F} = 12292 \mu\text{F}$$

$$\Delta T = \frac{1}{50} \text{ s}$$


$$\Delta V = 0.65 \text{ V}$$

$$I = 0.4 \text{ A}$$

9:30

2) Find the operating points of the transistors given below: ($\beta = 100$)


q:30

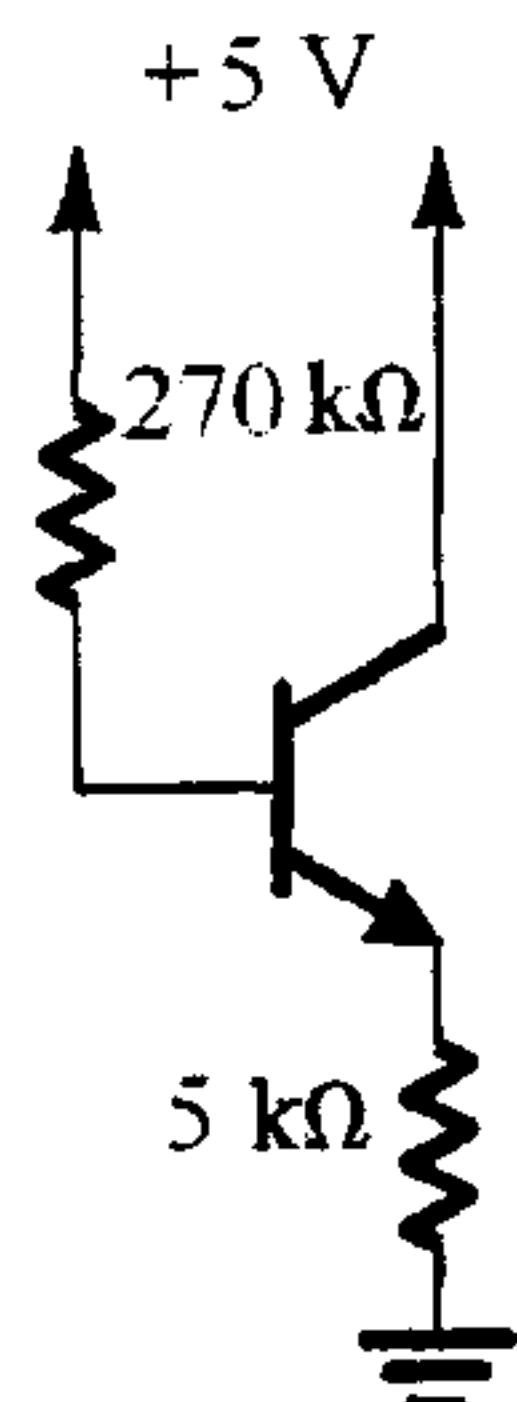

$$I_C = \frac{100(5 - 0.7)}{101 \times 5 + 270} = 0.554 \text{ mA}$$

$$V_{CE} = 5 - 5 \times 0.554 = 2.22 \text{ V}$$
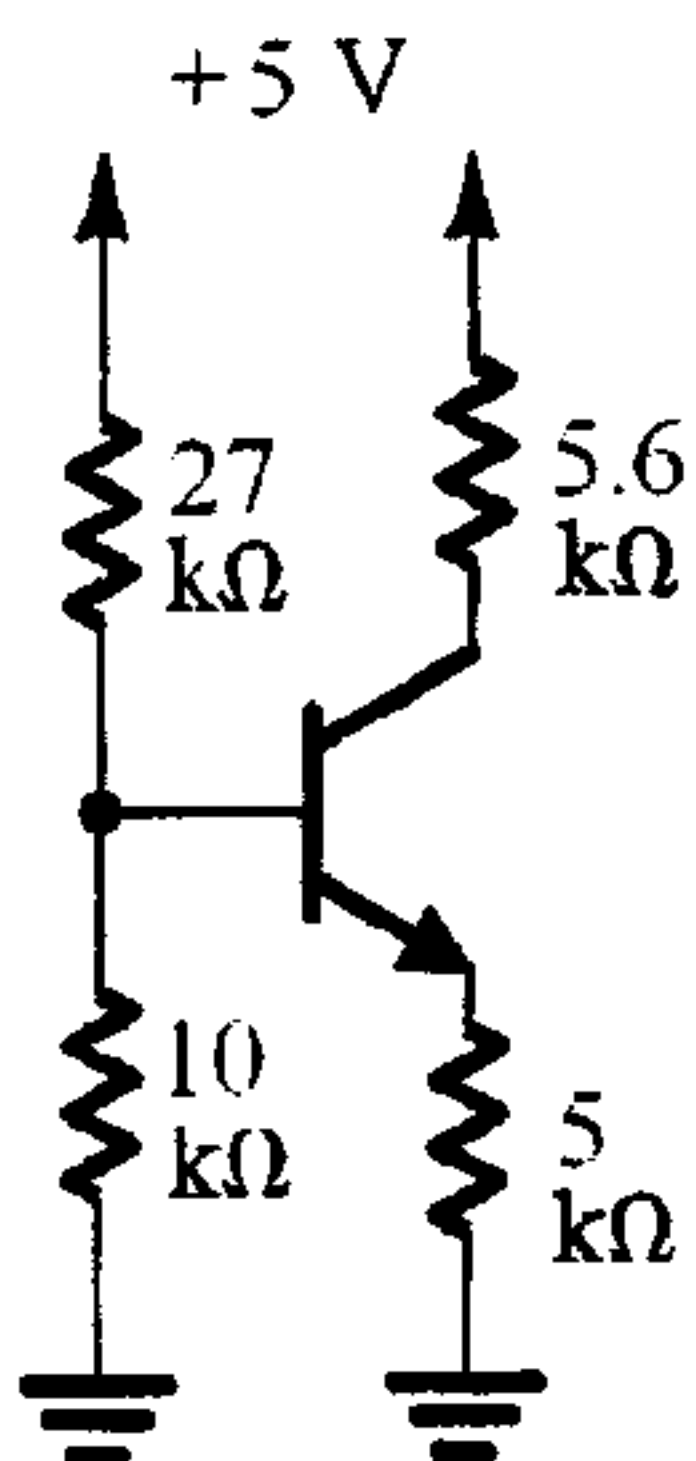
$$I_C = \underline{0.554 \text{ mA}} \quad V_{CE} = \underline{2.22 \text{ V}}$$



$$V_{th} = 5 \times \frac{10}{27 + 10} = 1.35 \text{ V}$$


$$R_{th} = 27 \parallel 10 = 7.29 \text{ k}\Omega$$

$$I_C = \frac{\beta(V_{th} - V_{BE})}{(\beta + 1)R_E + R_{th}}$$

$$I_C = \frac{100(1.35 - 0.7)}{101 \times 5 + 7.29} = 0.127 \text{ mA}$$

$$V_{CE} \approx 5 - 0.127 \times 5.6 - 0.127 \times 5 = 3.65 \text{ V}$$
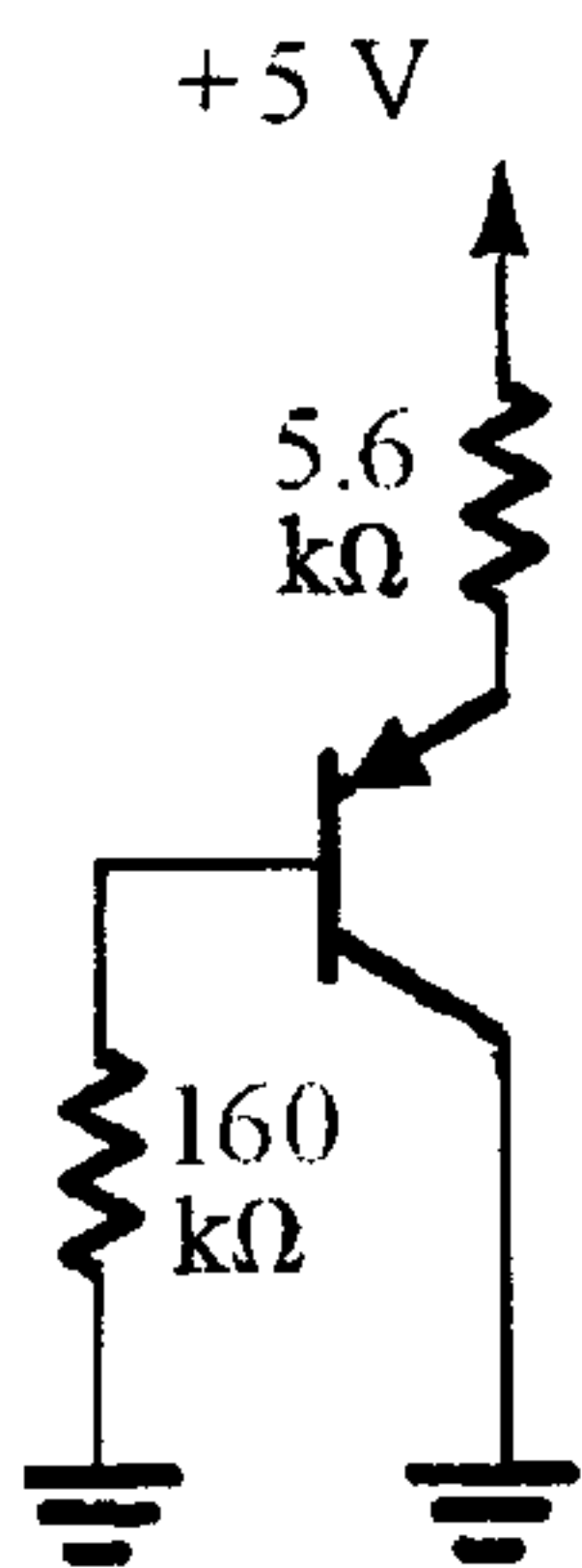
$$I_C = \underline{0.127 \text{ mA}} \quad V_{CE} = \underline{3.65 \text{ V}}$$




$$160 I_B + V_{EB} + 5.6 \times 101 \times I_B = 5 \text{ V}$$

$$I_C = \beta I_B = \beta \frac{5 - 0.7}{101 \times 5.6 + 160} = 0.592 \text{ mA}$$

$$V_{EC} = 5 - 5.6 \times 0.592 = 1.68 \text{ V}$$
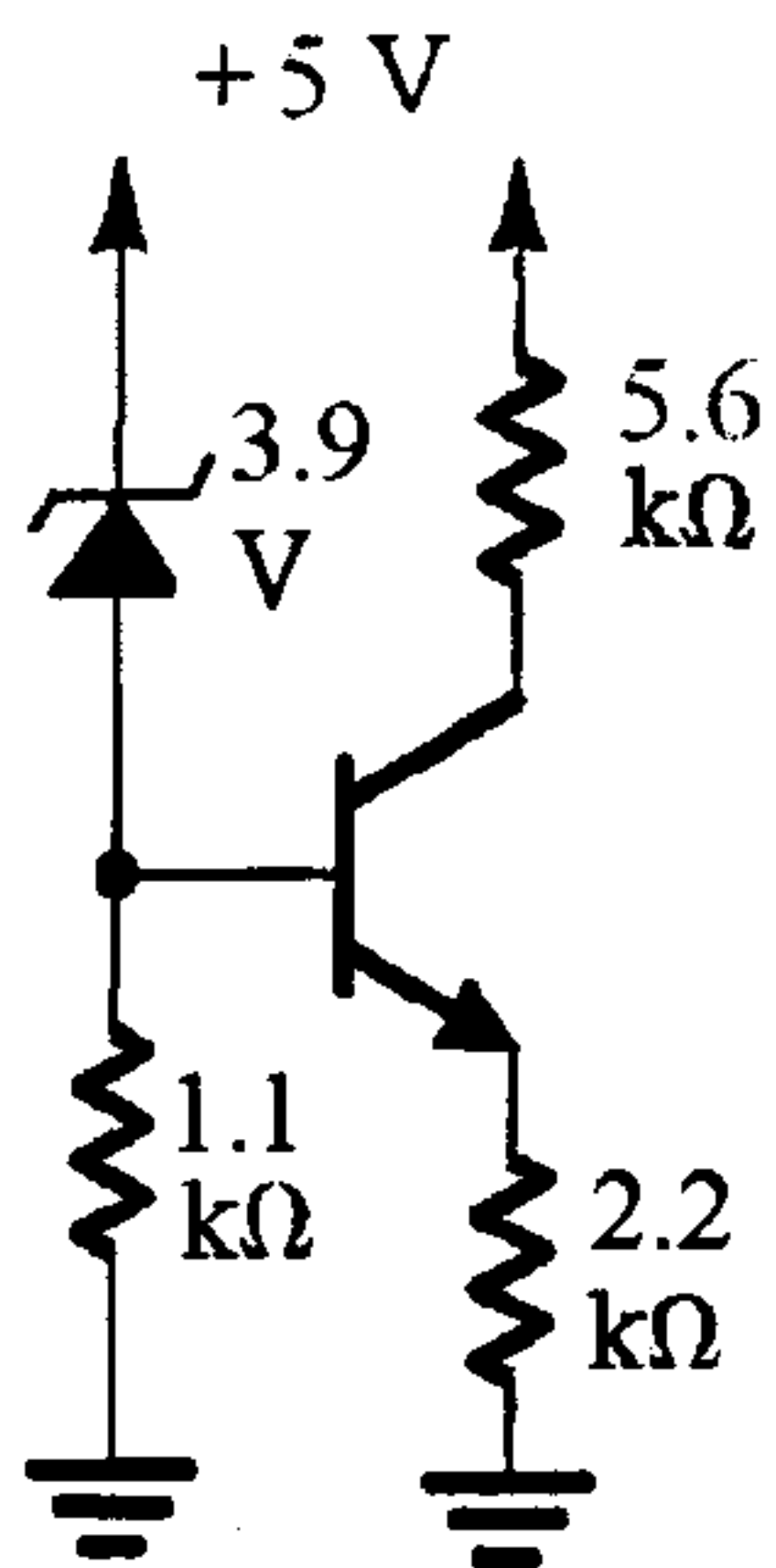
$$I_C = \underline{0.59 \text{ mA}} \quad V_{EC} = \underline{1.68 \text{ V}}$$



$$V_B = 5 - 3.9 = 1.1 \text{ V}$$

$$V_E = 1.1 - 0.7 = 0.4 \text{ V}$$

$$I_E = \frac{0.4}{2.2} = 0.182 \text{ mA}$$

$$I_C \approx I_E = 0.182 \text{ mA}$$


$$V_{CE} \approx 5 - 0.182(5.6 + 2.2) = 3.58 \text{ V}$$

$$I_C = \underline{0.18 \text{ mA}} \quad V_{CE} = \underline{3.58 \text{ V}}$$

q:39

3) Design a common collector BJT amplifier such that the BJT has 1.5 mA collector current. Find its voltage gain, input resistance and output resistance when it is operated with a signal source whose output resistance is 1 kohm and a load of 75 ohms. ($\beta=300$, $V_{CC}=9$ V)

Q:39

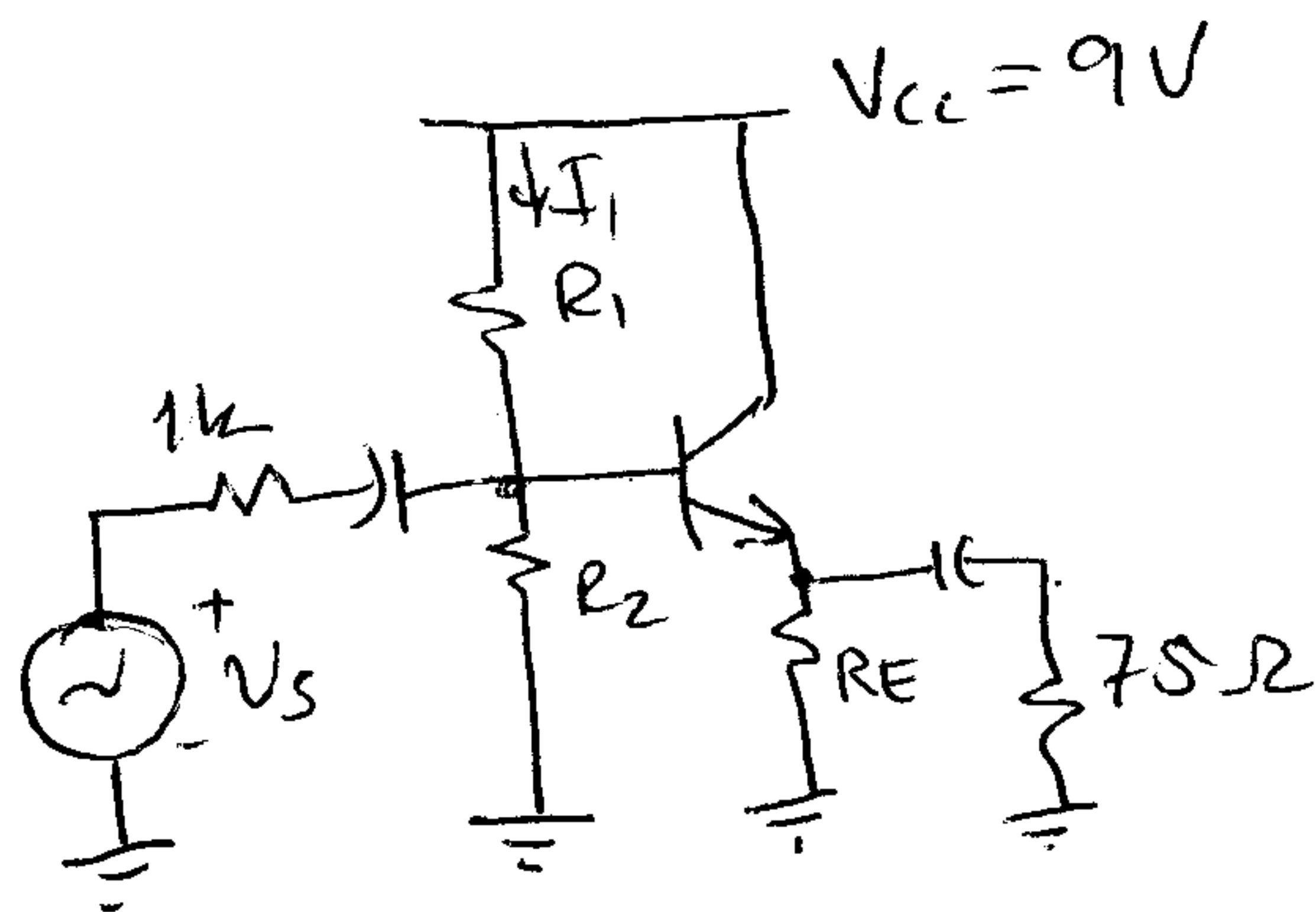

Let $V_{CE} \approx \text{half of } V_{CC}$

$$\rightarrow I_E R_E = 4.5V$$

$$R_E = \frac{4.5}{1.5} = 3k\Omega$$

$$I_B = \frac{1.5}{100} = 0.015 \text{ mA}$$

Let $I_1 \approx 20 I_B = 0.03 \text{ mA}$.


$$V_B = V_E + V_{BE} = 4.5 + 0.7 = 5.2 \text{ V}$$

$$I_{R1} \approx 9 - 5.2 = 3.8 \text{ V}$$

$$R_1 = \frac{3.8}{0.03} \approx 127 \text{ k}\Omega$$

$$R_2 = \frac{5.2}{0.03} = 173 \text{ k}\Omega$$

Small signal eq. ch

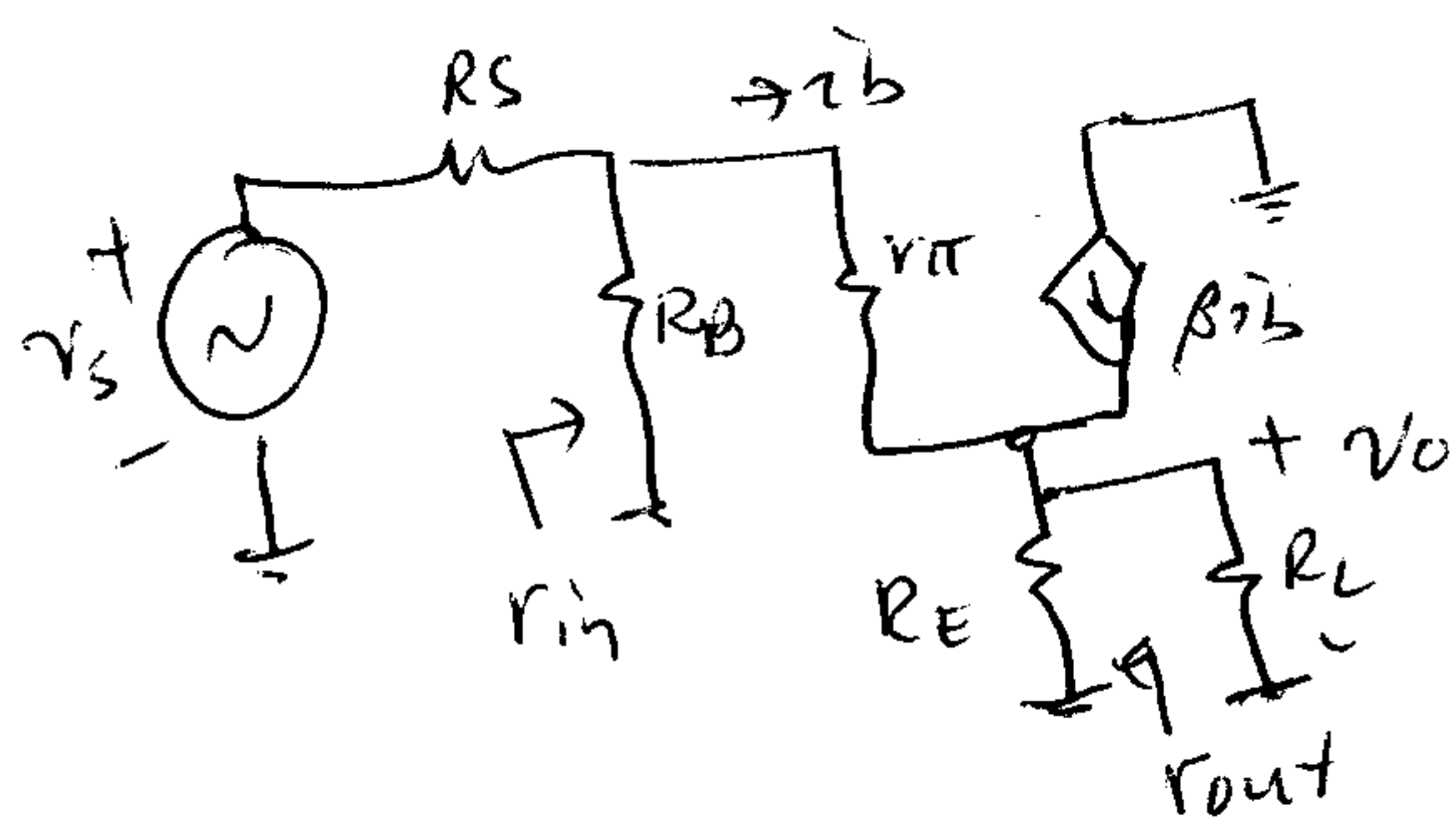

$$R_B = R_1 \parallel R_2 = 73.23 \text{ k}\Omega$$

$$g_m = \frac{1.5}{0.025} = 60 \text{ mA/V}$$

$$r_{\pi} = \frac{\beta}{g_m} = \frac{300}{60} = 5 \text{ k}\Omega$$

$$\frac{V_o}{V_i} = \frac{(\beta+1)(R_E \parallel R_L)}{r_{\pi} + (\beta+1)(R_E \parallel R_L)} \cdot \frac{r_{in}}{R_s + r_{in}} \approx \frac{301 \times (0.075 \parallel 3)}{5 + 301 \times (0.075 \parallel 3)} \cdot \frac{19.73}{1 + 19.73}$$

$$= 0.779$$

$$v_o/v_s = \underline{\hspace{2cm}}$$

$$r_{in} = \underline{\hspace{2cm}}$$

$$r_{out} = \underline{\hspace{2cm}}$$

$$r_{in} = R_B \parallel [r_{\pi} + (\beta+1)(R_E \parallel R_L)]$$

$$= 73.23 \parallel [5 + 301 \times 3 \parallel 0.075]$$

$$= 19.73 \text{ k}\Omega$$

$$r_{out} = R_E \parallel \frac{r_{\pi} + (R_B \parallel R_s)}{\beta+1}$$

$$= 3 \parallel \frac{5 + (73.23 \parallel 1)}{301} = 0.0198 \text{ k}\Omega$$

Q:50