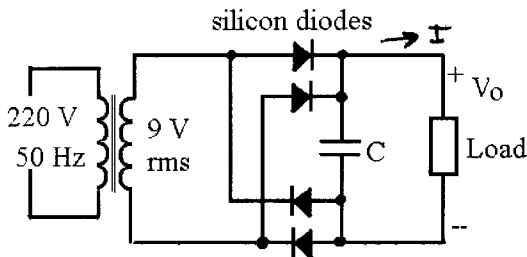


I have neither given nor received unauthorized help with this exam, nor do I believe anyone else has.

ID number: ERKAYA Name: SOLUTIONS Signature: _____

1) For the rectifier circuit below, find the peak-to-peak ripple and the average of the output voltage for a load current of 400 mA. ($C=1000\mu\text{F}$)




(Recommended time period for this question is 10 minutes.)

Peak-to-peak ripple voltage = 4V

Full-wave
rectifier with LP filter

Average of $V_o =$ 9.33V

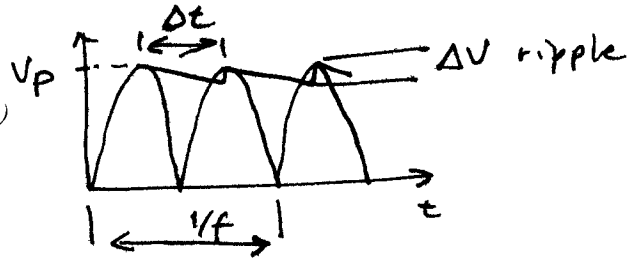


$$V_p \approx 9\sqrt{2} - 2 \times 0.7 = 11.33 \text{ V}$$

$$I = C \frac{\Delta V}{\Delta t} \rightarrow \Delta V = \frac{I \Delta t}{C} = \frac{0.4 \times \frac{1}{100}}{1000 \times 10^{-6}} = 4 \text{ V}$$

$$\langle V_o \rangle = V_p - \frac{\Delta V}{2} = 11.33 - 2 = 9.33 \text{ V}$$

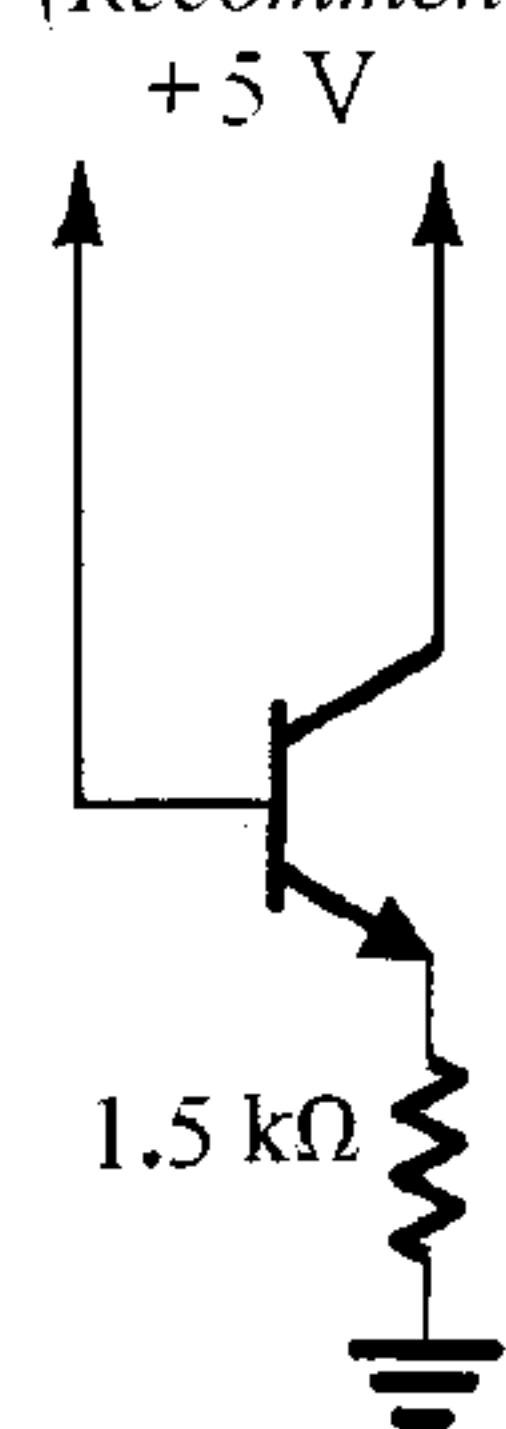2) Find the operating points of the transistors given below. Assume silicon BJTs with $\beta = 200$.
(Recommended time period for this question is 10 minutes.)




$$V_E = 5 - 0.7 = 4.3 \text{ V}$$

$$I_C \approx I_E = \frac{4.3}{1.5} = 2.87 \text{ mA}$$

$$V_{CE} = V_{BE} = 0.7 \text{ V}$$
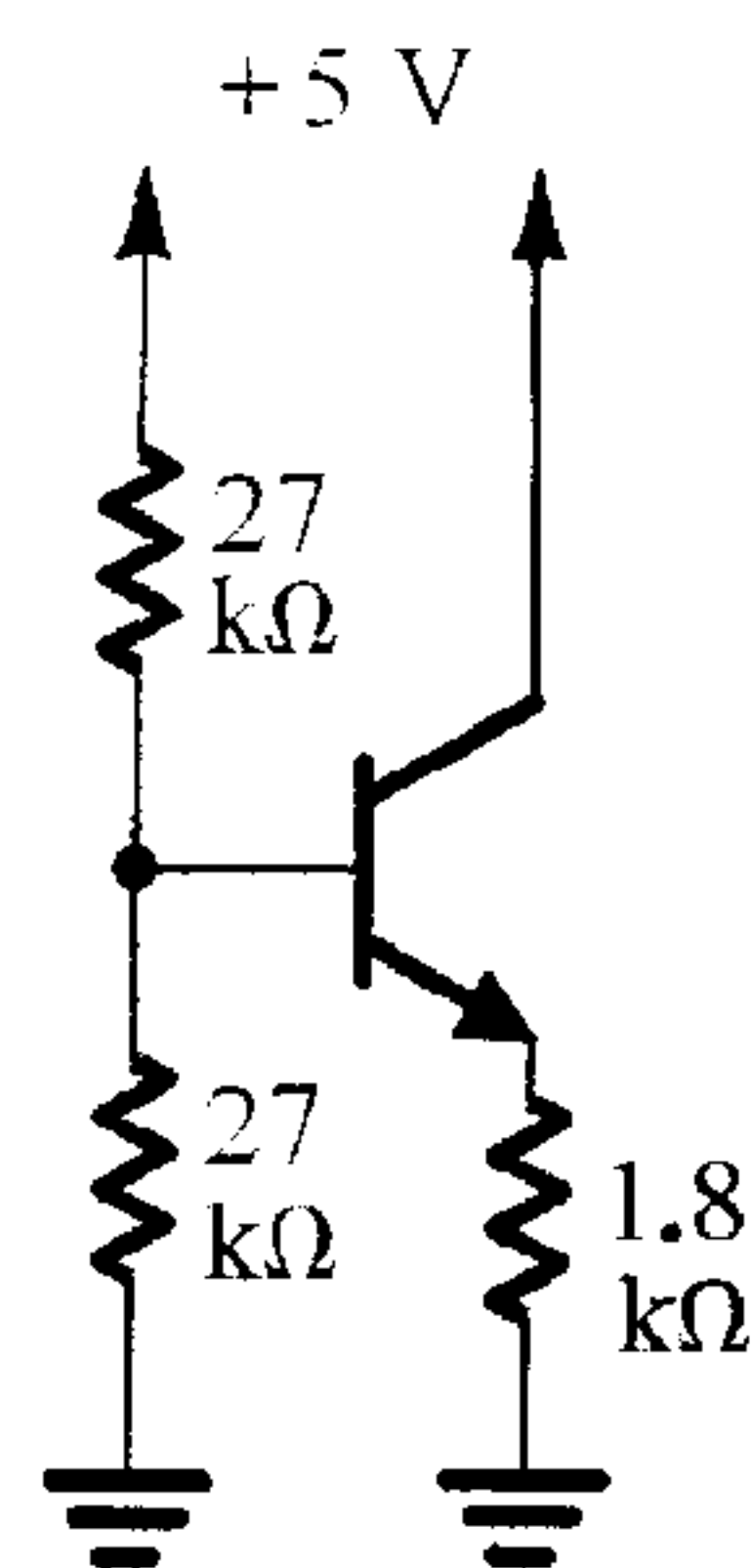
$$I_C = \underline{2.87 \text{ mA}} \quad V_{CE} = \underline{0.7 \text{ V}}$$




$$V_B \approx 5 \frac{27}{27+27} = 2.5 \text{ V}$$

$$V_E = 2.5 - 0.7 = 1.8 \text{ V}$$

$$I_C \approx I_E = \frac{1.8}{1.8} = 1 \text{ mA}$$


$$V_{CE} = 5 - 1.8 = 3.2 \text{ V}$$
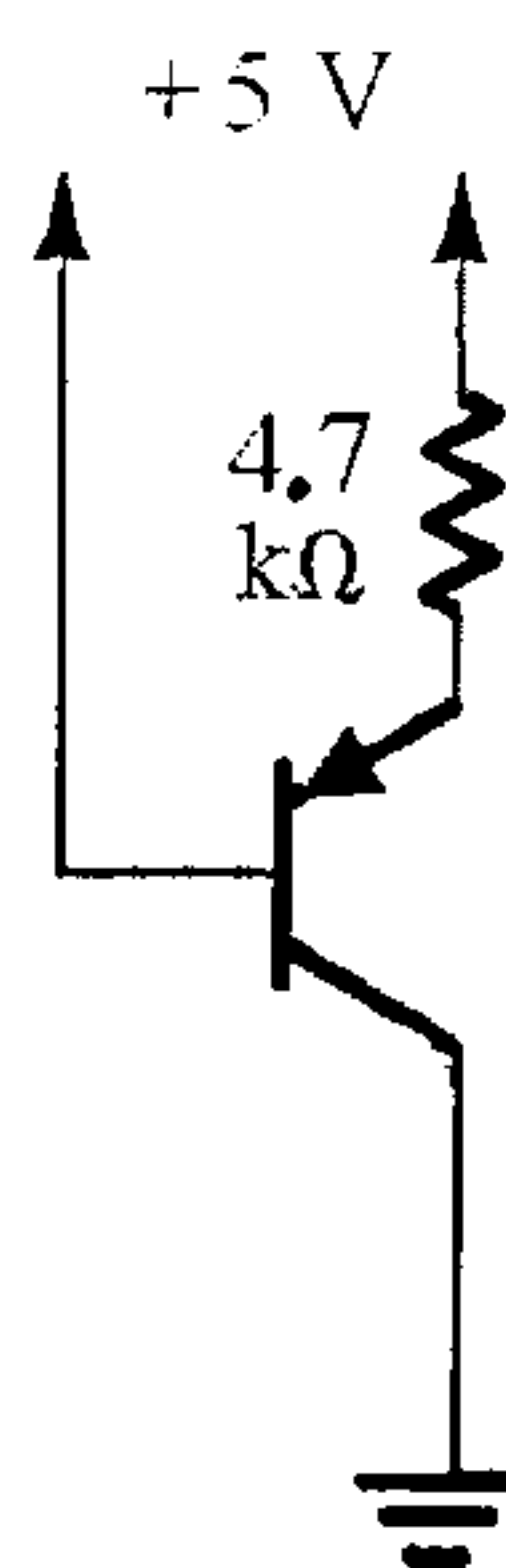
$$I_C = \underline{1 \text{ mA}} \quad V_{CE} = \underline{3.2 \text{ V}}$$



BE junction is not fwd biased
cut-off $I_C \approx 0$ $V_{EC} = 5 \text{ V}$
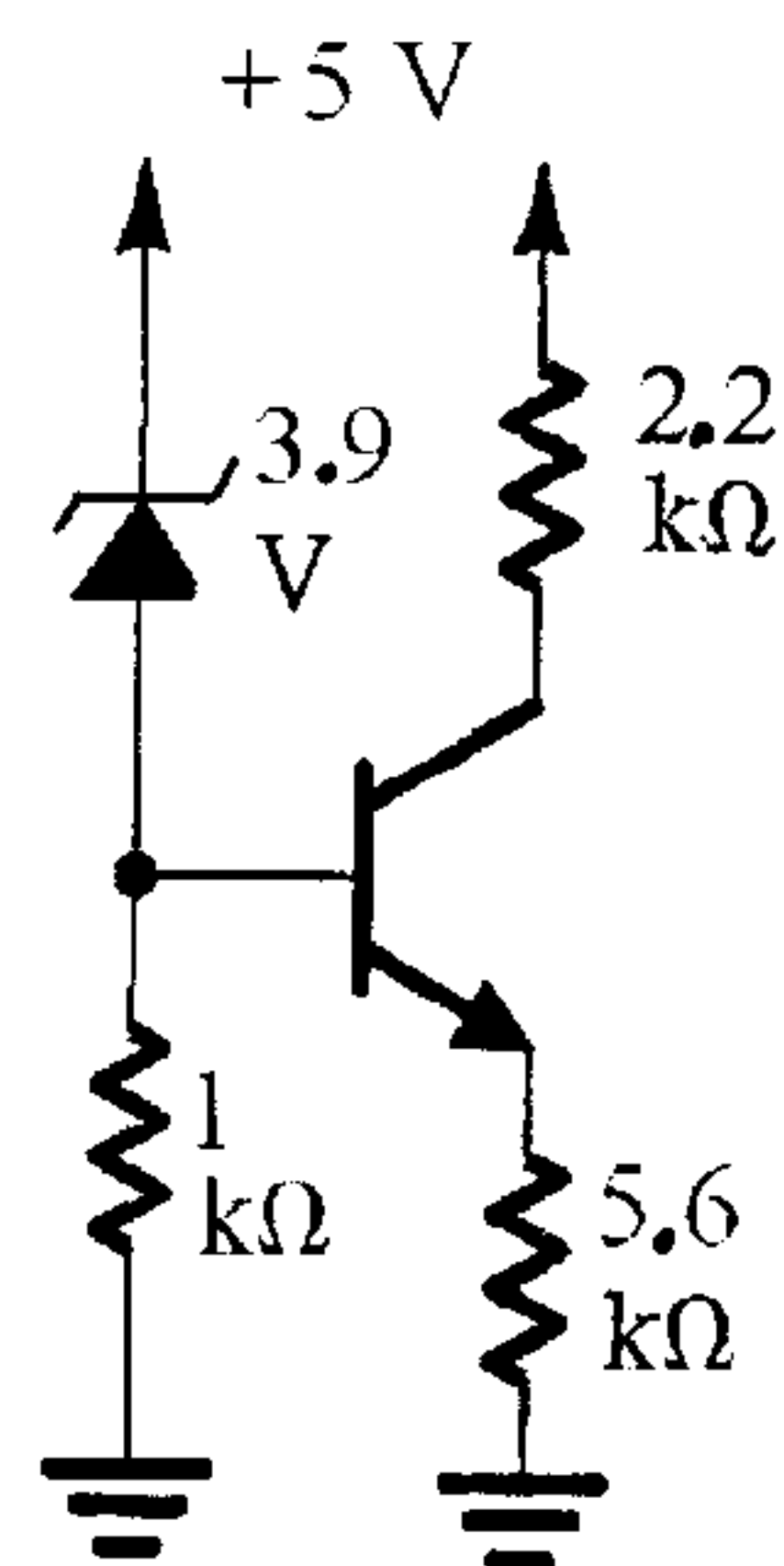
$$I_C = \underline{0} \quad V_{EC} = \underline{5 \text{ V}}$$



$$V_B = 5 - 3.9 = 1.1 \text{ V}$$

$$V_E = 1.1 - 0.7 = 0.4 \text{ V}$$


$$I_C \approx I_E = \frac{0.4}{5.6} = 0.07 \text{ mA}$$

$$V_{CE} \approx 5 - (2.2 + 5.6)0.07 = 4.44 \text{ V}$$

$$I_C = \underline{0.07 \text{ mA}} \quad V_{CE} = \underline{4.44 \text{ V}}$$

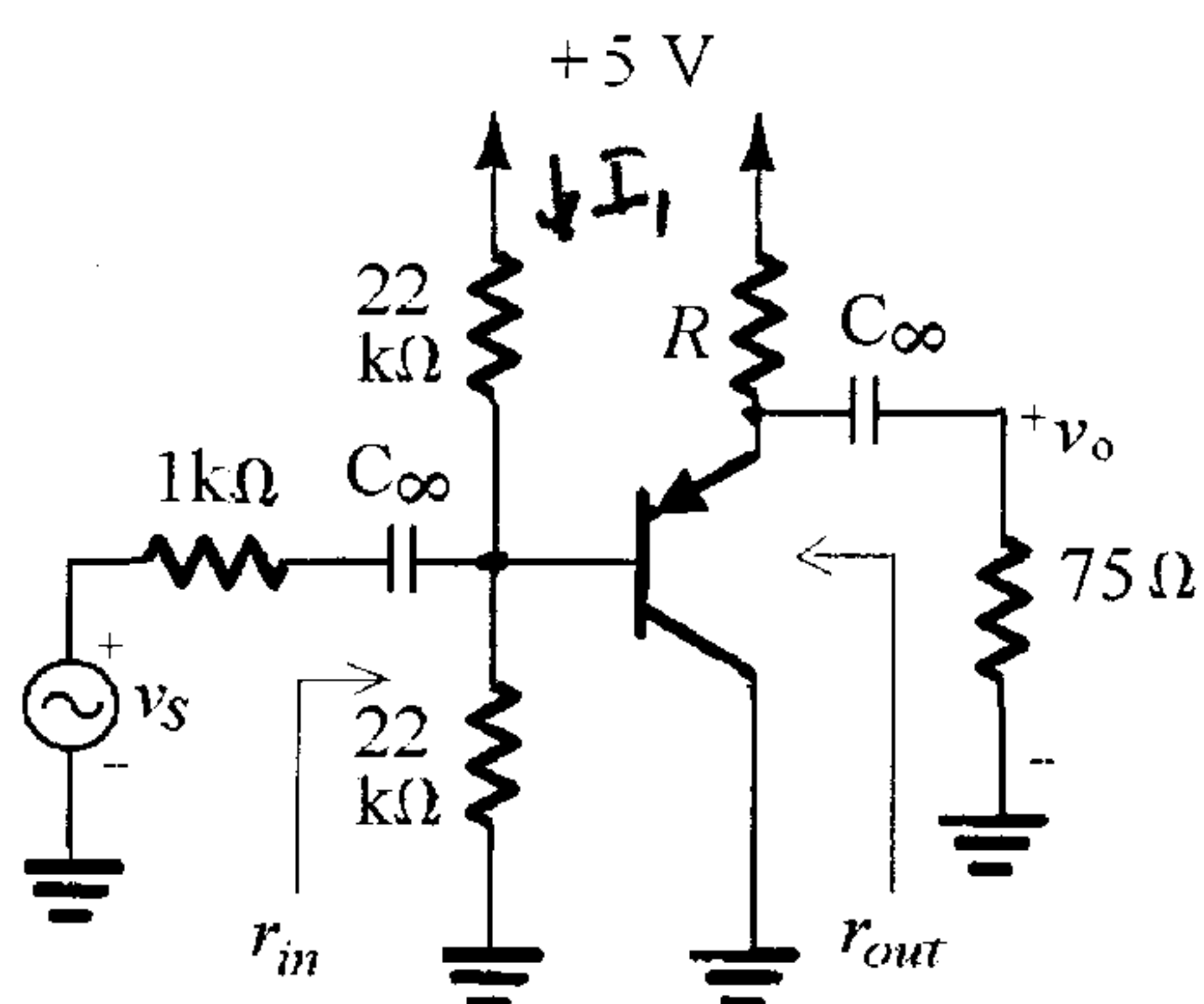3) Find the value of R in the amplifier circuit below such that the silicon PNP BJT has 1.5 mA collector current. Find its voltage gain, input resistance and output resistance. ($\beta=300$)

(Recommended time period for this question is 30 minutes.)



$$I_B = \frac{1.5}{300} = \frac{0.5}{100} = \frac{5}{1000}$$

Current in 22k resistors

$$I_1 \approx \frac{5}{22+22} = \frac{5}{44}$$


$I_1 \gg I_B \rightarrow$ ignore I_B while calculating V_B .

$$V_B \approx 5 \times \frac{22}{22+22} = 2.5V, V_E = 2.5 + 0.7 = 3.2V$$

$$I_E \approx I_C = 1.5mA, I_E = \frac{5-3.2}{R_E} \rightarrow R_E = \frac{1.8}{1.5} = 1.2k\Omega$$

$$g_m = \frac{1.5}{0.025} = 60mA/V, r_{\pi} = \frac{\beta}{g_m} = \frac{300}{60} = 5k\Omega$$

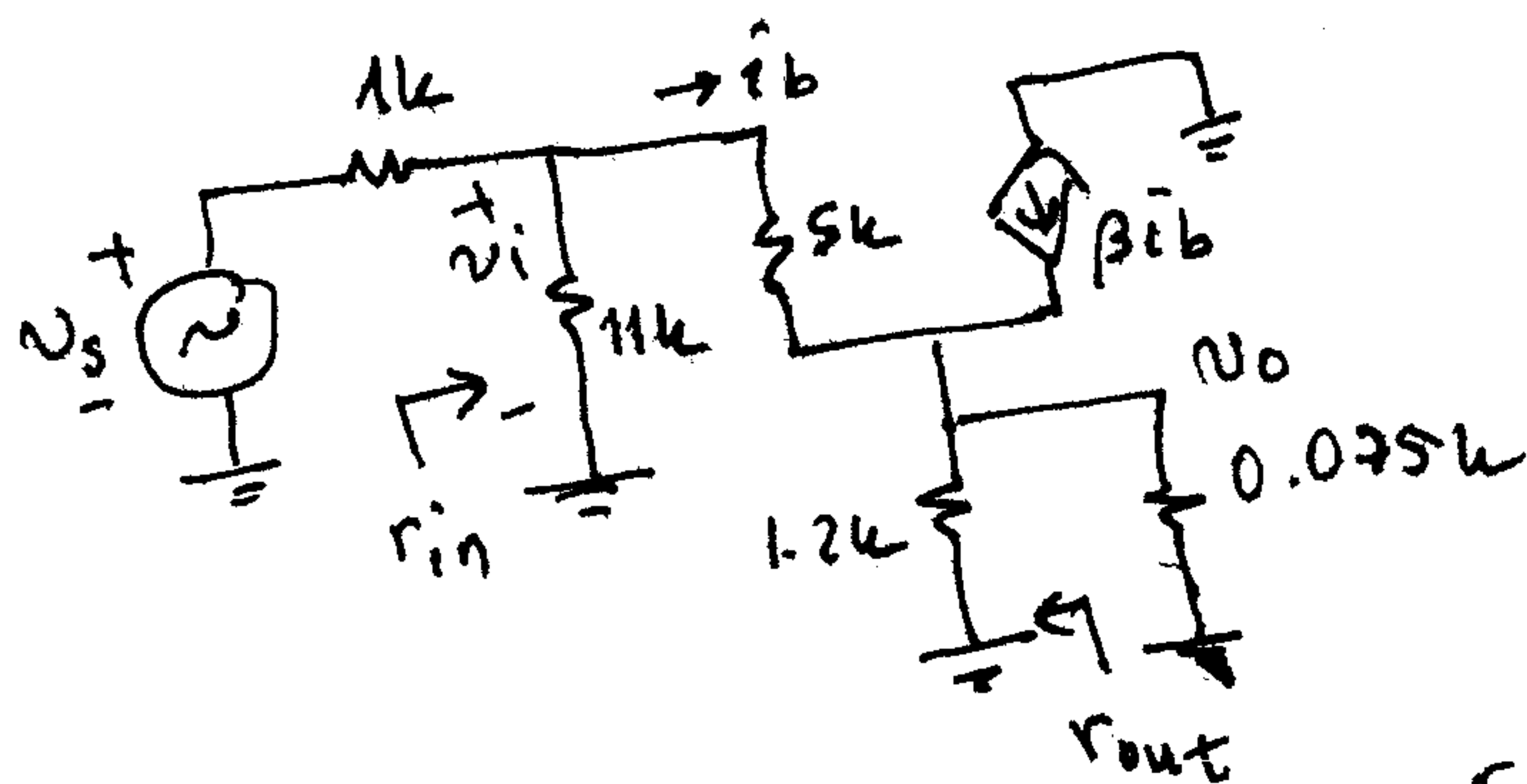Common collector amplifier - small signal equivalent ckt:



$$\frac{v_o}{v_i} = \frac{(\beta+1)(1.2 \parallel 0.075)}{r_{\pi} + (\beta+1)(1.2 \parallel 0.075)} = \frac{301 \times 0.07}{5 + 301 \times 0.07} = 0.808$$

$$r_{in} = 1k \parallel [5 + 301 \times 0.07] = 7.73k\Omega$$

$$\frac{v_i}{v_s} = \frac{r_{in}}{1k + r_{in}} = \frac{7.73}{8.73} = 0.885$$

$$\frac{v_o}{v_s} = 0.808 \times 0.885 = 0.715$$

$$r_{out} = 1.2k \parallel \frac{5k + (1k \parallel 1k)}{301} \approx 0.019k\Omega$$