 


INTRODUCTION TO MICROCOMPUTERS FINAL EXAM

Dr. Salih FADIL

January 21, 2009

#1) Consider the following memory decoder circuitry given in the following figure.




a) Fill the following table.

IC- #	Type	Capacity (KB)	Selected addr. range
1	-----	-----	-----
2	-----	-----	-----
3	-----	-----	-----
4	-----	-----	-----
5	-----	-----	-----

 b) Design the same circuitry by using the minimum capacity PROM. Give the programming of the PROM as truth table and also draw the corresponding circuitry. Assume that PROM has two enables where one of them is active-low and the other is active-high. Note that both circuitry have no overlapping addresses.

```
#2)  ORG 0000h
      LXI SP, N-1
      NOP
LP:   NOP
      CALL SBR-1
      NOP
KK:   NOP
      JMP LP
      MVI L, N-2
SBR-1: MVI H, N-3
LOOP-1: NOP
      CALL SBR-2
      DCR H
LL:   JNZ LOOP-1
      RET
SBR-2: PUSH H
      MVI H, 0FFh
LOOP-2: NOP
      NOP
AA:   DCR H
      JNZ LOOP-2
      POP H
      RET
```

When the program reaches the point AA first time, (SP) = FFF9h.



Consider the assembly program part written for an 8085 microprocessor based system. The 8085 has 6 MHz crystal.


a) Determine the values for N-1, N-2 and N-3. Determine also starting addresses of the instructions labeled as KK and LL in the program. This addresses must be found by using the stack content.

b) Calculate the execution time for SBR-1 subroutine as ms.

see back →

c) Can the program be run correctly on the system whose memory decoder circuitry gives in question 1, why?

#3)

 

USARTs shown in the figure will be used for synchronous serial communication. Consider the programming parts given in the following for 8251A-1 and 8251A-2.

1) for 8251A-1

ORG 0000h

LXI SP, 0FFFFh ; F000h - FFFFh, SRAM

```

MVI A, 1Ch
OUT N1
MVI A, 191h
OUT N3
MVI A, 92h
OUT N4
MVI A, N5
OUT N6
MVI A, 08h
SIM
EI
LOOP: NOP
      NOP
      JMP LOOP
      ORG N7
      JMP SUB
      NOP
SUB:  MVI A, 0FFh
      OUT N8
      NOP
      EI
      RET.

```

for 8251A-2

```

ORG 0000h
LXI SP, 0FFFFh ; EC00h-FFFFh. SRAM
MVI A, S1
OUT S2
MVI A, S3
OUT S4
MVI A, S5

```

```

OUT S6
MVI A, S7
OUT S8
LXI H, EC00h
LP:  NOP
      CALL SUB1
      NOP
      JMP LP
      NOP
SUB1: MVI A, S9
      OUT S10
LP1:  IN  S11
      ANI 40h
      JZ  LP1
LP2:  IN  S12
      ANI 02h
      JZ  LP2
      IN  S13
      ANI S14
      JNZ HOOPS
      IN  S15
      CMA
      MOV M, A

```

```

AA:  NOP
      RET
HOOPS: HLT

```

- a) Determine the values of $N_1, \dots, N_8$ in the program part written for 82S1A-1
- b) Determine the values of $S_1, \dots, S_{15}$ in the program part written for 82S1A-2
- c) What is the value of f_2 ? Determine the content of memory location whose address is FC00h at point AA in the system on the right hand side. If an error occurs in serial communication between 82S1A-1 and 82S1A-2, what happens to the system on the right-hand side?

INTRODUCTION TO MICROCOMPUTERS FINAL EXAM

SOLUTION MANUAL

Dr. Salih FADIL

January 21, 2009

#1) The following binary memory map can be drawn from
a) the examination of the given decoder circuit.

		$A_{15} A_{14} A_{13} A_{12}$				$A_{11} A_{10} A_9 A_8$				$A_7 A_6 A_5 A_4$				$A_3 A_2 A_1 A_0$				
15	32 KB	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	IC-1	
2		0	1	1	1	1	1	1	1	1	1	1	1	1	1			
$= 0000h$																		
13	8 KB	1	0	0	0	0	0	0	0	0	0	0	0	0	0	0	IC-2	
2		1	0	0	1	1	1	1	1	1	1	1	1	1	1			
$= 8000h$																		
																	$= 9FFFh$	
12	4 KB	1	0	1	0	0	0	0	0	0	0	0	0	0	0	0	IC-3	
2		1	0	1	0	1	1	1	1	1	1	1	1	1	1			
$= A000h$																		
																	$= AFFFh$	
11	2 KB	1	0	1	1	0	0	0	0	0	0	0	0	0	0	0	IC-4	
2		1	0	1	1	0	1	1	1	1	1	1	1	1	1			
$= B000h$																		
																	$= B7FFh$	
10	1 KB	1	0	1	1	1	0	0	0	0	0	0	0	0	0	0	IC-5	
2		1	0	1	1	1	0	1	1	1	1	1	1	1	1			
$= B800h$																		
																	$= BBFF$	

IC-1 — IC-4 : ROM type memory ICs, since they have only $\overline{OE}$ strobe signal inputs, because of it their data signals are unidirectional (input)

IC-5 : RAM type memory IC, since it has both $\overline{OE}$ and $\overline{WE}$ strobe signal inputs, because of it its data signals are bidirectional (input and output)

IC - #	Type	Capacity	Selected addr. range
1	ROM	32 KB	0000h - 7FFFh
2	ROM	8 KB	8000h - 9FFFh
3	ROM	4 KB	A000h - AFFFh
4	ROM	2 KB	B000h - B7FFh
5	RAM	1 KB	B800h - BBFFh

b) Since there is no any address bit that takes the same logic value, the number of necessary address inputs for PROM is ^{in the given memory address range (0000h - BBFFh)} determined by the capacity of the smallest memory IC (IC-5, 1KB).

$$2^6 = 64 \text{ Byte}$$

Connected addr. bits INPUTS						OUTPUTS								connected CS of ICs										
A ₁₅	A ₁₄	A ₁₃	A ₁₂	A ₁₁	A ₁₀	A ₅	A ₄	A ₃	A ₂	A ₁	A ₀	CS ₁ D ₇	CS ₂ D ₆		CS ₃ D ₅	CS ₄ D ₄	CS ₅ D ₃	N.C	N.C	N.C	D ₂	D ₁	D ₀	
for IC-1	0	0	0	0	0	0	0	0	0	0	0	0	1	1	1	1	1	1	1	1	1	1	1	2 ⁵ locations the same byte is written.
	0	1	1	1	1	1	0	1	1	1	1	0	1	1	1	1	1	1	1	1	1	1		
for IC-2	1	0	0	0	0	0	1	0	0	1	1	1	0	1	1	1	1	1	1	1	1	1	2 ³ locations	
	1	0	0	1	1	1	1	0	0	1	1	1	0	1	1	1	1	1	1	1	1	1		
for IC-3	1	0	1	0	0	0	1	0	1	0	0	1	1	0	1	1	1	1	1	1	1	1	2 ² locations	
	1	0	1	0	1	1	1	0	1	0	1	1	1	0	1	1	1	1	1	1	1	1		
for IC-4	1	0	1	1	0	0	1	0	1	1	0	1	1	1	0	1	1	1	1	1	1	1	2 ¹ locations	
	1	0	1	1	0	1	1	0	1	1	1	1	1	1	0	1	1	1	1	1	1	1		
the other locations						1	0	1	1	1	0	1	1	1	1	0	1	1	1	1	1	1	2 ⁰ = 1 location	
						1	1	1	1	1	1	1	1	1	1	1	1	1	1	1	1	1		


2^5 locations
the same byte
is written.

2^3 locations

2^2 locations

2^1 locations

$2^0 = 1$ location

 

#2) a)

* Since address for the bottom of the stack is $FFFFh$, $N-1 = 0FFFFh$

* the starting address of the NOP just after CALL SBR-1 is pushed onto stack in the order of High-Byte & Low-Byte. It is the first two-byte pushed onto stack.

NOP ; 0008h

KK: NOP ; 0009h, starting addr. in the memory

* the second two-byte pushed onto stack is the starting address of the instruction DCR H just after CALL SBR-2


DCR H ; 0015h
 LL: JNZ LOOP-1 ; 0016h

* the third two-byte pushed onto stack is the initial content of HL register pair (as High-Byte & Low-Byte)

$$(H) = 35h = N-2$$

$$(L) = 00h \quad \underline{N-3 \text{ can not be determined!}}$$

b) ; # of T-states

 

of T-states in SBR-2 subroutine

$$12 + 7 + 254 \overbrace{(4 + 4 + 4 + 10)}^{22} + 19 + 20 = 5646$$

of T-states in SBR-1 subroutine

$$7 + \underbrace{(4 + 18 + 5646 + 4 + 10)}_{5682} \times 52 + 5679 + 10 = 301160$$

Execution time for SBR.1 is

$$301160 \times \frac{1}{3 \times 10^6} = 0.100386 \text{ sec.}$$

$$= 100.3 \text{ msec.}$$

3) For 8251A-1, sync. serial communication

* It was isolated I/O decoder since $E_3=1$ for $\overline{IO/\overline{M}}=1$

OR


A_7	A_6	A_5	A_4	A_3	A_2	A_1	A_0
A_{15}	A_{14}	A_{13}	A_{12}	A_{11}	A_{10}	A_9	A_8
0	1	1	1	1	0	1	0

0 = 7Ah → Addr. of data reg.

1 = 7Bh → Addr. of control-command - status reg.

a) From examination of the program part written for 8251A-1 and the connection diagram, the followings can be deduced.

Mode word = 1Ch.

 

N1 = 0FBh addr. of control-command-status reg

Sync. char-1 = 91h

sync. char-2 = 92h

N3 = 7Bh

N4 = 7Bh

N5 = 00010101b = 15h = command word

enables transmitter and receiver and clears the error bits in the status register

$$N6 = 7Bh$$

N7 = 002Ch vector addr. of RST S.5 (6)

N8 = 7Ah addr. of data reg of 8251A-1

b) From examination of the program part written for 8251A-2 and the connection diagram, the followings can be deduced.

* It has I/O mapped I/O (isolated I/O) decoder since $E_3=1$ for $IO/\overline{M}=1$.

A ₁₅	A ₁₄	A ₁₃	A ₁₂	A ₁₁	A ₁₀	A ₉	A ₈	
0	0	0	0	1	1	1	0	= 0Eh ← Addr. of data reg.
							1	= 0Fh ← Addr. of Control-Command - Status reg.

S-

S1 = 1Ch ; mode word

S2 = 0Fh ; addr. of Control-Command-Status reg.

S3 = 91h ; sync. char.-1

S4 = 0Fh

S5 = 92h ; sync. char.-2

S6 = 0Fh

S7 = 15h ; Command word = 0001 1010

S8 = 0Fh

S9 = $\underbrace{10010}_{7} \underbrace{101}_{5} = 95h$ ⇒ command word 8251A-2 enters hunt mode (sync. detect mode)

S10 = 0Fh

S11 = 0Fh addr. of Status reg.

40h = sync. characters detect match!

S12 = 0Fh addr. of Status reg.

02h = receiver ready detect match!

S13 = 0Fh addr. of Status reg.

S14 = 00111000b = 38h FE & 0E & PE detect match

S15 = 0E Addr. of data reg.

c) * $f_2 = f_1 = 60 \text{ kHz}$.

* $(M) = \overline{FFh} = 00h$
 FC00h

- * If an error occurs (FE or OE or PE) during ^{the} communication between 8251A-1 and 8251A-2, the system on the right-hand side branches to label H00PS, that means enters halt state,