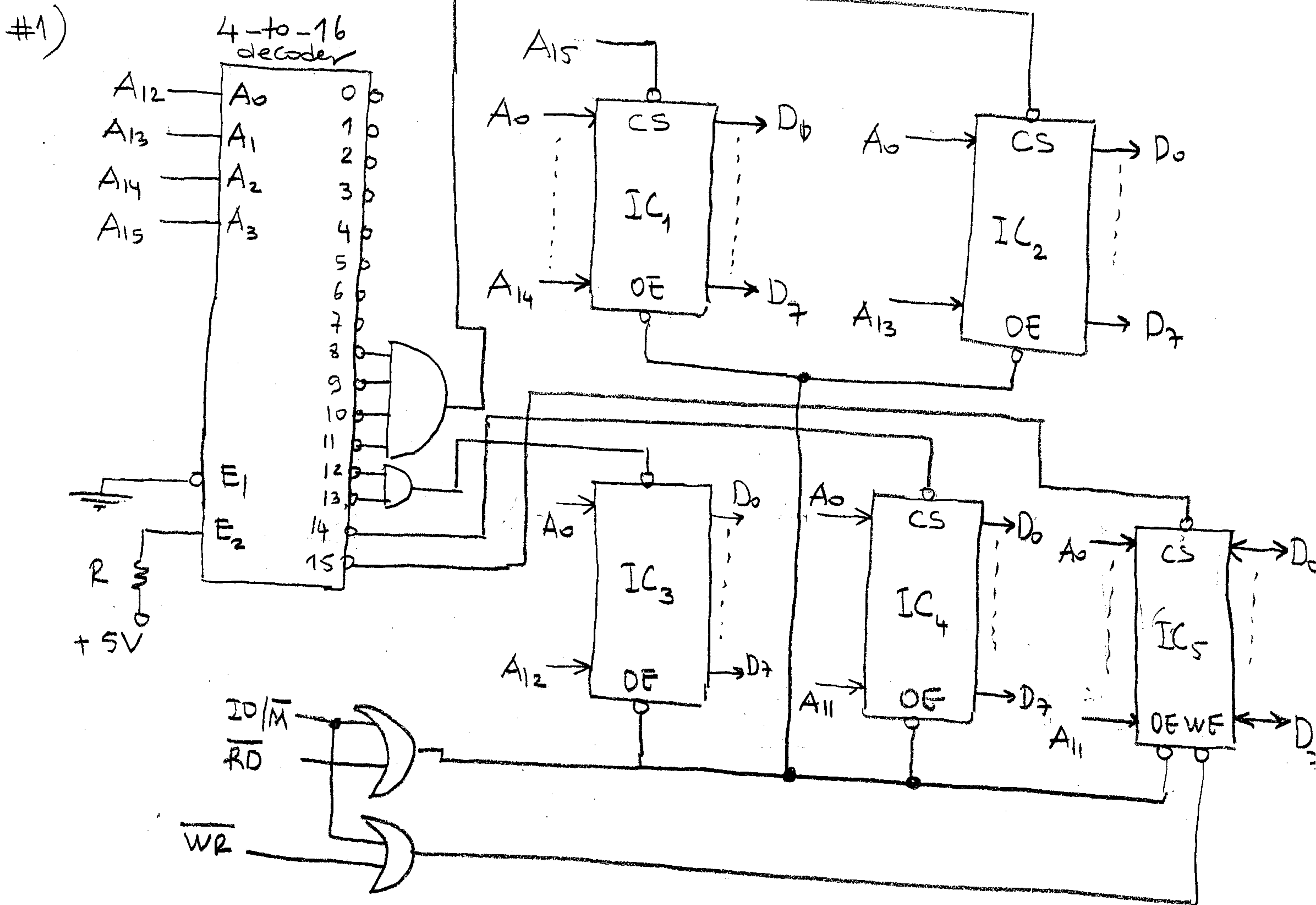


INTRODUCTION TO MICROCOMPUTERS FIRST EXAM

Dr. Salih FADIL

July 21, 2009



IC #	Type (RAM or ROM)	Capacity (KB)	Selected Address range
1	?	?	?
2	?	?	?
3	?	?	?
4	?	?	?
5	?	?	?

Fill in the above table according to the memory decoder circuitry given in the above figure

→ see back

#2) Realize a decoder circuitry that uses a PROM, which has one active high and one active low enables. This decoder circuitry places the memory IC's given in question 1 into the same address ranges. The capacity of the PROM should be the possible minimum capacity. Show connection of PROM decoder and programming of the PROM together.

#3)

I/O Device number	Selected Address Range
0	FF00h - FF07h
1	FF08h - FF0Fh
2	FF10h - FF17h
3	FF18h - FF1Fh
4	FF20h - FF27h
5	FF28h - FF2Fh
6	FF30h - FF37h
7	FF38h - FF3Fh

Cancelled

Realize a I/O decoder circuitry where the above I/O devices are selected in the corresponding address ranges. Assume that only data can be read from those I/O devices. Use one 138 (3-to-8) decoder and logic gates if necessary.

INTRODUCTION TO MICROCOMPUTERS FIRST EXAM (Summer - 2009)

Dr. Salih FADIL

July 21, 2009

#1) From the decoder circuitry given in question-1, the following binary memory map can be written.

selection bits

	A ₁₅ A ₁₄ A ₁₃ A ₁₂				A ₁₁ A ₁₀ A ₉ A ₈	A ₇ A ₆ A ₅ A ₄	A ₃ A ₂ A ₁ A ₀	Hex					
IC ₁	0	0	0	0	0	0	0	0	0	0	0	0	= 0000h
	0	1	1	1	1	1	1	1	1	1	1	1	= 7FFFh
IC ₂	1	0	0	0	0	0	0	0	0	0	0	0	= 8000h
	1	0	1	1	1	1	1	1	1	1	1	1	= BFFFh
IC ₃	1	1	0	0	0	0	0	0	0	0	0	0	= C000h
	1	1	0	1	1	1	1	1	1	1	1	1	= DFFFh
IC ₄	1	1	1	0	0	0	0	0	0	0	0	0	= E000h
	1	1	1	0	1	1	1	1	1	1	1	1	= EFFFh
IC ₅	1	1	1	1	0	0	0	0	0	0	0	0	= F000h
	1	1	1	1	1	1	1	1	1	1	1	1	= FFFFh

IC₁ : 15-bit addr input $\rightarrow 2^{15} = 2^5 \cdot 2^{10} = 32 \text{ KB}$

IC₂ : 14-bit " " $\rightarrow 2^{14} = 2^4 \cdot 2^{10} = 16 \text{ KB}$

IC₃ : 13-bit " " $\rightarrow 2^{13} = 2^3 \cdot 2^{10} = 8 \text{ KB}$

IC₄ : 12-bit " " $\rightarrow 2^{12} = 2^2 \cdot 2^{10} = 4 \text{ KB}$

IC₅ : 12-bit " " $\rightarrow 2^{12} = 2^2 \cdot 2^{10} = 4 \text{ KB}$

Total 64 KB

IC₁ - IC₄ only have $\overline{\text{OE}}$ strobe input $\rightarrow$ they are ROM memory

IC₅ has both $\overline{\text{OE}}$ and $\overline{\text{WE}}$ strobe inputs $\rightarrow$ It is RAM memory.

As a result

IC #	Type (ROM or RAM)	Capacity (KB)	Selected Address Range
1	ROM	32	0000h - 7FFFh
2	ROM	16	8000h - BFFFh
3	ROM	8	C000h - DFFFh
4	ROM	4	E000h - EFFFh
5	RAM	4	F000h - FFFFh

#2) The minimum capacity of the PROM is $2^4 = 16$ Byte.

The programming table of the PROM

INPUTS				OUTPUTS								
A ₁₅	A ₁₄	A ₁₃	A ₁₂									
A ₃	A ₂	A ₁	A ₀	D ₇	D ₆	D ₅	D ₄	D ₃	D ₂	D ₁	D ₀	
the same 8 Bytes	0	0	0	0	1	1	1	1	1	1	1	0
	0	0	0	1	1	1	1	1	1	1	1	0
	0	0	0	1	1	1	1	1	1	1	1	0
	0	1	1	1	1	1	1	1	1	1	1	0
4 Bytes	1	0	0	0	1	1	1	1	1	1	0	1
	1	0	0	1	1	1	1	1	1	0	1	1
	1	0	1	0	1	1	1	1	1	0	1	1
	1	0	1	1	1	1	1	1	1	0	1	1
2 Bytes	1	1	0	0	1	1	1	1	1	0	1	1
	1	1	0	1	1	1	1	1	1	0	1	1
1 Byte	1	1	1	0	1	1	1	1	0	1	1	1
1 Byte	1	1	1	1	1	1	1	0	1	1	1	1
+				1								
16 Bytes				1								

All locations are used

