

INTRODUCTION TO MICROCOMPUTERS FIRST MIDTERM EXAM

Dr. Salih FADIL

November 06, 2009

ROM1 (8 KB)	0000h
ROM2 (4 KB)	
ROM3 (2 KB)	
ROM4 (1 KB)	
RAM1 (1 KB)	
	FFFFh

#1) An 8085 based microprocessor system needs 15 Kbytes ROM and 1 Kbytes RAM memory. ROM and RAM memories are composed of memory ICs shown in the figure. Design a memory decoder circuitry that places the memory ICs into their respective address ranges shown in the figure. Use one '138 (3-to-8) decoder and minimum number of gates if necessary. The decoder circuitry will be a completely specified one.

#2) Realize the same decoder circuitry, which is asked in question 1, by using a PROM that has **the minimum capacity**. Show the programming of the PROM as a truth table. Draw also the circuitry of the decoder. Assume that the PROM has two enable inputs where one them is active high and the other one is active low.

#3) Consider the table where selection address ranges for each I/O device are shown. Realize the I/O decoder circuitry by using one '138 decoder and logic gates. Only data can be read from those I/O elements.

I/O Device number	Selected Address Range
0	FB00h – FB1Fh
1	FB20h – FB3Fh
2	FB40h – FB5Fh
3	FB60h – FB7Fh
4	FB80h – FB9Fh
5	FBA0h - FBBFh
6	FBC0h – FBDFh
7	FBE0h – FBFFh

INTRODUCTION TO MICROCOMPUTERST FIRST MIDTERM

EXAM SOLUTION MANUAL


Dr. Salih FADIL

November 06, 2008

#1)

	A ₁₅	A ₁₄	A ₁₃	A ₁₂	A ₁₁	A ₁₀	A ₉	A ₈	A ₇	A ₆	A ₅	A ₄	A ₃	A ₂	A ₁	A ₀	
ROM1	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	= 0000h
	0	0	0	1	1	1	1	1	1	1	1	1	1	1	1	1	= 1FFFh
ROM2	0	0	1	0	0	0	0	0	0	0	0	0	0	0	0	0	= 2000h
	0	0	1	0	1	1	1	1	1	1	1	1	1	1	1	1	= 2FFFh
ROM3	0	0	1	1	0	0	0	0	0	0	0	0	0	0	0	0	= 3000h
	0	0	1	1	0	1	1	1	1	1	1	1	1	1	1	1	= 37FFh
ROM4	0	0	1	1	1	0	0	0	0	0	0	0	0	0	0	0	= 3800h
	0	0	1	1	1	0	1	1	1	1	1	1	1	1	1	1	= 3BFFh
RAM1	0	0	1	1	1	1	0	0	0	0	0	0	0	0	0	0	= 3C00h
	0	0	1	1	1	1	1	1	1	1	1	1	1	1	1	1	= 3FFFh

23

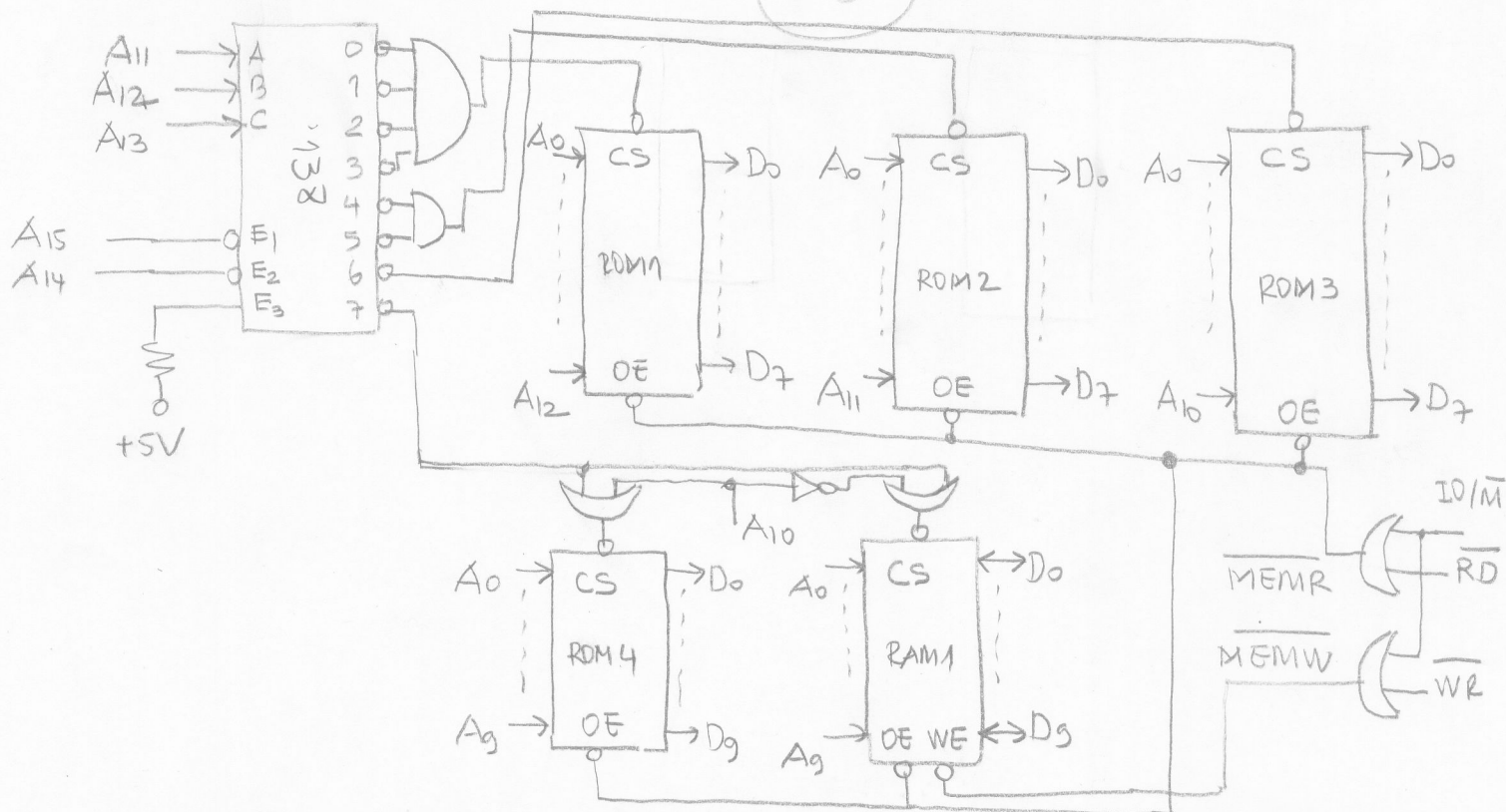

#2) Since $A_{15} A_{14}$ bits remains at logic 0 is the used memory region and the minimum capacity memory IC is 1 KByte, the inputs to the PROM will be $A_{13} A_{12} A_{11} A_{10}$. So the minimum capacity PROM will be $2^4 = 16$ Byte. Note that $A_{15} A_{14}$ are connected to the enables of the PROM.

Connected
Addr. bits
→

INPUTS				OUTPUTS							
A_{13}	A_{12}	A_{11}	A_{10}	O_7	O_6	O_5	O_4	O_3	O_2	O_1	O_0
A_3	A_2	A_1	A_0								
0	0	0	0	1	1	1	1	1	1	1	0
0	0	0	1	the same							
0	1	1	1								
1	0	0	0	1	1	1	1	1	1	0	1
1	0	0	1	1	1	1	1	1	1	0	1
1	0	1	0	1	1	1	1	1	1	0	1
1	0	1	1	1	1	1	1	1	1	0	1
1	1	0	0	1	1	1	1	1	0	1	1
1	1	0	1	1	1	1	1	1	0	1	1
1	1	1	0	1	1	1	1	0	1	1	1
1	1	1	1	1	1	1	0	1	1	1	1

8 location
(row 1)

4 location
(row 2)

2 location
row 3

1 location
row 4


1 location
row 5



programming truth table
of the PROM (16 Bytes)

All locations are
programmed!

17

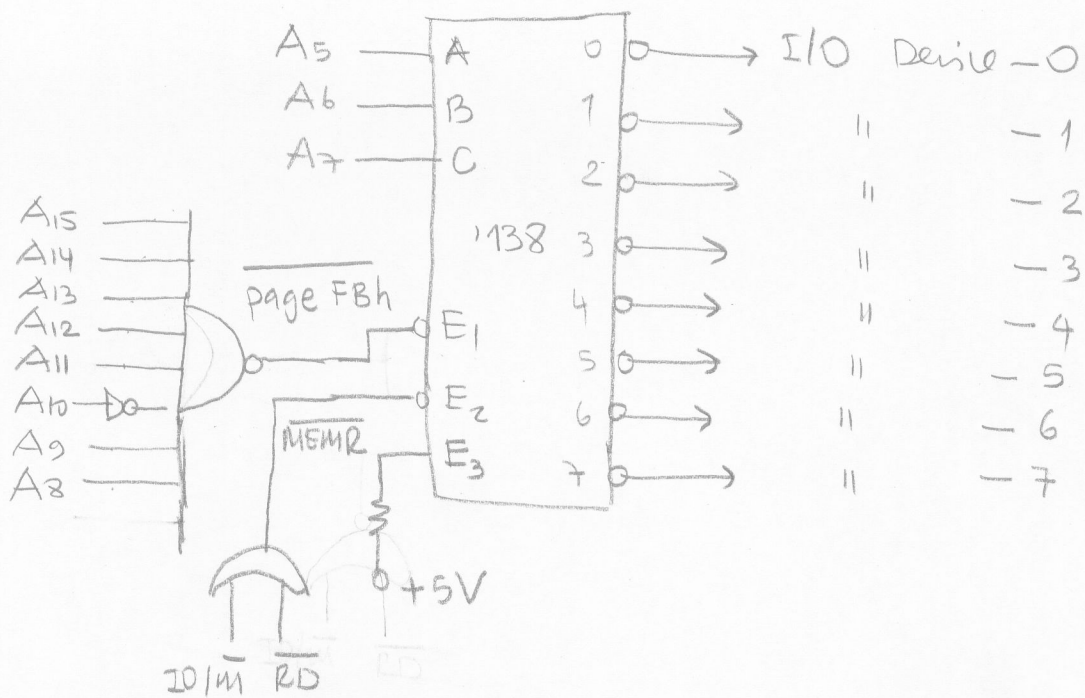

28