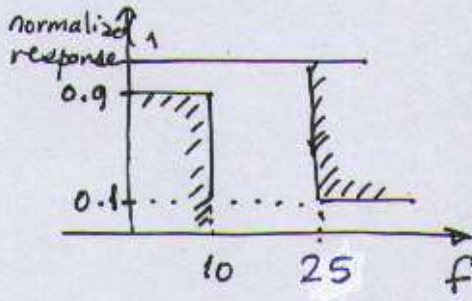


**Electronics II \* Final Exam \* June 17, 2004 \* 90 minutes**

ID number: \_\_\_\_\_ Name: SOLUTIONS Signature: \_\_\_\_\_ Grade: \_\_\_\_\_

30 pts

1) Determine the poles of the minimum order Butterworth filter for the filter specification given below:



$$\frac{1}{\sqrt{1 + (\frac{f}{f_n})^{2n}}} = \text{normalized response}$$

$$\left(\frac{1}{0.9}\right)^2 = \left(\sqrt{1 + \left(\frac{10}{f_n}\right)^{2n}}\right)^2 \rightarrow \frac{1}{0.81} - 1 = \left(\frac{10}{f_n}\right)^{2n} = 0.2346$$

$$\left(\frac{1}{0.1}\right)^2 = 1 + \left(\frac{25}{f_n}\right)^{2n} \rightarrow \frac{1}{0.01} - 1 = \left(\frac{25}{f_n}\right)^{2n} = 99$$

dividing side by side,  $\left(\frac{10}{25}\right)^{2n} = \frac{0.2346}{99} = 0.0024$


$$2n \log\left(\frac{10}{25}\right) = \log(0.0024), \quad n = \frac{\log(0.0024)}{2 \log\left(\frac{10}{25}\right)} = 3.29$$

to find  $f_n$ , substitute  $n = 3.29 \rightarrow \left(\frac{10}{f_n}\right)^{2n} = 0.2346$   $n \rightarrow 4$

$$6.58 \log\left(\frac{10}{f_n}\right) = \log(0.2346), \quad \log\left(\frac{10}{f_n}\right) = \frac{\log(0.2346)}{6.58} = -0.0957$$

$$\frac{10}{f_n} = 10^{-0.0957} = 0.8022$$
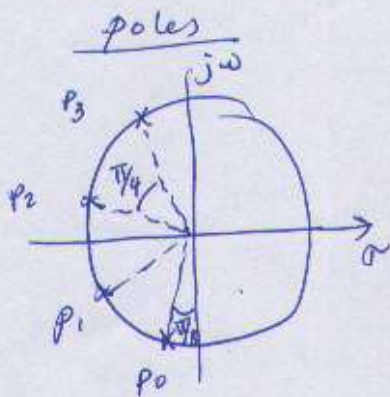
$$f_n = \frac{10}{0.8022} = 12.465 \text{ kHz}$$



$$p_0 = 2\pi f_n e^{-j\left(\frac{\pi}{8} + \frac{\pi}{2}\right)}$$

$$p_1 = 2\pi f_n e^{-j\left(\frac{\pi}{8} + \frac{\pi}{4} + \frac{\pi}{2}\right)}$$

$$p_2 = 2\pi f_n e^{-j\left(\frac{\pi}{8} + \frac{3\pi}{4} + \frac{\pi}{2}\right)}$$

$$p_3 = 2\pi f_n e^{-j\left(\frac{\pi}{8} + \frac{5\pi}{4} + \frac{\pi}{2}\right)}$$

$$p_0 = 2\pi f_n e^{-j\frac{5\pi}{8}} = -29973 - j72359$$


$$p_1 = 2\pi f_n e^{-j\frac{7\pi}{8}} = -72359 - j29973$$

$$p_2 = 2\pi f_n e^{+j\frac{7\pi}{8}} = -72359 + j29973$$

$$p_3 = 2\pi f_n e^{+j\frac{5\pi}{8}} = -29973 + j72359$$

30 pts

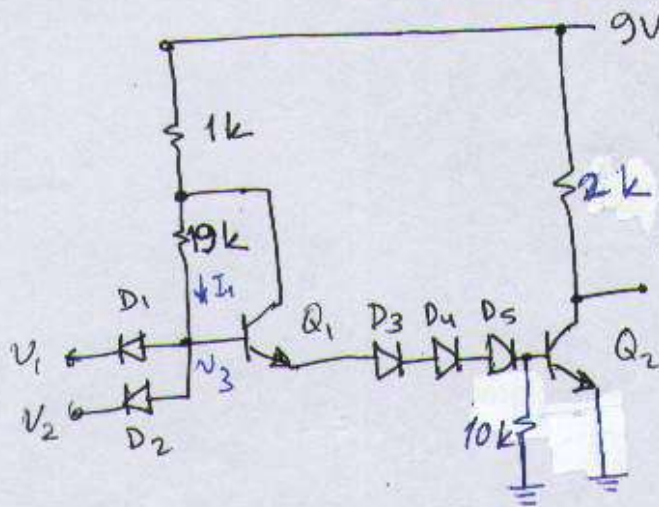2) Find the high and low logic voltages, noise margins and fanout for the gate given below:



$\beta_F = 20$   
 all silicon  
 when  $V_1 = V_2 = 0.2V$   
 $Q_2: sat \rightarrow V(0) = 0.2V$   
 $Q_2: OFF \rightarrow V(1) = 9V$   
 $NM0 = 2.2V$   
 $NM1 = -6.1V$   
 $Fanout = 125$   
 $\langle P_{diss} \rangle = 34.37mW$   
 $V_3 = 0.2 + 0.7 = 0.9V$   
 The current  $I_1 = \frac{9 - 0.9}{19 + 1} = 0.405mA$  (std load)

$P_1 = I_1 \times 9V = 0.405 \times 9 = 3.645mW$

To turn  $Q_2$  (active) on,  $V_3$  must be at least  $0.5 + 3 \times 0.7 + 0.5 = 3.1V$

$V_1$  can be increased to  $3.1 - 0.7 = 2.4V$  w/o affecting  $Q_2$ .

acceptable  $\rightarrow 2.4V$   
 expected  $\rightarrow 0.2V$  }  $NM1 = 2.4 - 0.2 = 2.2V$

Now make  $V_1 = V_2 = 9V \Rightarrow D_1, D_2: OFF, Q_1, Q_2, D_3, D_4, D_5 \rightarrow ON, V_0 = 0.2V$

$V_3 = 0.8 + 3 \times 0.7 + 0.7 = 3.6V, I_{B1} \times 19k + (\beta + 1)I_{B1} \times 1k = 9V$

$I_{B1} = \frac{9 - 3.6}{19 + 21} = 0.135V, I_{E1} = 21 \times 0.135 = 2.835mA$


$I_{B2} = I_{E1} - \frac{0.8}{10k} = 2.755mA, I_{C2} = \frac{9 - 0.2}{2k} = 4.4mA$

$P_0 = 9(I_{E1} + I_{C2}) = 9 \times (2.835 + 4.4) = 65.11mW, \langle P_{diss} \rangle = \frac{P_0 + P_1}{2} = 34.37mW$

$V_1$  and  $V_2$  can be lowered until  $D_1, D_2$  are turned on

$V_1$  expected  $\rightarrow 9V$   
 $V_1$  acceptable  $= 3.6 - 0.7 = 2.9V$  }  $NM0 = 2.9 - 9 = -6.1V$

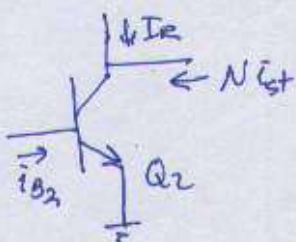For fanout, connect  $N$  identical stages:



saturation

$i_{C2} \leq \beta i_{B2}$

$I_R + N i_{st} \leq \beta i_{B2}$


$N \leq \frac{\beta i_{B2} - I_R}{i_{st}} = \frac{20 \times 2.755 - 4.4}{0.405} = 125.18$

$i_{st} = 0.405mA$  (std load)  
 $I_R = 4.4mA$  (found earlier)

$fanout = 125$

30 Pts

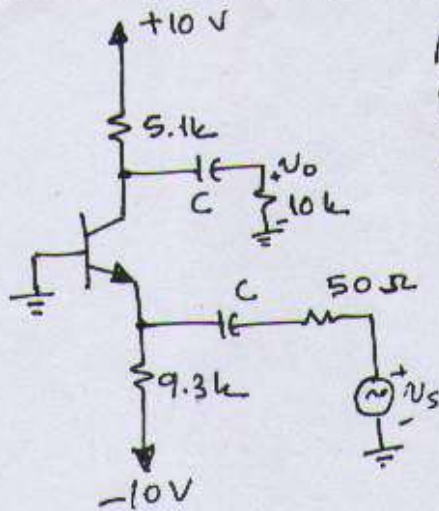3) In the amplifier below, the lower cut-off frequency is desired to be less or equal to 200 Hz. If the capacitors have the same value, what should be the minimum capacitance  $C$ ?



$$\beta = 250$$

$$V_A \rightarrow \infty$$

$$f_T = 500 \text{ MHz}$$

$$C_\pi = 1 \text{ pF}$$

$$I_C \cong I_E = \frac{-0.7 - (-10)}{9.3 \text{ k}} = 1 \text{ mA}$$

$$g_m = \frac{1}{0.025} = 40 \text{ mA/V}$$

$$r_\pi = \frac{\beta}{g_m} = \frac{250}{40} = 6.25 \text{ k}\Omega$$

Thevenin resistances seen by the capacitors

$$R_{th1} = (9.3 \text{ k} \parallel \frac{r_\pi}{\beta+1}) + 50 \Omega = 24.8 + 50 = 74.8 \Omega$$


$$R_{th2} = 5.1 \text{ k} + 10 \text{ k} = 15.1 \text{ k}\Omega$$

Superposition of poles  $\omega_L \cong \omega_1 + \omega_2$


$$= \frac{1}{C R_{th1}} + \frac{1}{C R_{th2}} = \frac{1}{C} \left( \frac{1}{R_{th1}} + \frac{1}{R_{th2}} \right)$$

$$C = \frac{1}{\omega_L} \left( \frac{1}{R_{th1}} + \frac{1}{R_{th2}} \right) = \frac{1}{200 \times 2\pi} \left( \frac{1}{15100} + \frac{1}{74.8} \right) = 1.069 \times 10^{-5} \text{ F} = 10.69 \text{ }\mu\text{F}$$

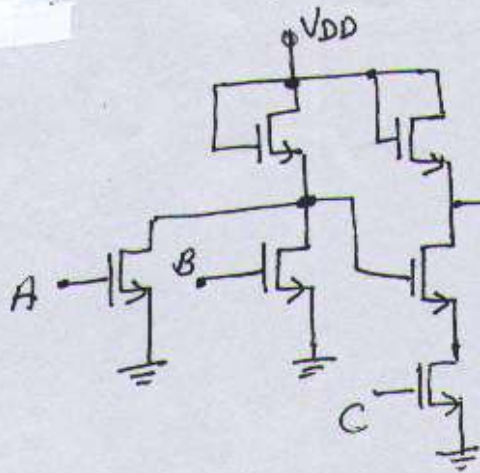
10 pts 4. Find the logic functions for the NMOS gates given below.  $V_{DD} \gg V_{th}$



$$v_o = \overline{A+B \cdot C}$$

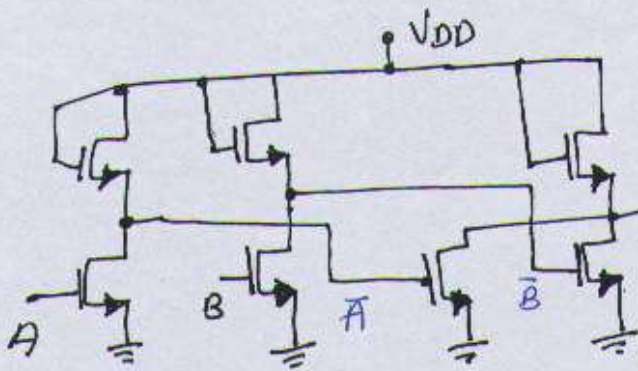

$$v_o = \overline{A+B}$$

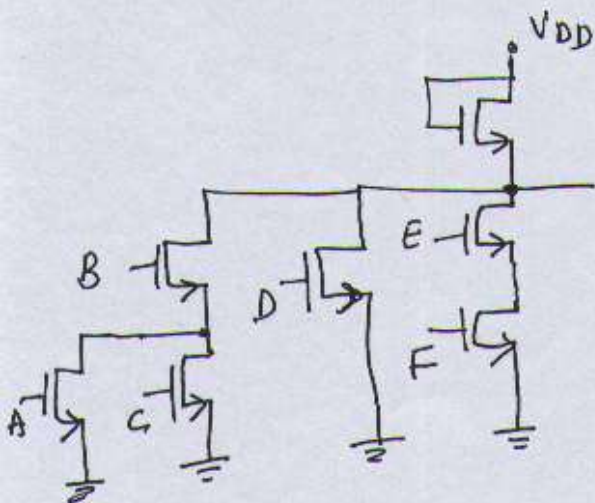


$$v_o = \overline{(A+C) \cdot B + D + E \cdot F}$$

# Electronics II - Exam 1 - Summer 2004

Name: SOLUTIONS ID number: ERKAYA Signature: 28.7.2004

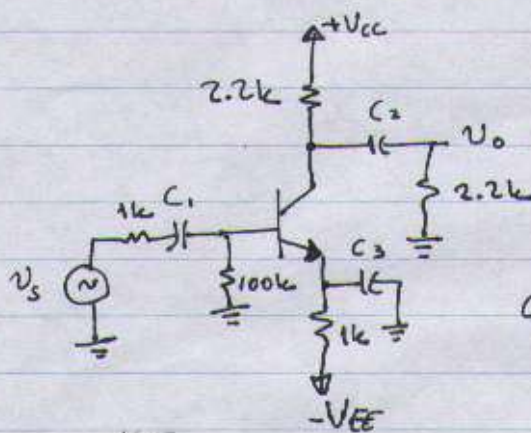
1) Find the high cut-off frequency for the <sup>amp</sup>circuit given below:



$$\begin{aligned} I_c &= 2 \text{ mA} \\ \beta_o &= 300 \\ C_{\mu} &= 2 \text{ pF} \\ f_T &= 400 \text{ MHz} \\ C_1 = C_2 = C_3 &= 100 \text{ nF} \\ V_A &= 200 \text{ V} \\ r_x &= 90 \Omega \end{aligned}$$

$$\begin{aligned} f_H &= \text{---} \\ g_m &= \frac{I_c}{V_T} = \frac{2}{0.025} = 80 \text{ mA/V} \\ C_{\pi} &= \frac{g_m}{\omega_{fT}} - C_{\mu} = \frac{80 \times 10^{-3}}{2\pi \times 4 \times 10^8} - 2 \times 10^{-12} \\ &= 30 \times 10^{-12} \text{ F} \\ r_o &= \frac{200 \text{ V}}{2 \text{ mA}} = 100 \text{ k}\Omega \\ r_{\pi} &= \frac{\beta_o}{g_m} = \frac{300}{80} = 3.75 \text{ k}\Omega \end{aligned}$$

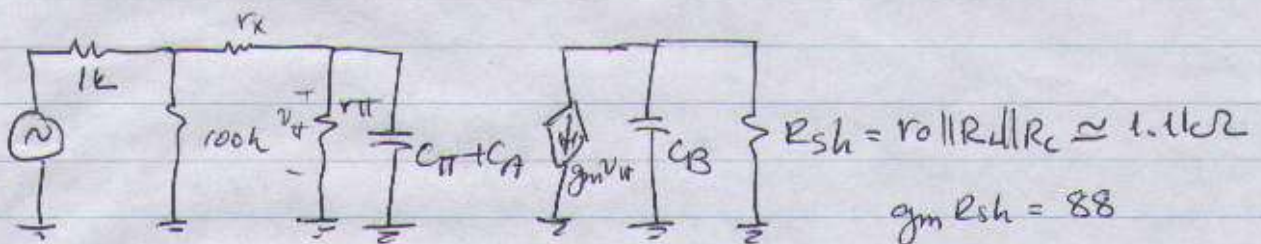HF Small signal eq. ch - Miller's Theorem is applied on  $C_{\mu}$



$$C_A = 2(1 + 88) = 178 \text{ pF}, C_{\mu} \approx C_{\mu} = 2 \text{ pF}$$

Thevenin resistance seen by  $C_{\pi} + C_A$

$$R_{thA} = r_{\pi} \parallel [r_x + (1 \text{ k} \parallel 100 \text{ k})] \approx 3.75 \parallel [0.09 + 1] = 844 \Omega$$


Thevenin resistance seen by  $C_{\mu}$   $R_{thB} = R_{sh} = 1.1 \text{ k}\Omega$

$$\omega_A = \frac{1}{(C_A + C_{\pi}) R_{thA}} = \frac{1}{(20 + 178) \times 10^{-12} \times 844} = 5.69 \times 10^6 \text{ rad/s}$$

$$\omega_B = \frac{1}{C_{\mu} R_{thB}} = \frac{1}{2 \times 10^{-12} \times 1100} = 454. \times 10^6 \text{ rad/s}$$

$$f_H = \frac{1}{2\pi} \omega_H = \frac{1}{2\pi} \frac{1}{\frac{1}{\omega_A} + \frac{1}{\omega_B}} = \frac{5.69 \times 10^6}{2\pi} = 0.906 \text{ MHz}$$

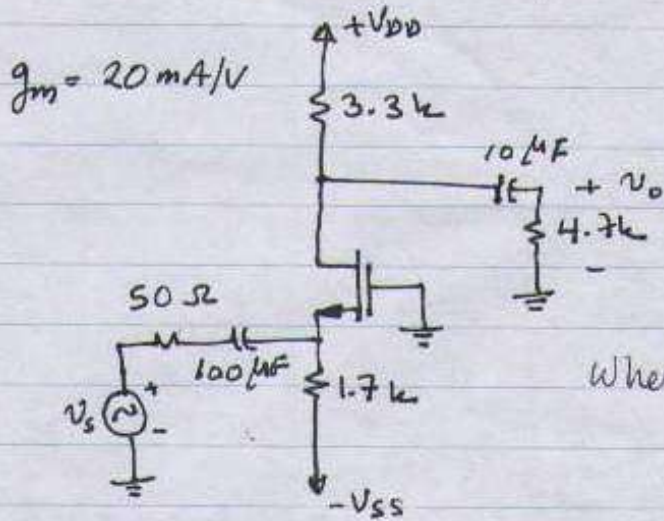2) Find the low cut-off frequency for the amplifier given below:



Common gate amplifier

$$f_L = 18.13$$

$$f_L \approx \frac{1}{2\pi C_1 R_{th1}} + \frac{1}{2\pi C_2 R_{th2}}$$

Where  $C_1 = 100 \mu\text{F}$

$$R_{th1} = 50 + \left( \frac{1}{g_m} \parallel 1.7k \right) = 98.6 \Omega$$


$$C_2 = 10 \mu\text{F}$$

$$R_{th2} = 3.3k + 4.7k = 8k$$

$$f_L \approx \frac{1}{2\pi \times 100 \times 10^{-6} \times 98.6} + \frac{1}{2\pi \times 10 \times 10^{-6} \times 8000} = 16.14 + 1.99 = 18.13 \text{ Hz}$$

ID Number: FRKAYA Name: SOLUZIONI Signature: 18.8.2004

- 1) Find the poles of the minimum order Butterworth filter to meet the specification given below:  
normalized gain

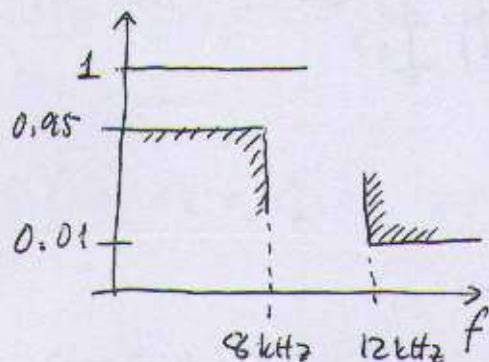 $Q=15$ 

$$\frac{1}{\sqrt{1 + \left(\frac{8}{f_a}\right)^{2n}}} = 0.95$$

$$\frac{1}{\sqrt{1 + \left(\frac{12}{f_a}\right)^{2n}}} = 0.01$$

$$\left(\frac{1}{0.95}\right)^2 - 1 = \left(\frac{8}{f_a}\right)^{2n} = 0.108$$

$$\left(\frac{1}{0.01}\right)^2 - 1 = \left(\frac{12}{f_a}\right)^{2n} = 9999$$

$$\left(\frac{8}{12}\right)^{2n} = 1.08 \times 10^{-5}$$

$$2n \log\left(\frac{8}{12}\right) = \log(1.08 \times 10^{-5})$$

$$n = \frac{\log(1.08 \times 10^{-5})}{2 \log\left(\frac{8}{12}\right)} = \frac{-4.966}{-0.35}$$

$$= +14.08$$

$n$  must be raised to 15.

$$\left(\frac{12}{f_a}\right)^{28.06} = 9999$$

$$28.06 \log\left(\frac{12}{f_a}\right) = \log(9999) = 4$$

$$\log\left(\frac{12}{f_a}\right) = \frac{4}{28.06} = 0.142$$

$$10^{\log\left(\frac{12}{f_a}\right)} = \frac{12}{f_a} = 10^{0.142} = 1.3869$$


Poles  $j(\pi + k\frac{\pi}{15})$   
 $\omega_a e$

$$f_a = \frac{12}{1.3869} = 8.65 \text{ kHz}$$

$$\omega_a = 2\pi 8.65 = 54.36 \times 10^3 \text{ rad/s}$$


where  $k = 0, \pm 1, \pm 2, \dots, \pm 7$
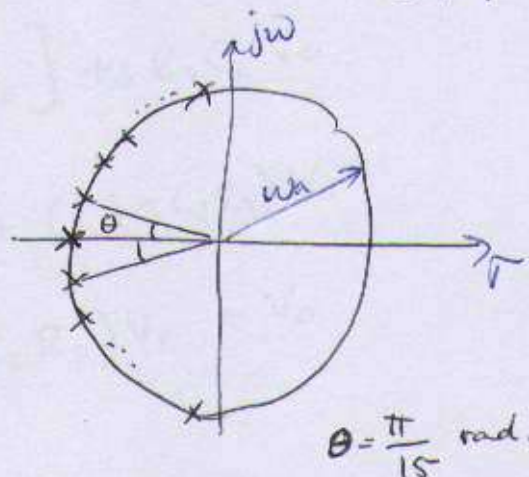
$$Q=25 \quad \omega_a = 54.36 \times 10^3 \text{ rad/s}$$



$$\theta = \frac{\pi}{15} \text{ rad.}$$

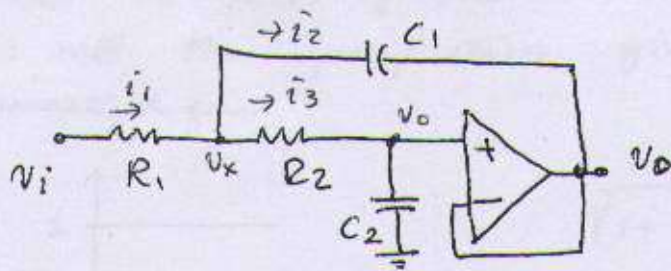- 2) Find the transfer function for the filter given below. Indicate what kind of a filter it is (Lowpass, bandpass, ...etc.) type =



$$\frac{V_o}{V_i} = \underline{\hspace{2cm}}$$

$$i_1 = i_2 + i_3$$

$$i_2 = \frac{V_x - V_o}{\frac{1}{sC_1}} = sC_1(V_x - V_o)$$

$$i_3 = \frac{V_x}{R_2 + \frac{1}{sC_2}} = \frac{V_x - V_o}{R_2} = \frac{V_o}{\frac{1}{sC_2}}$$

$$\frac{V_i - (1 + sC_2 R_2) V_o}{R_1} = sC_1 \left[ (1 + sC_2 R_2) V_o - V_o \right] + sC_2 V_o$$

$$i_1 = \frac{V_i - V_x}{R_1}$$

Solve for  $V_x$

$$V_x - V_o = sC_2 R_2 V_o$$

$$V_x = (1 + sC_2 R_2) V_o$$

$$V_i - (1 + sC_2 R_2) V_o = sC_1 R_1 [sC_2 R_2 V_o] + sR_1 C_2 V_o$$

$$V_i = s^2 C_1 C_2 R_1 R_2 V_o + sR_1 C_2 V_o + (1 + sC_2 R_2) V_o$$

$$= s^2 C_1 C_2 R_1 R_2 V_o + s(R_1 C_2 + C_2 R_2) V_o + V_o$$

$$\frac{V_o}{V_i} = \frac{1}{s^2 C_1 C_2 R_1 R_2 + s(R_1 C_2 + C_2 R_2) + 1}$$


$$\frac{V_o}{V_i} = \frac{1}{s^2 + s \frac{(R_1 + R_2)}{C_1 R_1 R_2} + \frac{1}{C_1 C_2 R_1 R_2}}$$

Second order  
Low Pass  
filter
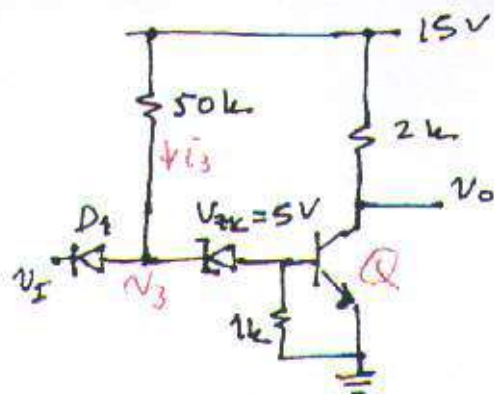
# Electronics II \* Exam 5 \* Aug 25, 2004

ID number: ERIKAYA Name: SOLUTIONS Signature: \_\_\_\_\_

- For the inverter given below, a) Find logic high and low voltages  
 b) Obtain the transfer characteristics ( $V_O$  vs.  $V_I$ )  
 c) Indicate  $V_{OH}$ ,  $V_{IH}$ ,  $V_{OL}$ ,  $V_{IL}$  on (b)  
 d) Calculate noise margins using the results of (c)  
 e) Calculate the power dissipation in the gate (average)



Silicon BJT

$$\beta = 70$$

D1: Silicon diode

$$V(1) = 15V$$

$$V(0) = 0.2V$$

$$V_{OH} = 15V$$

$$V_{OL} = 0.2V$$

$$V_{IH} = 5.1V$$

$$V_{IL} = 4.8V$$

$$NM_H = -9.9$$

$$NM_L = 4.6V$$

$$P_{diss} = 58.99mW$$

$$Q: \text{OFF}, V_O = V(1) = V_{OH} = 15V$$

$$Q: \text{ON}, V_O = V(0) = V_{OL} = 0.2V$$

$$V_I = 0.2V \rightarrow$$

To bring Q from OFF to active mode  $V_3$  must be raised to  $0.5 + 5.0 = 5.5V$ . This makes  $V_I = 5.5 - 0.7 = 4.8V$ .

This would be acceptable low input voltage:  $V_{IL} = 4.8V$

$V_I = 15V \rightarrow$  To bring Q from saturation to active mode, D1 must be turned on.  $V_3 = 0.8 + 5.0 = 5.8V$

$$V_{IH} = 5.8 - 0.7 = 5.1V$$

$$NM_H = 5.1 - 15 = -9.9V$$

$$NM_L = 4.8 - 0.2 = 4.6V$$

$$Q: \text{ON} \rightarrow i_{supply} = i_C + i_3 = \frac{15 - 0.2}{2k} + \frac{15 - 5.8}{50k} = 7.58mA \quad P_O = 15 \times 7.58 = 113.7mW$$

$$Q: \text{OFF} \rightarrow i_{supply} = i_3 = \frac{15 - 0.7}{50k} = 0.282mA \quad P_I = 15 \times 0.282 = 4.23mW$$

$$P_{avg} = \frac{P_O + P_I}{2} = 58.99mW$$


Electronics II \* Exam I \* March 29, 2006 \* 70 minutes

ID number: \_\_\_\_\_ Name: SOLUTIONS Signature: \_\_\_\_\_

30 pts

1) The lower 3 dB cutoff frequency of the amplifier below is desired to be below 300 Hz. If equal capacitor values are to be used, what should minimum value of the capacitors be?

8:43

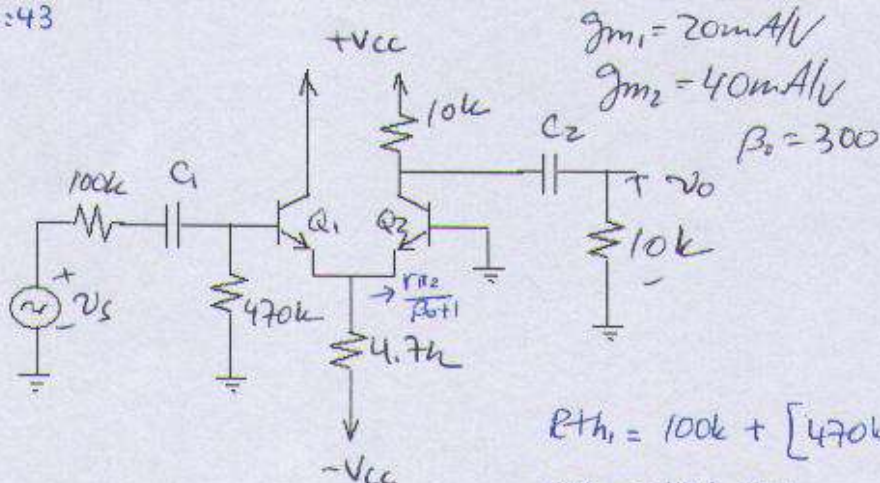

$$C_1 = C_2 = C = 3 \times 10^{-8} \text{ F}$$

$$r_{\pi 1} = \frac{\beta_0}{g_{m1}} = \frac{300}{20} = 15 \text{ k}\Omega$$

$$r_{\pi 2} = \frac{\beta_0}{g_{m2}} = \frac{300}{40} = 7.5 \text{ k}\Omega$$

$$R_{th1} = 100 \text{ k} + \left[ 470 \text{ k} \parallel \left( 15 \text{ k} + 301 \left( 4.7 \text{ k} \parallel \frac{7.5 \text{ k}}{301} \right) \right) \right]$$

$$R_{th1} = 121.43 \text{ k}$$

$$R_{th2} = 10 \text{ k} + 10 \text{ k} = 20 \text{ k}$$

$$300 = \frac{1}{2\pi} \left( \frac{1}{C_1 R_{th1}} + \frac{1}{C_2 R_{th2}} \right) = \frac{1}{2\pi C} \left( \frac{1}{R_{th1}} + \frac{1}{R_{th2}} \right)$$

$$C = \frac{1}{2\pi \cdot 300} \left( \frac{1}{121430} + \frac{1}{20000} \right) = 3 \times 10^{-8} \text{ F} = 30 \text{ nF}$$

8:49

35 pts

2) Find the high 3dB cutoff frequency of the amplifier given below.

8:49

$$I_C = 1.2 \text{ mA}$$

$$\beta_0 = 250$$

$$C_M = 2 \text{ pF}$$

$$f_T = 200 \text{ MHz}$$

$$C_1 = C_2 = C_3 = 100 \text{ nF}$$

$$V_A = 240 \text{ V}$$



$$r_x = 80 \Omega$$

$$g_m = \frac{1.2}{0.025} = 48 \text{ mA/V}$$

$$r_\pi = \frac{250}{48} = 5.2 \text{ k}\Omega$$

Small signal eq. ch w/ miller's theorem applied on  $C_M$
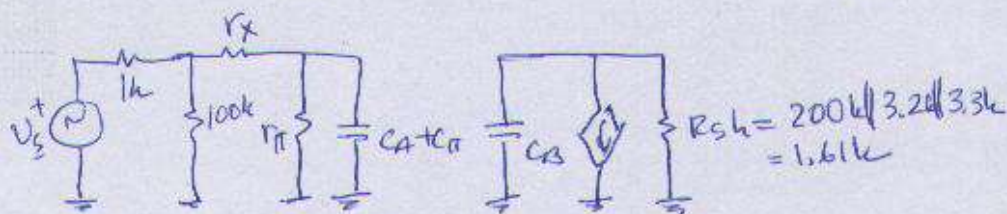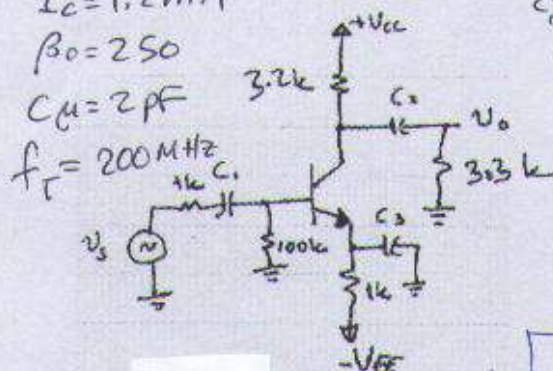
$$r_o = \frac{240}{1.2} = 200 \text{ k}\Omega$$



$$C_{\pi} = \frac{g_m}{2\pi f_T} - C_M = \frac{48 \times 10^3}{2\pi \times 200 \times 10^6} - 2 \times 10^{-12} = 36.2 \times 10^{-12} \text{ F}$$

$$g_m R_{sh} = 48 \times 1.61 = 77.28$$

$$C_A = C_M (1 + g_m R_{sh}) = 2 \times 77.28 = 156.6 \text{ pF}$$

$$C_B = C_M \left(1 + \frac{1}{g_m R_{sh}}\right) \approx 2 \text{ pF}$$

$$R_{thA} = r_\pi \parallel (r_x + 1k \parallel 100k) \approx 5.2k \parallel 1.080 = 0.894 \text{ k}\Omega$$

$$\omega_A = \frac{1}{(C_A + C_{\pi}) R_{thA}}, \quad \omega_B = \frac{1}{C_B R_{sh}}$$

$$\omega_A = \frac{1}{(156.6 + 36.2) \times 10^{-12} \times 894} = 5.8 \times 10^6 \text{ rad/s}$$

$$\omega_B = \frac{1}{2 \times 10^{-12} \times 1610} = 310 \times 10^6 \text{ rad/s}$$

$$\omega_H = \frac{1}{\frac{1}{\omega_A} + \frac{1}{\omega_B}} \approx \omega_A = 5.8 \times 10^6 \text{ rad/s}$$


$$f_H = \frac{5.8 \times 10^6}{2\pi} = 923 \text{ kHz}$$

8:58

35 Pts

3) Find the gain, input resistance and output resistance of the amplifier given below.

8-5B

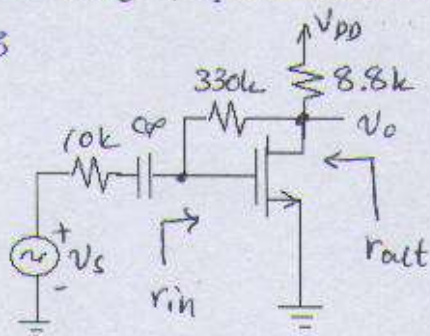

$$r_o = 500k\Omega$$


$$g_m = 20 \text{ mA/V}$$

Apply Miller's Theorem on 330k resistor

$$\frac{v_o}{v_s} \approx -27.5$$

$$r_{in} = 1.94 k\Omega$$

$$r_{out} = 1.41 k\Omega$$

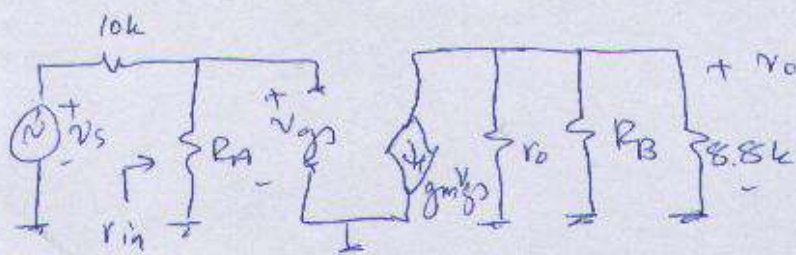

$$R_{sh} = r_o \parallel R_B \parallel 8.8k$$

$$R_B \approx 330k$$

$$R_{sh} \approx 8.42 k\Omega$$


$$g_m R_{sh} = 168.5$$

$$R_A = \frac{330k}{1 + 168.5} = 1.94 k\Omega$$

$$\frac{v_o}{v_s} = -g_m R_{sh} \frac{1.94}{1.94 + 10k} = -27.5$$

$$r_{in} \approx R_A = 1.94 k\Omega$$

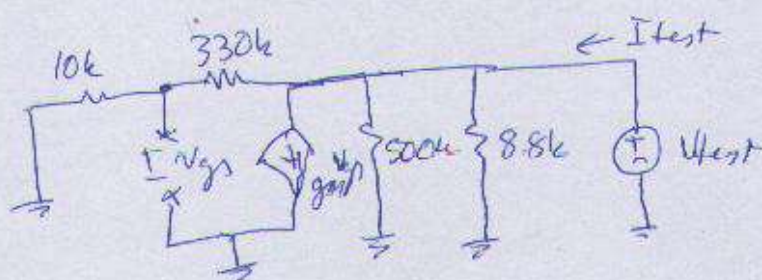$r_{out}$  must be found from the following circuit:



$$r_{out} = \frac{v_{test}}{i_{test}}$$


$$g_m v_{gs} = g_m \frac{10}{340} v_{test} = \frac{v_{test}}{\frac{34}{g_m}} = \frac{v_{test}}{1.7k}$$

$$r_{out} = \frac{v_{test}}{\frac{v_{test}}{500k} + \frac{v_{test}}{8.8k} + \frac{v_{test}}{340k} + \frac{v_{test}}{1.7k}} = 500k \parallel 8.8k \parallel 340k \parallel 1.7k = 1.41 k\Omega$$

9-06

ID number: \_\_\_\_\_ Name: SOLUTIONS Signature: \_\_\_\_\_ Grade: \_\_\_\_\_

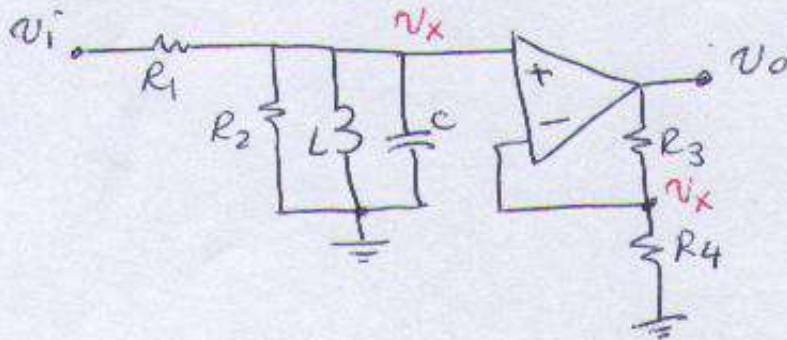- 1) Find the transfer function of the circuit given below. Indicate what kind of a filter it is (i.e., high-pass, low-pass, band-pass). Put the transfer function in the form as follows:  
 $(as^2 + bs + c)/(s^2 + s\omega_o/Q + \omega_o^2)$



$$a = 0$$

$$b = \frac{1}{C} \left( \frac{R_3 + R_4}{R_1 R_4} \right)$$

$$c = 0$$

$$\omega_o = \frac{1}{\sqrt{LC}}$$

$$\omega_o/Q = \frac{1}{C} \left( \frac{1}{R_1} + \frac{1}{R_2} \right)$$

$$\text{type} = \text{bandpass}$$

$$\frac{V_i - V_x}{R_1} = \frac{V_x}{R_2} + \frac{V_x}{sL} + \frac{V_x}{sC}$$

$$V_x = V_o \frac{R_4}{R_3 + R_4}$$

$$\frac{V_i}{R_1} = \left( \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{sL} + sC \right) V_x$$

$$V_i = \frac{R_1 R_4}{R_3 + R_4} \left( \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{sL} + sC \right) V_o$$

$$\frac{V_o}{V_i} = \frac{1}{\frac{R_1 R_4}{R_3 + R_4} \left( \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{sL} + sC \right)} \quad \frac{sL}{sL}$$


multiply by 1

$$= \frac{sL}{\frac{R_1 R_4}{R_3 + R_4} \left( \frac{sL}{R_1} + \frac{sL}{R_2} + 1 + s^2 LC \right)}$$

dividing by LC

$$\frac{V_o}{V_i} = \frac{R_3 + R_4}{R_1 R_4} \frac{s \frac{1}{C}}{s^2 + s \left( \frac{1}{R_1 C} + \frac{1}{R_2 C} \right) + \frac{1}{LC}}$$

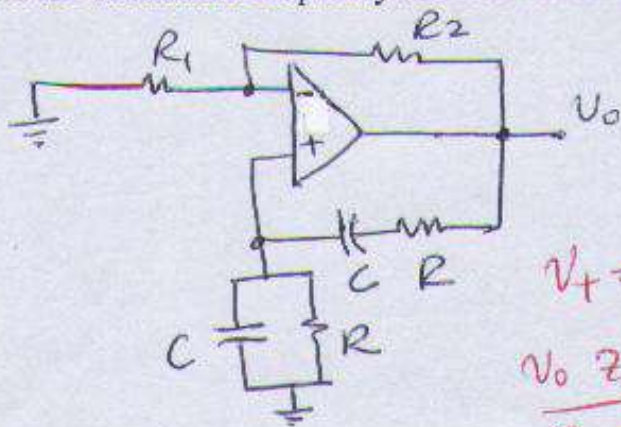2) Find the oscillation frequency and oscillation condition for the circuit given below:



$$\omega_o = \frac{1}{CR}$$

$$\text{condition: } \frac{R_2}{R_1} = 2$$

$$V_+ = V_-$$

$$\frac{V_o Z_1}{Z_1 + Z_2} = \frac{V_o R_1}{R_1 + R_2}$$

$$Z_1 = R \parallel \frac{1}{j\omega C} = \frac{R}{1 + j\omega CR}$$

$$Z_2 = R + \frac{1}{j\omega C}$$

$$\frac{\frac{R}{1 + j\omega CR}}{\frac{R}{1 + j\omega CR} + R + \frac{1}{j\omega C}} = \frac{R_1}{R_1 + R_2}$$

$$\frac{R}{R + (R + \frac{1}{j\omega C})(1 + j\omega CR)} = \frac{R_1}{R_1 + R_2}$$

$$\frac{R}{R + R + R + j\omega CR^2 + \frac{1}{j\omega C}} = \frac{R_1}{R_1 + R_2}$$

$$\text{Real parts} \rightarrow \frac{R}{3R} = \frac{R_1}{R_1 + R_2}$$

$$\frac{1}{3} = \frac{1}{1 + \frac{R_2}{R_1}}$$

$$\rightarrow \boxed{\frac{R_2}{R_1} = 2}$$

Imaginary part

$$j\omega CR^2 + \frac{1}{j\omega C} = 0$$

$$j\omega CR^2 = -\frac{1}{j\omega C}$$


$$-\omega^2 = -\frac{1}{C^2 R^2}$$

$$\rightarrow \boxed{\omega = \frac{1}{CR}}$$

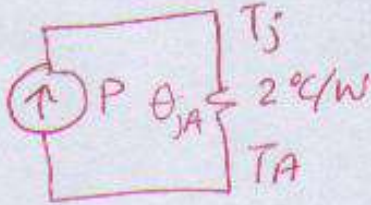- 3) A particular transistor having a thermal resistance  $\theta_{JA} = 2^\circ\text{C/W}$  is operating at an ambient temperature of  $30^\circ\text{C}$  with a collector-emitter voltage of  $20\text{ V}$ . If long life requires a maximum junction temperature of  $130^\circ\text{C}$ , what is the corresponding device power rating? What is the greatest average collector current that should be considered?

$$P = \underline{50\text{ W}}$$

$$I_{C-\text{ave-max}} = \underline{2.5\text{ A}}$$




$$T_J = T_A + \theta_{JA} P$$

$$\frac{T_J - T_A}{\theta_{JA}} = P \rightarrow P = \frac{130 - 30}{2} = 50\text{ W}$$

$$50\text{ W} = 20\text{ V } I_C \rightarrow I_C = \frac{50}{20} = 2.5\text{ A}$$

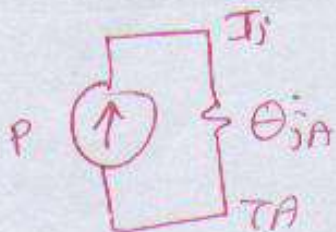- 4) A particular transistor has a power rating at  $25^\circ\text{C}$  of  $200\text{ mW}$ , and a maximum junction temperature of  $150^\circ\text{C}$ . What is its thermal resistance? What is its power rating when operated at an ambient temperature of  $70^\circ\text{C}$ ? What is its junction temperature when dissipating  $100\text{ mW}$  at an ambient temperature of  $50^\circ\text{C}$ ?



$$\theta_{JA} = \frac{T_J - T_A}{P} = \frac{150 - 25}{0.2}$$

$$\theta_{JA} = \underline{625^\circ\text{C/W}}$$

$$= \frac{125}{0.2} = 625^\circ\text{C/W}$$

$$P = \underline{0.13\text{ W}}$$

$$T_J = \underline{112.5^\circ\text{C}}$$

$$P = \frac{150 - 70}{625} = \frac{80^\circ\text{C}}{625^\circ\text{C/W}} =$$

$$T_J = 50 + 0.100 \times 625 = 112.5^\circ\text{C}$$