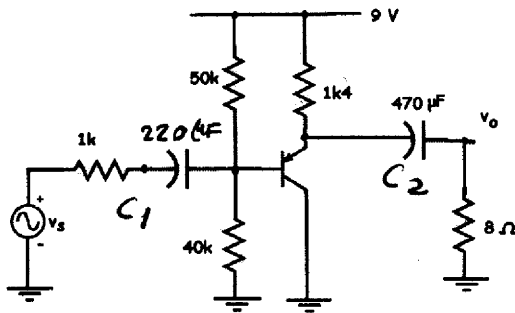


ID number: ERKAYA Name: SOLUTIONS Signature: _____

30 pts 1) Find the low 3 dB cutoff frequency of the amplifier given below. ($\beta = 250$) $f_L = \underline{16.96 \text{ Hz}}$



DC analysis: $V_B \approx 9 \times \frac{40}{40+50} = 4V$

$V_E = V_B + 0.7 = 4.7V$

$I_E = \frac{9 - 4.7}{1.4k} = 3.07 \text{ mA}$

$I_C \approx I_E = 3 \text{ mA}$, $g_m = \frac{3}{0.025} = 120 \text{ mA/V}$

$r_{\pi} = \frac{\beta}{g_m} = \frac{250}{120} = 2.08 \text{ k}\Omega$

Possible dominant pole frequencies:

$f_1 = \frac{1}{2\pi C_1 R_{th1}}$

$R_{th1} = 1k + 40k \parallel 50k \parallel [2k + (250+1)(0.008 \parallel 1.4)k]$
 $= 4.387 \text{ k}\Omega$ (C_2 short)

$f_1 = \frac{1}{2\pi \cdot 220 \times 10^{-6} \times 4387} = 0.16 \text{ Hz}$

$f_2 = \frac{1}{2\pi C_2 R_{th2}}$, $R_{th2} = 8 + 1400 \parallel \frac{(1k \parallel 40k \parallel 50k) + 2k}{251} \approx 20 \Omega$ (C_1 short)

$f_2 = \frac{1}{2\pi \times 470 \times 10^{-6} \times 20} = 16.93 \text{ Hz} \rightarrow \text{dominant}$


f_1 must be recalculated with C_2 open circuit

$R_{th1} = 1k + 40k \parallel 50k \parallel [2k + 251 \times 1.4k] = 21.9 \text{ k}\Omega$

$f_1 = \frac{1}{2\pi \times 220 \times 10^{-6} \times 21900} = 0.033 \text{ Hz}$

$f_L \approx f_1 + f_2 = 0.033 + 16.93 = 16.96 \text{ Hz}$

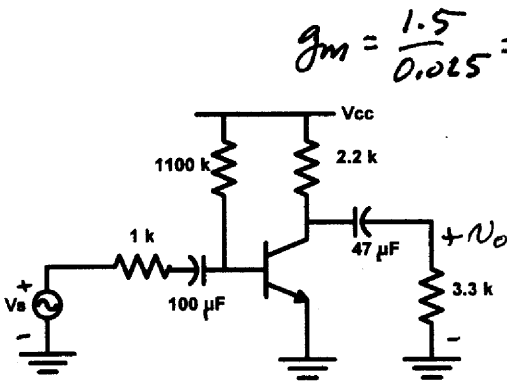35 pts 2) Using Miller's theorem, find the high 3dB cutoff frequency of the amplifier given below. Assume $\beta = 200$, $I_C = 1.50$ mA, $C_\mu = 1.2$ pF, $f_T = 400$ MHz, $r_x = 100$ ohms, $r_o = 120$ k



$$g_m = \frac{1.5}{0.025} = 60 \text{ mA/V}$$

$$f_H = 1.61 \text{ MHz}$$

$$r_\pi = \frac{\beta}{g_m} = \frac{200}{60} = 3.33 \text{ k}\Omega$$

P.S. eg. det - Miller's theorem applied on C_μ

$$R_{sh} = 2.2 \text{ k} \parallel 3.3 \text{ k} \parallel 120 \text{ k} = 1.3 \text{ k}$$

$$C_A = C_\mu (1 + g_m R_{sh})$$

$$g_m R_{sh} = 60 \times 1.3 = 78$$

$$C_A = 1.2 \text{ pF} (1 + 78) = 94.8 \text{ pF}$$

$$C_B \approx C_\mu = 1.2 \text{ pF}$$

$$C_\pi = \frac{g_m}{2\pi f_T} - C_\mu = \frac{60 \times 10^{-3}}{2\pi \times 400 \times 10^6} - 1.2 \times 10^{-12} = 22.67 \times 10^{-12} \text{ F}$$

$$C_A + C_\pi = 117.47 \text{ pF}$$

pole frequencies


$$f_A = \frac{1}{2\pi (C_A + C_\pi) R_{thA}}$$

$$R_{thA} = r_\pi \parallel [r_x + 1 \text{ k} \parallel 1100 \text{ k}] = 3.33 \parallel [0.1 + 1] = 0.826 \text{ k}\Omega$$

$$f_A = \frac{1}{2\pi \times 117.47 \times 10^{-12} \times 826} = 1.64 \times 10^6 \text{ Hz}$$


$$f_B = \frac{1}{2\pi C_B R_{sh}} = \frac{1}{2\pi \times 1.2 \times 10^{-12} \times 1300} = 102 \times 10^6 \text{ Hz}$$

$$f_H = \frac{1}{\frac{1}{f_A} + \frac{1}{f_B}} = 1.61 \times 10^6 \text{ Hz}$$

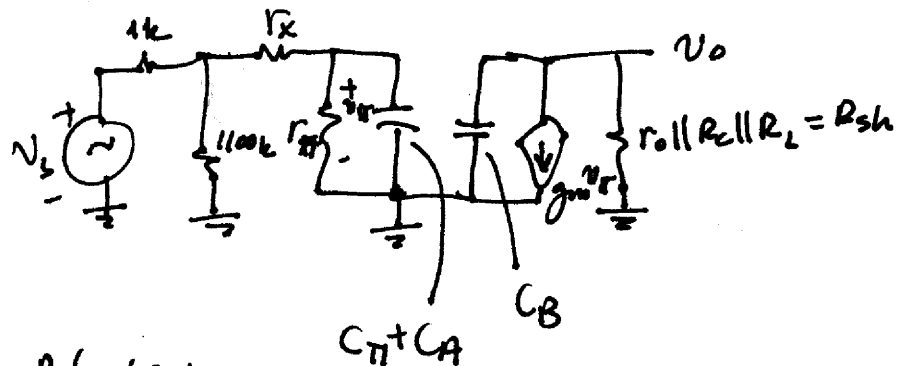


Pts 3) Find the voltage gain of the amplifier given below.

$$\frac{v_o}{v_i} = \underline{982}$$

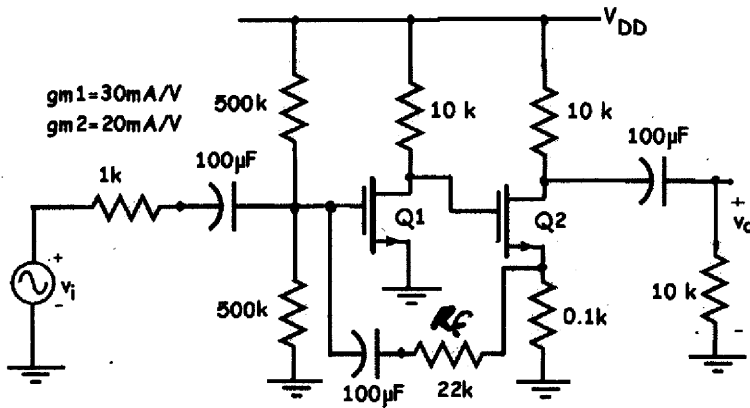

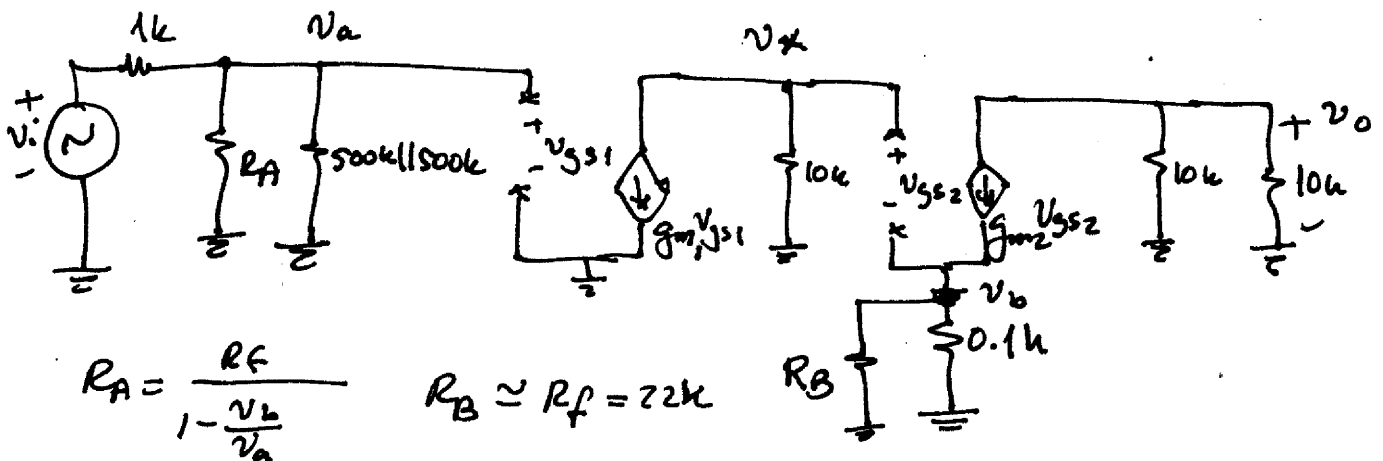Apply Miller's Theorem on R_f and get small signal eq. ckt.



$$R_A = \frac{R_f}{1 - \frac{v_b}{v_a}}$$

$$R_B \approx R_f = 22k$$

$$R_B$$

$$\left. \begin{aligned} \frac{v_b}{v_x} &= \frac{(R_B \parallel 0.1) g_{m2}}{1 + (R_B \parallel 0.1) g_{m2}} \approx \frac{0.1 \times 20}{1 + 0.1 \times 20} = \frac{2}{3} \\ \frac{v_x}{v_a} &= -g_{m1} \parallel 10k = -300 \end{aligned} \right\} \frac{v_b}{v_a} = -300 \times \frac{2}{3} = -200$$

$$R_A = \frac{22k}{1 + 200} = 0.109k = 109\Omega$$

$$\frac{v_o}{v_x} = \frac{-g_{m2} (10k \parallel 10k)}{1 + g_{m2} (R_B \parallel 0.1k)} = \frac{-100}{3}$$

$$\frac{v_x}{v_a} = -300$$

$$\frac{v_a}{v_i} = \frac{R_A \parallel 500k \parallel 500k}{1 + R_A \parallel 500k \parallel 500k} \approx \frac{R_A}{1 + R_A} = \frac{0.109}{1.109} = 0.0982$$

$$\frac{v_o}{v_i} = \frac{v_o}{v_x} \cdot \frac{v_x}{v_a} \cdot \frac{v_a}{v_i} = \left(-\frac{100}{3}\right) (-300) (0.0982) = 982$$