

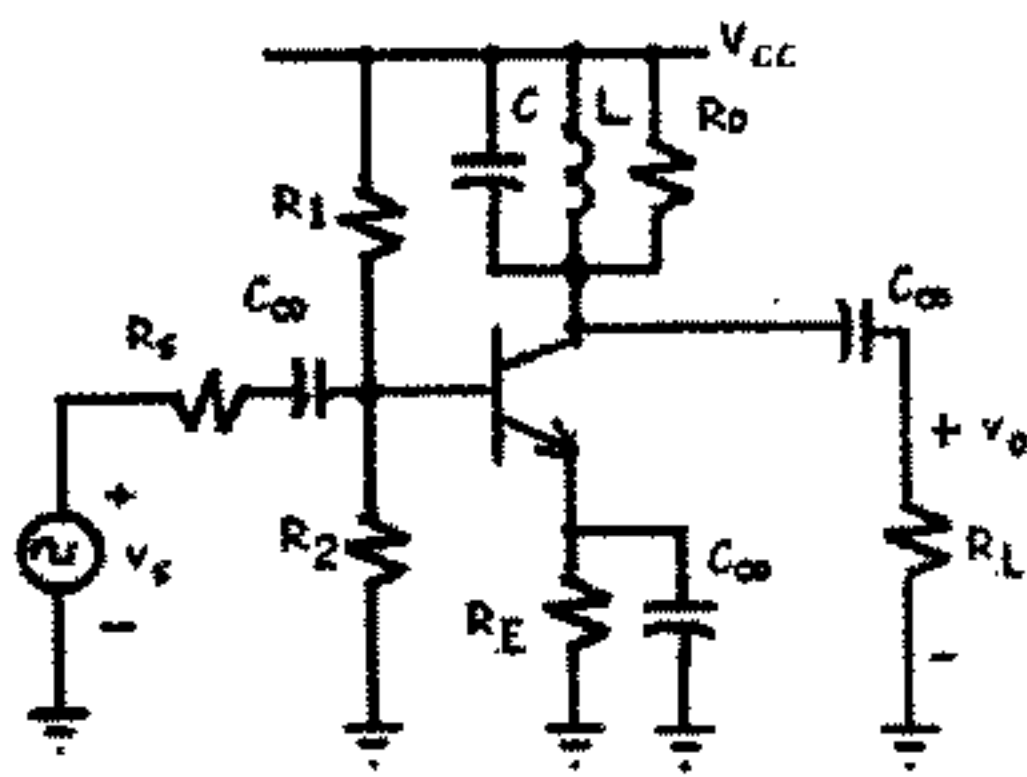


ID number: ERKAYA Name: SOLUTIONS Signature: _____

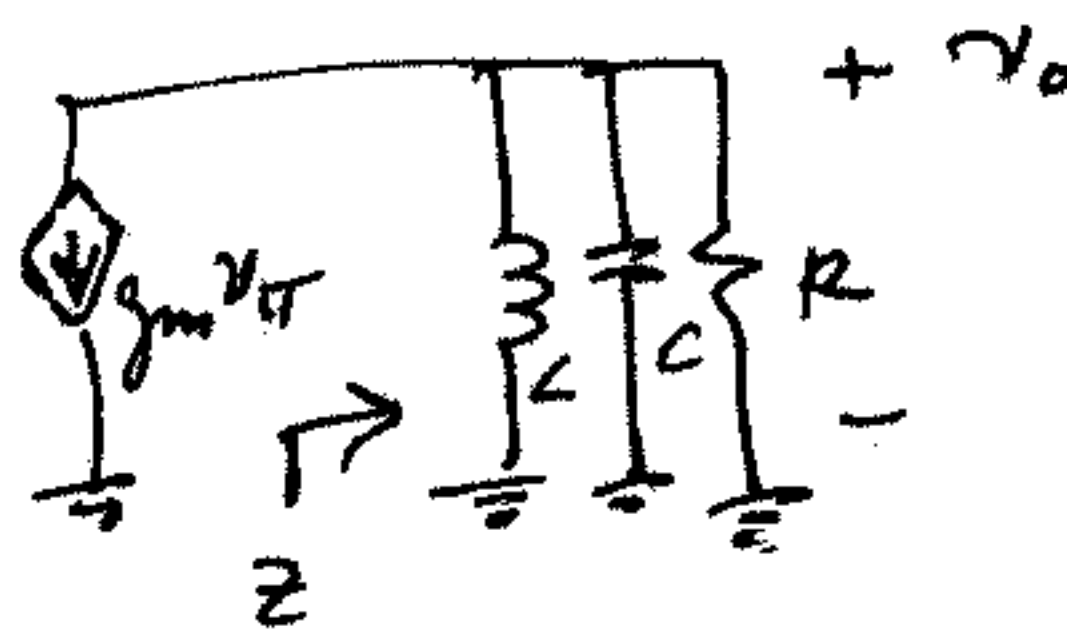- 1) Find the small signal transfer function of the circuit given below. Indicate what kind of a filter it is (i.e., high-pass, low-pass, band-pass). Put the transfer function in the form as follows:
 $V_o/V_s = (as^2 + bs + c)/(s^2 + s\omega_o/Q + \omega_o^2)$. Ignore internal capacitances and Early effect.



S.S. eq. det:

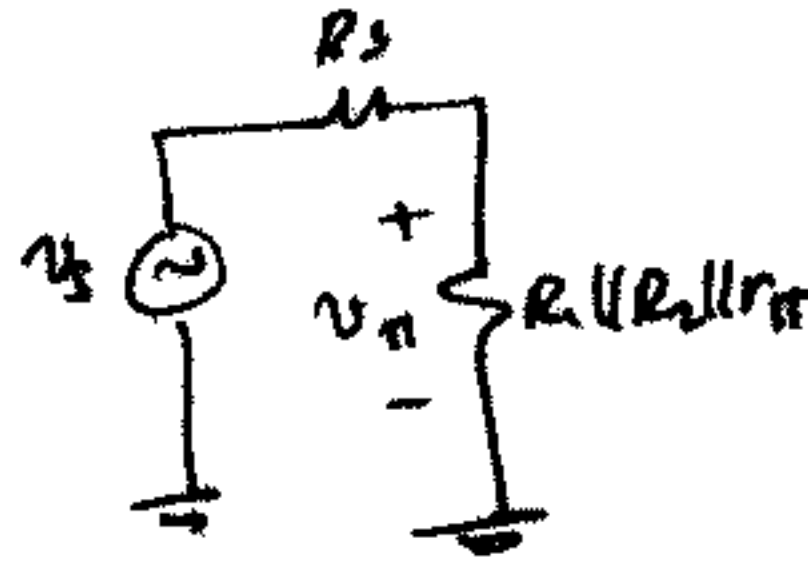

$$a = 0$$

$$b = -\frac{g_m K}{C}$$

$$c = 0$$

$$\omega_o = \frac{1}{\sqrt{LC}}$$

$$\omega_o/Q = \frac{1}{RC}$$

type = Band pass

$$R = R_o \parallel R_L$$

$$Z = \frac{1}{\frac{1}{sL} + \frac{1}{R} + sC} = \frac{\frac{s}{C}}{\frac{1}{CL} + \frac{s}{RC} + s^2}$$


$$Z = \frac{\frac{s}{C}}{s^2 + s \frac{1}{RC} + \frac{1}{LC}}$$

$$\frac{V_o}{V_s} = -g_m Z \frac{R_1 \parallel R_2 \parallel r_{\pi}}{R_s + R_1 \parallel R_2 \parallel r_{\pi}} = \frac{-g_m \frac{s}{C} K}{s^2 + s \frac{1}{RC} + \frac{1}{LC}}$$

$\equiv K$

(Loading effect at the input)

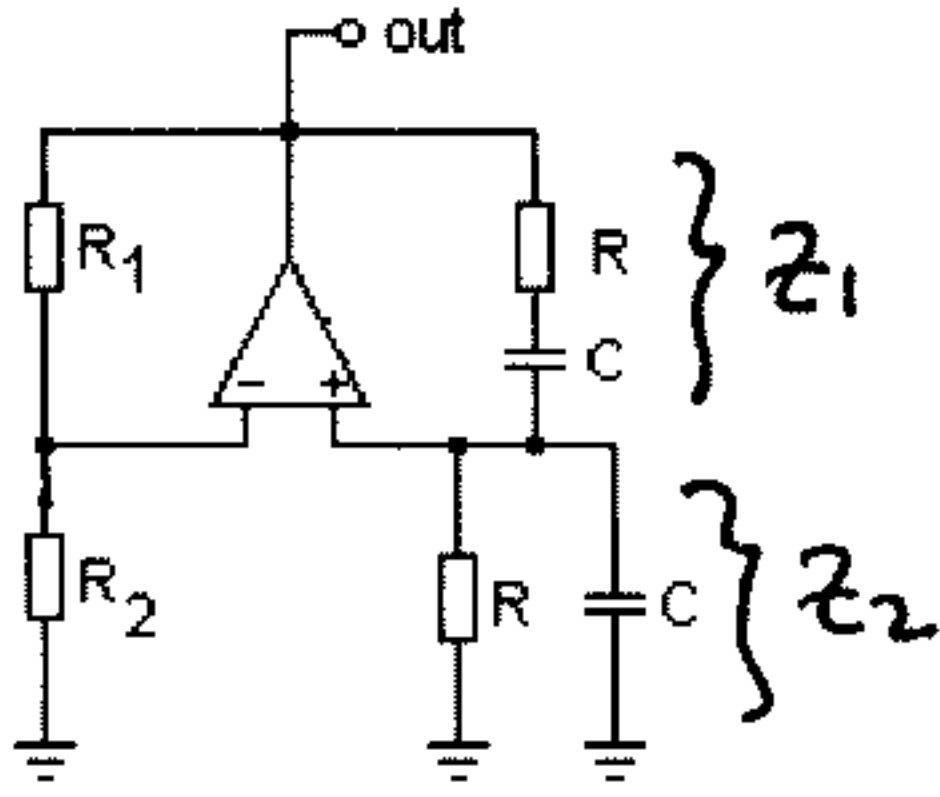2) Find the oscillation frequency and oscillation condition for the circuit given below:



$$\omega_o = \frac{1}{CR}$$

$$\text{condition: } R_1 = 2R_2$$

$$\frac{R_2}{R_1 + R_2} = \frac{Z_2}{Z_1 + Z_2}$$

$$Z_1 = R + \frac{1}{j\omega C} = \frac{1 + j\omega CR}{j\omega C}$$

$$Z_2 = \frac{R \cdot \frac{1}{j\omega C}}{R + \frac{1}{j\omega C}} = \frac{R}{1 + j\omega CR}$$

$$\frac{R_2}{R_1 + R_2} = \frac{\frac{R}{1 + j\omega CR}}{\frac{1 + j\omega CR}{j\omega C} + \frac{R}{1 + j\omega CR}} = \frac{R}{\frac{(1 + j\omega CR)^2}{j\omega C} + R} = \frac{j\omega CR}{(1 + j\omega CR)^2 + j\omega CR}$$

$$\frac{R_2}{R_1 + R_2} = \frac{j\omega CR}{1 - \omega^2 C^2 R^2 + 2j\omega CR + j\omega CR} = \frac{j\omega CR}{(1 - \omega^2 C^2 R^2) + 3j\omega CR}$$


$$\text{Real part} = \frac{R_2}{R_1 + R_2}$$

$$\text{Im part} = 0 \rightarrow 1 - \omega^2 C^2 R^2 = 0 \rightarrow \boxed{\omega = \frac{1}{CR}} \text{ oscill. freq.}$$

$$\text{Real part } \frac{R_2}{R_1 + R_2} = \frac{j\omega CR}{3j\omega CR} = \frac{1}{3}$$

$$\frac{1}{\frac{R_1}{R_2} + 1} = \frac{1}{3} \rightarrow \boxed{R_1 = 2R_2} \text{ osc. cond.}$$

A switching bipolar transistor is mounted on a heat sink. Its total thermal resistance $\theta_{ja} = 0.1^\circ\text{C/W}$. The thermal resistance between the junction and the case $\theta_{jc} = 0.03^\circ\text{C/W}$ while the thermal resistance between the case and the heat sink $\theta_{cs} = 0.05^\circ\text{C/W}$. The transistor has the following collector current and collector-emitter voltage in time:

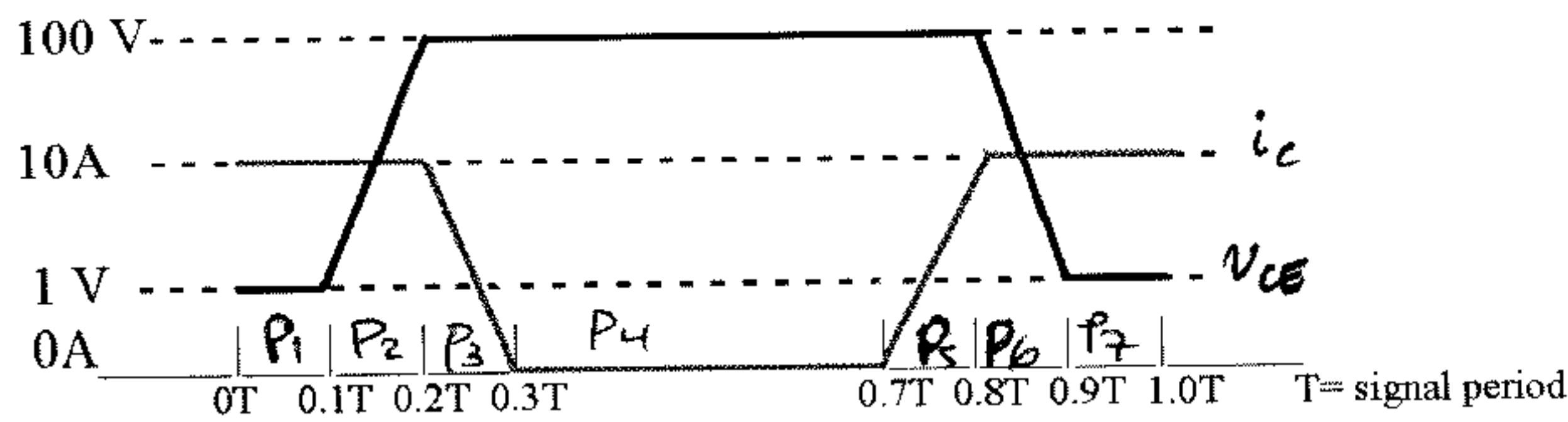

- Find the average power dissipation in the transistor.
- Find the temperature of the heat sink if the ambient room temperature is 20°C .
- If the max allowed junction temperature is 145°C , what would be the max room temperature the transistor can be operated safely?

$$P_D = 203\text{W}$$

$$T_s = 24.06^\circ\text{C}$$

$$T_{\max} = 124.7^\circ\text{C}$$

$$a) \quad P_D = \frac{P_1 + P_2 + P_3 + 4P_4 + P_5 + P_6 + P_7}{10}$$

$$P_1 = 10 \times 1 = 10\text{W}$$

$$P_2 = 10 \times \left(\frac{1+100}{2} \right) = 505\text{W}$$

$$P_3 = 100 \times \left(\frac{10+0}{2} \right) = 500\text{W}$$

$$P_4 = 0$$

$$P_5 = P_3 = 500\text{W}$$

$$P_6 = P_2 = 505\text{W}$$

$$P_7 = P_1 = 10\text{W}$$

$$P_D = \frac{10 + 505 + 500 + 0 + 500 + 505 + 10}{10} = \frac{2030}{10} = 203\text{W}$$

$$b) \quad \theta_{ja} = \theta_{jc} + \theta_{cs} + \theta_{sa}, \quad \theta_{sa} = \theta_{ja} - \theta_{cs} - \theta_{jc}$$

$$= 0.1 - 0.03 - 0.05 = 0.02^\circ\text{C/W}$$

$$T_s = T_a + P_D \theta_{sa} = 20^\circ\text{C} + 203 \times 0.02 = 24.06^\circ\text{C}$$

$$c) \quad T_{\max} + \theta_{ja} P_D = T_{j\max}$$

$$T_{\max} = T_{j\max} - \theta_{ja} P_D = 145^\circ\text{C} - 203 \times 0.1 = 124.7^\circ\text{C}$$