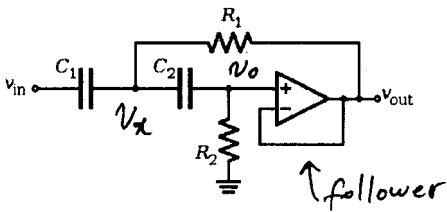


ID number: _____ Name: _____ Signature: _____

(40 pts)

- 1) Find the transfer function of the circuit given below. Indicate what kind of a filter it is (i.e., high-pass, low-pass, band-pass). Put the transfer function in the form as follows:
 $(as^2 + bs + c)/(s^2 + s\omega_0/Q + \omega_0^2)$.



$$\frac{V_x - V_o}{\frac{1}{sC_2}} = \frac{V_{out}}{R_2} \quad (1)$$

$$V_x - V_{out} = \frac{V_{out}}{sC_2 R_2} \quad (2)$$

$$a = 1$$

$$b = 0$$

$$c = 0$$

$$\frac{V_{in} - V_x}{\frac{1}{sC_1}} = \frac{V_x - V_{out}}{R_1} + \frac{V_x - V_{out}}{\frac{1}{sC_2}} \quad (4)$$

$$V_x = \left(1 + \frac{1}{sC_2 R_2}\right) V_{out} \quad (3)$$

$$\omega_0 = \frac{1}{\sqrt{R_1 C_1 R_2 C_2}}$$

$$\omega_0/Q = \frac{\frac{1}{C_1 R_2} + \frac{1}{C_2 R_2}}{1}$$

$$\text{type} = \text{High pass}$$

Substituting (2) and (3) into (4):

$$sC_1 \left[V_{in} - \left(1 + \frac{1}{sC_2 R_2}\right) V_{out} \right] = \frac{V_{out}}{sR_1 R_2 C_2} + \frac{sC_2 V_{out}}{sC_2 R_2}$$

$$V_{in} - \left(1 + \frac{1}{sC_2 R_2}\right) V_{out} = \frac{V_{out}}{s^2 C_1 R_1 C_2 R_2} + \frac{V_{out}}{sC_1 R_2}$$


$$V_{in} = V_{out} \left[1 + \frac{1}{sC_2 R_2} + \frac{1}{s^2 C_1 R_1 C_2 R_2} + \frac{1}{sC_1 R_2} \right]$$

$$\frac{V_{out}}{V_{in}} = \frac{1}{1 + \frac{1}{s} \left(\frac{1}{C_2 R_2} + \frac{1}{C_1 R_2} \right) + \frac{1}{s^2 C_1 R_1 C_2 R_2}}$$

$$\frac{V_{out}}{V_{in}} = \frac{s^2}{s^2 + s \left(\frac{1}{C_1 R_2} + \frac{1}{C_2 R_2} \right) + \frac{1}{C_1 R_1 C_2 R_2}} = \frac{as^2 + bs + c}{s^2 + s \frac{\omega_0}{Q} + \omega_0^2}$$

(40 pts)

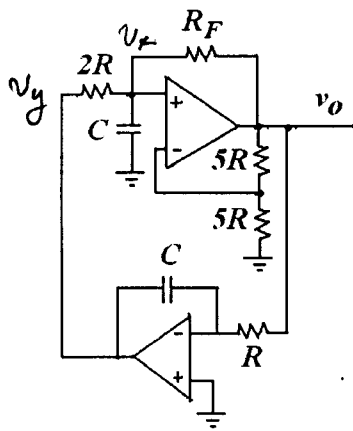2) Find the oscillation frequency and oscillation condition for the circuit given below:



$$\frac{v_o}{v_x} = 1 + \frac{5R}{5R} = 2 \rightarrow v_x = \frac{v_o}{2} \quad (1)$$

$$\omega_o = \frac{1}{CR}$$

$$\text{condition: } R_F = 2R$$

$$\frac{v_y}{v_o} = -\frac{\frac{1}{5C}}{R} = -\frac{1}{5CR} \rightarrow v_y = -\frac{v_o}{5CR} \quad (2)$$

$$\text{KCL at } v_x: \frac{v_y - v_x}{2R} = \frac{v_x}{\frac{1}{5C}} + \frac{v_x - v_o}{R_F} \quad (3)$$

Substituting (1) and (2) in (3):

$$\frac{-\frac{v_o}{5CR} - \frac{v_o}{2}}{2R} = 5C \frac{v_o}{2} + \frac{\frac{v_o}{2} - v_o}{R_F}$$

dividing by v_o ,

$$-\frac{1}{25CR^2} - \frac{1}{4R} = \frac{5C}{2} - \frac{1}{2R_F}$$

$$\text{Substitute } s = j\omega$$


$$-\frac{1}{2j\omega CR^2} - \frac{1}{4R} = \frac{j\omega C}{2} - \frac{1}{2R_F}$$

Imaginary parts: $-\frac{1}{2j\omega CR^2} = \frac{j\omega C}{2} \rightarrow \frac{1}{\omega^2 CR^2} = 1 \rightarrow \boxed{\omega = \frac{1}{CR}}$

Real parts: $-\frac{1}{4R} = -\frac{1}{2R_F} \rightarrow \boxed{R_F = 2R}$

(20 pts)

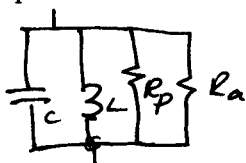3) A coil having an inductance of $10 \mu\text{H}$ is intended to be used around 1-MHz frequency. Its Q is specified to be 200. Find its equivalent parallel resistance R_p . What is the value of the capacitor required to produce resonance at 1 MHz? What additional parallel resistance R_a is required to produce a 3-dB bandwidth of 10 kHz?



$$Q = \frac{R_p}{\omega_o L} \rightarrow R_p = Q \omega_o L = 200 \times 2\pi \times 10^6 \times 10 \times 10^{-6} \quad R_p = 12566 \Omega$$

$$R_p = 12566 \Omega$$

$$C = \frac{2.53 \times 10^{-9}}{F}$$

$$\omega_o^2 = \frac{1}{LC} \rightarrow C = \frac{1}{\omega_o^2 L} = \frac{1}{(2\pi \times 10^6)^2 \times 10 \times 10^{-6}}$$

$$R_a = 12566 \Omega$$

$$B = 2\pi \times 10 \times 10^3 \text{ rad/s}$$

$$C = 2.53 \times 10^{-9} F$$

$$B = \frac{1}{CR} \rightarrow R = \frac{1}{BC} = \frac{1}{2\pi \times 10000 \times 2.53 \times 10^{-9}} = 6283 \Omega$$

$$\frac{1}{R} = \frac{1}{R_a} + \frac{1}{R_p} \rightarrow \frac{1}{R_a} = \frac{1}{R} - \frac{1}{R_p} = \frac{1}{6283} - \frac{1}{12566} = \frac{1}{12566}$$

$$R_a = 12566 \Omega$$