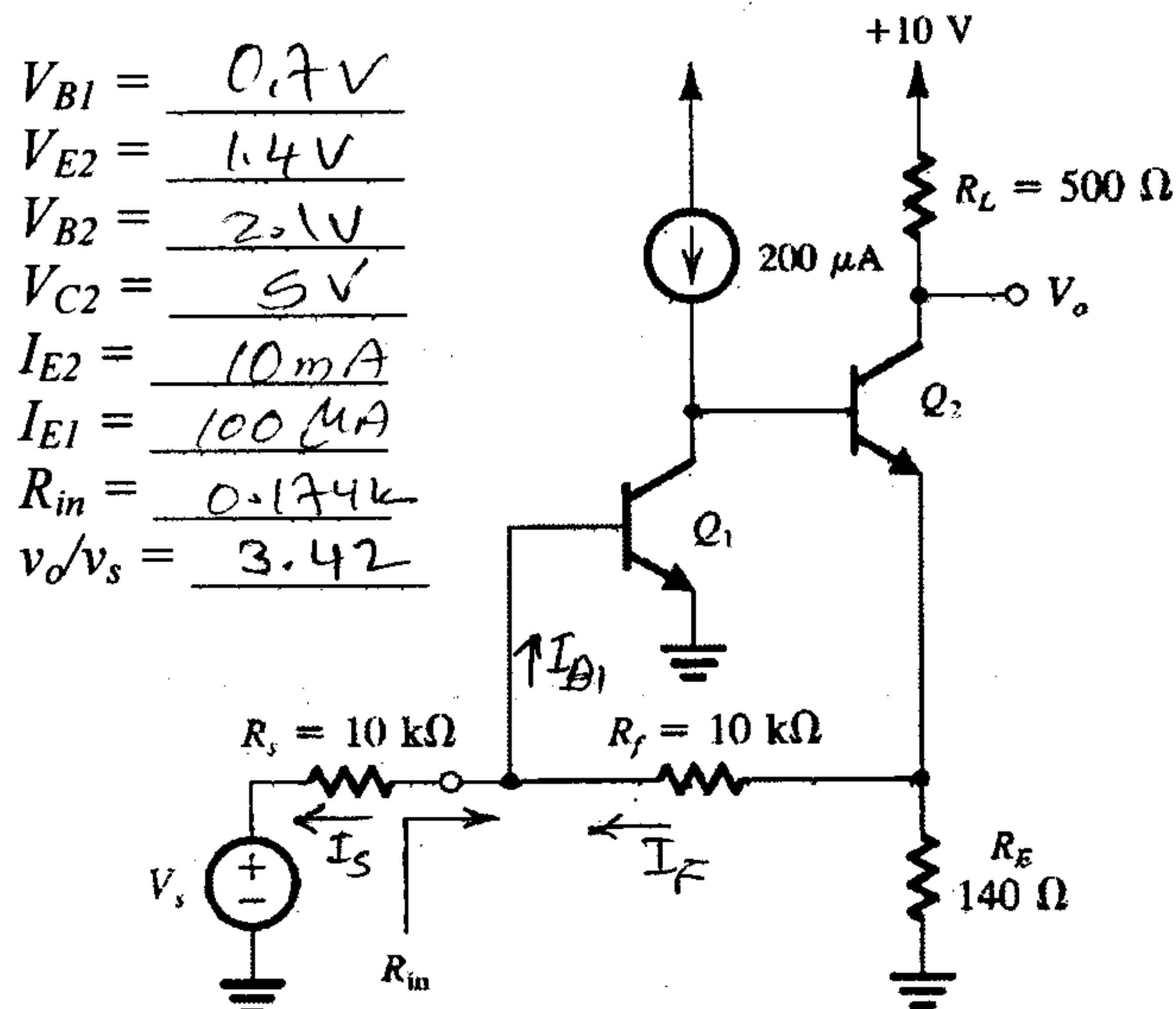


I have neither given nor received unauthorized help with this exam, nor do I have reason that anybody else has.

ID no: ERICAYA Name: SOLUTIONS Signature: _____

1) For the amplifier circuit below, assume that V_s has a zero dc component and that I_{B1} is much smaller than the current in R_f . Find the dc voltages at all nodes and the dc emitter currents of Q_1 and Q_2 . Let the BJTs have $\beta = 100$. Find small signal voltage gain v_o/v_s and R_{in} .



q:32

$$\begin{aligned} V_{B1} &= 0.7V \\ V_{E2} &= 1.4V \\ V_{B2} &= 2.1V \\ V_{C2} &= 5V \\ I_{E2} &= 10mA \\ I_{E1} &= 100\mu A \\ R_{in} &= 0.174k \\ v_o/v_s &= 3.42 \end{aligned}$$

$I_{B1} \ll I_F$ given

Q_1 : active mode $\rightarrow V_{SE1} = 0.7V$

$V_{E1} = 0 \rightarrow V_{B1} = 0.7V$

Bias current $I_S \approx I_F = \frac{0.7}{10k}$

$V_{E2} = 2 \times I_S \times 10k = 1.4V$

$V_{B2} = V_{BE2} + V_{E2} = 2.1V$

$I_{E2} = \frac{V_{E2}}{0.140 \parallel 20k} \approx \frac{1.4}{0.14} = 10mA$

$I_{C2} \approx I_{E2} \quad V_{C2} = 10 - 10 \times 0.5 = 5V$


$I_{B2} = \frac{10}{100} mA = 0.1mA = 100\mu A$

$I_{C1} = 200 - 100 = 100\mu A = I_{E1}$

$g_{m1} = \frac{0.1}{0.025} = 4mA/V, \quad r_{\pi1} = \frac{\beta}{g_{m1}} = \frac{100}{4} = 25k\Omega$

$g_{m2} = \frac{10}{0.025} = 400mA/V, \quad r_{\pi2} = \frac{\beta}{g_{m2}} = \frac{100}{400} = 0.25k\Omega$


Small signal eq. ckt:

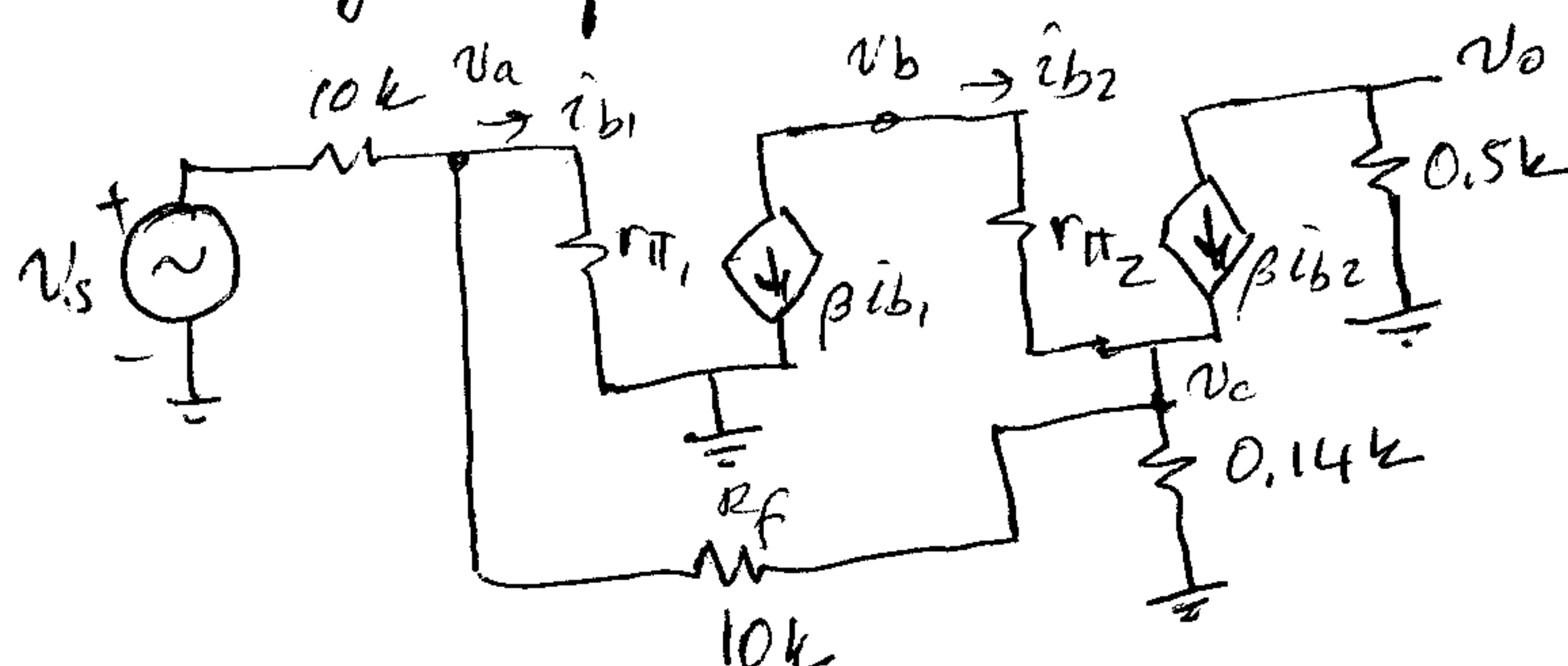

Apply Miller's theorem on R_f

$R_A = \frac{R_f}{1 - \frac{v_c}{v_a}}, \quad R_B \approx R_f$

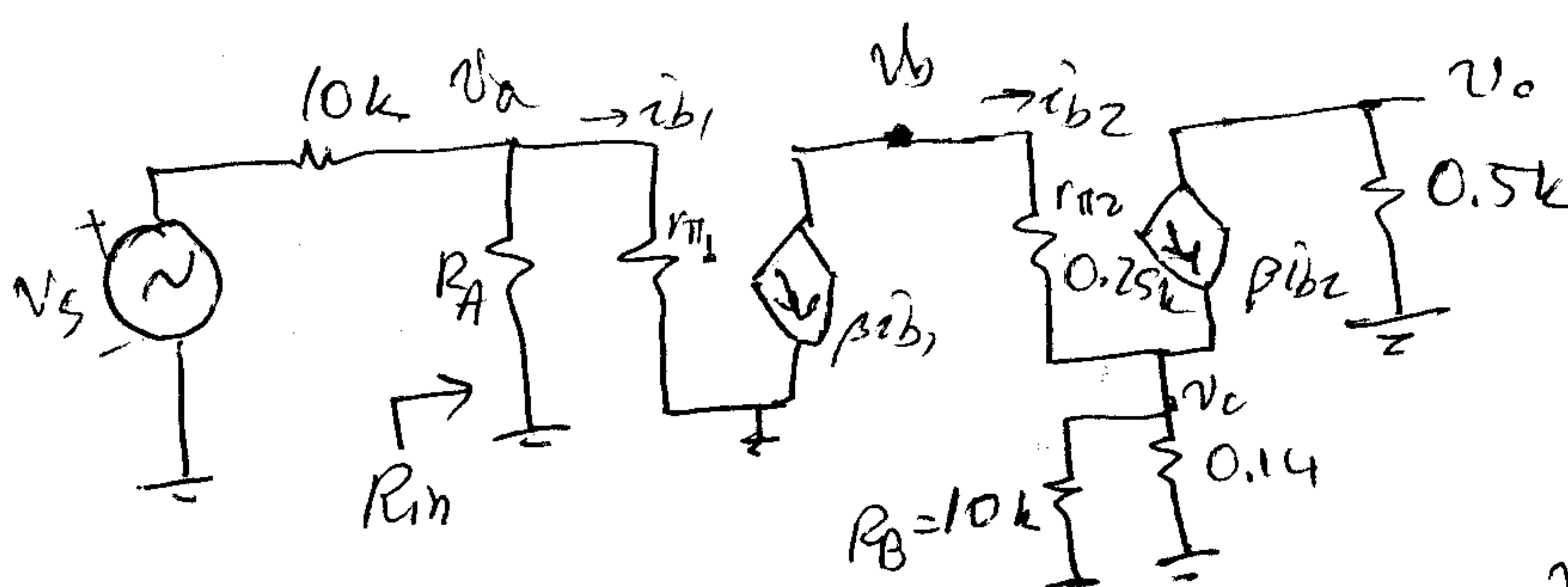$R_{in} = R_A \parallel r_{\pi1} \approx 0.174 \parallel 25 = 0.174k$



$\frac{v_c}{v_b} = \frac{(101)(0.14 \parallel 10)}{0.25 + (101)(0.14 \parallel 10)} = 0.98$

$\frac{v_b}{v_a} = \frac{-\beta(r_{\pi2} + (\beta+1)(0.14 \parallel 10))}{r_{\pi1}} = \frac{-100 \times 14.36}{25} = -57.44$

$\frac{v_o}{v_b} = \frac{-100 \times 0.5}{14.36} = -3.48$

$\frac{v_o}{v_a} = (-3.48)(-57.44) = 200$

$\frac{v_o}{v_s} = 200 \frac{0.174}{10.174} = 3.42$

$\frac{v_c}{v_a} = -57.44 \times 0.98 = -56.44$


$R_A = \frac{10}{57.44} = 0.174k$

q: 46

9246

2) Select C_1 and C_2 in the circuit below so that the low 3dB cutoff frequency is 10 Hz. The BJTs have $\beta = 120$.

$C_1 = 0.8 \mu F$ $C_2 = 3 \mu F$

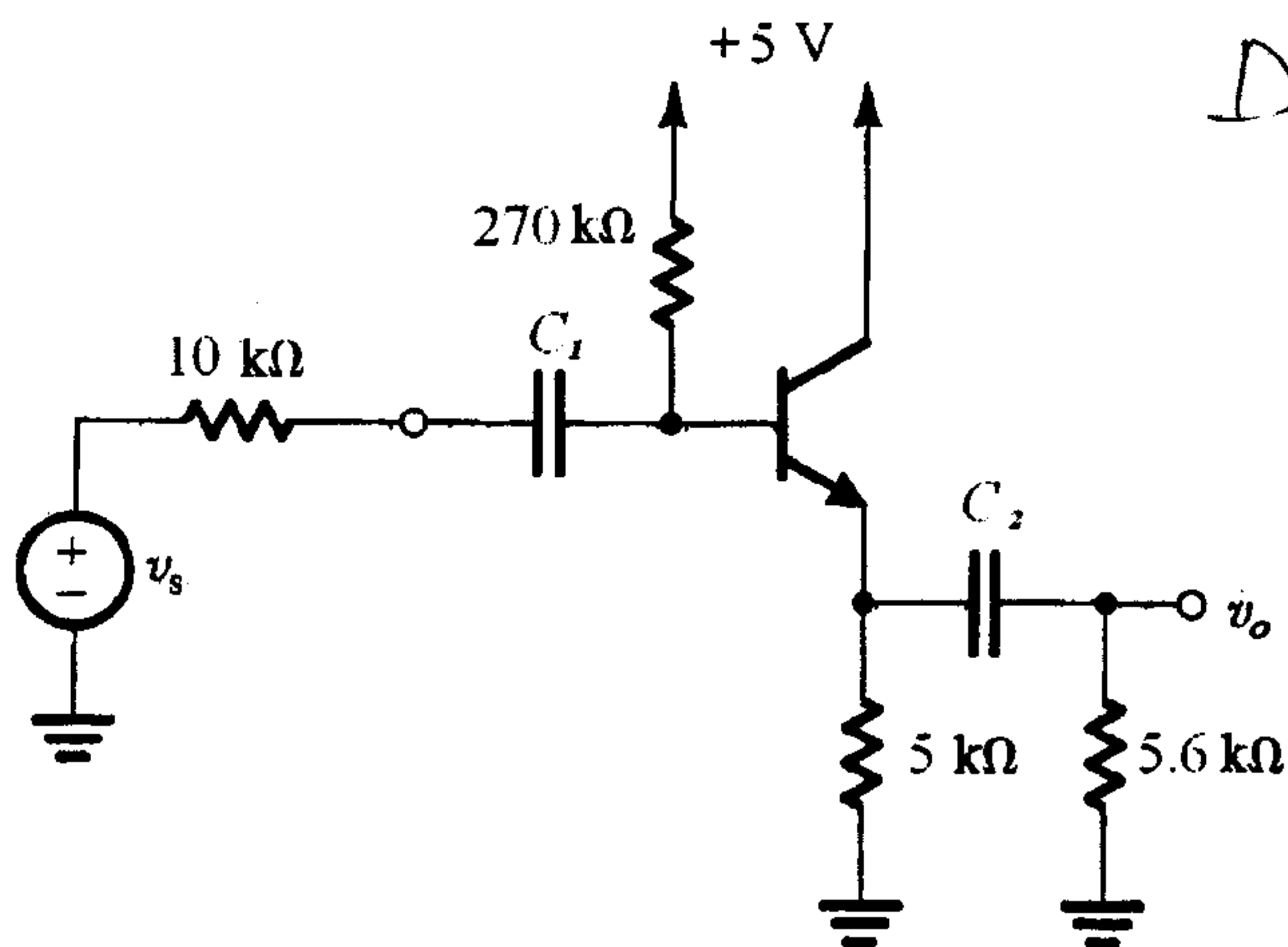


DC analysis: $5 \times (\beta + 1) I_B + 0.7 + 270 I_B = 5$

$$I_B = \frac{5 - 0.7}{121 \times 5 + 270} = 0.0049$$

$$I_C = 120 I_B = 0.589 \text{ mA}$$

$$g_m = \frac{0.589}{0.025} = 23.58$$
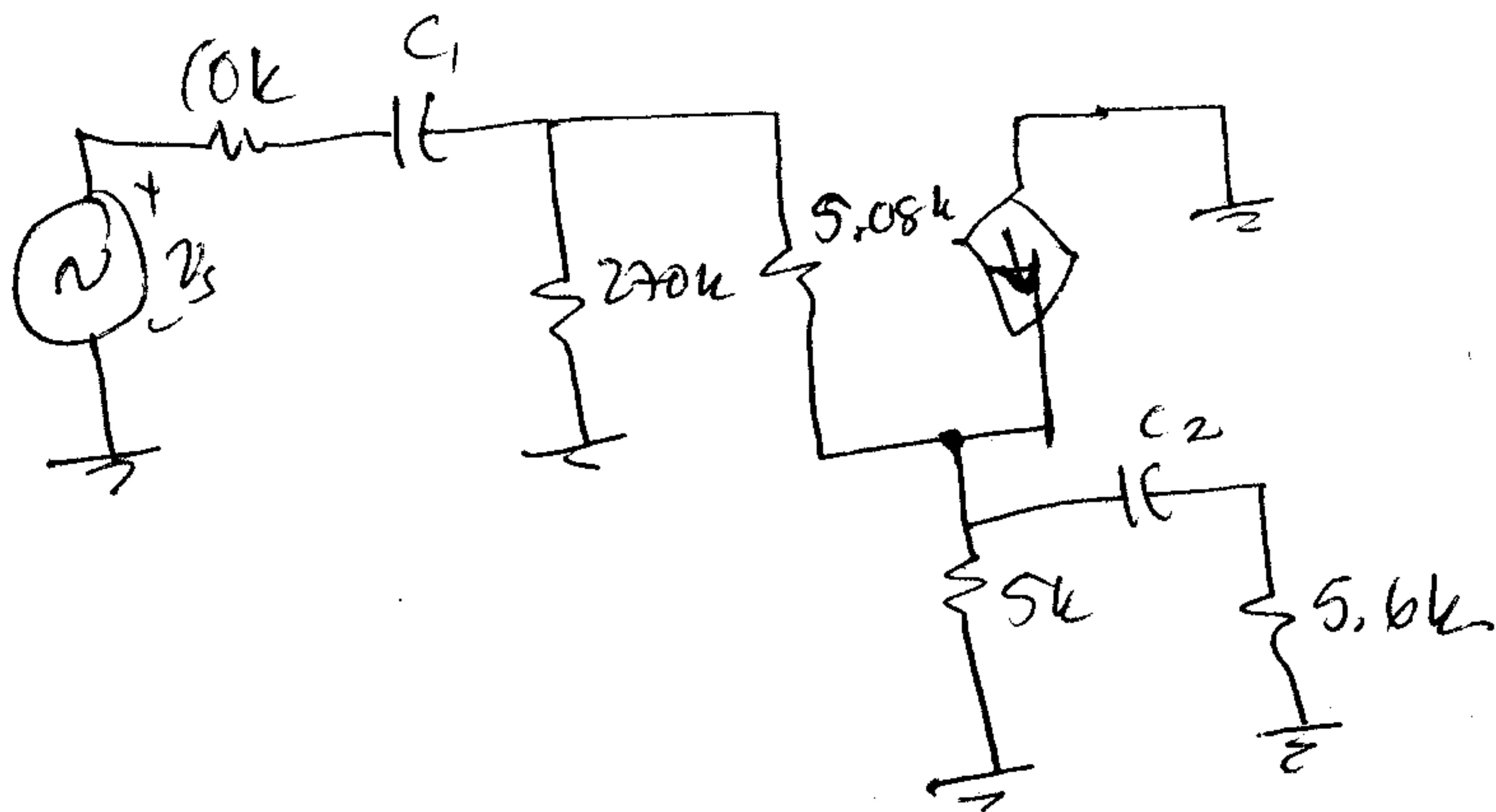
$$r_\pi = \frac{\beta}{g_m} = \frac{120}{23.58} = 5.08 \text{ k}\Omega$$



C_2 has smaller Thevenin resistance; hence, its pole frequency should be larger for a small cap. value.

$$\left. \begin{array}{l} f_2 = 9 \text{ Hz} \\ f_1 = 1 \text{ Hz} \end{array} \right\} f_c \cong f_1 + f_2 = 10 \text{ Hz}$$

C_1 is short cut when finding R_{th2}

C_2 is open cut " " R_{th1}

(C_2 open)

$$R_{th1} = 10 + 270 \parallel [5.08 + 121 \times 5] = 197.16 \text{ k}\Omega$$

$$R_{th2} = 5.6 + 5 \parallel \frac{(10 \parallel 270) + 5.08}{\beta + 1} = 5.6 + 0.118 = 5.718 \text{ k}\Omega \text{ (} C_1 \text{ short)}$$

$$C_1 = \frac{1}{2\pi f_1 R_{th1}} = \frac{1}{2\pi \times 1 \times 197160} = 0.8 \times 10^{-6} \text{ F}$$


$$C_2 = \frac{1}{2\pi f_2 R_{th2}} = \frac{1}{2\pi \times 9 \times 5718} = 3.09 \times 10^{-6} \text{ F}$$

Q: 58

3) Using Miller's theorem, find the high 3-dB cutoff frequency for the amplifier given below.

Assume $I_C = 0.3 \text{ mA}$.

$$f_H = 1.78 \text{ MHz}$$

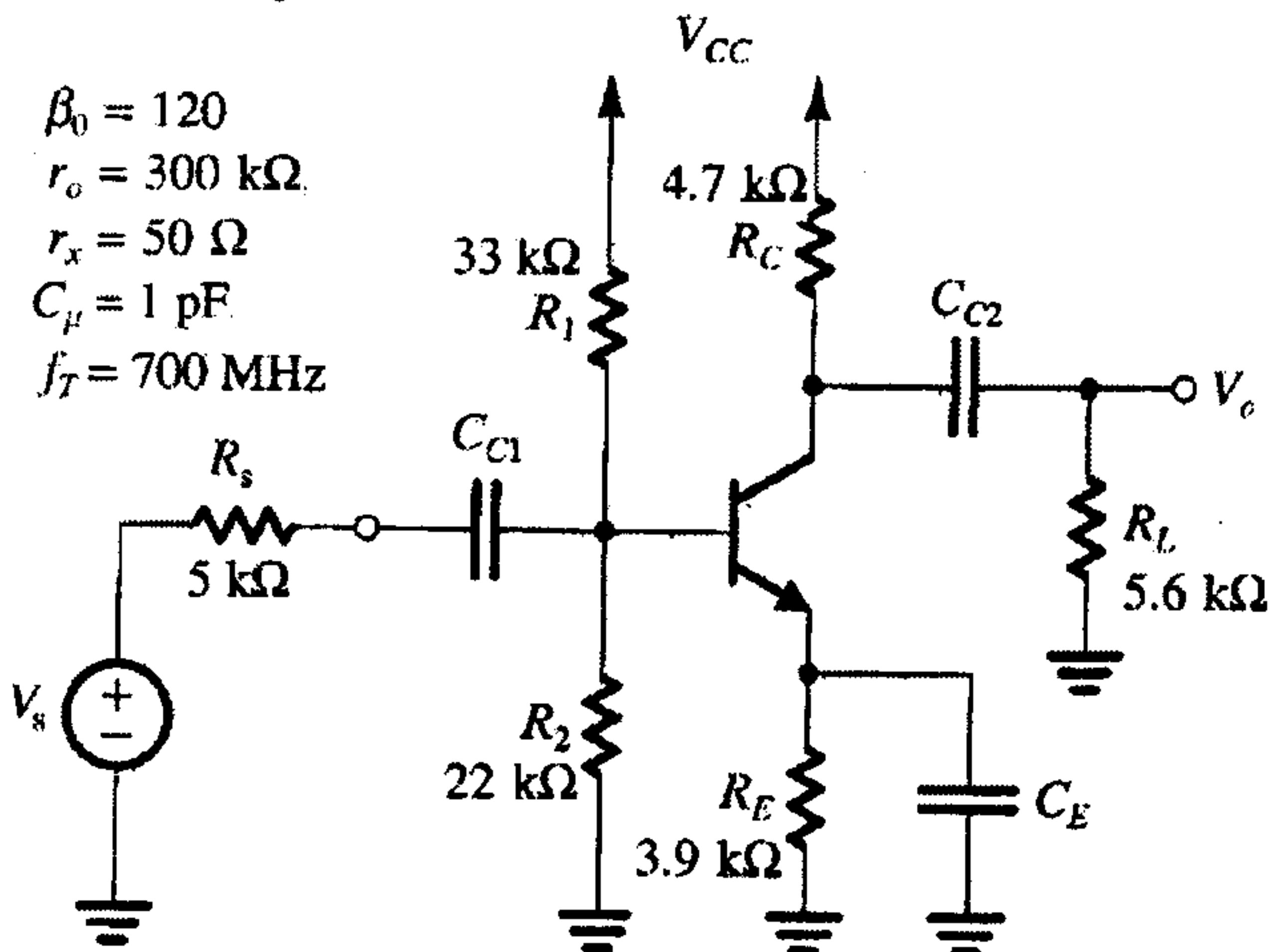


$$I_C = 0.3 \text{ mA}, \quad g_m = \frac{0.3}{0.025} = 12 \text{ mA/V}$$

$$r_{\pi} = \frac{\beta}{g_m} = \frac{120}{12} = 10 \text{ k}\Omega$$

$$C_{\pi} = \frac{g_m}{2\pi f_T} - C_{\mu} = \frac{12 \times 10^{-3}}{2\pi \times 700 \times 10^6} - 1 \times 10^{-12} = 1.73 \text{ pF}$$

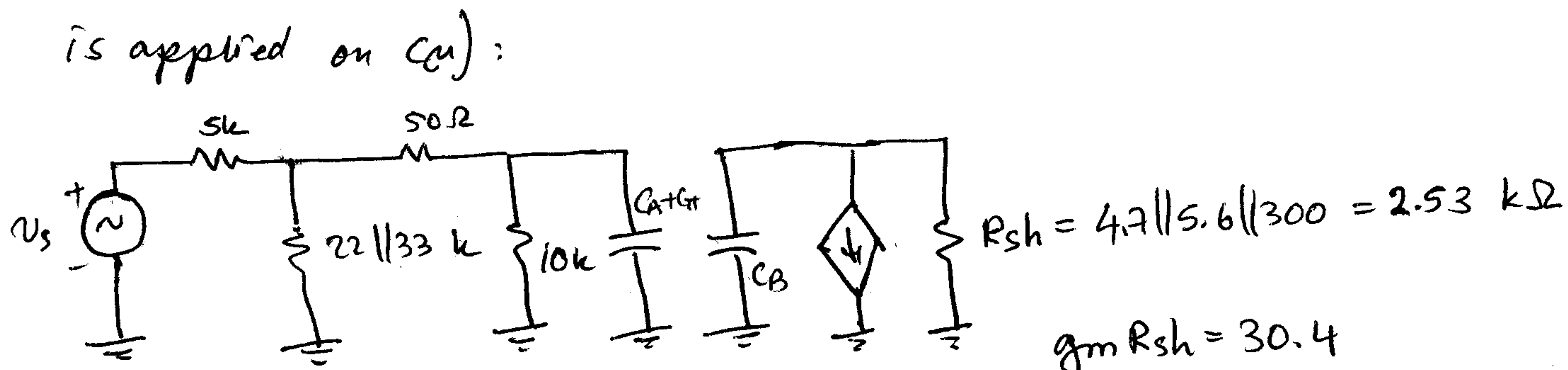Small signal equivalent circuit (Miller's Theorem is applied on C_{μ}):



$$C_A = C_{\mu}(1 + g_m R_{sh}) = 1 \text{ pF}(30.4 + 1) = 31.4 \text{ pF}$$

$$C_B = C_{\mu}\left(1 + \frac{1}{g_m R_{sh}}\right) \approx 1 \text{ pF}$$

There are two HF poles:

$$\omega_A = \frac{1}{(C_A + C_{\pi}) R_{thA}}, \quad \omega_B = \frac{1}{C_B R_{thB}}$$

$$R_{thA} = 10 \text{ k} || [50 + 5 \text{ k} || 22 \text{ k} || 33 \text{ k}] = 2.68 \text{ k}\Omega$$

$$R_{thB} = R_{sh} = 2.53 \text{ k}\Omega$$

$$\omega_A = \frac{1}{(31.4 + 1.73) \times 10^{-12} \times 2680} = 11.23 \times 10^6 \text{ rad/s}$$

$$\omega_B = \frac{1}{1 \times 10^{-12} \times 2530} = 395 \times 10^6 \text{ rad/s}$$

$$\omega_H = \frac{1}{\frac{1}{\omega_A} + \frac{1}{\omega_B}} \approx \omega_A \quad \text{for } \omega_B \gg \omega_A$$

$$f_H = \frac{\omega_H}{2\pi} = \frac{11.23 \times 10^6}{2\pi} = 1.78 \text{ MHz}$$