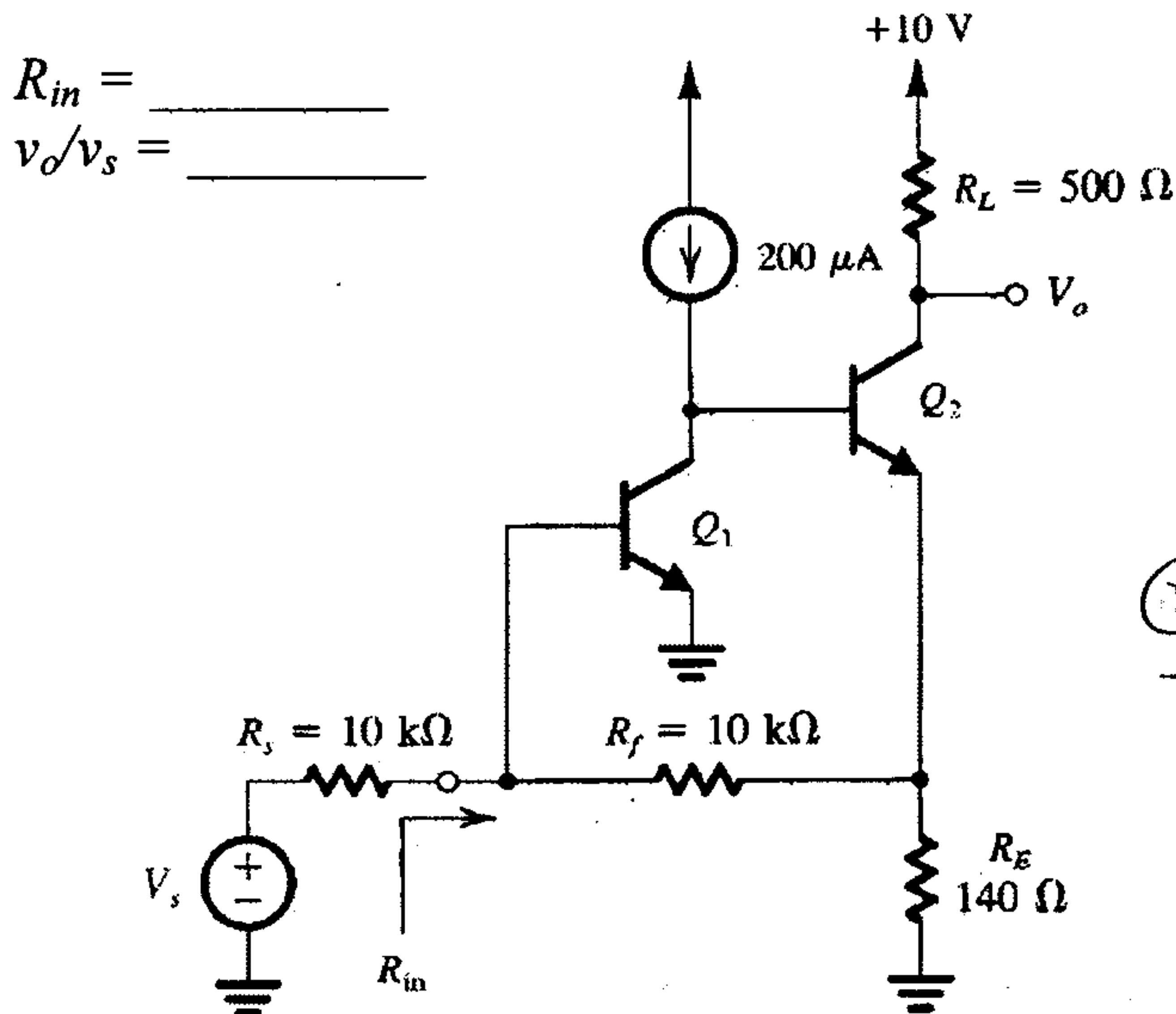


I have neither given nor received unauthorized help with this exam, nor do I have reason that anybody else has.

ID no: ERKAYA Name: SOLUTIONS Signature: _____


1) For the amplifier circuit below, assume that V_s has a zero dc component and that I_{B1} is much smaller than the current in R_f . The dc emitter currents of Q_1 and Q_2 can be shown to be $I_{E1} = 0.101$ mA and $I_{E2} = 10.1$ mA. Let the BJTs have $\beta = 100$. Find small signal voltage gain v_o/v_s and R_{in} .



Small Signal Eq Ckt

$$g_{m1} = \frac{0.1}{0.025} = 4 \text{ mA/V} \quad r_{\pi1} = \frac{100}{4} = 25 \text{ k}\Omega$$
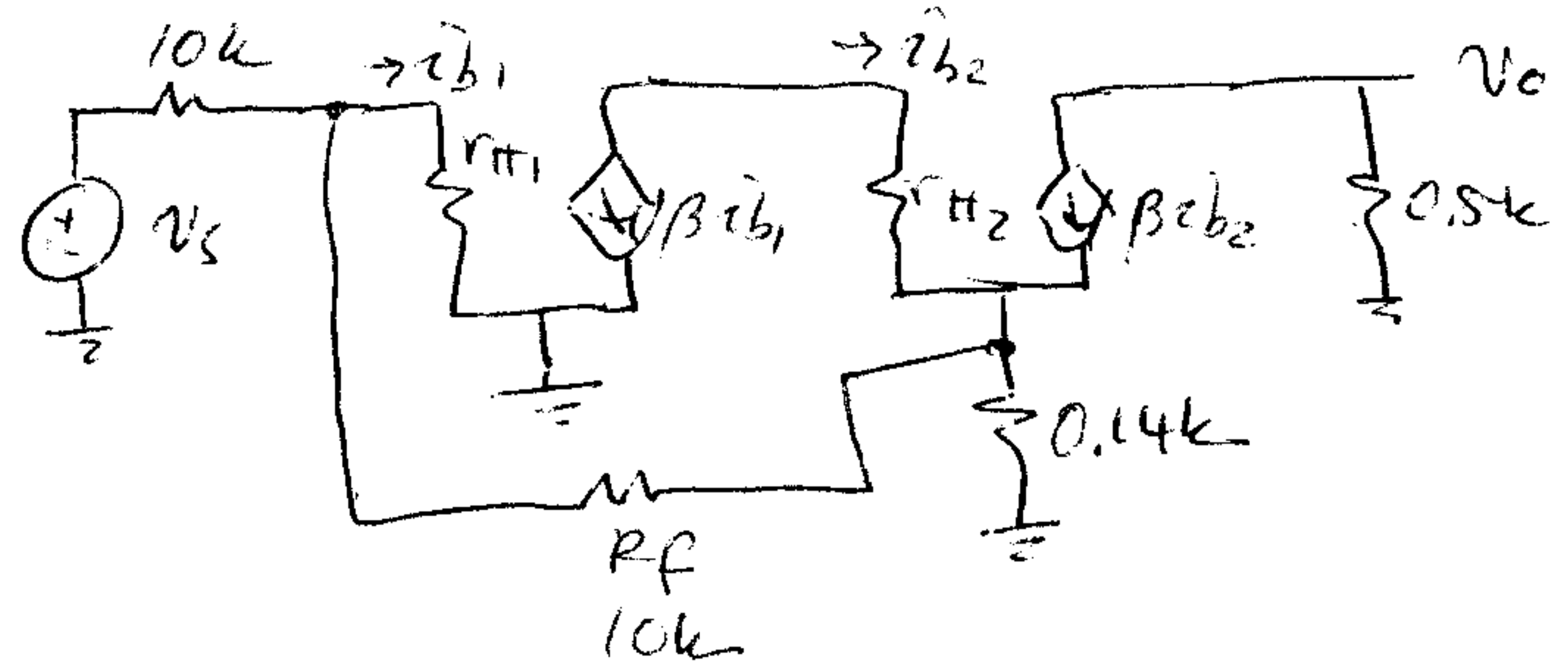
$$g_{m2} = \frac{10}{0.025} = 400 \text{ mA/V}, \quad r_{\pi2} = \frac{100}{400} = 0.25 \text{ k}\Omega$$



Apply miller's theorem on R_f

$$R_A = \frac{R_f}{1 - \frac{v_x}{v_i}}, \quad R_B = \frac{R_f}{1 - \frac{v_i}{v_x}} \approx R_B$$

$$\frac{v_x}{v_i} = \frac{v_x}{v_y} \cdot \frac{v_y}{v_i}, \quad \frac{v_x}{v_y} = \frac{(\beta+1)(R_B \parallel R_E)}{r_{\pi2} + (\beta+1)(R_B \parallel R_E)} \approx \frac{101 \times 0.14}{0.25 + 101 \times 0.14} = 0.9826$$

$$\frac{v_y}{v_i} = -g_m (r_{\pi2} + (\beta+1)(R_B \parallel R_E)) = -400 \times (0.25 + 101 \times 0.14) = -5756$$

$$R_A = \frac{10 \text{ k}\Omega}{1 + 5756} = 1.737 \text{ }\Omega$$

$$r_{in} = R_A \parallel r_{\pi1} = 1.737 \parallel 25 \text{ k}\Omega \approx 1.737 \text{ }\Omega$$


$$\frac{v_o}{v_y} = \frac{-\beta R_L}{r_{\pi2} + (\beta+1)(R_B \parallel R_E)} = \frac{-50}{14.39} = -3.47$$

$$\frac{v_i}{v_s} = \frac{r_{in}}{R_s + r_{in}} = \frac{1.737}{10000 + 1.737} \approx 1.737 \times 10^{-4}$$

$$\frac{v_o}{v_s} = \frac{v_o}{v_y} \cdot \frac{v_y}{v_i} \cdot \frac{v_i}{v_s} = (-3.47)(-5756)(1.737 \times 10^{-4}) = 3.469$$

2) Find the oscillation frequency and oscillation condition for the circuit given below.

Q: 53

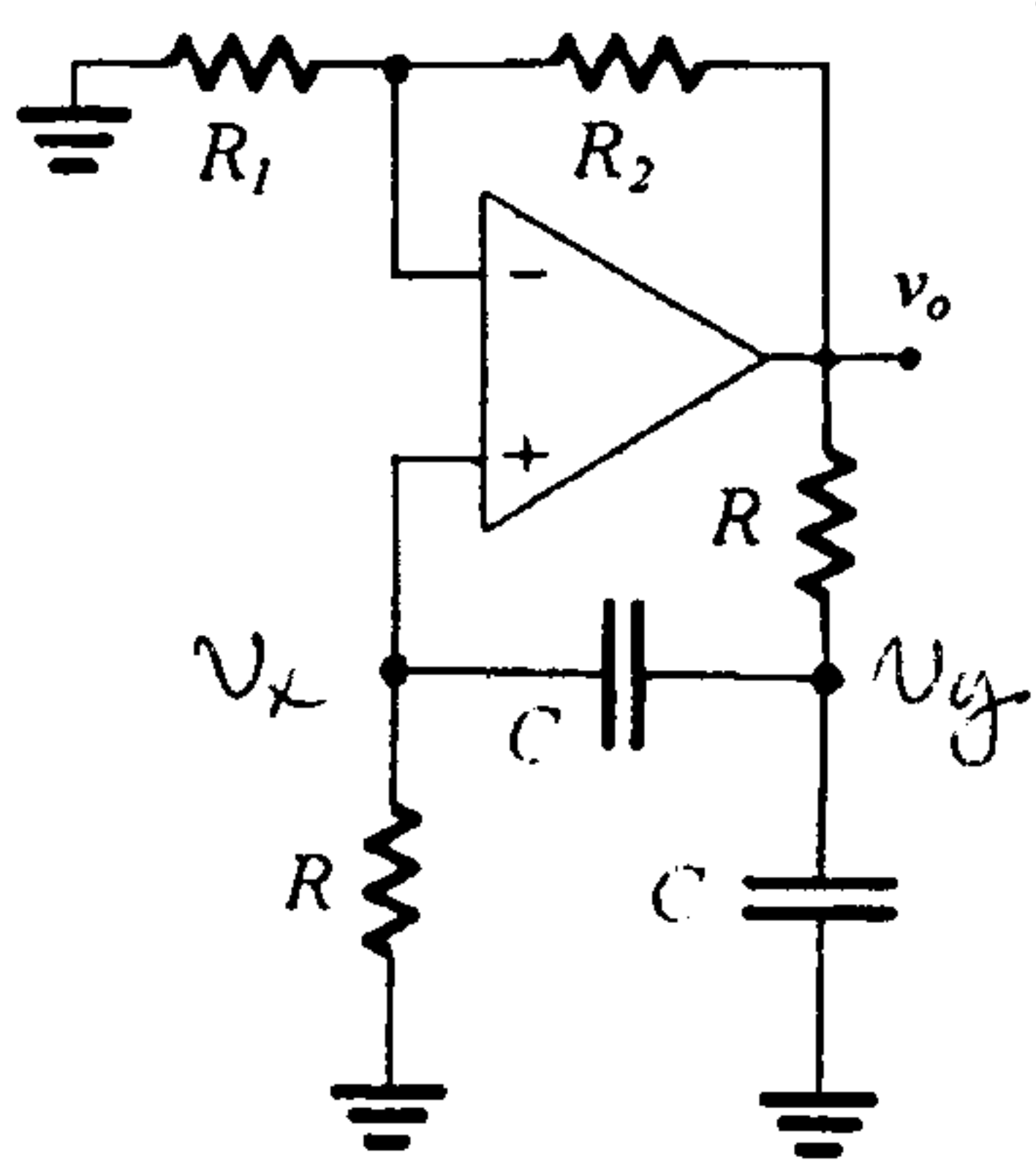

$$V_o = V_x \left(\frac{R_1 + R_2}{R_1} \right)$$

$$\omega_o = \frac{1}{CR}$$

$$\text{condition: } \frac{R_2}{R_1} = 2$$

$$\frac{V_x}{R} = \frac{V_y}{R + \frac{1}{j\omega C}}$$

$$\frac{V_o}{R \left(\frac{R_1 + R_2}{R_1} \right)} = \frac{V_y}{R + \frac{1}{j\omega C}}, \quad V_o = V_y \frac{R \left(\frac{R_1 + R_2}{R_1} \right)}{\left(R + \frac{1}{j\omega C} \right)}$$

$$\frac{V_o - V_y}{R} = j\omega C V_y + V_y \frac{1}{R + \frac{1}{j\omega C}}$$

$$\frac{V_y \left(\frac{R_1 + R_2}{R_1} \right)}{R + \frac{1}{j\omega C}} - \frac{V_y}{R} = j\omega C V_y + V_y \frac{1}{R + \frac{1}{j\omega C}}$$

$$\frac{R_1 + R_2}{R_1} - \frac{1}{R} \left(R + \frac{1}{j\omega C} \right) = 1 + j\omega C \left(R + \frac{1}{j\omega C} \right)$$

$$1 + \frac{R_2}{R_1} - 1 - \frac{1}{j\omega CR} = 1 + j\omega CR + 1$$

$$\frac{R_2}{R_1} - 2 = j\omega CR + \frac{1}{j\omega CR}$$

$$\boxed{\frac{R_2}{R_1} = 2}$$

$$j\omega CR - \frac{j}{\omega CR} = 0$$


$$\omega CR = \frac{1}{\omega CR}$$

$$\omega^2 C^2 R^2 = 1$$

$$\boxed{\omega = \frac{1}{CR}}$$

10:02

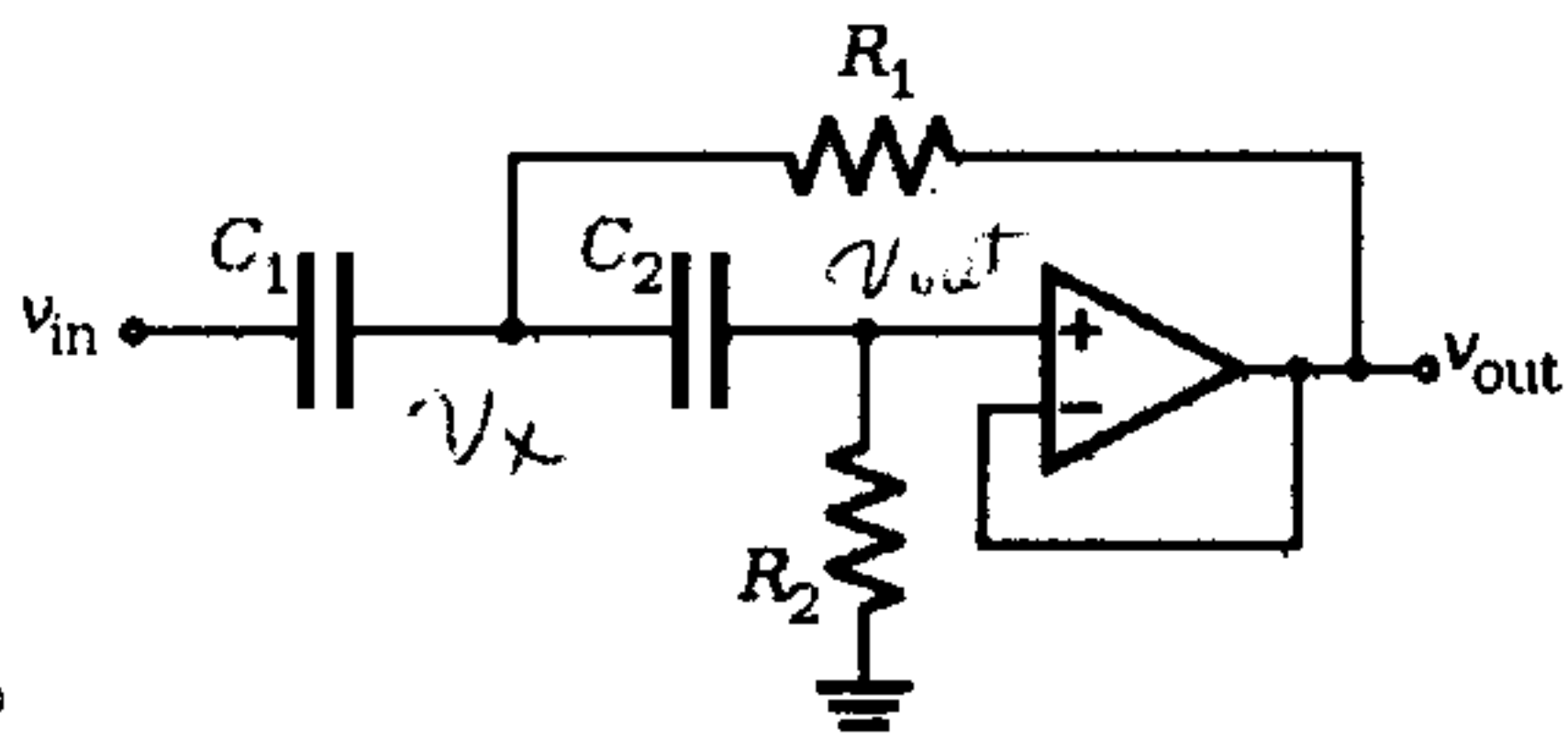3) Find the transfer function of the circuit given below. Indicate what kind of a filter it is (i.e., high-pass, low-pass, band-pass). Put the transfer function in the form as follows: $(as^2 + bs + c)/(s^2 + s\omega_o/Q + \omega_o^2)$.



Q:40

$$a = 1$$

$$b = 0$$

$$c = 0$$

$$\omega_o = \sqrt{\frac{1}{C_1 R_2 R_2 C_2}}$$

$$\omega_o/Q = \frac{1}{R_2} \left(\frac{1}{C_1} + \frac{1}{C_2} \right)$$

$$\text{type} = \text{HP}$$

$$\frac{v_{in} - v_x}{\frac{1}{sC_1}} = \frac{v_x - v_{out}}{R_1} + \frac{v_x - v_{out}}{\frac{1}{sC_2}}$$

$$v_x = \left(R_2 + \frac{1}{sC_2} \right) \frac{v_{out}}{R_2}$$

$$\frac{v_x - v_{out}}{\frac{1}{sC_2}} = \frac{v_{out}}{R_2}$$

$$sC_1(v_{in} - v_x) = \frac{v_x - v_{out}}{R_1} + \frac{v_{out}}{R_2}$$

$$sC_1 \left(v_{in} - \left(1 + \frac{1}{sC_2 R_2} \right) v_{out} \right) = \frac{\left(1 + \frac{1}{sC_2 R_2} \right) v_{out} - v_{out}}{R_1} + \frac{v_{out}}{R_2}$$

$$sC_1 v_{in} - sC_1 v_{out} - \frac{C_1}{C_2 R_2} v_{out} = \frac{1}{sC_2 R_2 R_1} v_{out} + \frac{v_{out}}{R_2}$$

$$sC_1 v_{in} = v_{out} \left(sC_1 + \frac{C_1}{C_2} \frac{1}{R_2} + \frac{1}{sC_2 R_2 R_1} + \frac{1}{R_2} \right)$$

$$\frac{v_{out}}{v_{in}} = \frac{sC_1}{sC_1 + \left(\frac{C_1}{C_2} \frac{1}{R_2} + \frac{1}{R_2} \right) + \frac{1}{sC_2 R_2 R_1}} = \frac{s^2 C_1}{s^2 C_1 + s \left(\frac{1}{R_2} \left(1 + \frac{C_1}{C_2} \right) \right) + \frac{1}{R_1}}$$

$$s^2$$

$$= \frac{s^2}{s^2 + s \frac{1}{R_2} \left(\frac{1}{C_1} + \frac{1}{C_2} \right) + \frac{1}{C_1 C_2 R_1 R_2}}$$


Q:50

4) A power transistor is specified to have a maximum junction temperature of 130°C . When operated at this temperature with a heat sink, the case temperature is found to be 90°C . The case is attached to a heat sink with a bond having a thermal resistance $\theta_{CS} = 0.5^\circ\text{C/W}$ and the thermal resistance of the heat sink $\theta_{SA} = 0.1^\circ\text{C/W}$. If the ambient temperature is 30°C what is the power being dissipated in the device? What is its thermal resistance θ_{JC} from junction to case?

$$P_D = \underline{100\text{ W}}$$

$$\theta_{JC} = \underline{0.4^\circ\text{C/W}}$$

Q=50

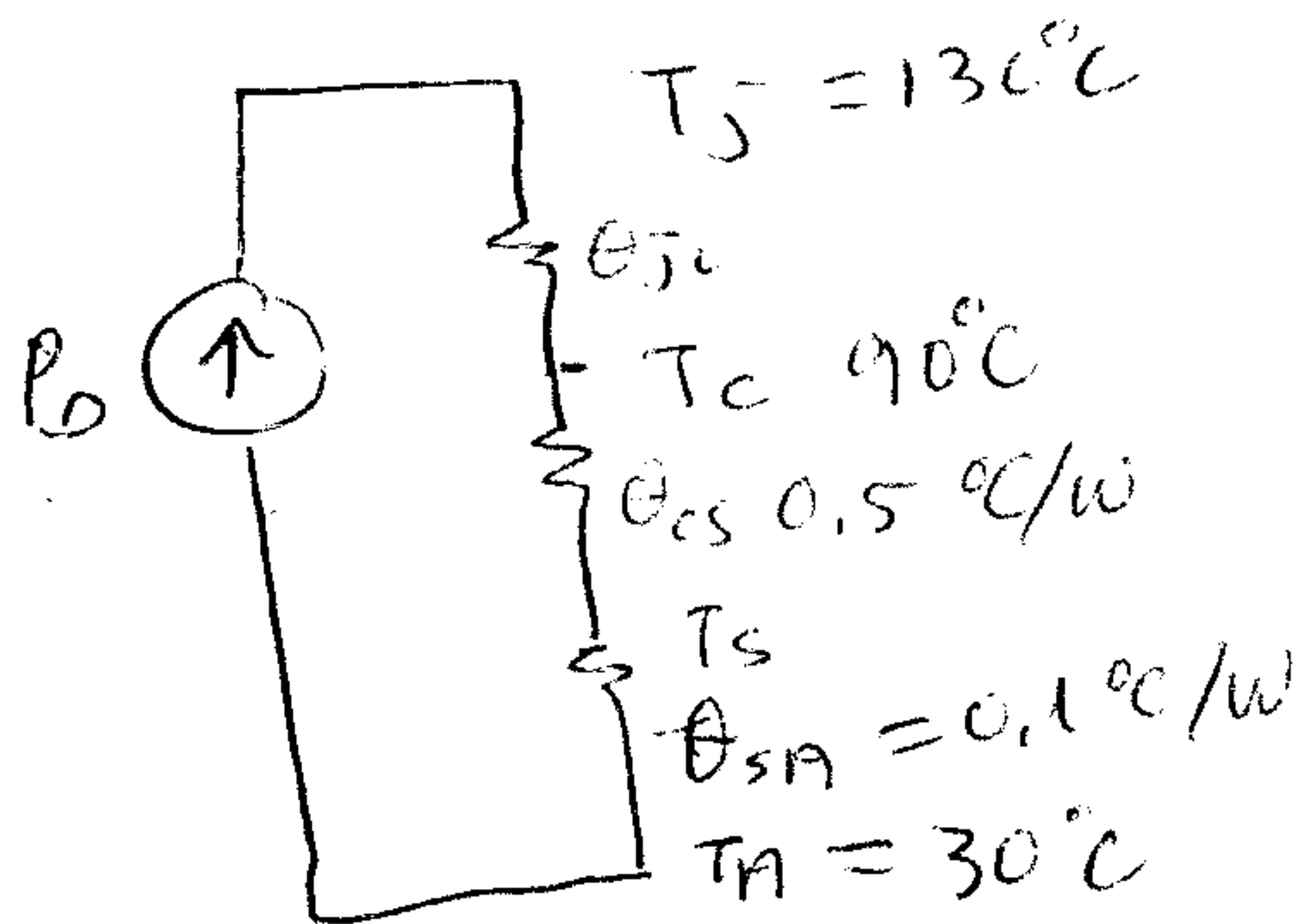

$$T_C - T_A = P_D (\theta_{CS} + \theta_{SA})$$

$$\frac{T_C - T_A}{(\theta_{CS} + \theta_{SA})} = P_D$$

$$\frac{90^\circ - 30^\circ}{0.5 + 0.1} = \frac{60^\circ}{0.6^\circ\text{C/W}} = 100\text{ W} = P_D$$

$$\theta_{JC} = \frac{T_J - T_C}{P_D} = \frac{130^\circ - 90^\circ}{100\text{ W}} = \frac{40^\circ}{100\text{ W}} = 0.4^\circ\text{C/W}$$

Q=53

$$16 + 9 + 10 + 3 = 38\text{ min} \rightarrow 11\frac{1}{4}\text{ mil.}$$