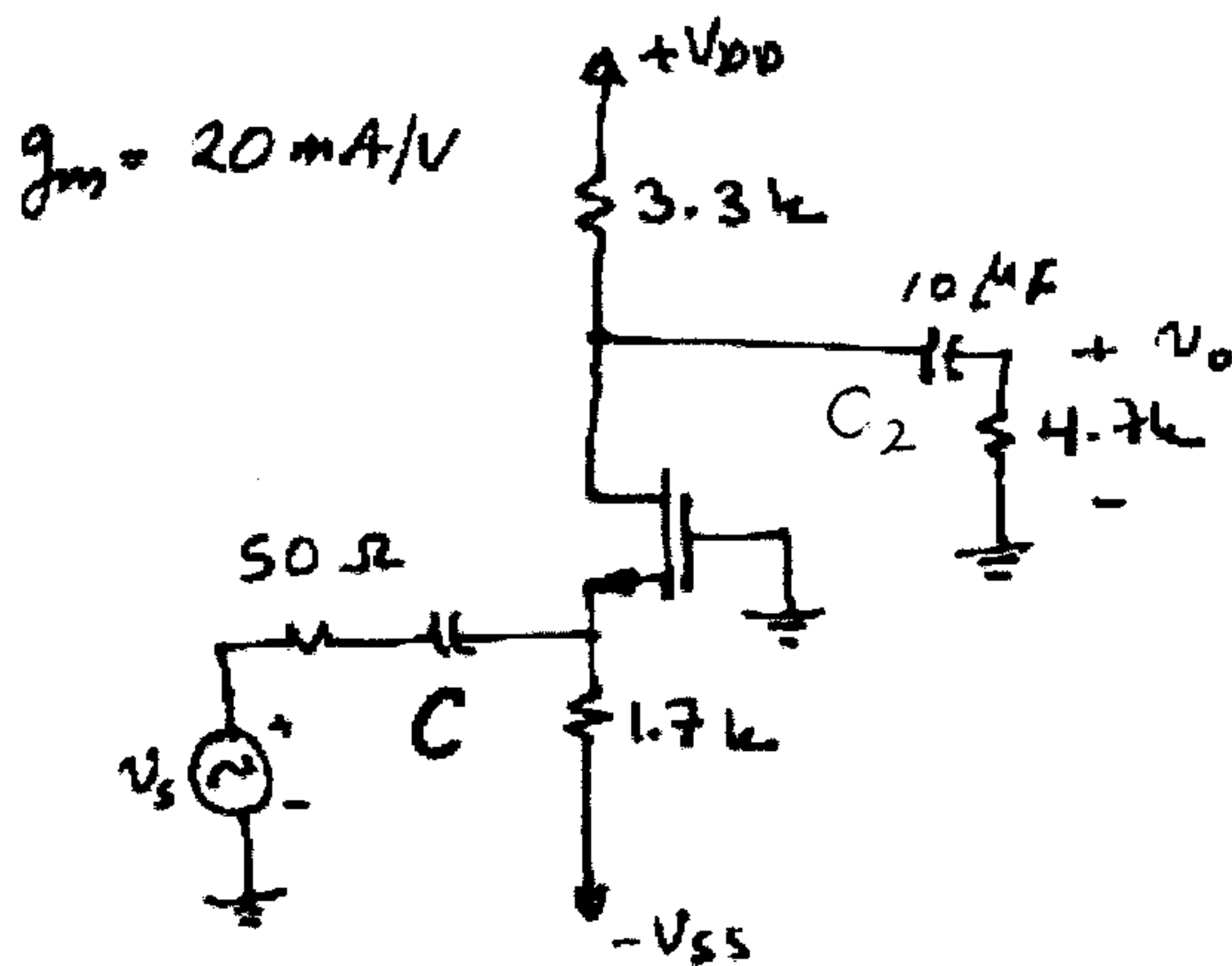


ID number: _____ Name: _____ Signature: _____

- 40 pts 1) Find the minimum value of C in the circuit below such that the low 3 dB cutoff frequency of the amplifier is equal or below 20 Hz.

5:34



$C = C_1$ pole frequencies

$$f_1 = \frac{1}{2\pi C_1 R_{th1}}$$

$$R_{th1} = 50\Omega + \left(\frac{1}{g_m} \parallel 1700\Omega\right)$$

$$f_2 = \frac{1}{2\pi C_2 R_{th2}}$$

$$R_{th2} = 3.3k + 4.7k = 8k$$

$$f_c \approx f_1 + f_2 \leq 20 \text{ Hz}$$

$$R_{th1} = 50 + \left(\frac{1}{0.02} \parallel 1700\right) = 50 + 50 \parallel 1700 = 98.57\Omega$$

$$f_2 = \frac{1}{2\pi (10 \times 10^{-6}) \times 8000} = 1.989 \text{ Hz}$$


$$f_1 \leq 20 - 1.989 \approx 18 \text{ Hz}$$

$$C = C_1 \geq \frac{1}{2\pi f_1 R_{th1}} = \frac{1}{2\pi \times 18 \times 98.57} = 8.96 \times 10^{-5} \text{ F} = 89.6 \mu\text{F}$$

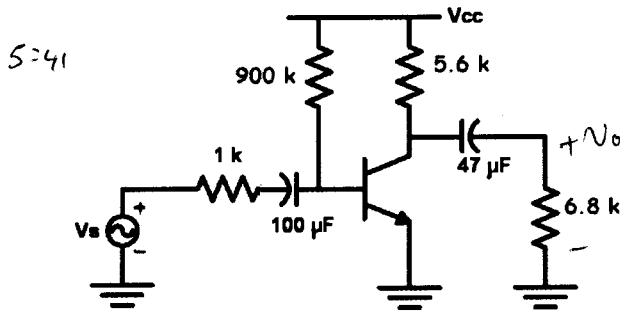5:41

40 pts 2) Using Miller's theorem, find the high 3dB cutoff frequency of the amplifier given below.

Assume $\beta = 250$, $I_C = 1.25$ mA, $C_\mu = 1.5$ pF, $f_T = 400$ MHz, $r_x = 100$ ohms, $r_o = 80$ k




$$g_m = \frac{1.25}{0.025} = 50 \text{ mA/V}$$

$$f_H = \text{_____ Hz}$$

$$r_\pi = \frac{\beta}{g_m} = \frac{250}{50} = 5 \text{ k}\Omega$$

$$C_\pi = \frac{g_m}{2\pi f_T} - C_\mu = \frac{50 \times 10^3}{2\pi \times 400 \times 10^6} - 1.5 \times 10^{-12} = 18.39 \times 10^{-12} \text{ F}$$

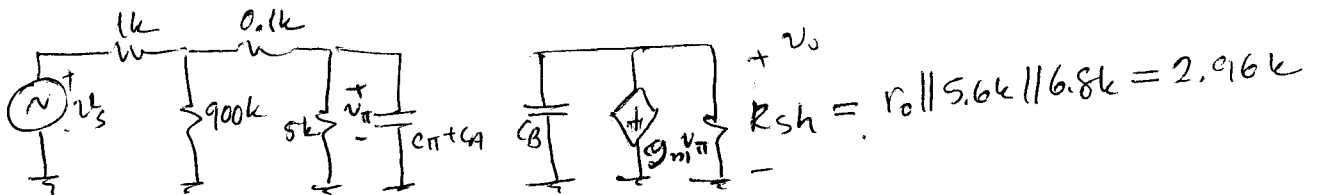HF Small signal eq. circuit - Miller's Theorem applied on C_μ :



$$C_A = C_\mu (1 + g_m R_{sh}) = 1.5 \times 10^{-12} (1 + 50 \times 2.96) \approx 223 \times 10^{-12} \text{ F}$$

$$C_B \approx C_\mu = 1.5 \text{ pF}$$

$$f_A = \frac{1}{2\pi (C_A + C_B) R_{thA}}, \quad R_{thA} = 5 \text{ k} \parallel [0.1 \text{ k} + 1 \text{ k} \parallel 900 \text{ k}] = 0.90 \text{ k}$$

$$f_H = \frac{1}{2\pi (223 + 18.39) \times 10^{-12} \times 900} = 732.6 \text{ kHz}$$

$$f_B = \frac{1}{2\pi C_B R_{sh}} = \frac{1}{2\pi \times 1.5 \times 10^{-12} \times 2960} = 35.8 \text{ MHz}$$

$$f_H = \frac{1}{\frac{1}{f_A} + \frac{1}{f_B}} \approx 730 \text{ kHz}$$

20 pts 3) What are the effects of negative feedback on an amplifier circuit?

- 1- Gain stability. Dependence on active device parameters is reduced by neg. feedback
2. S/N ratio is improved by negative fb
3. Bandwidth is increased by a factor of $(1 - \beta A)$
4. Input resistance increased by series fb
decreased by shunt fb
5. Output resistance decreased by voltage fb
increased by current fb
6. if $1 - \beta A = 1 \rightarrow$ oscillation may occur.