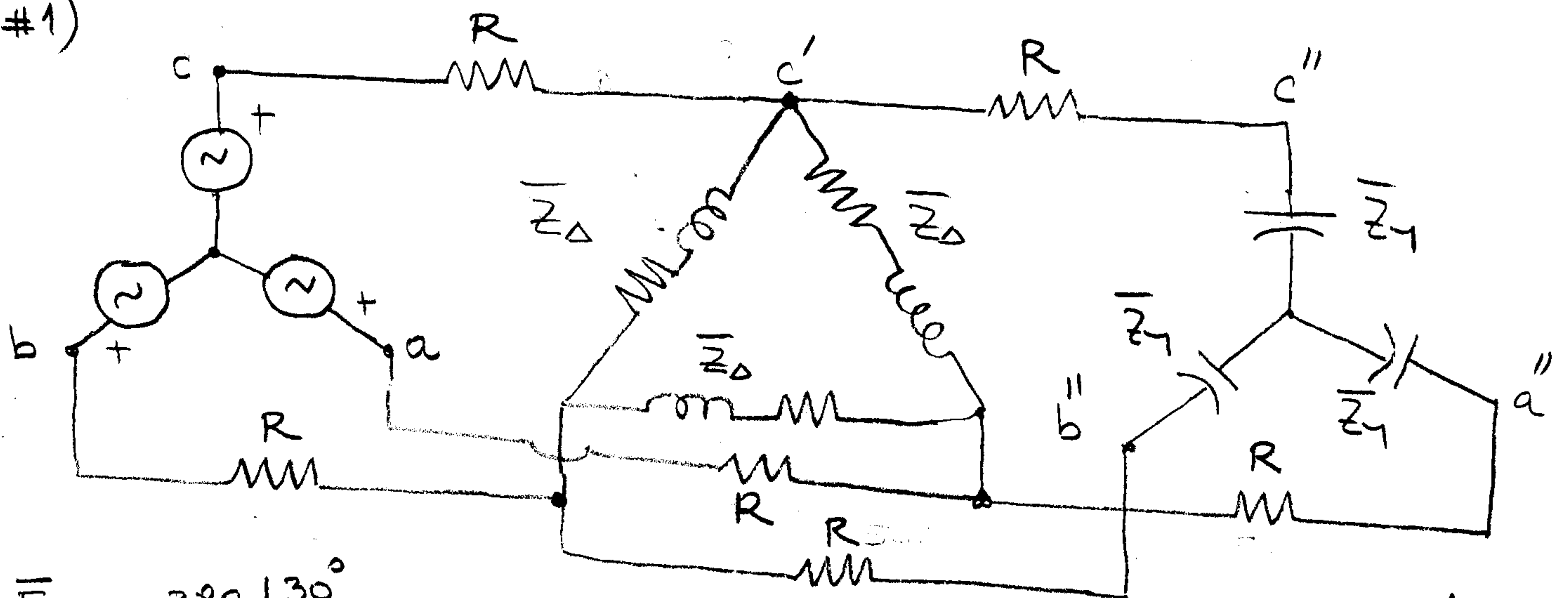


# PRINCIPLES OF ENERGY CONVERSION FINAL EXAM

Dr. Salih FADIL

June 12, 2009

#1)



$$\bar{E}_{ab} = 380 \angle 30^\circ, R = 5 \Omega, \bar{Z}_\Delta = 15 \angle 30^\circ \Omega$$

$$\bar{Z}_Y = -j \frac{1}{5} \Omega$$

Three phase system given in the figure is balanced and its phase sequence is abc.

a) Calculate three phase active and reactive power delivered by the ~~source~~ source.

b) Calculate


- three phase active power absorbed by the series resistances
- three phase active and reactive powers, absorbed by  $\Delta$ -connected load and Y-connected loads.
- Is conservation of active and reactive power satisfied in this circuit.

#2) A three phase load draws 30 kW active power from 3 kV<sub>LL</sub> system at 0.75 lagging power factor. A capacitor bank, which is connected as  $\Delta$ , is connected across the load to make its new power factor unity.

→ see back!

- Calculate the capacity value of the capacitors in each branch of the capacitor bank.
- If the capacitors are connected as  $Y$ , what is the new power factor seen across the capacitor bank?
- The load is fed through a three-phase line whose series impedance is  $5 + j10 \Omega$ . If phase a to neutral voltage across the load is  $\frac{3000}{\sqrt{3}} \angle 0^\circ$  V and kept constant. Calculate the total active power loss on the line before and after the capacitor bank ( $\Delta$ -connected) connection.

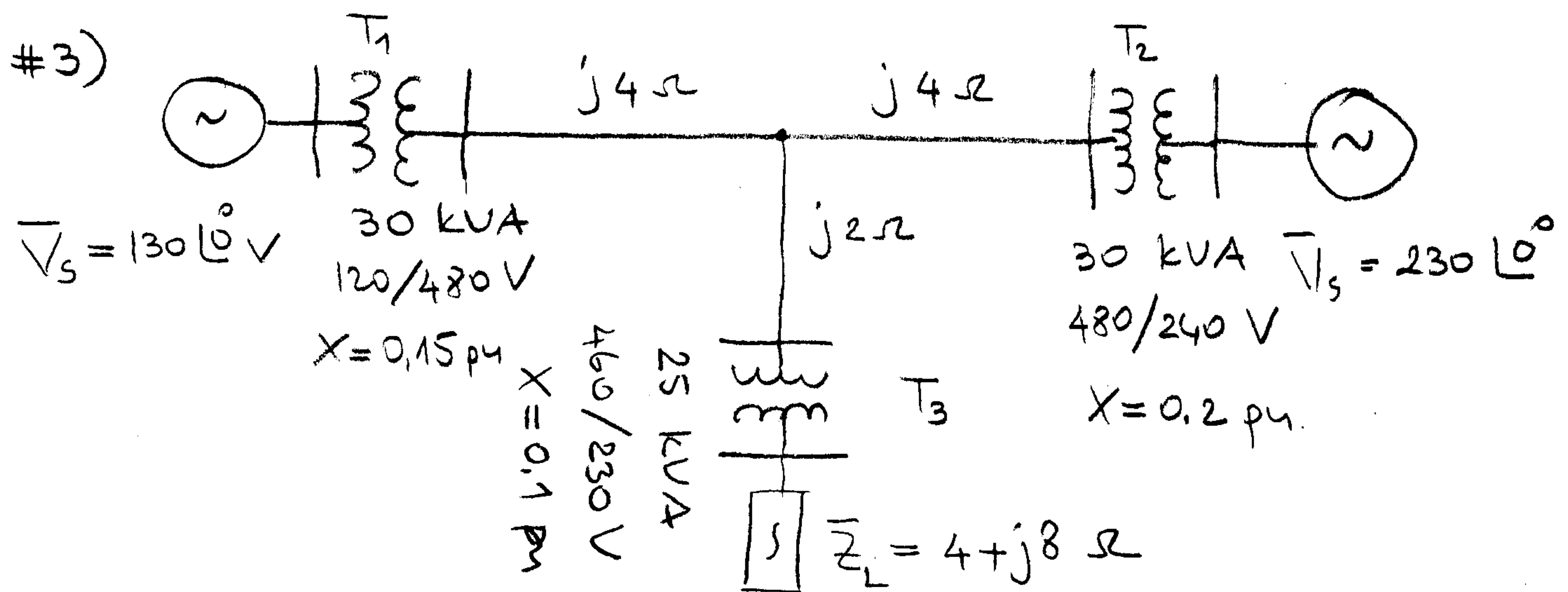Assume that voltage across the load is kept constant at 3 kV<sub>LL</sub> in part a and b. Frequency of the applied voltage is 50 Hz.




Consider the single phase power system given in the above figure. Take  $S_{base} = 30$  kVA, and voltage base in the load region 240 V.

- Draw the pu equivalent circuit of the system
- Find the complex power delivered by the source located on the left hand side.

Dr. Salih FADIL

June 12, 2009

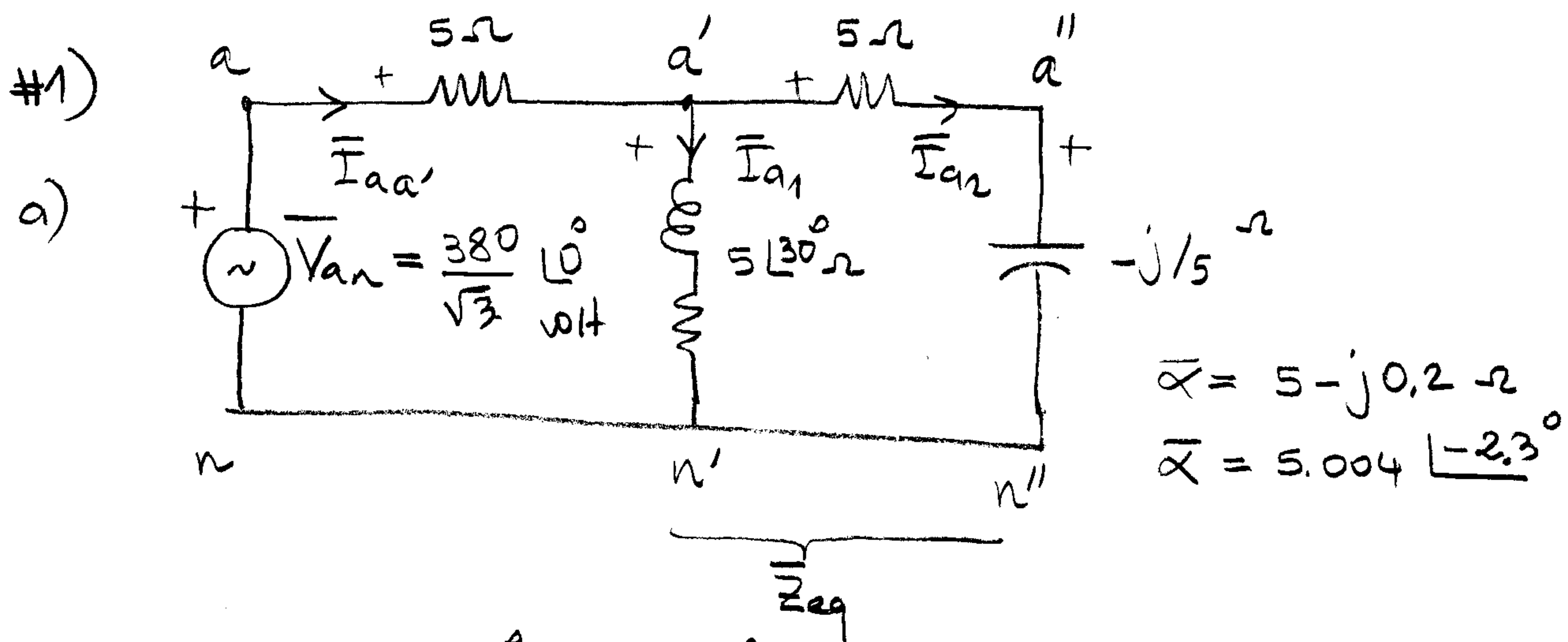

$$\bar{Z}_{eq} = \frac{5.004 \angle -2.3^\circ \times 5 \angle 30^\circ}{5 - j0.2 + 4.33 + j2.5} = \frac{25.02 \angle 27.7^\circ}{9.609 \angle 13.8^\circ} = 2.6038 \angle 13.9^\circ$$

$$= 2.527 + j0.625$$

$$\bar{I}_{aa'} = \frac{(\frac{380}{\sqrt{3}}) \angle 0^\circ}{7.527 + j0.625} = \frac{(\frac{380}{\sqrt{3}}) \angle 0^\circ}{7.553 \angle 4.746^\circ} = 29.04 \angle -4.746^\circ \text{ A.}$$

$$\bar{S}_{s,3\phi} = 3 \cdot \frac{380}{\sqrt{3}} \cdot 29.04 \angle +4.746^\circ = 19113.5 \angle 4.746^\circ$$

$$= 19047.99 + j1581.4 \text{ VA}$$

$$P_{s,3\phi} = 19048 \text{ W delivered}$$

$$Q_{s,3\phi} = 1581 \text{ VAR. delivered.}$$

b)

$$\bar{I}_{a1} = 29.04 \angle -4.746^\circ \cdot \frac{5.004 \angle -2.3^\circ}{9.609 \angle 13.8^\circ} = 15.123 \angle -20.846^\circ \text{ A.}$$

$$\bar{I}_{a2} = 29.04 \angle -4.746^\circ \cdot \frac{5 \angle 30^\circ}{9.609 \angle 13.8^\circ} = 15.11 \angle 11.454^\circ \text{ A.}$$

$$i) P_{R,3\phi} = 3 \left\{ (29.04)^2 5 + (15.11)^2 5 \right\} = 16074.50 \text{ W. absorbed} \quad (2)$$

$$ii) P_{\Delta} = 3 \left\{ (15.123)^2 (5 \cos 30^\circ) \right\} = 2971 \text{ W absorbed}$$

$$Q_{\Delta} = 3 \left\{ (15.123)^2 (5 \sin 30^\circ) \right\} = 1715.29 \text{ VAR. absorbed}$$

$$P_{\lambda} = 0 \text{ W}$$

$$Q_{\lambda} = -3 \left\{ (15.11)^2 (0.2) \right\} = -136.987 \text{ VAR absorbed}$$

$$= +136.987 \text{ VAR delivered}$$

iii)

$$P_{\text{absorb}}^{\text{total}} = 16074.50 + 2971 = 19045 \text{ W}$$


$$Q_{\text{absorb}}^{\text{total}} = 1715.29 - 136.987 = 1578.303 \text{ VAR}$$


$$P_{\text{delivered}}^{\text{total}} = 19048 \text{ W}$$

$$Q_{\text{delivered}}^{\text{total}} = 1581 \text{ VAR}$$

Conservation of active and reactive power (delivered power = absorbed power) is satisfied. The small discrepancies between the figures come from the rounding error in used arithmetic.

#2)

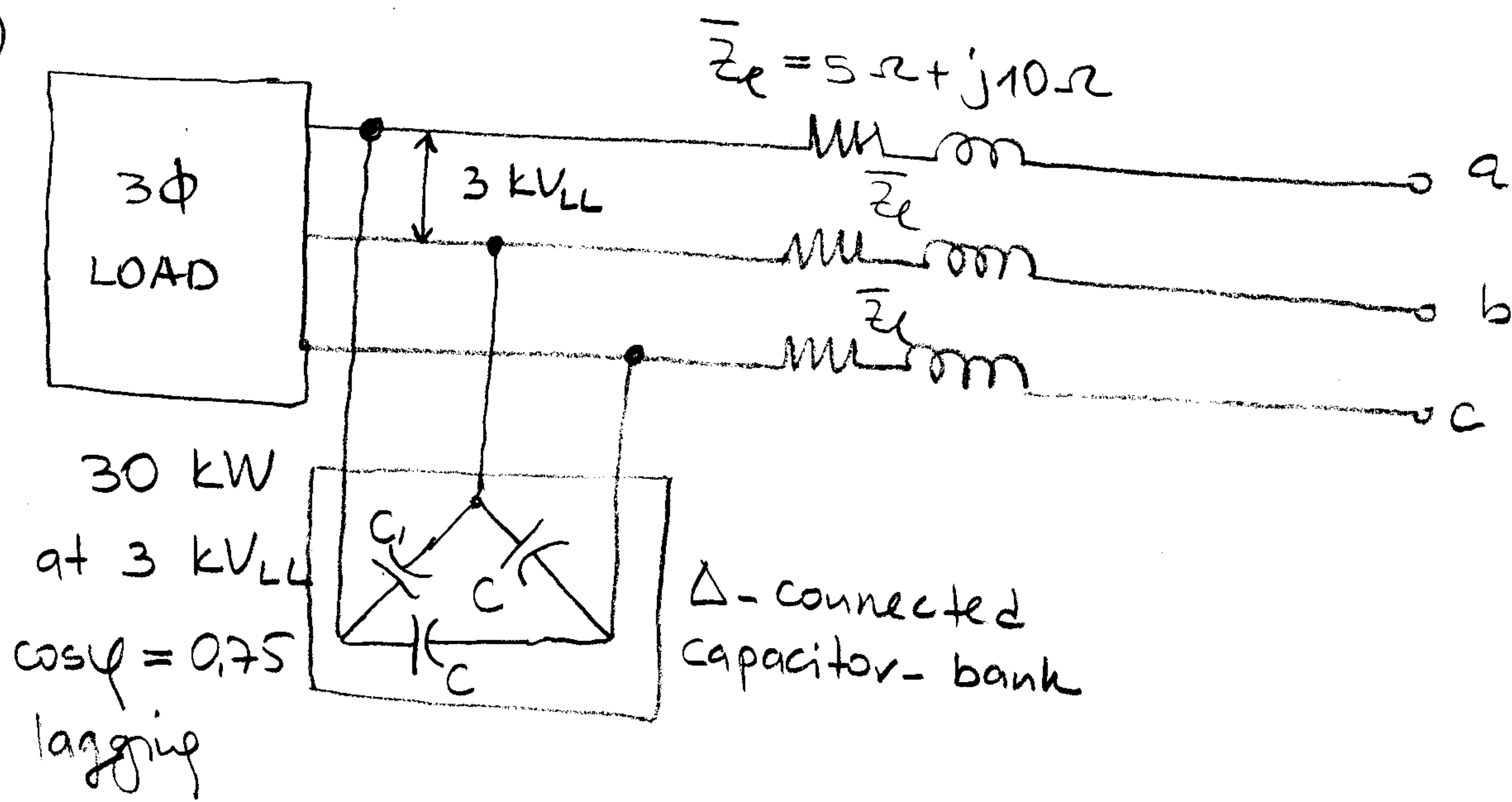

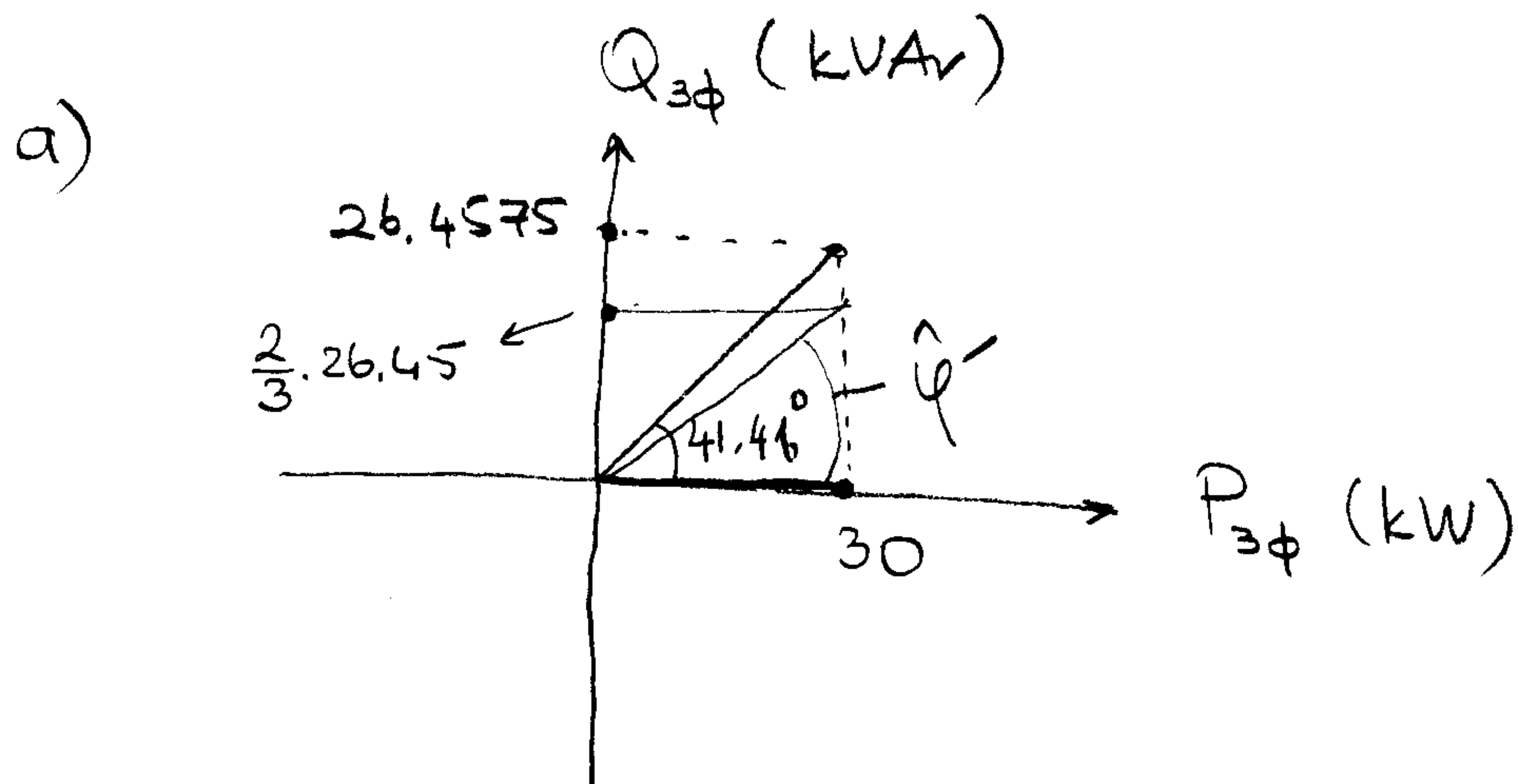

$$P_{3\phi} = 30 \text{ kW}$$

$$Q_{3\phi} = P_{3\phi} \tan \varphi$$

$$\varphi = \cos^{-1}(0.75) = 41.41^\circ$$

$$Q_{3\phi} = 30 \tan(41.41^\circ) = 26.4575 \text{ kVAr}$$

After connection of the capacitor bank ( $\Delta$ -connected), the new power factor will be unity (one), (i.e., the new power angle will be zero). Therefore;

$$\hat{\varphi} = 0 \rightarrow Q_{C,3\phi}^{\Delta} = 26.4575 \text{ kVAr} = 3 \omega C V_{LL}^2$$

$$26.4575 \cdot 10^3 = 3 (2\pi 50) C (3 \cdot 10^3)^2$$

$$C = \frac{26457.5}{3 (100\pi) 9 \cdot 10^6} = \underline{3.1191 \mu\text{F}}$$

b) If the capacitors are connected as  $Y$ ;

$$\begin{aligned} Q_{C,3\phi}^Y &= 3 (100\pi) 3.11914 \cdot 10^{-6} \left( \frac{3 \cdot 10^3}{\sqrt{3}} \right)^2 \text{ or} \\ &= \frac{26457.5}{3} = 8819.16 \text{ VAR.} \end{aligned}$$

$$\tan \hat{\varphi}' = \frac{\frac{2}{3} \cdot 26.4575}{30} = \frac{2 \times 26.4575}{90} = 0.58794 \quad \hat{\varphi}' = 30.45^\circ \text{ lagging}$$

$$\boxed{\cos \hat{\varphi}' = 0.862 \text{ lagging}}$$

c) Before capacitor bank connection

$$I_L = \frac{30 \cdot 10^3}{\sqrt{3} \times 3000 \times 0.75} = 7.698 \text{ A.}$$

$$P_{\text{loss}, 3\phi} = 3 (7.698)^2 5 = 888.88 \text{ W}$$


After capacitor bank ( $\Delta$ -connected)

$$\hat{I}_L = \frac{30 \cdot 10^3}{\sqrt{3} \times 3000 \times 1} = 5.7735 \text{ A.}$$

$$\hat{P}_{\text{loss}, 3\phi} = 3 (5.7735)^2 5 = 500 \text{ W} < 889 \text{ W}$$

# 3)

a)

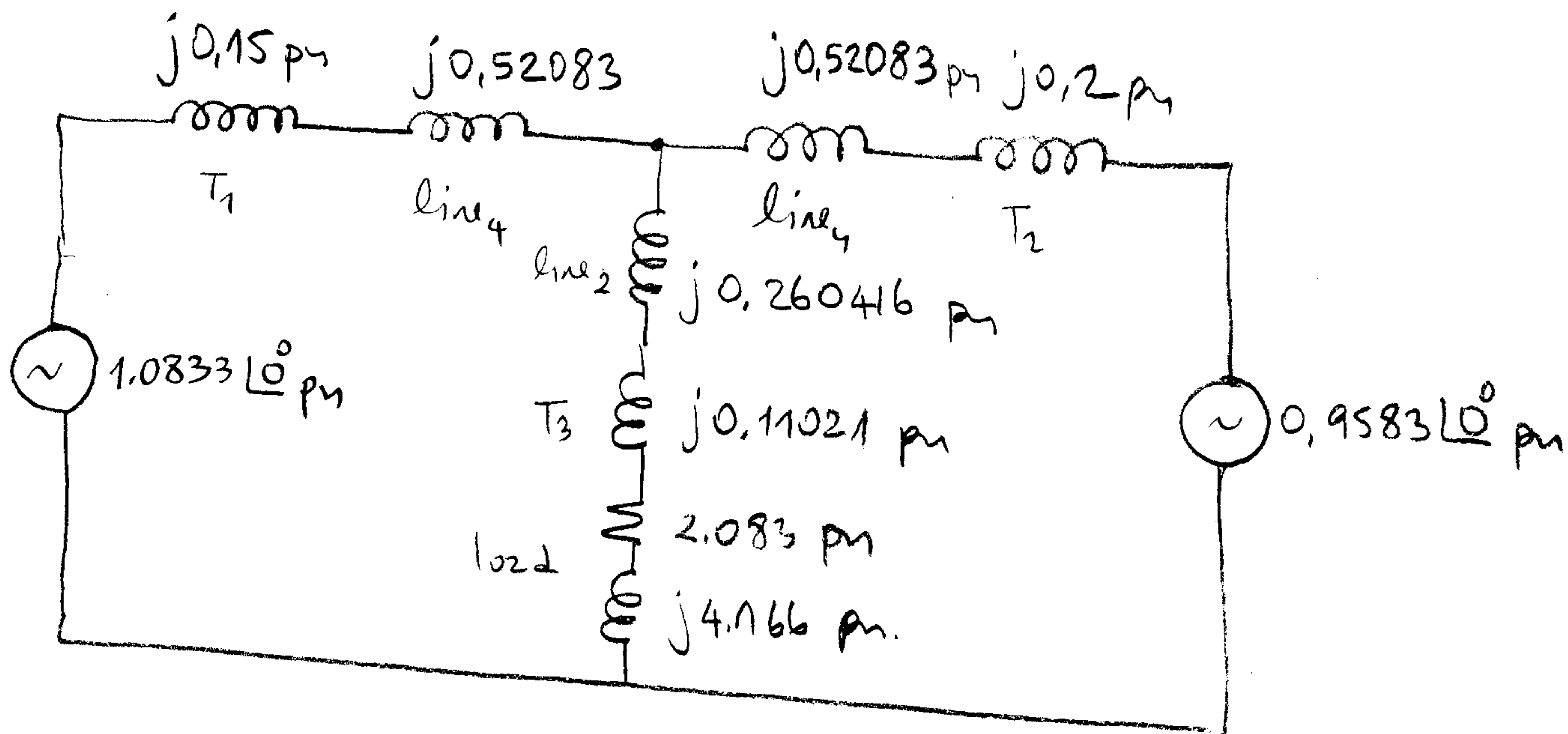

$$V_{\text{base}} = 240 \text{ load region}$$

$$V_{\text{base}} = 480 \text{ line region}$$

$$V_{\text{base}} = 120 \text{ source-left region}$$

$$V_{\text{base}} = 240 \text{ source-right region}$$

$$S_{\text{base}} = 30 \text{ kVA.}$$

$$\bar{V}_{s-\text{left}} = \frac{130 \angle 0^\circ}{120} = 1.0833 \angle 0^\circ \text{ pu.}$$

$$X_{T_1} = 0.15 \text{ pu}$$

$$X_{4\Omega} = \frac{4}{\left(\frac{(480)^2}{30 \cdot 10^3}\right)} = \frac{120 \cdot 10^3}{(480)^2} = 0.52083 \text{ pu.}$$



$$X_{2\Omega} = \frac{1}{2} X_{4\Omega} = 0.260416$$

$$X_{T_2} = 0.2 \text{ pu}$$

$$V_{s\text{-right}} = \frac{230 \angle 0^\circ}{240} = 0.9583 \angle 0^\circ \text{ pu.}$$

$$X_{T_3} = 0.1 \left(\frac{460}{480}\right)^2 \left(\frac{30}{25}\right) = 0.11021 \text{ pu}$$
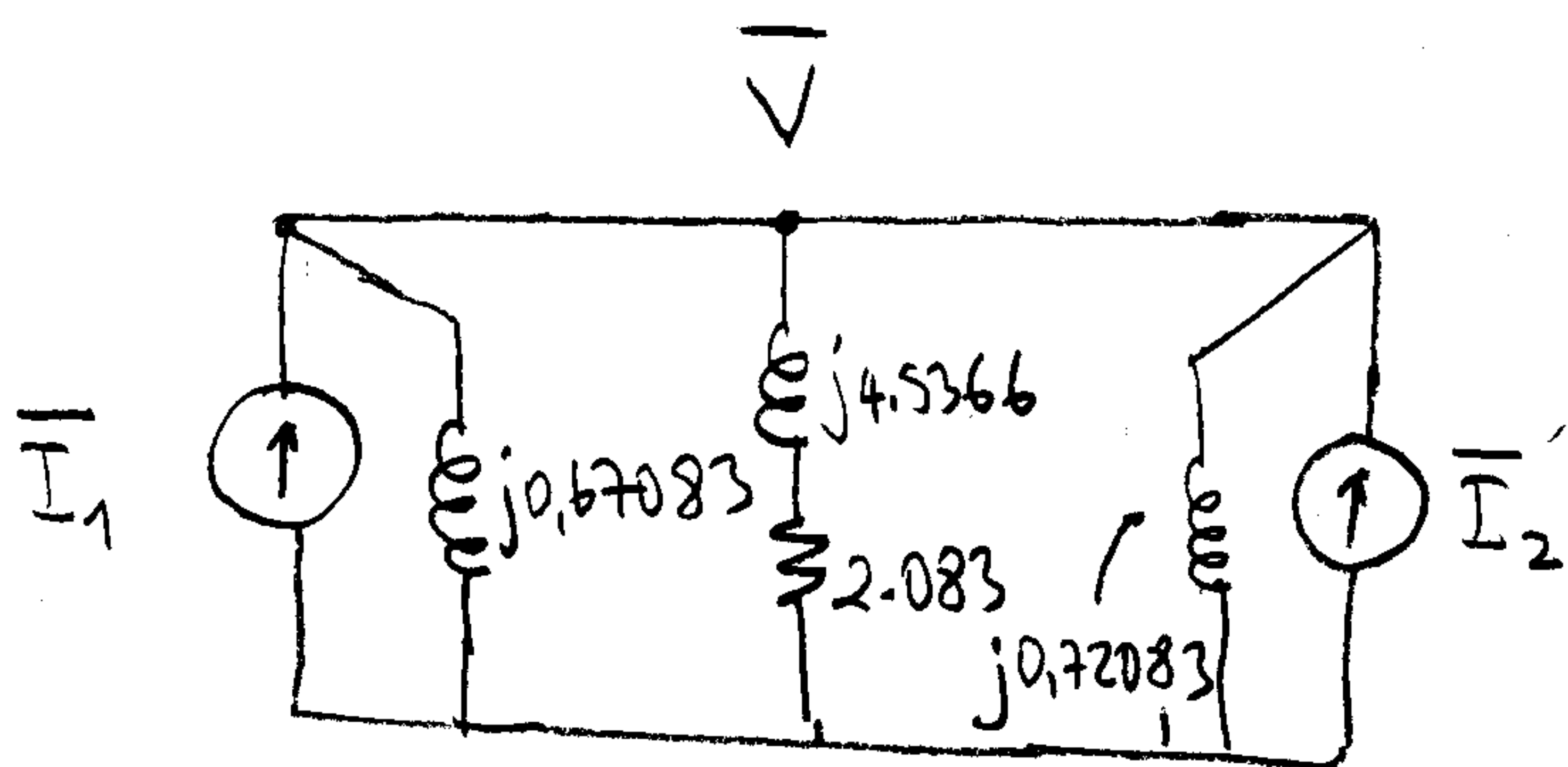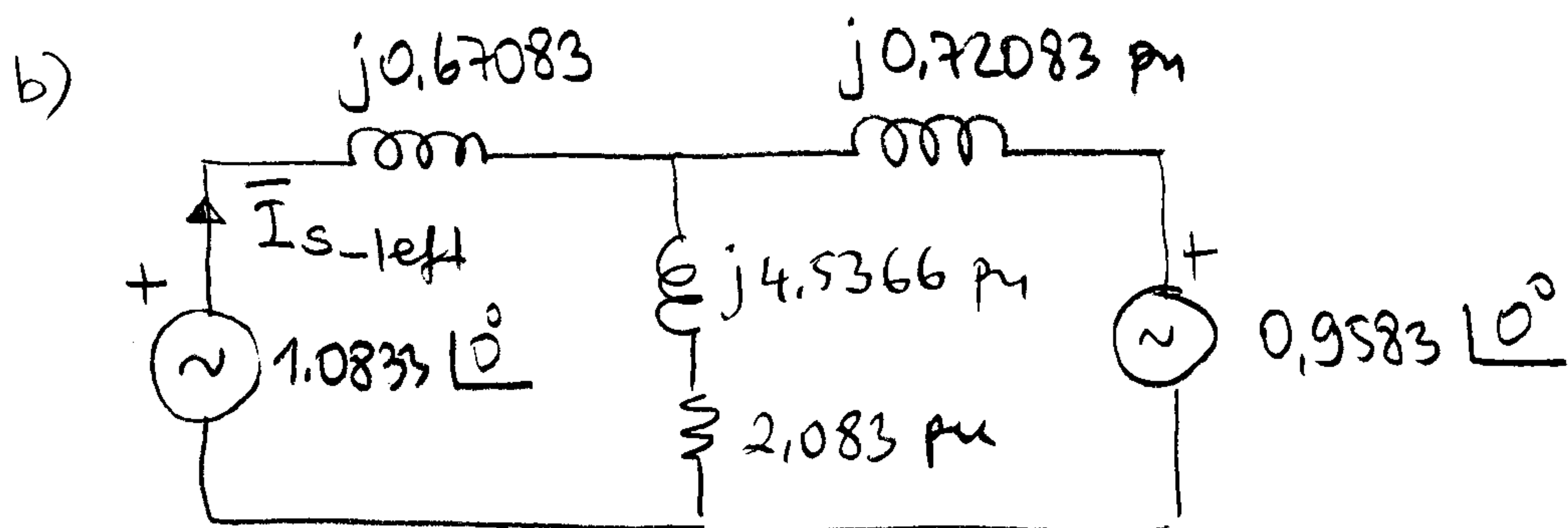
$$\bar{Z}_{load} = \frac{4 + j8}{\frac{(240)^2}{30 \cdot 10^3}} = \frac{120 \cdot 10^3}{(240)^2} + j \frac{240 \cdot 10^3}{(240)^2} = 2.083 + j 4.166 \text{ pu}$$



$$\bar{I}_1 = \frac{1.0833 \angle -90^\circ}{0.67083} = 1.6148 \angle -90^\circ \text{ pu}$$

$$\bar{I}_2 = \frac{0.9583 \angle -90^\circ}{0.72083} = 1.3294 \angle -90^\circ \text{ pu}$$

$$\left(-j \frac{1}{0.67083} + \frac{1}{\underbrace{2.083 + j 4.5366}_{4.992 \angle 65.3^\circ}} + \frac{-j}{0.72083}\right) \bar{V} = (1.6148 + 1.3294) \angle -90^\circ$$

$$\bar{V} [(1.490 + 1.387) \angle -90^\circ + 0.2 \angle -65^\circ] = 2.9442 \angle -90^\circ$$

$$\bar{V} [-j 2.887 + 0.0845 - j 0.1812] = -j 2.9442$$

$$\overline{V} [0.0845 - j 3.068] = 2.9442 \angle -90^\circ, \quad \overline{V} 3.069 \angle -88.4^\circ = 2.9442 \angle -90^\circ$$

$$\overline{V} = \frac{2.9442 \angle -90^\circ}{3.069 \angle -88.4^\circ} = \underline{\underline{0.9593 \angle -1.6^\circ}} \text{ pu}$$

$$\overline{I}_{s-\text{left}} = \frac{1.0833 - 0.9593 \angle -1.6^\circ}{0.67083 \angle 90^\circ} = \frac{1.0833 - 0.9589 + j0.0267}{0.67083 \angle 90^\circ}$$

$$\overline{I}_{s-\text{left}} = \frac{0.1244 + j0.0267}{0.67083 \angle 90^\circ} = \frac{0.1272 \angle 12.11^\circ}{0.67083 \angle 90^\circ} = 0.18966 \angle -77.89^\circ \text{ pu}$$

$$\overline{S}_{s-\text{left}} = (1.0833 \times 0.18966) \angle [0 + 77.89] \times 30 \times 10^3 \text{ VA.}$$

$$\overline{S}_{s-\text{left}} = (0.043103 + j 0.20088) 30 \times 10^3$$

$$\overline{S}_{s-\text{left}} = 1293.09 + j 6026.4$$

$$P_{s-\text{left}} = 1293.09 \text{ W delivered.}$$

$$Q_{s-\text{left}} = 6026.4 \text{ VAR delivered.}$$