

# Power Electronics Applications, Midterm I

Dr. Bunyamin Tamyurek

Saturday, April 09, 2005

35pt


1)

The following graph shows the control signals of PWM with **unipolar** voltage switching method used for a full-bridge dc/dc converter. The average input voltage to the converter is  $V_g = 40$  V, and the switching frequency is 10 kHz.

20pt a. Plot the instantaneous voltages shown in the graph.

10pt b. Find the average output voltage  $V_o = \langle v_o(t) \rangle$ .

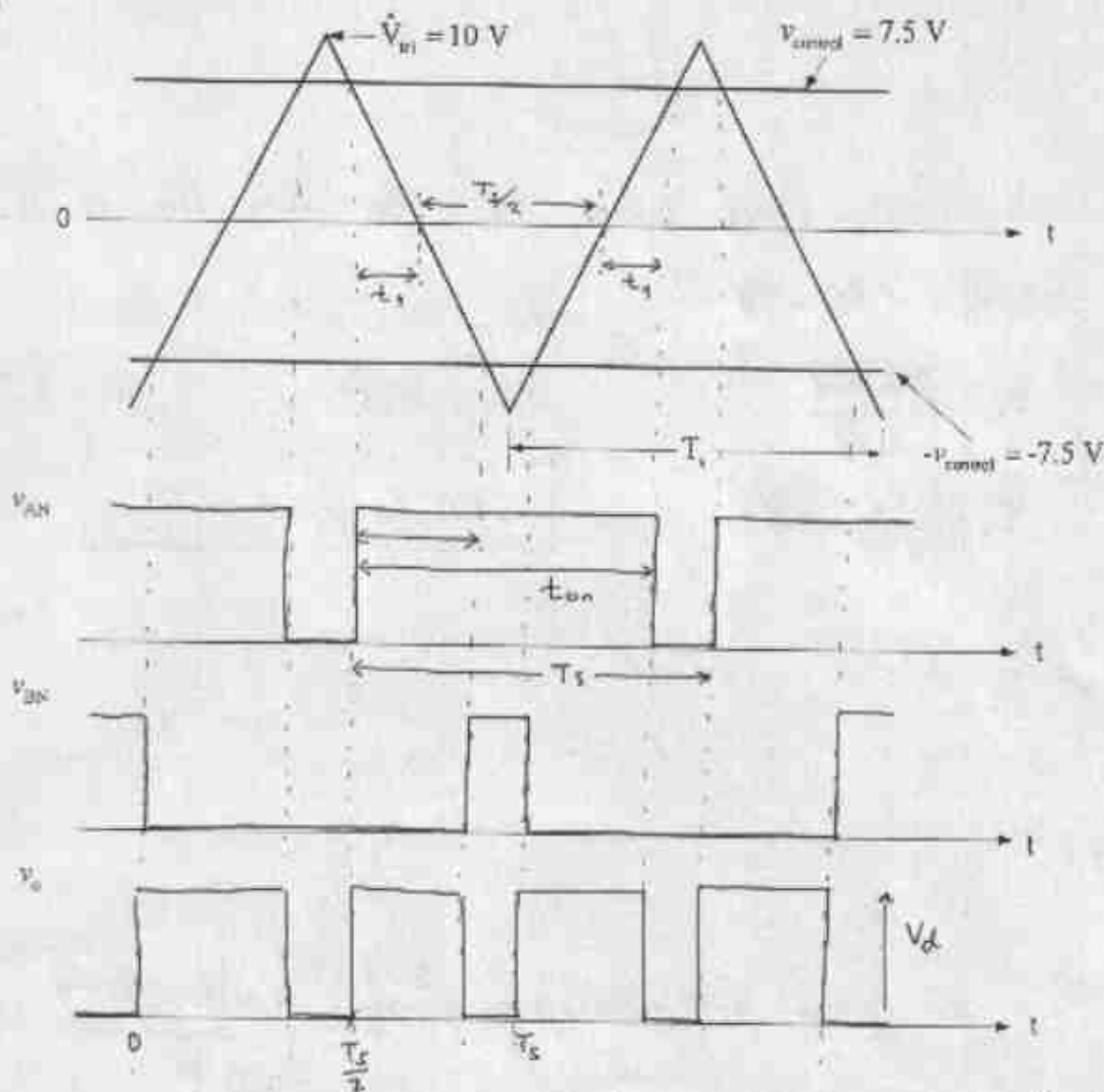5pt c. What is the frequency of output voltage waveform  $v_o(t)$ ?



$$b) \quad V_o = (2D_1 - 1)V_d \quad D_1 = \frac{t_{on}}{T_s} = \frac{(2t_1 + \frac{T_s}{2})}{T_s} = \frac{\frac{T_s}{2}(1 + \frac{V_{control}}{\hat{V}_{tri}})}{T_s}$$

$$D_1 = \frac{1}{2} \left( 1 + \frac{V_{control}}{\hat{V}_{tri}} \right) = 0.5 \left( 1 + \frac{7.5}{10} \right) = 0.875$$

$$\text{Then } V_o = [2(0.875) - 1] \times 40$$


$$= 30 \text{ V}$$

c) The frequency of the output voltage waveform is twice the switching frequency; so, it is 20 kHz

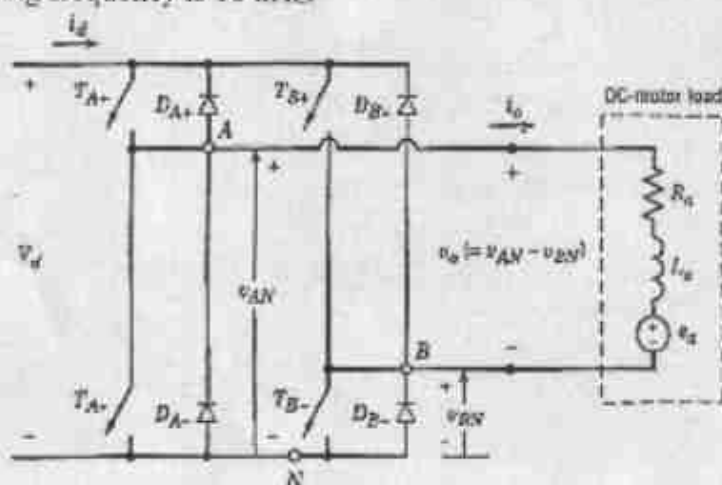2)

(20 pt)

The full-bridge converter shown below is controlled using PWM with **bipolar** voltage switching. The dc motor load shown in the figure requires a dc voltage between  $-24\text{ V}$  and  $+24\text{ V}$  in order to achieve speed control. Find the range of duty ratio of the switch  $T_A$  that would provide the desired output. The average input voltage to the converter is  $V_d = 100\text{ V}$ , and the switching frequency is  $10\text{ kHz}$ .



$$\langle v_o \rangle = (2D_1 - 1)V_d \quad \text{where } D_1 \text{ is the duty ratio of } T_{A+}$$

$$2D_1 V_d = \langle v_o \rangle + V_d$$

$$D_1 = \frac{V_o + V_d}{2V_d}$$

$$D_1 = \left( \frac{V_o}{2V_d} + 0.5 \right)$$

$$\text{for } V_o = +24$$

$$D_1 = 0.62$$

$$\text{for } V_o = -24$$

$$D_1 = 0.38$$

$$0.38 \leq D_1 \leq 0.62$$

3)

(15 pt)

In a single-phase full-bridge PWM inverter, the input dc voltage comes from a stack of batteries that are connected in series. The number of series connected batteries is 30, and a fully charged battery voltage is approximately  $13.5\text{ V}$ . Because of the low distortion required in the output  $v_o(t)$ , the inverter should be operated in the linear region ( $m_a \leq 1.0$ ). The desired output voltage is  $220\text{ Vrms}$ . Based on these conditions, answer the following questions:


- 7 pt a. What is the minimum level of discharge that can be allowed for the batteries?  
8 pt b. What will be the range of modulation index ( $m_a$ ) that controller needs to generate in order to produce  $220\text{ Vrms}$  at the output of the inverter?

$$a) \quad V(\text{minimum battery voltage}) = \frac{220 \times \sqrt{2}}{30} = \boxed{10.371\text{ V}} \\ 23.17\%$$

$$b) \quad (V_o)_{\text{rms}} = \frac{m_a V_d}{\sqrt{2}} \quad \text{when } V_d = 405 \quad m_a = \frac{220 \sqrt{2}}{405} \\ m_a = 0.768$$


$$405 \leq V_d \leq 311.13$$
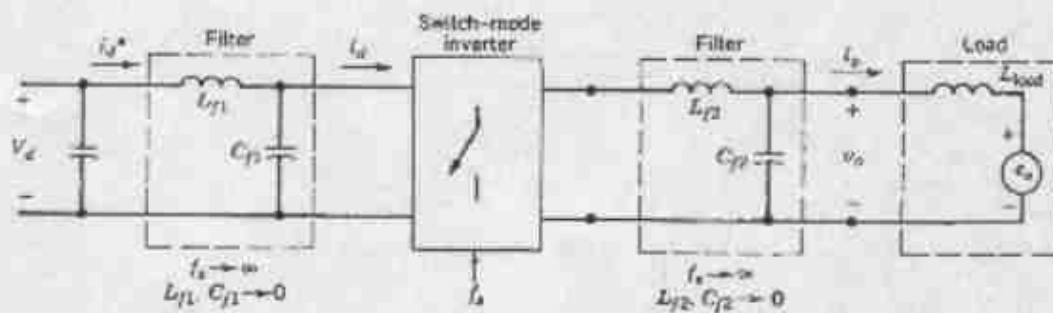
$$\boxed{0.768 \leq m_a \leq 1.0} \rightarrow \text{to generate } 220\text{ Vrms} \text{ at the output.}$$



30pt  
4)

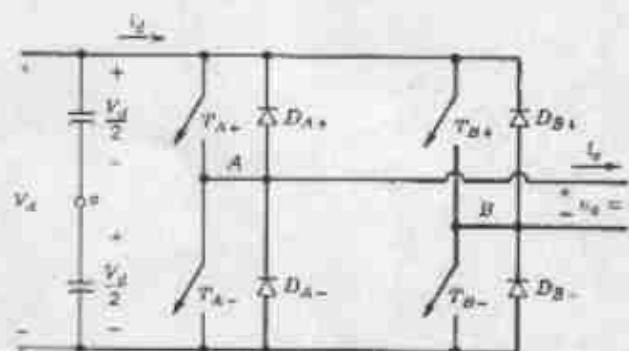The switch-mode inverter shown in the figure above can be represented by the following full-bridge topology.



20pt  
a) Draw the waveform of the dc side current ( $i_d$ ) when the inverter is operated with PWM bipolar voltage switching.

10pt  
b) Indicate the devices conducting during each interval of the switching cycle for only 3 cycles.

