

## Power System Analysis I \*\*\* Midterm I \*\*\* Sample problems

**P1** (50pt): A single-phase source supplies power to a single-phase load. The load is a small manufacturing plant absorbing 40 kVA at 0.8 power factor **lagging** from the source. Assume the source voltage is 220 V and the frequency is 50 Hz.

- a) Does this plant need power factor correction? In either case, explain your reasoning.
- b) For this plant, find the minimum value of the shunt capacitance in order to satisfy the regulation requirements that regulate the reactive power usage in Turkey.
- c) While the shunt capacitor is in place, a new load is added to the plant. The new load absorbs 28 kW at 0.87 **leading** power factor. Analyze the new case and draw the power triangle for the source side. Does this new case require a new action as far as the regulations are concerned?

### Answers:

- a)
- b) 1.1575 mF
- c)

**P2** (50pt): An ideal balanced three-phase, 50 Hz, positive sequence, Y-connected generator has an internal impedance of  $0.25 + j0.5 \Omega/\text{phase}$  and supplies power to two balanced three-phase loads that are connected in parallel. The generator feeds these two loads through a line having an impedance of  $0.3 + j2.0 \Omega/\text{phase}$ . One of the loads is Y-connected with an impedance of  $25 + j15 \Omega/\text{phase}$ . The other load is  $\Delta$ -connected with an impedance of  $60 - j9 \Omega/\text{phase}$ . The line-to-line voltage across the load terminals is  $\bar{V}_{BC} = 440 \angle -80^\circ$ .

- a) Calculate the Delta load current.
- b) Calculate the line-to-line voltage across the generator terminal.
- c) Calculate the complex power delivered by the generator.
- d) Check that the total active power delivered by the generator is equal to the total active power absorbed by the line and the load.

### Answers:

- a)  $I_{AB} = 7.251 / -48.53$ ,  $I_{BC} = \dots$
- b)  $V_{ab} = 464.3 / -48.4$ ,  $V_{bc} = \dots$
- c)  $15511.2 + j4418.48$
- d)