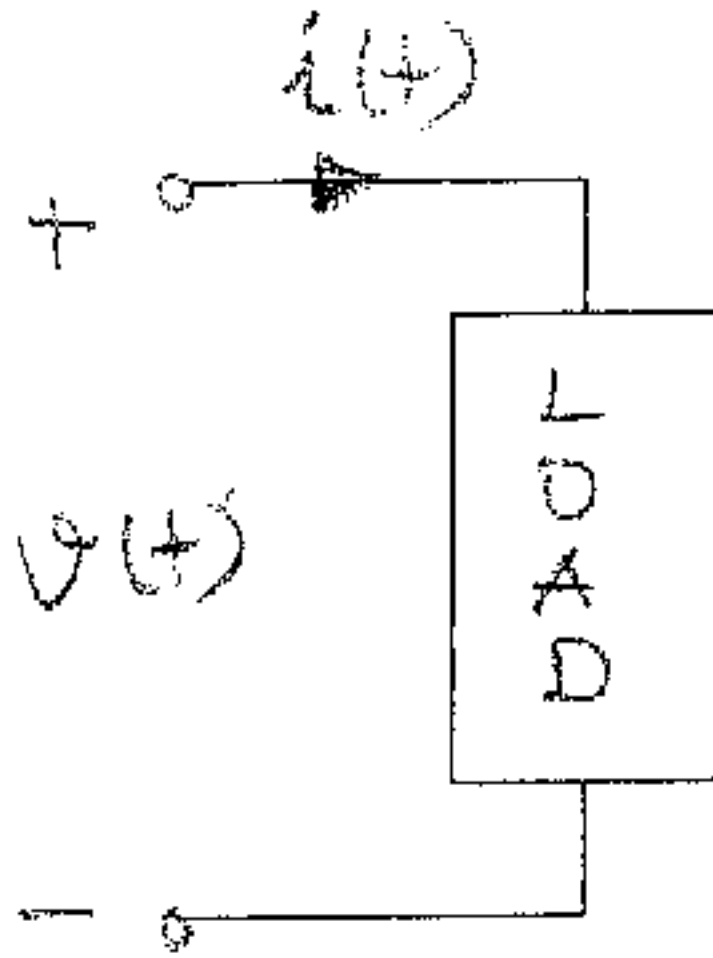


POWER SYSTEM ANALYSIS – I FIRST MIDTERM EXAM

Dr. Salih FADIL

July 13, 2011


#1) Consider a single phase load with an applied voltage $v(t) = 150 \cos(\omega t + 10^\circ)$ volts and load current $i(t) = 5 \cos(\omega t - 50^\circ)$ A.



- a) Find the power factor, specify whether it is lagging or leading.
- b) Determine the active and reactive power absorbed by the load.
- c) Calculate the reactive power supplied by the capacitor in parallel with the load that correct the power factor to 0.9 lagging.
- d) Assume that the voltage across the load is kept constant. Calculate the capacitance value of the capacitor mentioned in part c. Take the frequency of the supply voltage as 50 Hz.

#2) The three phase system shown in the figure is balanced and $v_{bc}(t) = \sqrt{2} 380 \cos(\omega t + 90^\circ)$ volt. By using one line to neutral equivalent circuit, find;

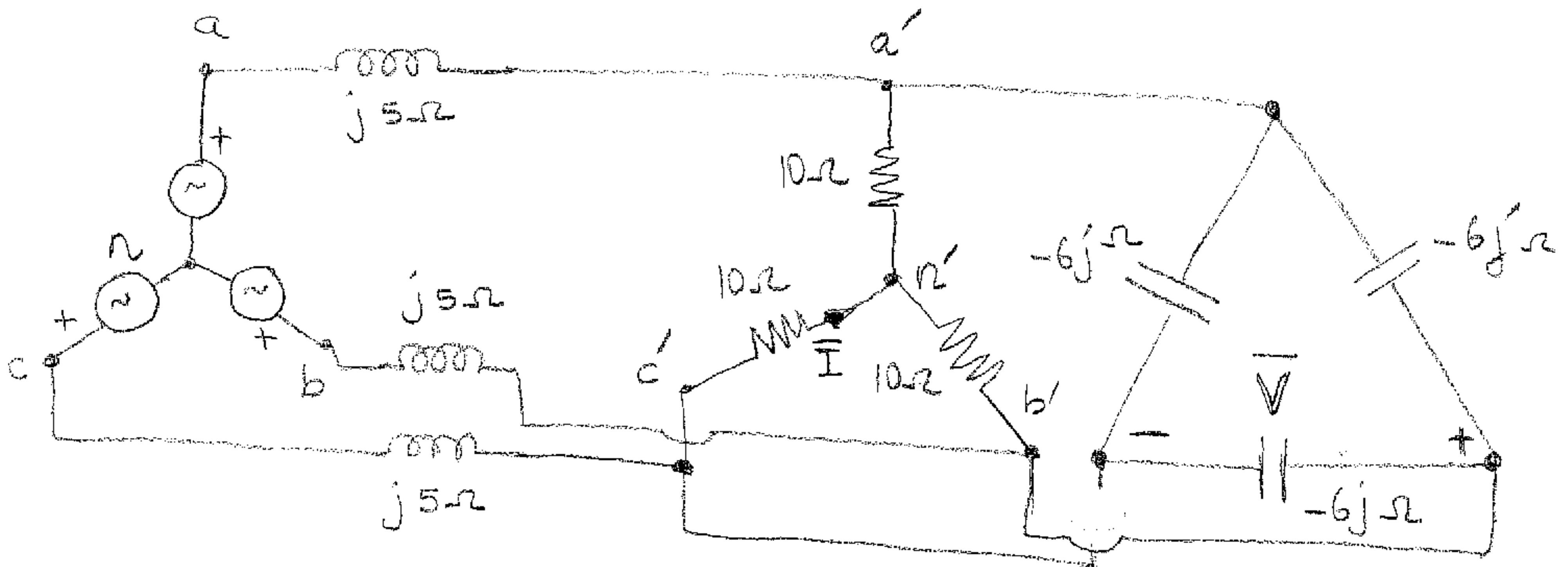- a) $\bar{I}$ and $\bar{V}$ phasor values shown in the figure ,
- b) three phase complex power delivered by the source.



#3) The real power delivered by a source to two impedances $\bar{Z}_1 = 3 + j4 \Omega$ and $\bar{Z}_2 = 10 \Omega$ connected in parallel, is 1100 W. Determine

- a) the real power absorbed by each of the impedances
- b) the rms source current

GOOD LUCK..... 😊


POWER SYSTEM ANALYSIS FIRST MIDTERM

EXAM SOLUTION MANUAL

Dr. Salih FADIL

July 13, 2011

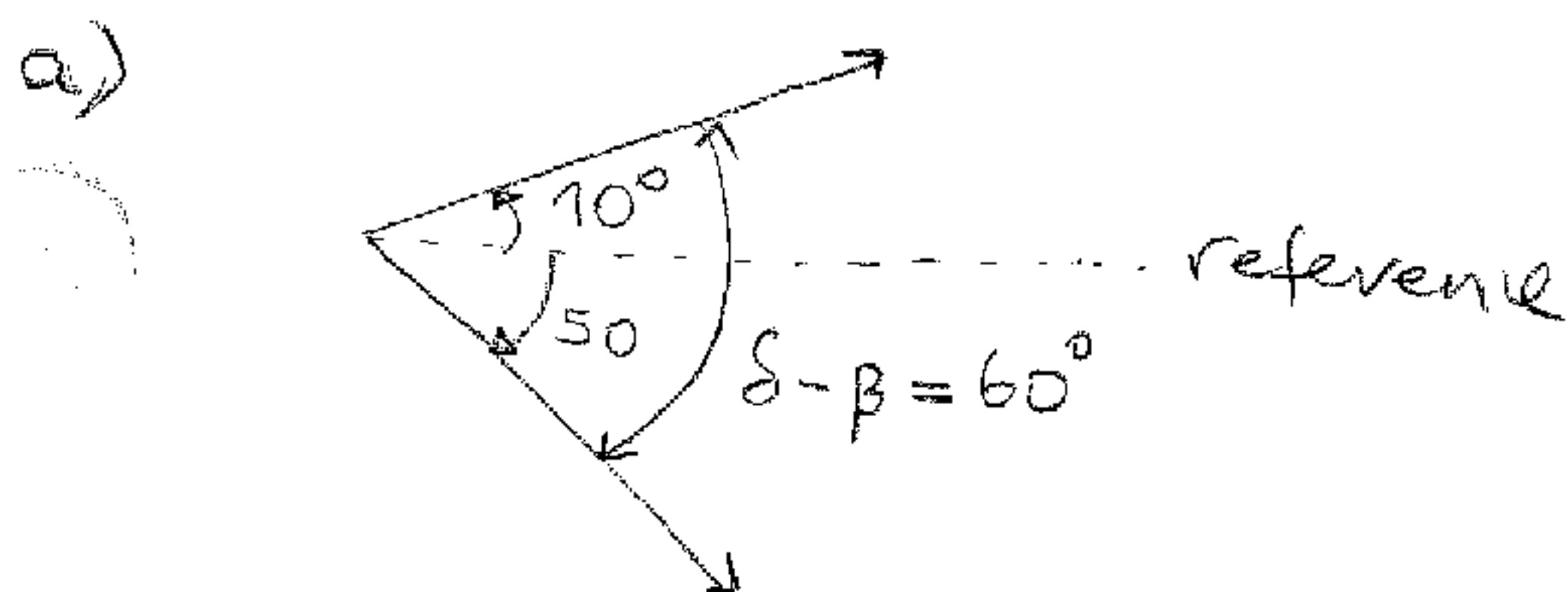
#1) $v(t) = 150 \cos(\omega t + 10^\circ) \text{ V}$
 $i(t) = 5 \cos(\omega t - 50^\circ) \text{ A}$



$$\varphi = \delta - \beta = 10 - (-50) = 60^\circ$$

power factor = $\cos(60^\circ) = 0.5$

lagging

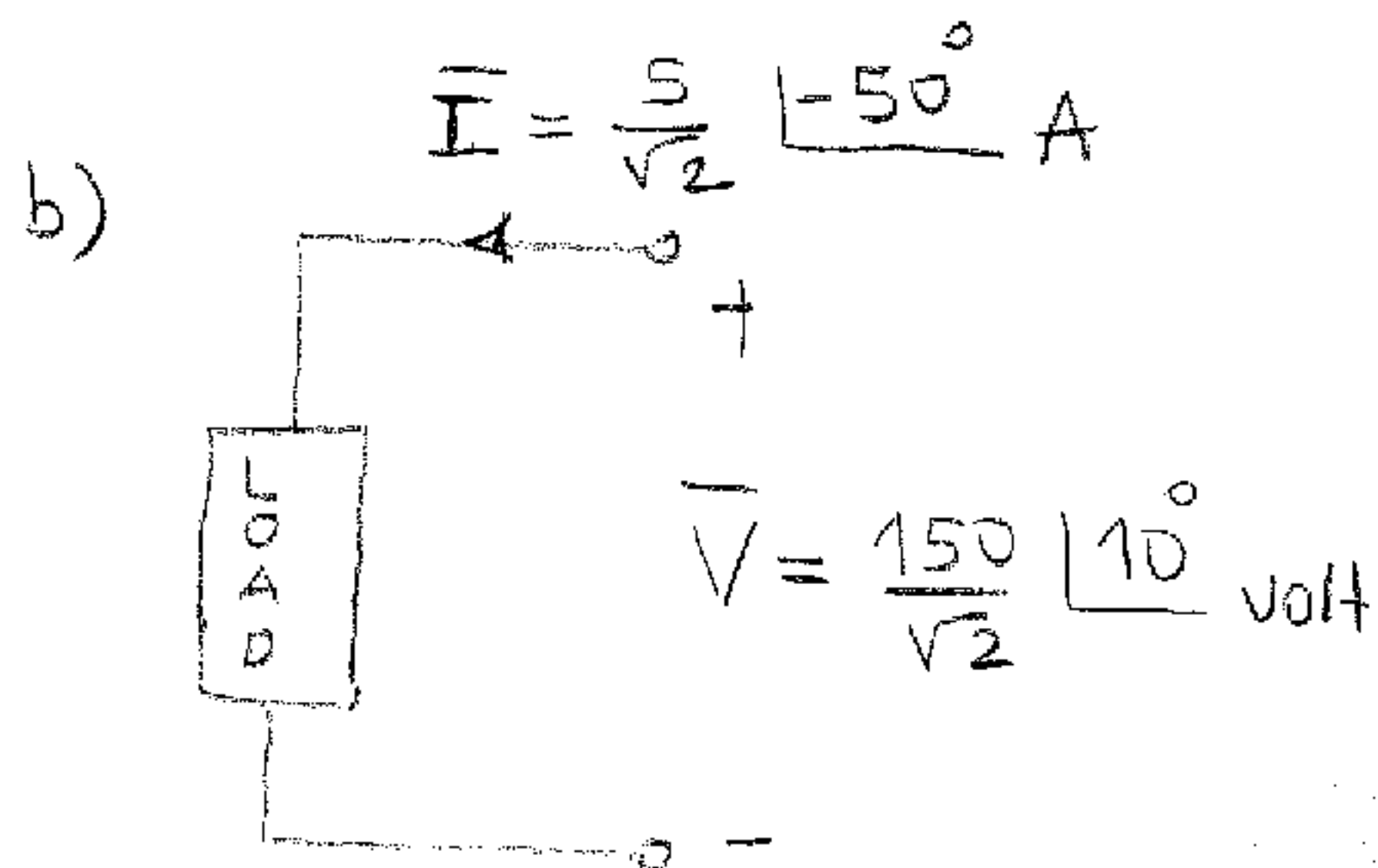


$$P = \frac{150}{\sqrt{2}} \frac{5}{\sqrt{2}} \cos(60^\circ) \text{ W}$$

$$P = 187.5 \text{ W absorbs.}$$

$$Q = \frac{750}{2} \sin(60^\circ) \text{ VAR}$$

$$Q = 324.76 \text{ VAR absorbs}$$

Load representation

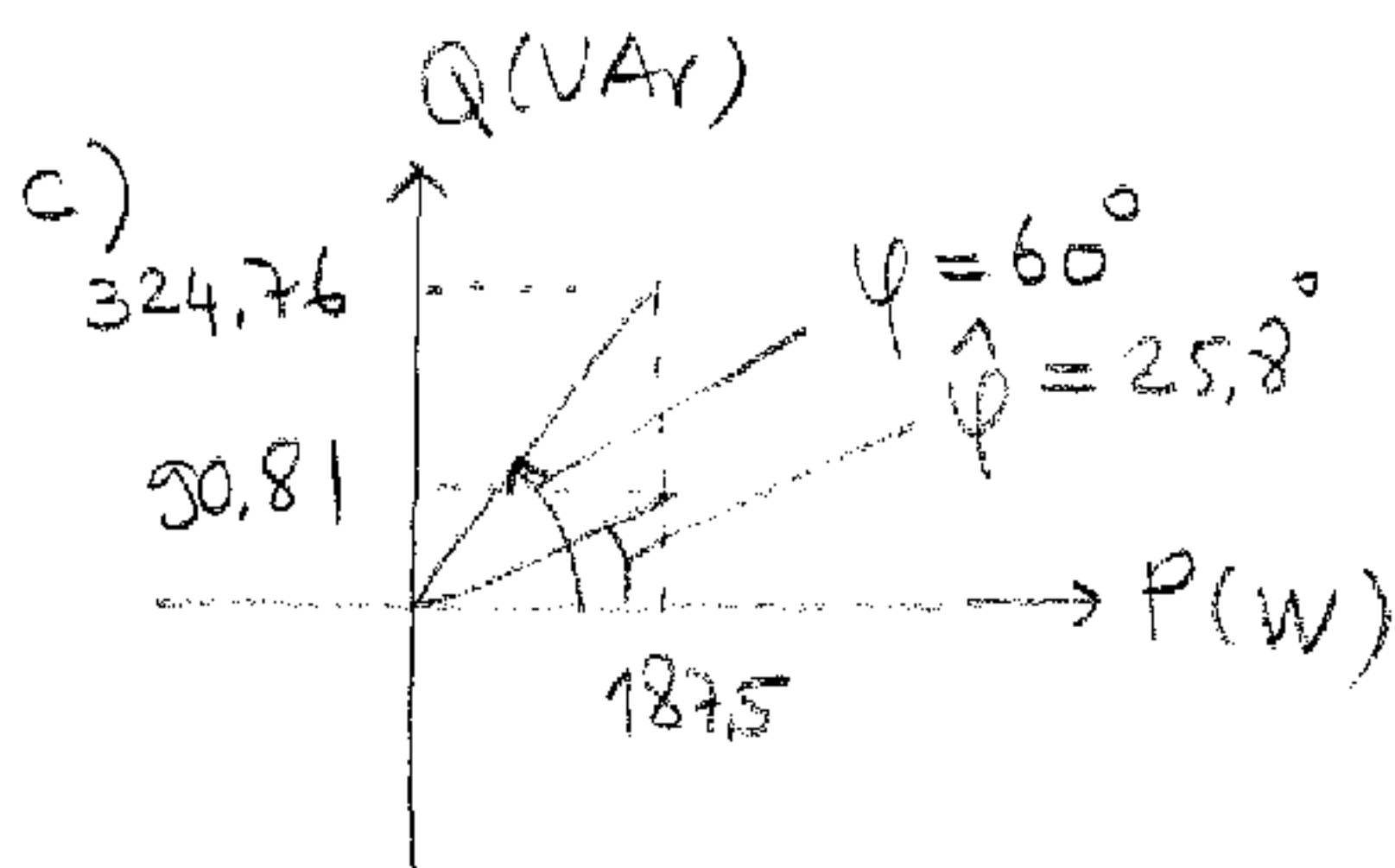

$$\cos \hat{\varphi} = 0.9 \rightarrow \hat{\varphi} = \cos^{-1}(0.9) = 25.8^\circ$$


$$\hat{Q} = 187.5 \tan(25.8^\circ) = 90.8 \text{ VAR}$$

$$Q_c = 324.76 - 90.81 = \underline{\underline{234 \text{ VAR}}}$$

d)

$$324 = 2\pi 50 C \left(\frac{150}{\sqrt{2}}\right)^2$$
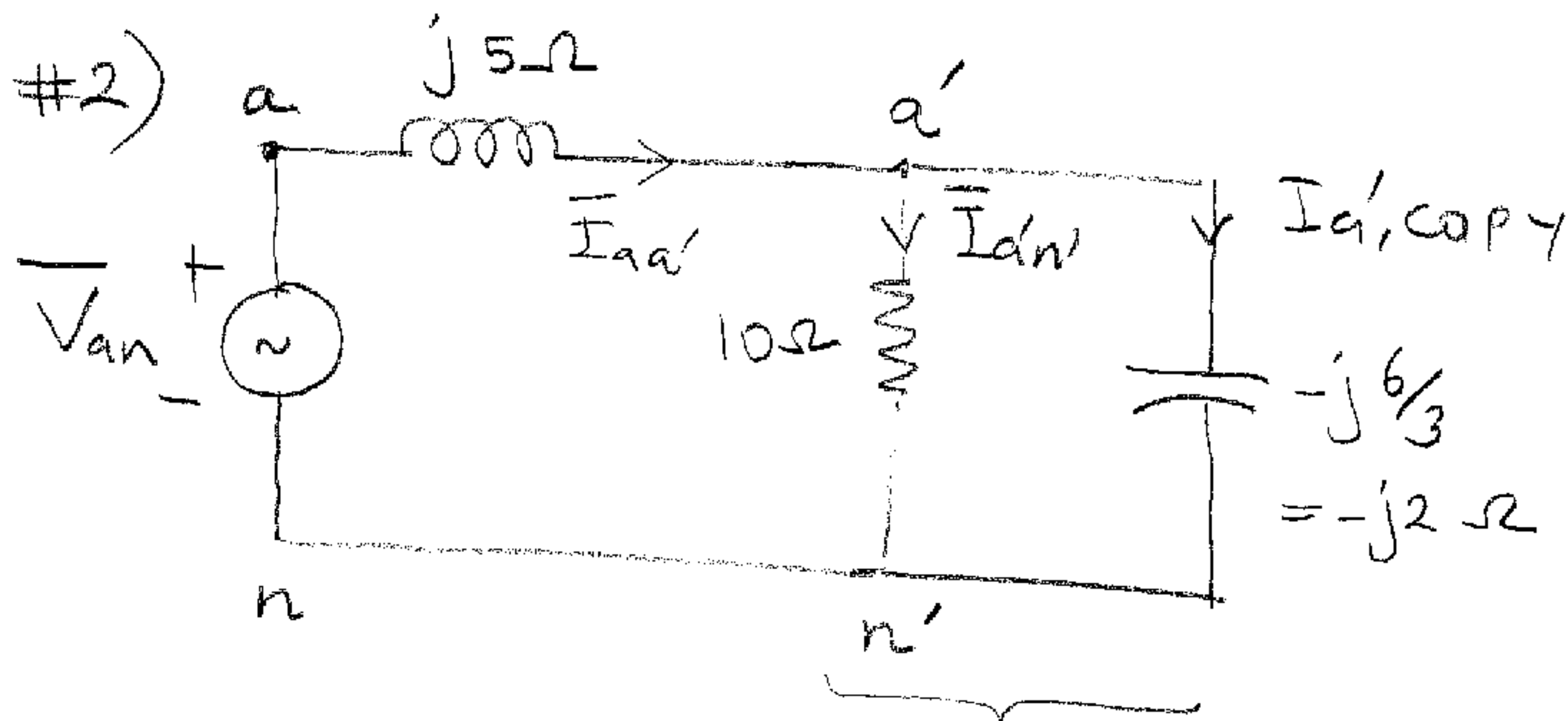
$$C = \frac{234}{100\pi \left(\frac{150}{\sqrt{2}}\right)^2} = 66.2 \mu\text{F}$$



$$\bar{V}_{bc} = 380 \angle 90^\circ$$

$$\bar{V}_{bn} = \frac{380}{\sqrt{3}} \angle 90-30^\circ = 220 \angle 60^\circ \text{ volt}$$

$$\bar{V}_{an} = \bar{V}_{bn} \angle 60-240^\circ = 220 \angle -180^\circ$$

$$\bar{V}_{an} = -220 \text{ volt}$$

$$\bar{Z}_{eq} = \frac{2 \angle -90^\circ \times 10}{10 - 2j} = \frac{20 \angle -90^\circ}{10.198 \angle -11.3^\circ} = 1.961 \angle -78.7^\circ = 0.384 - j1.923 \Omega$$

$$\bar{I}_{aa'} = \frac{220 \angle 180^\circ}{0.384 + j(5 - 1.923)} = \frac{220 \angle 180^\circ}{3.1 \angle 82.8^\circ} = 70.96 \angle 97.2^\circ \text{ A}$$

$$\bar{I}_{a'n'} = 70.96 \angle 97.2^\circ \frac{2 \angle -90^\circ}{10.198 \angle -11.3^\circ} = 13.908 \angle 18.5^\circ \text{ A}$$

$$\bar{I}_{a',copy} = 70.96 \angle 97.2^\circ \frac{10}{10.198 \angle -11.3^\circ} = 69.582 \angle 108.5^\circ \text{ A}$$

$$\bar{I} = \bar{I}_{c'n'} = \bar{I}_{a'n'} \angle +120^\circ = 13.908 \angle 138.5^\circ \text{ A}$$

$$\bar{I}'_{b',copy} = 69.582 \angle 108.5^\circ + 240^\circ = 69.582 \angle 348.5^\circ \text{ A}$$


$$\bar{I}'_{b'c'} = \frac{69.582}{\sqrt{3}} \angle 348.5^\circ + 30^\circ = 40.173 \angle 18.5^\circ \text{ A}$$

$$\bar{V}_{b'c'} = 40.173 \times 6 \angle 18.5^\circ - 90^\circ = 241 \angle -71.5^\circ \text{ Volt}$$

b) $\bar{S}_s = 3 \frac{220 \angle 180^\circ}{\sqrt{3}} 70.96 \angle -97.2^\circ = 46883.6 \angle 82^\circ = 6525 + j46427$
 $P_s = 6525 \text{ W del.}, Q_s = 46427 \text{ VAR del.}$

#3)

a)

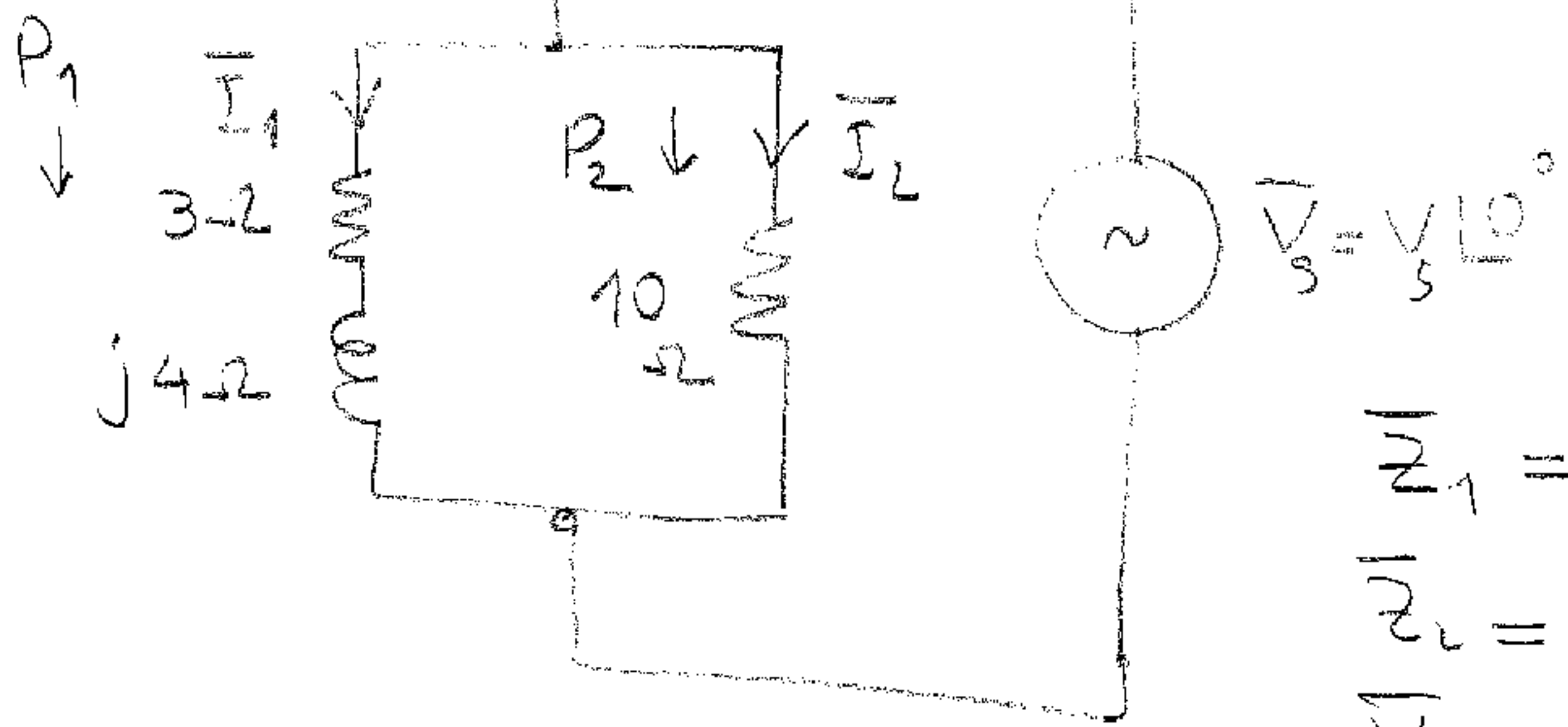

$$\bar{Z}_1 = 3 + j4\Omega = 5 \angle 53.13^\circ \Omega$$

$$\bar{Z}_2 = 10 \angle 0^\circ \Omega$$

$$\bar{V}_s = V_s \angle 0^\circ \text{ Volt}$$

$$\bar{I}_1 = \frac{V_s}{5} \angle -53.13^\circ, \quad \bar{I}_2 = \frac{V_s}{10} \angle 0^\circ$$

$$3 \left(\frac{V_s}{5} \right)^2 + 10 \left(\frac{V_s}{10} \right)^2 = 1100 \quad \left(\frac{3}{25} + \frac{10}{100} \right) V_s^2 = 1100$$

(4)

$$\frac{22}{100} V_s^2 = 1100 \quad V_s^2 = \frac{1100 \times 100}{22} \Rightarrow V_s = \pm \left(\frac{110000}{22} \right)^{1/2}$$

$$= \pm 70.7106 \text{ Volt}$$

select $V_s = 70.7106$

$$P_1 = \left(\frac{70.7106}{5} \right)^2 \times 3 = 600 \text{ W}$$

$$P_2 = \left(\frac{70.7106}{10} \right)^2 \times 10 = 500 \text{ W}$$

1100 W

(17)

b)

$$\bar{I}_s = \frac{70.7106}{5} \angle -53.13^\circ + \frac{70.7106}{10} \angle 0^\circ$$

$$= (8.4850 + 7.071) - j 11.313$$

$$= 15.5562 - j 11.313$$

$$= \underline{\underline{19.234 \angle -36.02^\circ \text{ A}}}$$

(16)