

POWER SYSTEM ANALYSIS-I FIRST EXAM

(Summer School - 2009)

Dr. Salih FADIL


July 23, 2009

#1) Consider a single-phase load with an applied voltage $v(t) = 150 \cos(\omega t + 10^\circ)$ volts and load current $i(t) = 5 \cos(\omega t - 50^\circ)$

A.

- Determine the power triangle.
- Find the power factor and specify whether it is lagging or leading
- Calculate the reactive power supplied by the capacitor in parallel with the load that correct the power factor to 0.9 lagging.

#2)

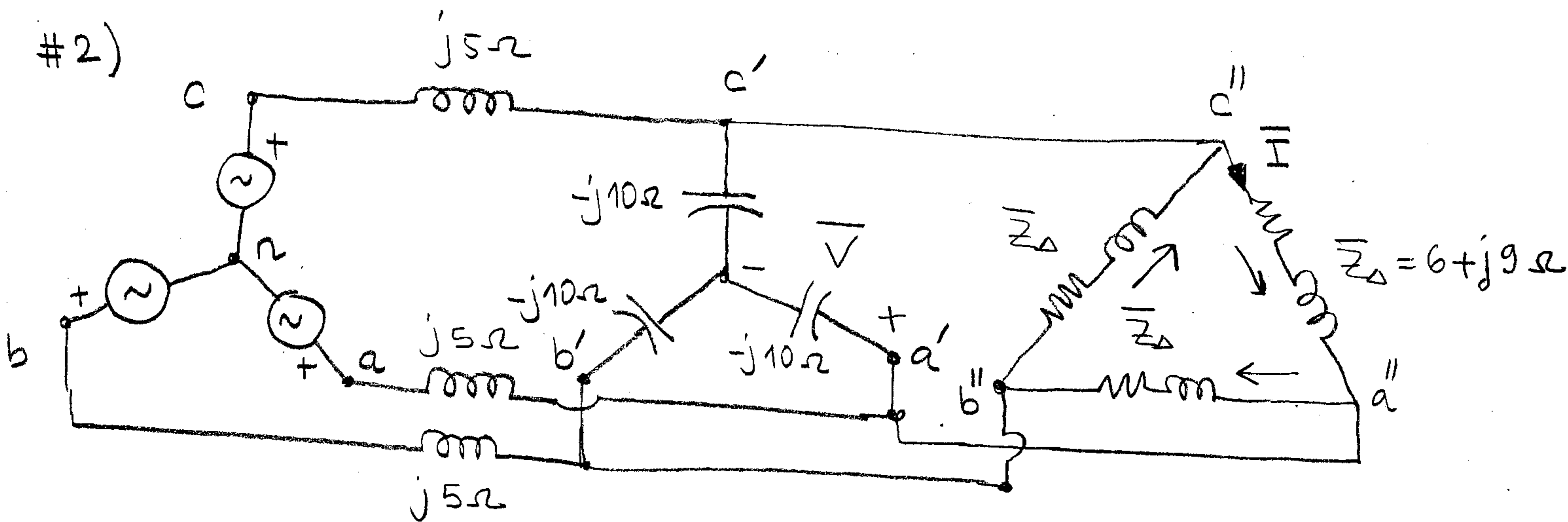

Three-phase system given in the above figure is balanced and its phase sequence is abc. Calculate $\bar{I}$ and $\bar{V}$ values shown in the figure. Calculate also the complex power given by the source. Take $v_{bc}(t) = \sqrt{2} 380 \cos(\omega t)$ volt for the source.

#3) The real power delivered by the source to two impedances, $\bar{Z}_1 = 3 + j4\Omega$, $\bar{Z}_2 = 10\Omega$ connected in parallel, is 1100 W. Determine:

- the real power absorbed by each of the impedances
- the source current.

①

POWER SYSTEM ANALYSIS - I FIRST EXAM


SOLUTION MANUAL (Summer School - 2009)

Dr. Salih FADIL

July 23, 2009


#1) $v(t) = 150 \cos(\omega t + 10^\circ)$ $V \rightarrow \bar{V} = \frac{150}{\sqrt{2}} \angle 10^\circ$ wlt

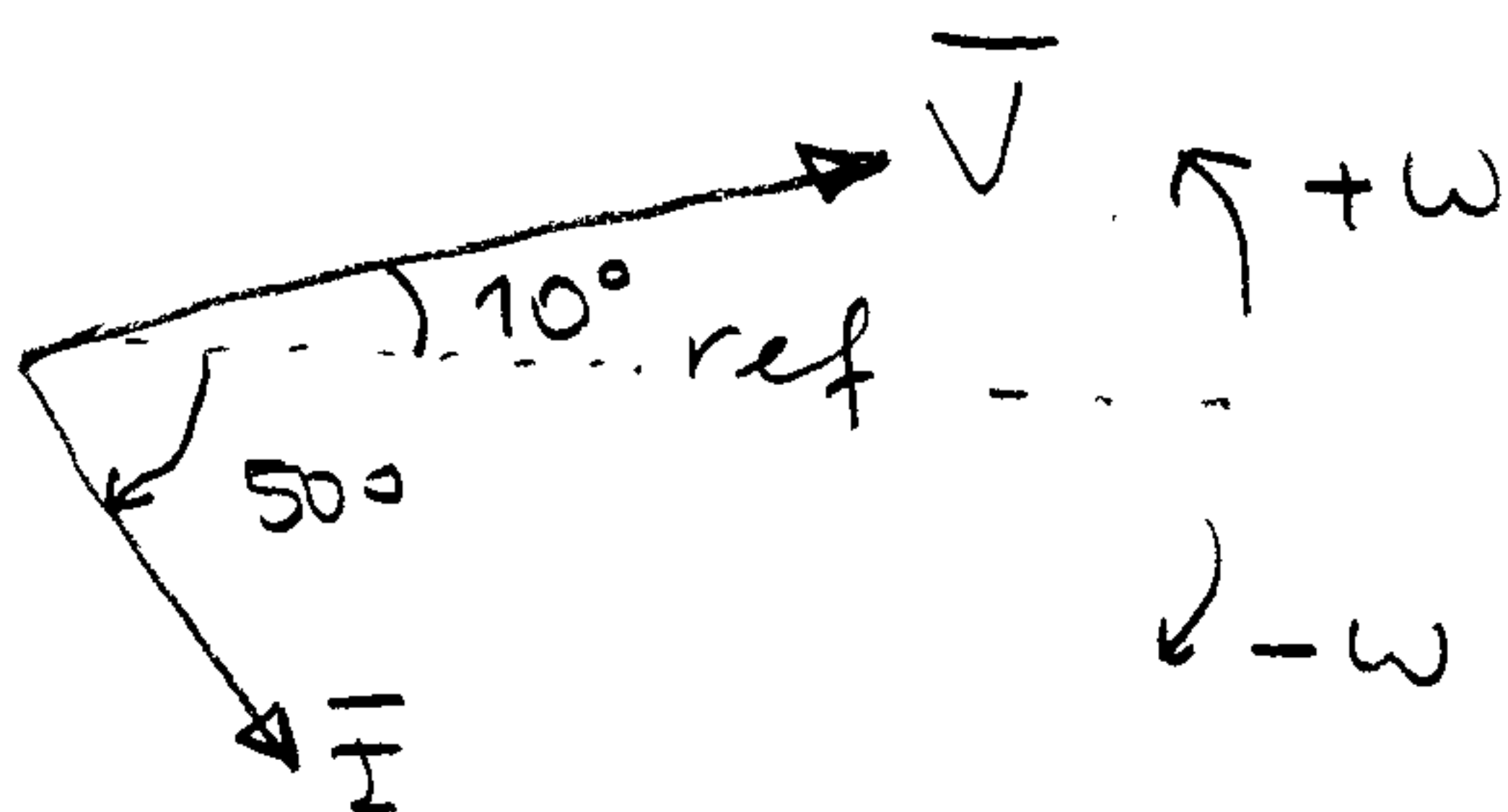a) $i(t) = 5 \cos(\omega t - 50^\circ)$ A $\rightarrow \bar{I} = \frac{5}{\sqrt{2}} \angle -50^\circ$ A.



$$\bar{S} = V \bar{I}^* = \frac{150 \times 5}{2} \angle 10 + 50$$
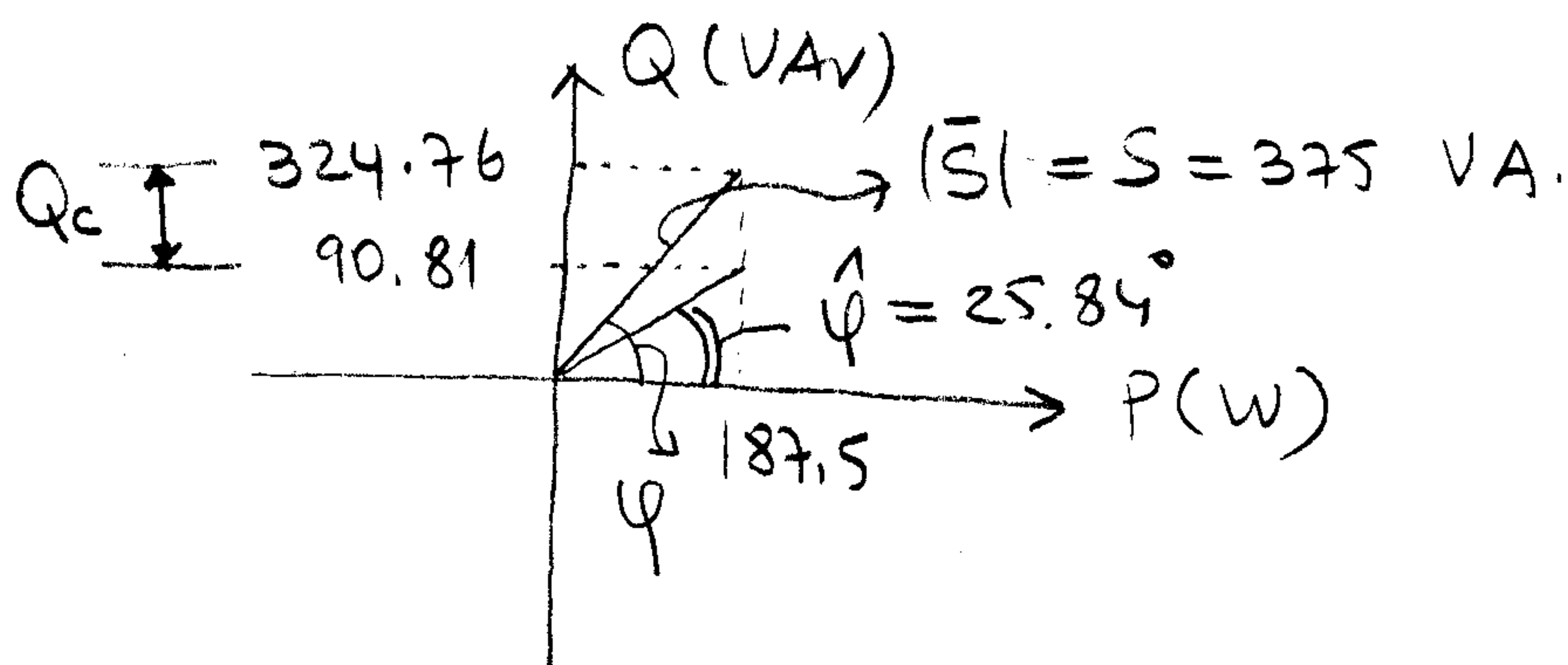
$$\bar{S} = 375 \angle 60^\circ = 187.5 + j 324.76 \text{ VA}$$



b) power angle $= \varphi = \delta - \beta = 10^\circ - (-50^\circ) = 60^\circ$


power factor $= \cos 60^\circ = 0.5$ lagging (current phasor lags voltage phasor)

c) $0.9 = \cos \hat{\varphi} \rightarrow \hat{\varphi} = \cos^{-1}(0.9) = 25.84$ lagging

$$\hat{Q} = P \tan \hat{\varphi} = 187.5 \times \tan(25.84^\circ) = 90.81 \text{ VAR}$$

$$Q_c = 324.76 - 90.81 = 234 \text{ VAR}$$
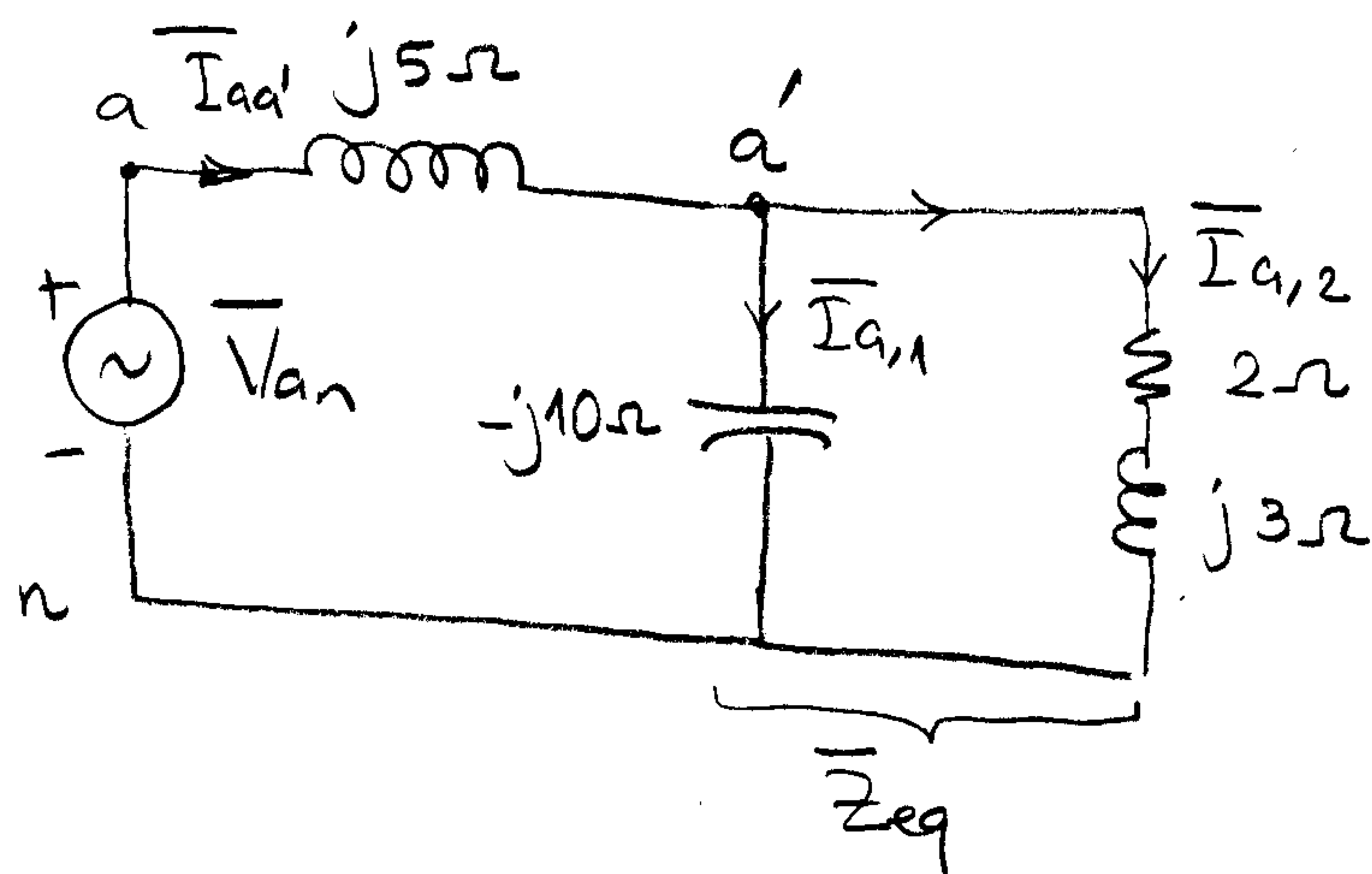
#2) Line-to-neutral equivalent circuit will be as follows;



$$v_{bc}(t) = \sqrt{2} 380 \cos(\omega t) \text{ V}$$

$$\bar{V}_{bc} = 380 \angle 0^\circ$$

$$\bar{V}_{bn} = \frac{380}{\sqrt{3}} \angle -30^\circ = 220 \angle -30^\circ$$

$$\bar{V}_{an} = 220 \angle 120^\circ - 30^\circ$$

$$\bar{V}_{an} = 220 \angle 90^\circ \text{ Volt}$$

$$2 + 3j = 3.605 \angle 56.3^\circ \Omega$$

$$\bar{Z}_{eq} = \frac{10 \angle -90^\circ \times 3.605 \angle 56.3^\circ}{-j10 + 2 + 3j}$$

$$\bar{Z}_{eq} = \frac{36.05 \angle -33.7^\circ}{7.28 \angle -74.05^\circ} = 4.952 \angle 40.35^\circ \Omega = 3.774 + j3.206$$

$$\bar{I}_{aa'} = \frac{220 \angle 90^\circ}{3.774 + j(3.206 + 5)} = \frac{220 \angle 90^\circ}{9.032 \angle 65.3^\circ} = 24.357 \angle 24.7^\circ \text{ A}$$

By using current division rule

$$\bar{I}_{a,1} = 24.357 \angle 24.7^\circ \times \frac{3.605 \angle 56.3^\circ}{7.28 \angle -74.05^\circ} = 12.06 \angle 155.05^\circ \text{ A}$$

$$\bar{I}_{a,2} = 24.357 \angle 24.7^\circ \times \frac{10 \angle -90^\circ}{7.28 \angle -74.05^\circ} = 33.45 \angle 8.75^\circ \text{ A}$$

$$\bar{V} = \bar{V}_{a'n} = 10 \angle -90^\circ \times 12.06 \angle 155.05^\circ = 120.6 \angle 65.05^\circ \text{ Volt}$$

$$\bar{I}_{c,2} = 33.45 \angle 8.75^\circ + 120^\circ = 33.45 \angle 128.75^\circ$$

$$\bar{I} = I_{c''a''}_{\Delta} = \frac{\bar{I}_{c,2}}{\sqrt{3}} \angle 30^\circ = \frac{33.45 \angle 128.75^\circ}{\sqrt{3}} = 19.312 \angle 158.75^\circ$$

$$\bar{S}_S = 3 \bar{V}_{an} \bar{I}_{aa'}^*$$

$$\bar{S}_{S,3\phi} = 3 \times 220 \angle 90^\circ \times 24.357 \angle -24.7^\circ = 16075.62 \angle 65.3^\circ \text{ VA}$$


$$= 6717.47 + j 14604.8 \text{ VA}$$

$$P_{S,3\phi} = 6717.47 \text{ W delivers}$$

$$Q_{S,3\phi} = 14604.8 \text{ VAR delivers}$$

#3)

a)

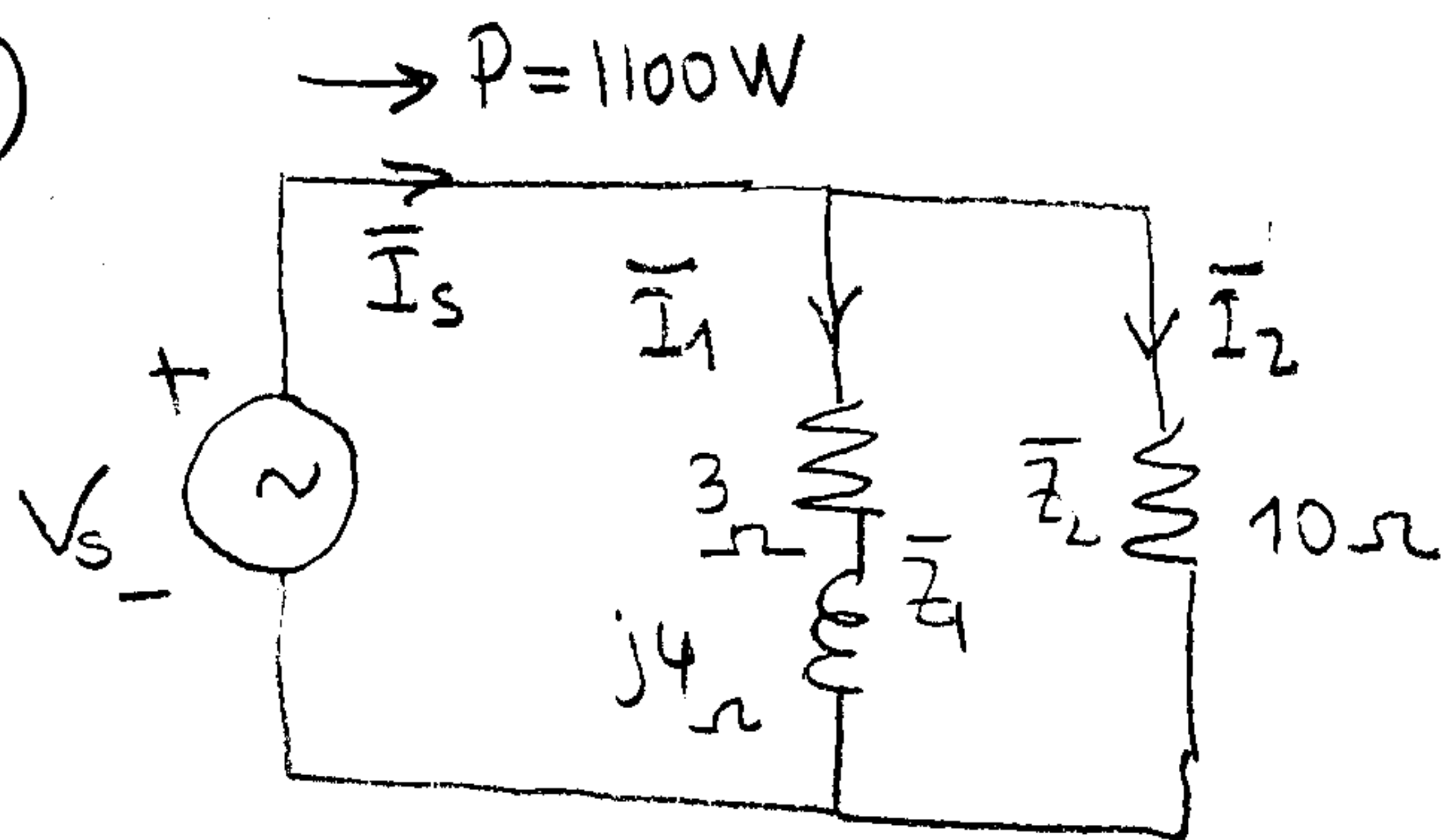

$$\bar{Z}_1 = 3 + j4 = 5 \angle 53.13^\circ \Omega$$

$$\bar{Z}_2 = 10 \angle 0^\circ \Omega$$

$$\bar{V}_s = V_s \angle 0^\circ \text{ volt}$$

$$\bar{I}_1 = \frac{V_s}{5} \angle -53.13^\circ \text{ A}, \bar{I}_2 = \frac{V_s}{10} \angle 0^\circ \text{ A}$$

$$\frac{V_s^2}{25} 3 + \frac{V_s^2 10}{100} = 1100$$

$$\frac{V_s^2 (12 + 10)}{100} = 1100$$

$$V_s = \left(\frac{1100 \times 100}{22} \right)^{1/2}$$

(4)

$$V_s = 70.7106 \text{ Volt}$$

$$\bar{I}_1 = \frac{70.7106}{5} \angle -53.13^\circ = 14.142 \angle -53.13^\circ \text{ A} = 8.4852 - j 11.313$$

$$\bar{I}_2 = \frac{70.7106}{10} = 7.071 \angle 0^\circ \text{ A}$$

$$P_1 = (14.142)^2 \times 3 = \underline{\underline{600 \text{ W}}}$$

$$P_2 = (7.071)^2 \times 10 = \underline{\underline{500 \text{ W}}}$$

$$b) \bar{I}_s = (8.4852 + 7.071) - j 11.313 = 15.5562 - j 11.313$$

$$= \underline{\underline{19.234 \angle 36.02^\circ \text{ A}}}$$