
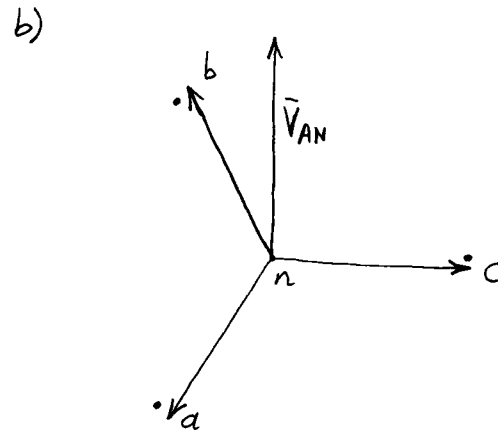





SOLUTIONS

P1 (30): The following schematic shows three identical single-phase two-winding transformers. Using these single-phase transformers, we want to construct a three-phase transformer bank. Assume positive-sequence balanced three-phase system.

- 5 a) Connect the high-voltage side as delta (Δ) and the low-voltage side as solidly grounded wye (Y).
- 15 b) Assume that the phasor voltages shown below are applied to the high-voltage side windings, draw the phasor voltage diagram for the low-voltage side and find the phase shift between $\bar{V}_{AN}$ and $\bar{V}_{an}$.
- 10 c) For the same given input voltages, modify the low-voltage terminal connections and labeling so that $\bar{V}_{an}$ lags $\bar{V}_{AN}$ by 90° .

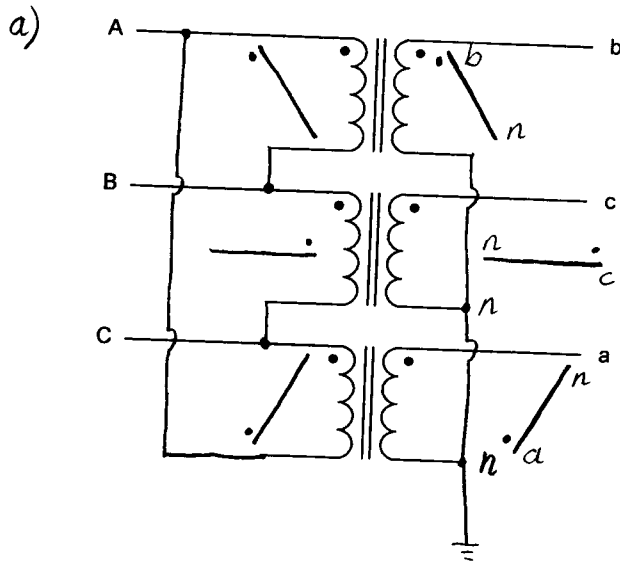


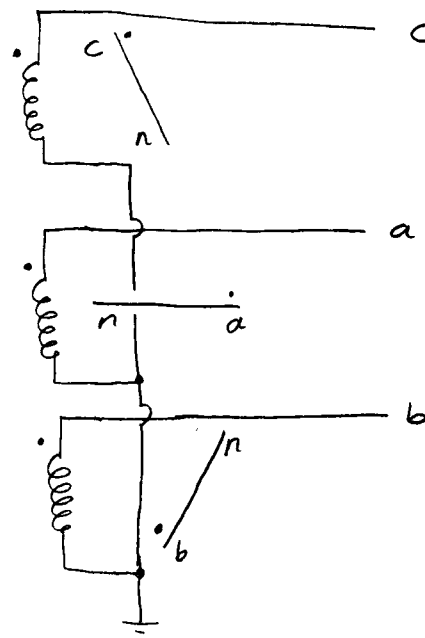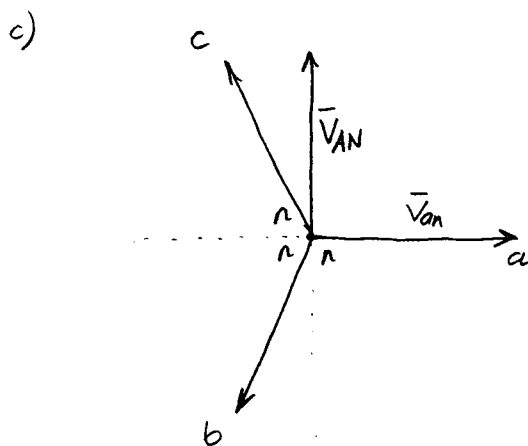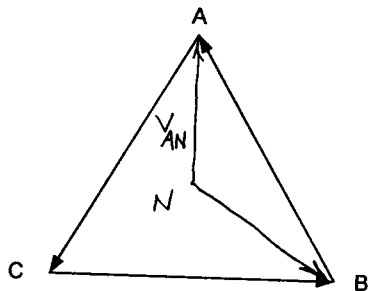$\bar{V}_{AN}$ lags $\bar{V}_{an}$ by 150° .



P2 (35): The figure below shows the one-line diagram of a three-phase power system.


- 20 a) Draw the per-unit impedance diagram of the system including the transformer phase shifts. Use the ratings of the generator as the base values.
- 15 b) The motors are drawing their rated powers from the system at the unity power factor with the bus 4 voltage is at 16 kV. Determine the voltage at bus 1 and the current supplied by the generator. Include the phase shifts of the transformers in your solution.

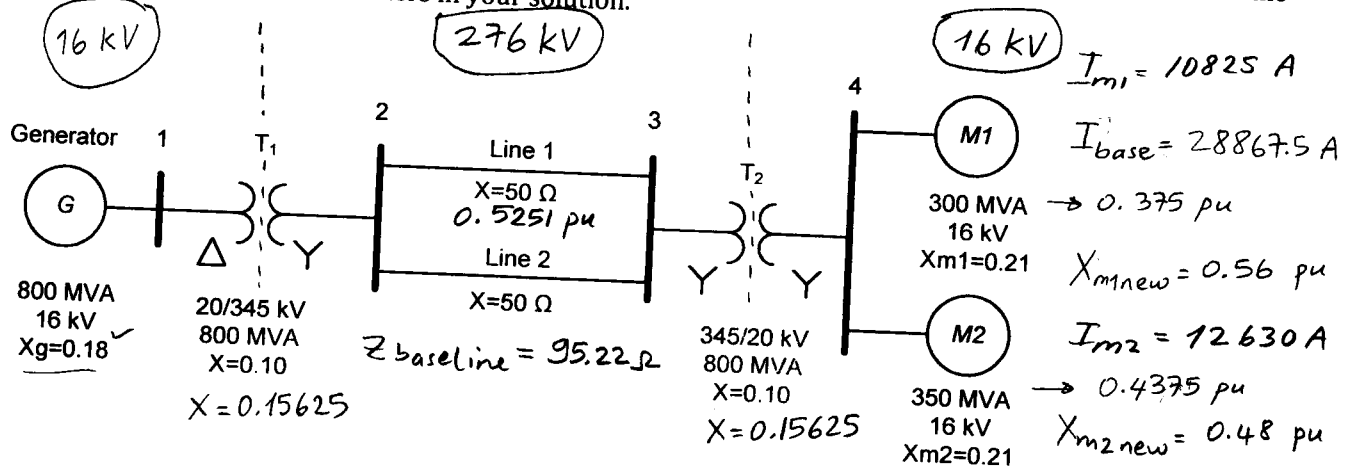

$$Z_{new} = Z_{old} \left(\frac{V_{baseold}}{V_{basenew}} \right)^2 \left(\frac{S_{basenew}}{S_{baseold}} \right)$$

$$I_{base} = \frac{S_{base1\phi}}{V_{base1,N}} = \frac{S_{base3\phi}}{\sqrt{3}V_{baseLL}}$$
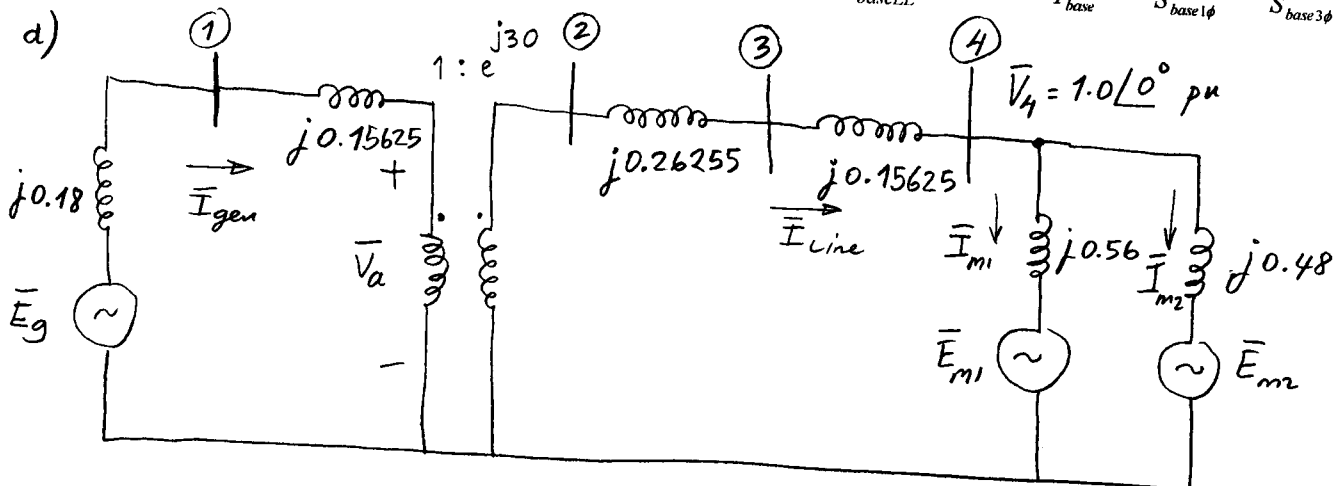
$$Z_{base} = \frac{V_{base1,N}}{I_{base}} = \frac{V_{base1,N}^2}{S_{base1\phi}} = \frac{V_{baseLL}^2}{S_{base3\phi}}$$



b)
$$\left. \begin{aligned} \bar{I}_{m1} &= 0.375 \text{ pu} \\ \bar{I}_{m2} &= 0.4375 \text{ pu} \end{aligned} \right\} \bar{I}_{line} = 0.8125 \text{ pu}$$

first find the voltage at bus 2

$$\bar{V}_2 = 1.0 + (0.8125)(0.4188 \angle 90^\circ) = 1.0563 \angle 18.792^\circ$$

$$\bar{V}_a = \bar{V}_2 \angle -30^\circ = 1.0563 \angle -11.208^\circ$$

Also
$$\bar{I}_{gen} = \bar{I}_{line} \angle -30^\circ = 0.8125 \angle -30^\circ \text{ pu}$$

$$\bar{V}_1 = 1.0563 \angle -11.208^\circ + (0.8125 \angle -30^\circ)(0.15625 \angle 90^\circ) = 1.104 \angle -4.96^\circ$$

$$\bar{I}_{gen} = 0.8125 \angle -30^\circ \text{ pu} \quad (5)$$

$$\bar{V}_1 = 1.104 \angle -4.96^\circ \quad (5)$$