

P1 (10): Consider a single-phase load with an applied voltage of  $v(t) = 400 \sin(\omega t + 40^\circ)$  Volts and a load current of  $i(t) = 50 \sin(\omega t + 20^\circ)$  Amperes.

- Find the real and reactive power absorbed by the load.
- Find the power factor and specify whether it is lagging or leading.

$$\bar{V} = \frac{400}{\sqrt{2}} \angle 40^\circ$$

$$a) \bar{S} = \bar{V} \bar{I}^* = \frac{400}{\sqrt{2}} \cdot \frac{50}{\sqrt{2}} \angle 40 - 20^\circ = 10000 \angle 20^\circ \quad \bar{I} = \frac{50}{\sqrt{2}} \angle 20^\circ$$

$$\text{Real power } P = 9396.93 \text{ W} \quad (3)$$


$$\text{Reactive power } Q = 3420.20 \text{ W} \quad (2)$$

$$b) pf = \cos(20) = 0.94 \quad (3) \quad \delta - \beta = 40 - 20 = 20 > 0$$

power factor is lagging (2)

P2 (40): A source delivers power to an industrial load consists of the following three loads connected in parallel: (1) a heater load drawing 10 kW, (2) an induction motor drawing 100 kVA at 0.8 power factor lagging, and (3) a synchronous motor drawing 48 kW at 0.96 power factor leading.


- Determine the real, reactive, and apparent power delivered by the source. Also, draw the source power triangle.
- Find the minimum value of capacitance of the shunt capacitor bank in  $\mu\text{F}$  that is needed to satisfy the reactive power regulation requirements set forth in Turkey. Assume that the source voltage and frequency are constant and equal to 220 V and 50 Hz, respectively.
- Draw the power triangle after the power factor correction and determine the new source power factor.

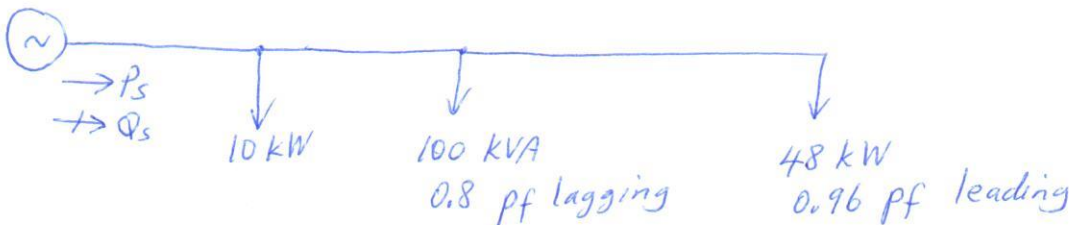

$$a) P_s = 10 + 100(0.8) + 48 = 138 \text{ kW} \quad (5)$$

$$Q_s = 60 - 14 = 46 \text{ kVar} \quad (5)$$


$$S_s = 145.5 \text{ kVA} \quad (5)$$

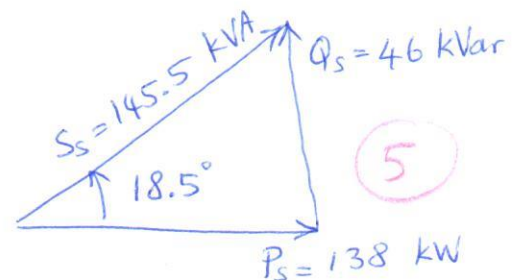

$$b) Q_{s\max} = 0.2 \times 138 = 27.6 \text{ kVar}$$

$$Q_{c\min} = 46 - 27.6 = 18.4 \text{ kVar}$$
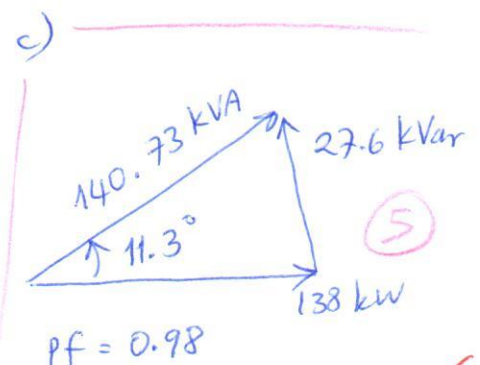
$$C_{\min} = \frac{18400}{(2\pi 50)(220)^2} = 1.21 \text{ mF} = 1210 \mu\text{F} \quad (15)$$



**P3 (40):** Two three-phase generators supply a three-phase load through separate three-phase lines. The load absorbs 50 kW at 0.8 power factor lagging. The line impedance is  $(1.5 + j2) \Omega$  per phase between generator G1 and the load, and  $(1 + j1.2) \Omega$  per phase between generator G2 and the load. If generator G2 supplies 20 kW at 0.8 power factor lagging, with a terminal voltage of 500 V line-to-line, determine


- The voltage at the load terminals
- The voltage at the terminals of generator G1,
- And the real and reactive power supplied by generator G1.

Assume balanced operation.

*The solution is at the next page.*

**P4 (10):** A 100 V 100 W lamp is going to be operated on 220 V 50 Hz AC supply. Normally this operation is not possible. Nevertheless, it can be possible after addition of a component to the circuit. There are two possible ways to make the lamp operable on 220 V supply.

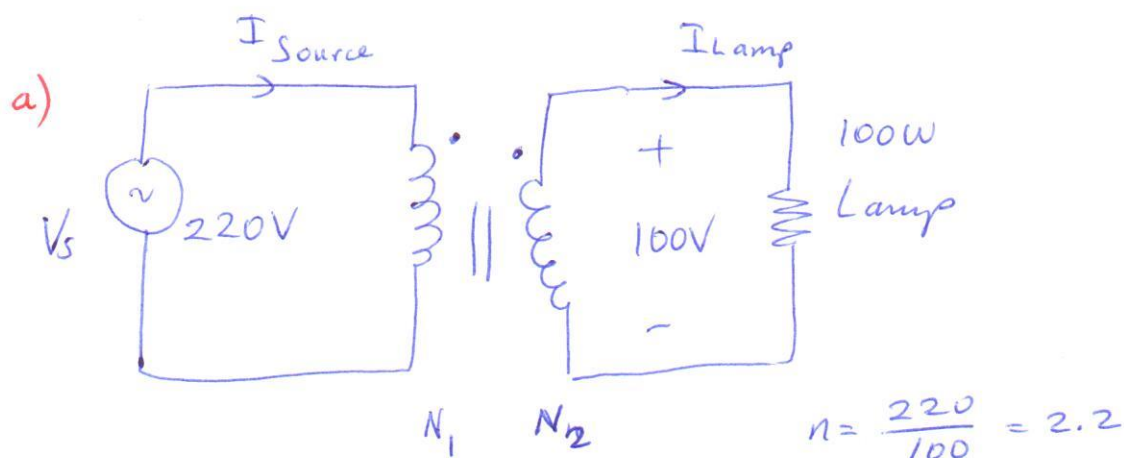- Suggest one of the ways.
- Based on your solution method. Find the current supplied by the source.




We can use a transformer to provide the proper interface. Transformer turns ratio is selected as 2.2 so that the voltage across the lamp is 100 V.

b)

$$I_{Lamp} = \frac{100}{100} = 1 \text{ A}$$
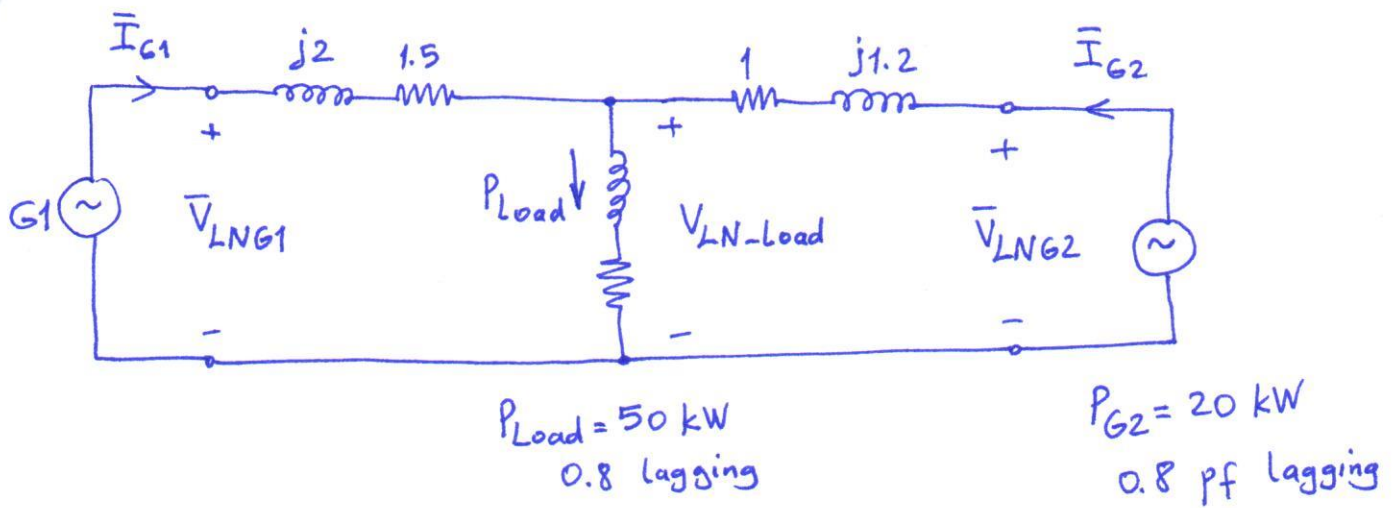
$$I_{source} = \frac{1}{2.2} = 0.4545 \text{ A}$$



a) 
$$\bar{I}_{G2} = \frac{20000}{\sqrt{3}(500)(0.8)} \angle -36.87^\circ = 28.87 \angle -36.87^\circ \text{ A} \quad (5)$$

$$\bar{V}_{LN-Load} = \frac{500}{\sqrt{3}} \angle 0^\circ - (28.87 \angle -36.87^\circ)(1 + j1.2)$$

$$= 288.7 - 43.88 - j10.4 = 244.82 - j10.4$$

$$\bar{V}_{LN-load} = 245 \angle -2.43^\circ \quad (5)$$

b) 
$$\bar{I}_{Load} = \frac{50000}{3(245)(0.8)} \angle -2.43^\circ - 36.87^\circ = 85 \angle -39.3^\circ \text{ A} \quad (5)$$

$$\bar{I}_{G1} = \bar{I}_{Load} - \bar{I}_{G2} = 85 \angle -39.3^\circ - 28.87 \angle -36.87^\circ$$

$$\bar{I}_{G1} = 56.17 \angle -40.55^\circ \text{ A} \quad (5)$$

$$\bar{V}_{G1-LN} = 245 \angle -2.43^\circ + (56.17 \angle -40.55^\circ)(1.5 + j2)$$

$$= 382.4 \angle 3.03^\circ \text{ V} \quad (10)$$

c) 
$$P_{G1} = 3(382.4)(56.17) \cos(3.03 + 40.55^\circ)$$

$$= 46679.9 \text{ Watt} \quad (7)$$

$$Q_{G1} = 3(382.4)(56.17) \sin(43.58^\circ)$$

$$= 44421.6 \text{ Var} \quad (3)$$