# **Microwave** Techniques

### Impedance Matching

ESKİŞEHİR OSMANGAZİ UNIVERSITY ELECTRICAL AND ELECTRONICS ENGINEERING



Prof. Dr. Gökhan Çınar Autumn 2016

### Impedance Matching and Tuning

Impedance matching is important because it provides

- · maximum power delivered to the load,
- · improvement of the Signal-to-Noise ratio.



- Matching networks are ideally lossless.
- It is always possible to design a matching network as long as the load has a non-zero real part

Prof. Dr. Gökhan Çınar Autumn 2016	ESKİŞEHİR OSMANGAZİ UNIVERSITY ELECTRICAL AND ELECTRONICS ENGINEERING	

### Selection Criteria of Matching Network

exity - As with most engineering solutions, the simplest design that satisfies the required specifications is generally preferable. A simpler matching network is usually cheaper, smaller, more reliable, and less lossy than a more complex design. B width-Any type of matching network can ideally give a perfect match (zero reflection) at a single frequency. In many applications, however, it is desirable to match a load over a band of frequencies. There are several ways of doing this, with, of course, a corresponding increase in complexity.

antation - Depending on the type of transmission line or waveguide being Imp used, one type of matching network may be preferable to another. For example, tuning stubs are much easier to implement in waveguide than are multisection quarter-wave transformers.

Adjustability- In some applications the matching network may require adjustment to match a variable load impedance. Some types of matching networks are more amenable than others in this regard.

Prof. Dr. Gökhan Çınar Autumn 2016



### Matching with Lumped Elements (L Networks)

- L section uses two reactive elements to match an arbitrary load impedance to the line.





### Matching with Lumped Elements (L Networks)

- Actual lumped element capacitors and inductors can be used up to several GHz. However,
- there is a large range of frequencies and circuit sizes where lumped elements cannot be realized.

This is the major limitation of the L-Section networks.

Prof. Dr. Gökhan Çınaı Autumn 2016



### Matching with Lumped Elements (L Networks)

Frequency response of a lumped inductor:



### Matching with Lumped Elements (L Networks)

Frequency response of a lumped capacitor:



### Matching with Lumped Elements (L Networks)

Realizations of inductors from transmission line sections



### Matching with Lumped Elements (L Networks)

Realizations of capacitors from transmission line sections



Prof. Dr. Gökhan Çınar Autumn 2016



# Example 1





## Example 2

Design an L section matching network to match a load  $Z_L = (50 + j100)$  $\Omega$  to a 100  $\Omega$  line at 1 GHz.





# In-class Design two lossless L-section matching circuits to match each of the following loads to a 100 Ω generator at 3 GHz. (a) $Z_L = 150 - j200 \Omega$ (b) (b) $Z_L = 20 - j90 \Omega$ .