


# Microwave Techniques

## Impedance Matching - Single Stub Tuning

Prof. Dr. Gökhan Çınar  
Autumn 2016

ESKİŞEHİR OSMANGAZI UNIVERSITY  
ELECTRICAL AND ELECTRONICS ENGINEERING

## Single Stub Tuning

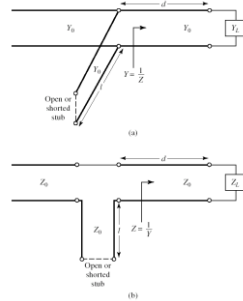


- ❖ Another popular matching technique uses a single O-C or S-C terminated transmission line (a stub) connected either in parallel or in series with the TL.
- ❖ Tuning circuit is very convenient because the stub can be fabricated as part of the
- ❖ transmission line media of the circuit, and lumped elements are avoided.
- ❖ Shunt stubs are preferred for microstrip line or stripline, while series stubs are preferred for slotline or coplanar waveguide.

Prof. Dr. Gökhan Çınar  
Autumn 2016

ESKİŞEHİR OSMANGAZI UNIVERSITY  
ELECTRICAL AND ELECTRONICS ENGINEERING


## Single Stub Tuning

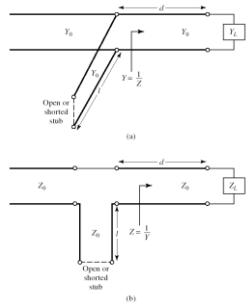



- ❖ In single-stub tuning, two adjustable parameters are  $d$  (the distance of the stub position to the load) and  $l$  (length of the stub).
- ❖ For the shunt-stub case, the task is to select  $d$  so that the admittance,  $Y$ , seen looking into the line at distance  $d$  from the load is of the form  $Y_0 + jB$ . Then the stub susceptance is chosen as  $-jB$ , resulting in a matched condition.
- ❖ For the series-stub case, the distance  $d$  is selected so that the impedance,  $Z$ , seen looking into the line at a distance  $d$  from the load is of the form  $Z_0 + jX$ . Then the stub reactance is chosen as  $-jX$ , resulting in a matched condition.

Prof. Dr. Gökhan Çınar  
Autumn 2016

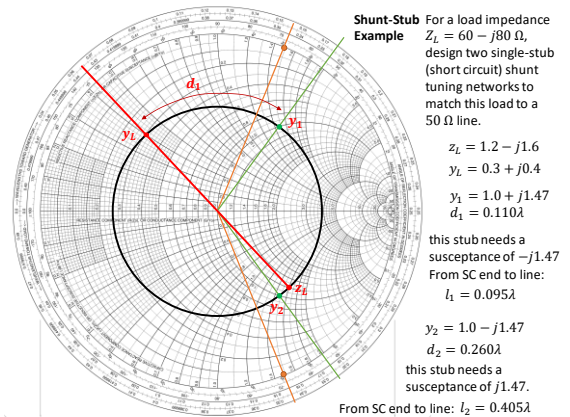ESKİŞEHİR OSMANGAZI UNIVERSITY  
ELECTRICAL AND ELECTRONICS ENGINEERING




## Single Stub Tuning Example

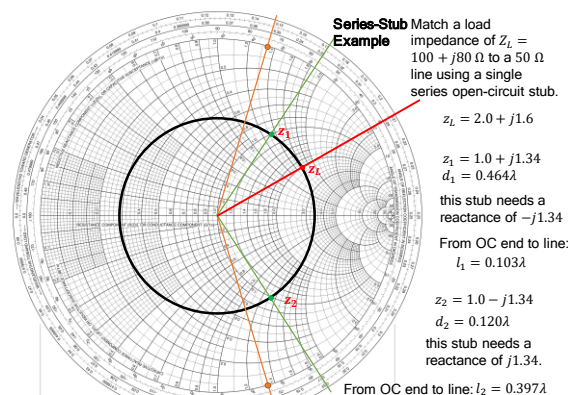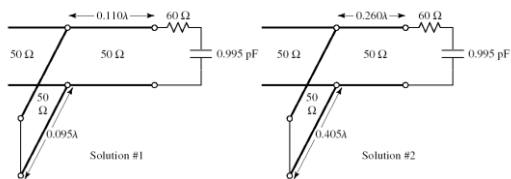

Prof. Dr. Gökhan Çınar  
Autumn 2016

ESKİŞEHİR OSMANGAZI UNIVERSITY  
ELECTRICAL AND ELECTRONICS ENGINEERING

### Single Stub Series Example

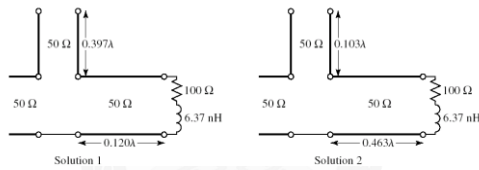

Prof. Dr. Gökhan Çınar  
Autumn 2016

ESKİŞEHİR OSMANGAZİ UNIVERSITY  
ELECTRICAL AND ELECTRONICS ENGINEERING



### Single Stub Exercise 1

A load impedance  $Z_L = 100 + j80\ \Omega$  is to be matched to a  $75\ \Omega$  line using a single shunt-stub tuner. Find two designs using open-circuited stubs.

Repeat the problem for short-circuited stubs.

Prof. Dr. Gökhan Çınar  
Autumn 2016

ESKİŞEHİR OSMANGAZİ UNIVERSITY  
ELECTRICAL AND ELECTRONICS ENGINEERING



### Single Stub Exercise 2

A load impedance  $Z_L = 90 + j60\ \Omega$  is to be matched to a  $75\ \Omega$  line using a single series-stub tuner. Find two designs using short-circuited stubs.

Repeat the problem for open-circuited stubs.

Prof. Dr. Gökhan Çınar  
Autumn 2016

ESKİŞEHİR OSMANGAZİ UNIVERSITY  
ELECTRICAL AND ELECTRONICS ENGINEERING

