SIMPLE RESISTIVE CIRCUITS

OSMAN PARLAKTUNA Osmangazi University Eskişehir, TURKEY www.ogu.edu.tr/~oparlak

RESISTORS IN SERIES

Elements are connected in series when they carry the same current.



Sum of the five resistors can be replaced by a single resistor as $R_{eq} = R_1 + R_2 + R_3 + R_4 + R_5$ and $V_s = iR_{eq} R_{eq}$ is the equivalent resistance of series resistor. In genera,1 if k resistors are connected in series, then

$$R_{eq} = \sum_{i=1}^{k} R_i = R_1 + R_2 + \dots + R_k$$

Circuit Analysis I

Osman Parlaktuna

EQUIVALENT CIRCUITS

Two circuits are said to be equivalent if they have the same voltage and current values at the corresponding terminals.



Replacing five resistors by their equivalent R_{eq}



These two circuits are equivalent because they have the same voltage current relationship at their input terminals.

Circuit Analysis I

Osman Parlaktuna Fall 2004

RESISTORS IN PARALLEL



 $V_{s}(+)^{i_{s}}R_{1} \stackrel{\downarrow}{\underset{>}{>}} R_{2} \stackrel{\downarrow}{\underset{>}{>}} R_{3} \stackrel{\downarrow}{\underset{>}{>}} R_{4} \stackrel{\downarrow}{\underset{>}{>}} H_{4}$ Elements are said to be in **parallel** when they have the same voltage across their Elements are said to be in **parallel** when terminals.

The KCL equation is : $i_s = i_1 + i_2 + i_3 + i_4$



Circuit Analysis I

Osman Parlaktuna



For k resistors connected in parallel, the equivalent resistance is

$$\frac{1}{R_{eq}} = \sum_{i=1}^{k} \frac{1}{R_i} = \frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_k}$$

For 2 resistors in parallel, we may use the following simple equation

$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} = \frac{R_1 + R_2}{R_1 R_2}$$
$$R_{eq} = \frac{R_1 R_2}{R_1 R_2}$$

Circuit Analysis I

Osman Parlaktuna



Find i_s , i_1 , and i_2 in the circuit.

Finding the equivalent resistance of the three resistor in the right side.



$$R_{eq} = (3+6)||(18) = \frac{(9)(18)}{9+18} = 6\Omega$$

$$i_{s} = \frac{120}{4+6} = 12A \implies v_{1} = (12)6 = 72V$$
$$i_{1} = \frac{v_{1}}{18} = \frac{72}{18} = 4A, \quad i_{2} = \frac{v_{1}}{9} = \frac{72}{9} = 8A$$

Circuit Analysis I

Osman Parlaktuna

THE VOLTAGE-DIVIDER CIRCUIT

Some times, in electrical circuits, developing more than one voltage level from a single supply is necessary. One way of doing this is by using a **voltage-divider circuit**.



$$v_s = iR_1 + iR_2 \Longrightarrow i = \frac{v_s}{R_1 + R_2}$$
$$v_1 = iR_1 = \frac{R_1}{R_1 + R_2} v_s$$
$$v_2 = iR_2 = \frac{R_2}{R_1 + R_2} v_s$$

Circuit Analysis I

Osman Parlaktuna

LOADING



A load in any circuit consists of one or more circuit elements that draw power from the circuit.R_L acts as a load on the voltage-^L divider circuit. With the R_I, V₂ becomes

$$V_{2} = \frac{R_{eq}}{R_{1} + R_{eq}} V_{s} \qquad R_{eq} = \frac{R_{2}R_{L}}{R_{2} + R_{L}}$$
$$V_{2} = \frac{R_{2}}{R_{1}[1 + (R_{2} / R_{L})] + R_{2}} v_{s}$$

The voltage V_2 with the load is smaller than the voltage V_2 of the unloaded circuit.

Circuit Analysis I

Osman Parlaktuna



 $R_{1=}25$ KΩ, $R_{2}=100$ KΩ. If the resistors have a tolerance of ±10%, find the minimum and maximum value of V_{2}

$$V_2 = \frac{R_2}{R_1 + R_2} 100$$

The maximum value of V_2 occurs when R_2 is 10% high and R_1 is 10% low, and the minimum value of V_2 occurs when R_2 is 10% low and R_1 is 10% high.

$$V_2(\max) = \frac{110}{22.5 + 110} 100 = 83.02V$$
$$V_2(\min) = \frac{90}{27.5 + 90} 100 = 76.60V$$

Circuit Analysis I

Osman Parlaktuna

THE CURRENT-DIVIDER CIRCUIT



The current divides between two resistors in parallel such that the current in one resistor equals the current entering the parallel pair multiplied by the other resistance and divided by the sum of the resistors.

Circuit Analysis I

Osman Parlaktuna





Find the power dissipated in the 6Ω resistor.

$$R_{eq1} = (4||6) + 1.6 = 4\Omega$$

$$i_o = \frac{16}{4+16} 10 = 8A$$
$$i_{6\Omega} = \frac{4}{4+6} 8 = 3.2A$$
$$p_{6\Omega} = (3.2)^2 (6) = 61.44W$$

Circuit Analysis I

Osman Parlaktuna

MEASURING VOLTAGE AND CURRENT

An **ammeter** is an instrument designed to measure current; it is placed in series with the circuit element whose current is being measured. A voltmeter is an instrument designed to measure voltage; it is placed in parallel with the element whose voltage is being measured.



An ideal ammeter has an equivalent resistance of 0Ω , and an ideal voltmeter has an infinite equivalent resistance.

Circuit Analysis I

Osman Parlaktuna

THE WHEATSTONE BRIDGE



The Wheatstone bridge circuit is used to measure resistances in the range of 1Ω to $1M\Omega$.

To find the value of R_x , R_3 is adjusted until $i_g=0$. Then, $i_1=i_3$ and $i_2=i_x$ $i_3R_3=i_xR_x$ and $i_1R_1=i_2R_2$ $i_1R_3=i_2R_x$

$$\frac{R_3}{R_1} = \frac{R_x}{R_2} \Longrightarrow R_x = \frac{R_2}{R_1} R_3$$

Circuit Analysis I

Osman Parlaktuna

$\begin{array}{l} \textbf{DELTA-TO-WYE} (\triangle \text{ TO Y}) \\ \textbf{EQUIVALENT CIRCUITS} \end{array}$



This circuit cannot be reduced to a single resistance circuit across the terminals of the battery is restricted to simple series or parallel resistance procedures. This circuit can be reduced to a single resistance using delta-to-wye transformation.



Circuit Analysis I



$$R_{ab} = \frac{R_c (R_a + R_b)}{R_a + R_b + R_c} = R_1 + R_2$$

$$R_{bc} = \frac{R_a (R_b + R_c)}{R_a + R_b + R_c} = R_2 + R_3 \implies$$

$$R_{ca} = \frac{R_b (R_a + R_c)}{R_a + R_b + R_c} = R_1 + R_3$$

$$R_{1} = \frac{R_{b}R_{c}}{R_{a} + R_{b} + R_{c}}$$

$$R_{2} = \frac{R_{c}R_{a}}{R_{a} + R_{b} + R_{c}}$$

$$R_{3} = \frac{R_{a}R_{b}}{R_{a} + R_{b} + R_{c}}$$

$$R_{a} = \frac{R_{1}R_{2} + R_{1}R_{3} + R_{2}R_{3}}{R_{1}}$$

$$R_{b} = \frac{R_{1}R_{2} + R_{1}R_{3} + R_{2}R_{3}}{R_{2}}$$

$$R_{c} = \frac{R_{1}R_{2} + R_{1}R_{3} + R_{2}R_{3}}{R_{3}}$$

Circuit Analysis I

Osman Parlaktuna



25Ω

Find the power supplied by the 40V source.

Replacing the upper Δ by its Y equivalent

$$R_{1} = \frac{(100)125}{100 + 125 + 25} = 50\Omega$$
$$R_{2} = \frac{(25)125}{100 + 125 + 25} = 12.5\Omega$$
$$R_{3} = \frac{(100)25}{100 + 125 + 25} = 10\Omega$$

Circuit Analysis I

250

100Ω

Osman Parlaktuna



Circuit Analysis I

Osman Parlaktuna