

# **THEVENIN AND NORTON EQUIVALENTS**



**OSMAN PARLAKTUNA  
OSMANGAZİ UNIVERSITY  
ESKİŞEHİR, TURKEY**

**[www.ogu.edu.tr/~oparlak](http://www.ogu.edu.tr/~oparlak)**

# THEVENIN EQUIVALENT




- At times in circuit analysis, we want to determine terminal behavior of a circuit.
- Thevenin and Norton equivalents are circuit simplification techniques that focus on terminal behavior.
- The Thevenin equivalent circuit is an independent voltage source  $V_{TH}$  in series with a resistor  $R_{TH}$  which replaces an interconnection of sources and resistors.

- 
- This series combination is equivalent to the original circuit such that if we connect a load across the terminals of each circuit, we get the same voltage and current at the terminals of the load.
  - To calculate the Thevenin voltage  $V_{TH}$ , we simply calculate the open-circuit voltage at the terminals of the original circuit.

- 
- If we place a short circuit across the terminals of the Thevenin equivalent circuit, the short-circuit current is  $i_{sc} = V_{TH}/R_{TH}$ .
  - This short-circuit current must be identical to the short-circuit current in the original network. Thus,  $R_{TH} = V_{TH}/i_{sc}$

# EXAMPLE

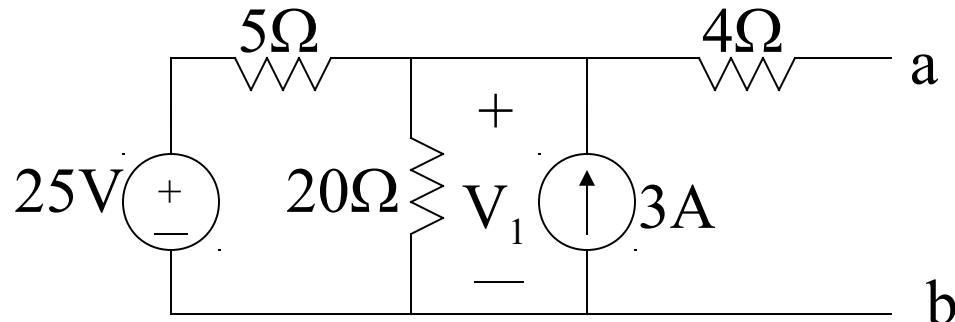


Find the Thevenin equivalent of the circuit at the terminals a and b.

$$V_{TH} = V_{ab}$$

$$\frac{V_1 - 25}{5} + \frac{V_1}{20} - 3 = 0 \Rightarrow V_1 = 32V$$


$$V_{TH} = V_1 = 32V$$

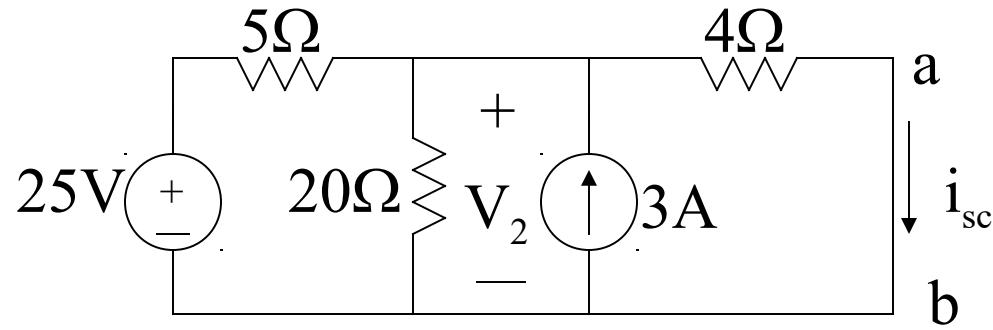

$$\frac{V_2 - 25}{5} + \frac{V_2}{20} - 3 + \frac{V_2}{4} = 0$$

$$V_2 = 16V \quad i_{sc} = \frac{16}{4} = 4A$$

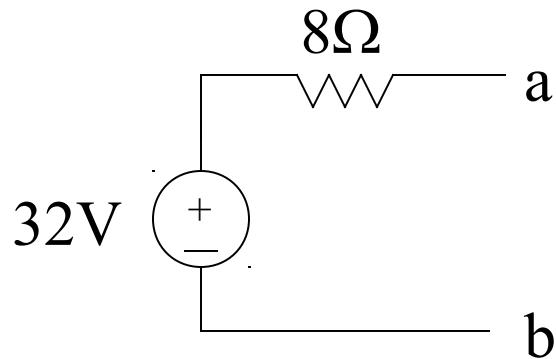
$$R_{TH} = \frac{V_{TH}}{i_{sc}} = \frac{32}{4} = 8\Omega$$



Thevenin Equivalent
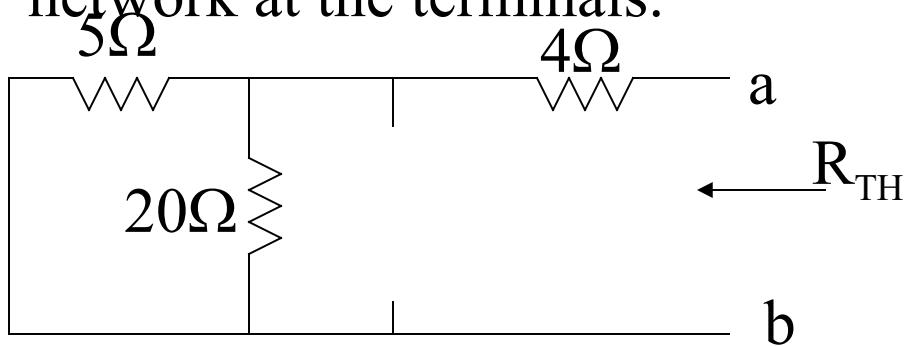
# CALCULATING $R_{TH}$


When the circuit has only independent sources, it is possible to calculate  $R_{TH}$  by killing the sources. A voltage source is killed by short circuiting and a current source is killed by open circuiting. Then  $R_{TH}$  is the equivalent resistance of the dead network at the terminals.




$$R_{TH} = (5||20) + 4 = 8\Omega$$
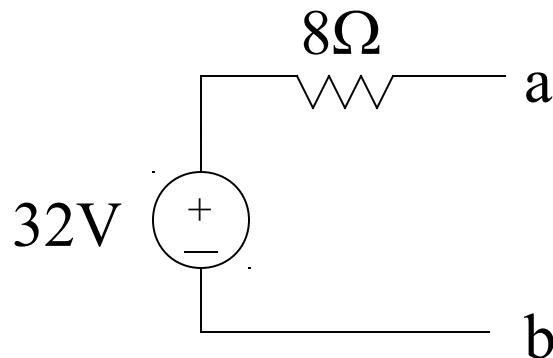
# NORTON EQUIVALENT

A **Norton Equivalent Circuit** consists of an independent current source in parallel with the Norton equivalent resistance. It can be derived from a Thevenin equivalent circuit simply by making a source transformation.




Thevenin equivalent

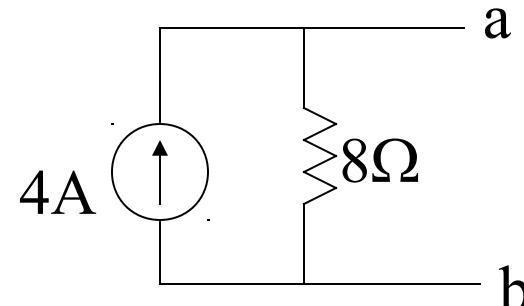

Norton equivalent


# EXAMPLE

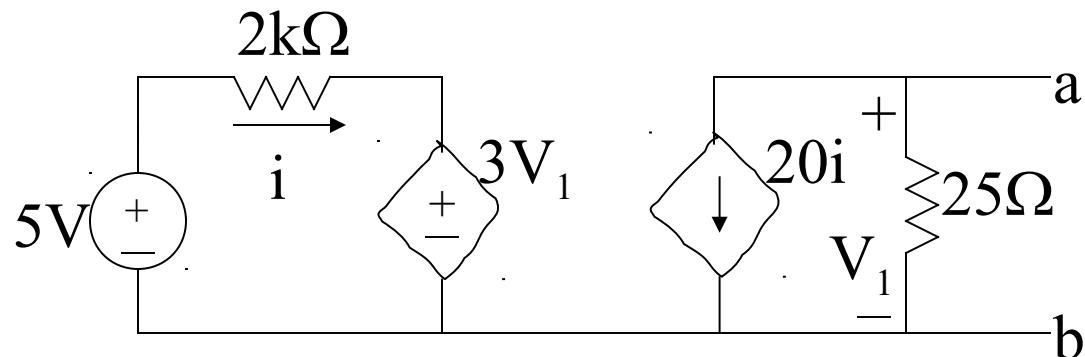

$$V_{TH} = V_{ab} = (-20i)(25) = -500i$$

$$i = \frac{5 - 3V_1}{2000} = \frac{5 - 3V_{TH}}{2000}$$


$$V_{TH} = -5V$$

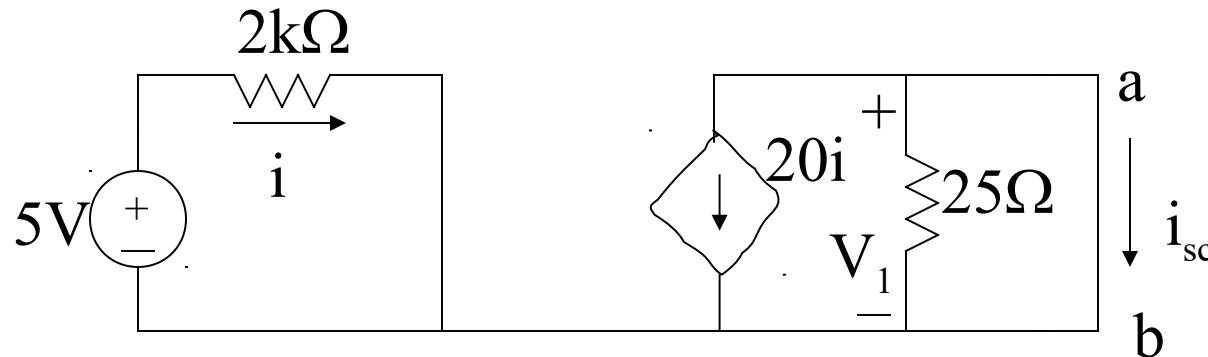



$$i_{sc} = -20i \quad i = \frac{5}{2000} = 2.5mA$$

$$i_{sc} = -20(2.5) = -50mA$$
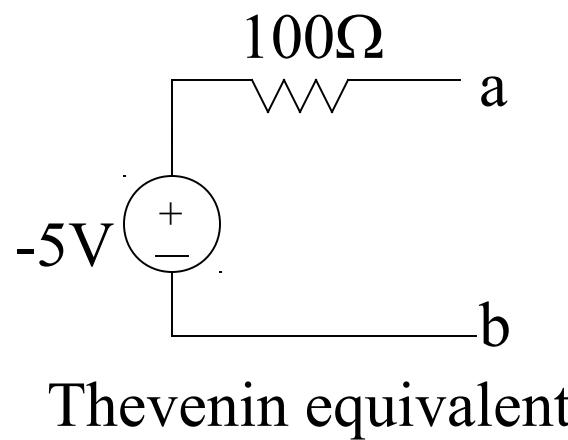
$$R_{TH} = \frac{V_{TH}}{i_{sc}} = \frac{-5}{-50 \times 10^{-3}} = 100\Omega$$



# NO INDEPENDENT SOURCE CASE

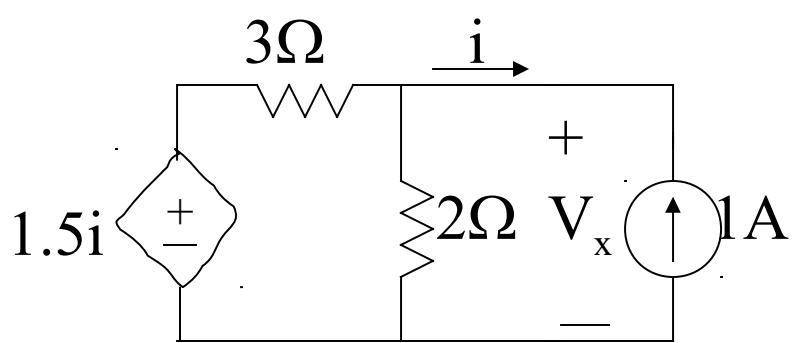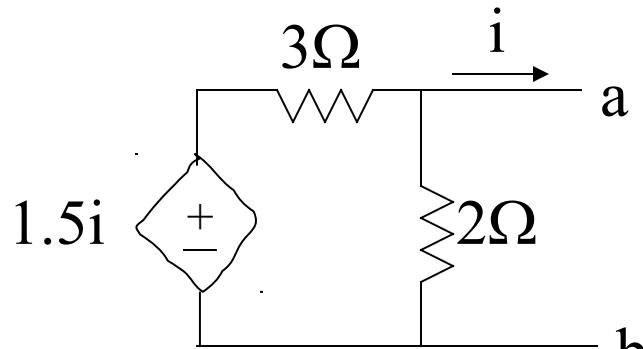


$0.6\Omega$    
Thevenin equivalent

Since there is no independent source, both  $V_{TH}$  and  $i_{sc}$  are zero. In this case, the equivalent circuit is only a resistor equal to  $R_{TH}$ . To determine  $R_{TH}$ , we connect a source (voltage or current) across the terminals. The value of the source is not important.


$$\frac{V_x - 1.5(-1)}{3} + \frac{V_x}{2} - 1 = 0$$

$$V_x = 0.6V \Rightarrow R_{TH} = \frac{0.6}{1} = 0.6\Omega$$

# EXAMPLE

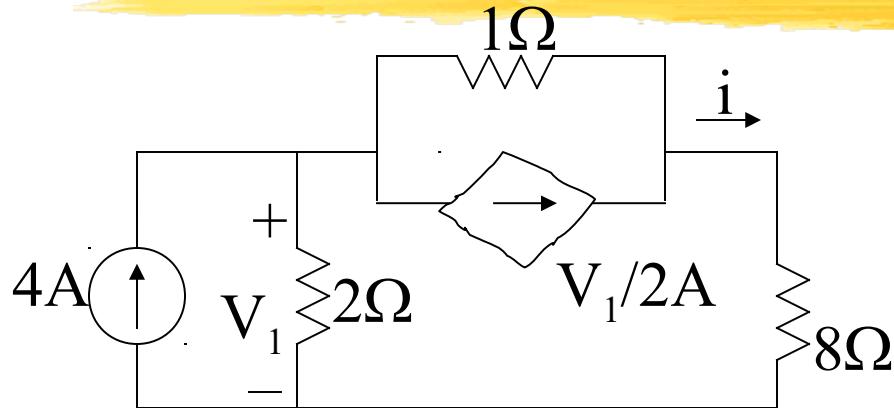


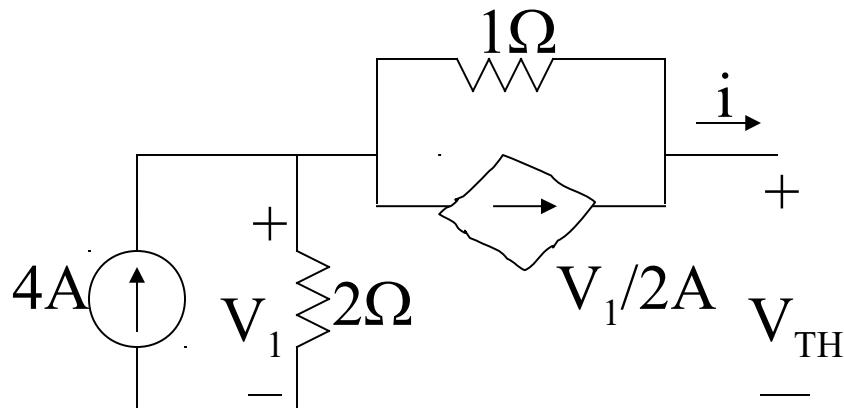Find  $i$  by using the Norton equivalent circuit seen by  $8\Omega$  resistor.



$$V_1 = 4(2) = 8V$$

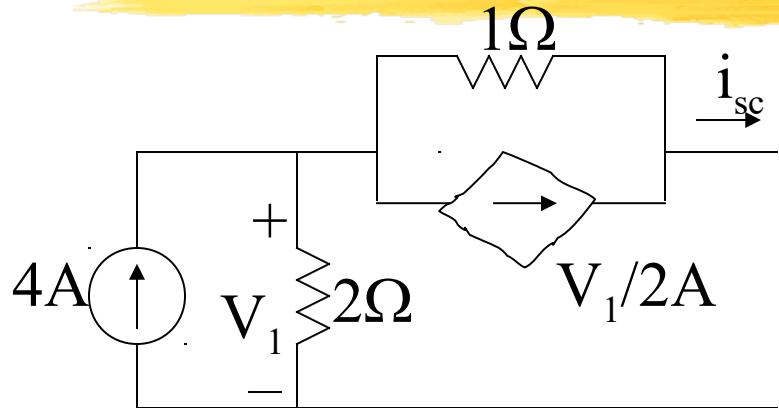
$$V_{TH} = 1\left(\frac{V_1}{2}\right) + V_1 = 4 + 8 = 12V$$



$$-4 + \frac{V_1}{2} + \frac{V_1}{2} + \frac{V_1}{1} = 0$$



$$V_1 = 2V \Rightarrow i_{sc} = \frac{V_1}{2} + \frac{V_1}{1} = 1 + 2 = 3A$$
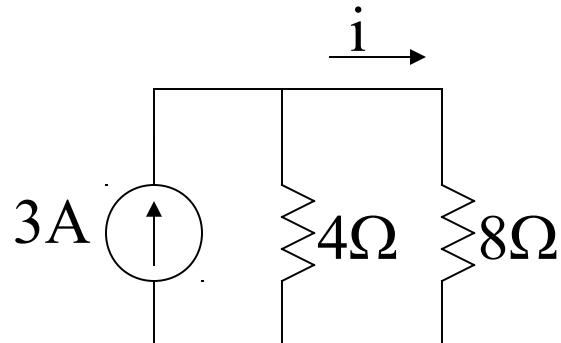
$$R_{TH} = \frac{V_{TH}}{i_{sc}} = \frac{12}{3} = 4\Omega$$




$$i = \frac{4}{4+8} 3 = 1A$$

# EXAMPLE

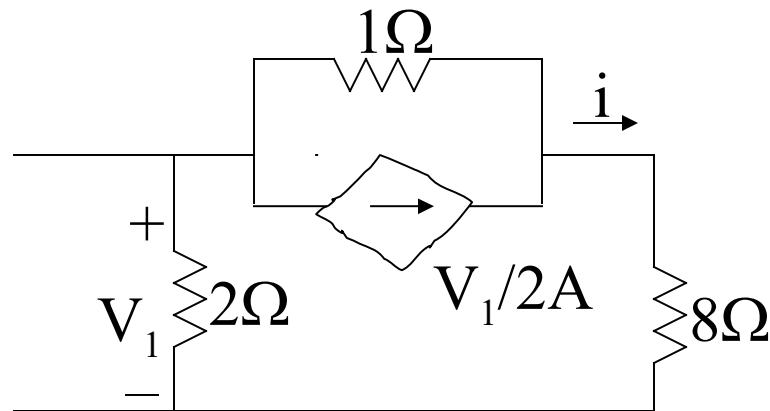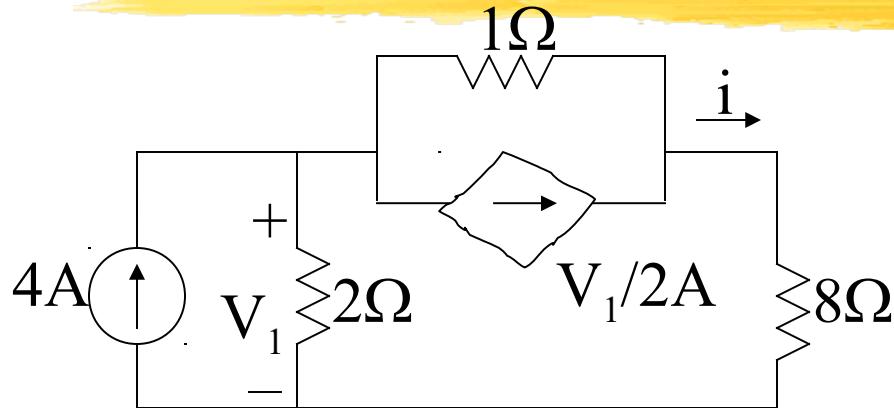

Find  $V_1$  by using the Thevenin equivalent seen by 4A current source.

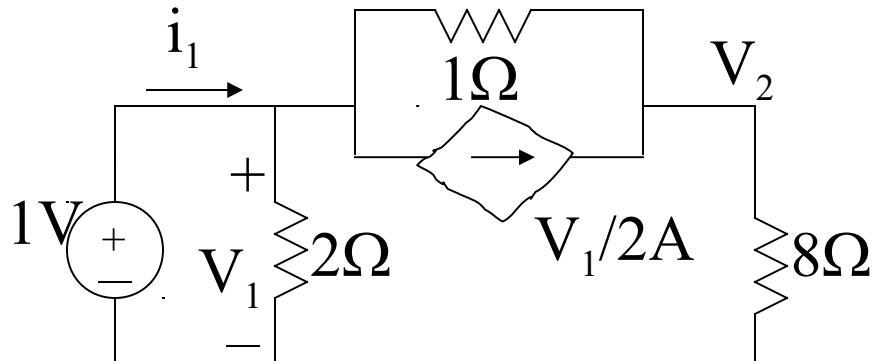When we remove the current source to find  $V_{TH}$ , no independent source is present in the circuit. Therefore the Thevenin equivalent is only  $R_{TH}$ .




Connect a 1V voltage source  
and determine the current  
through it.

$$\frac{V_2 - 1}{1} - \frac{V_1}{2} + \frac{V_2}{8} = 0 \Rightarrow V_2 = \frac{4}{3}V$$

$$-i_1 + \frac{1}{2} + \frac{1}{2} + \frac{1 - \frac{4}{3}}{1} = 0 \Rightarrow i_1 = \frac{2}{3}A$$


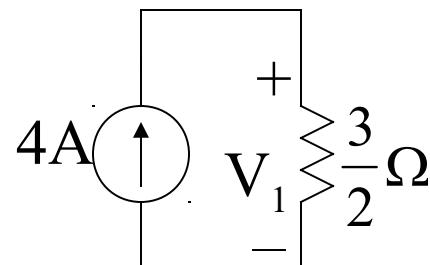
$$R_{TH} = \frac{1}{i_1} = \frac{3}{2}\Omega$$



$$V_1 = 4 \left( \frac{3}{2} \right) = 6V$$
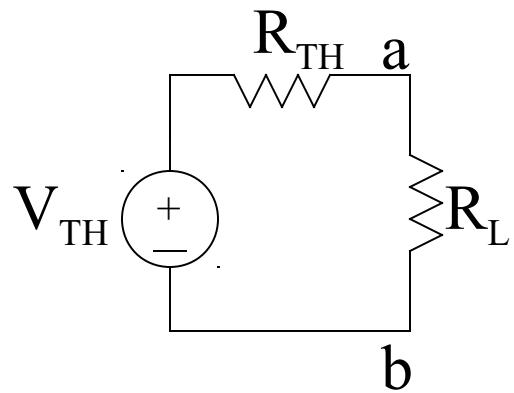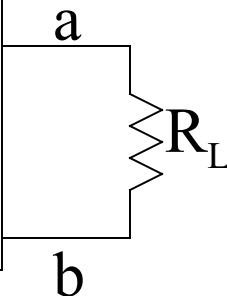
# MAXIMUM POWER TRANSFER

Resistive network  
with independent  
and dependent  
sources



Determine the value of  $R_L$  that permits maximum power delivery to  $R_L$ .




$$p = i^2 R_L = \left( \frac{V_{TH}}{R_{TH} + R_L} \right)^2 R_L$$

$$\frac{dp}{dR_L} = V_{TH}^2 \left[ \frac{(R_{TH} + R_L)^2 - R_L \cdot 2(R_{TH} + R_L)}{(R_{TH} + R_L)^4} \right]$$

$$(R_{TH} + R_L)^2 = R_L \cdot 2(R_{TH} + R_L)$$

$$R_L = R_{TH} \Rightarrow p_{\max} = \frac{V_{TH}^2 R_L}{(2R_L)^2} = \frac{V_{TH}^2}{4R_L}$$


# EXAMPLE

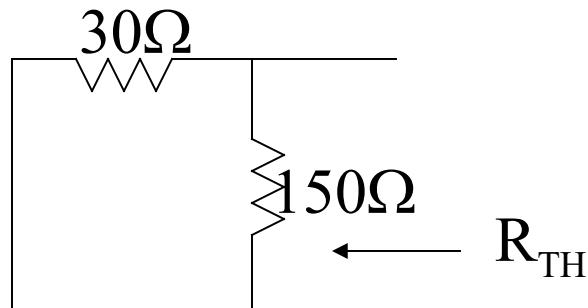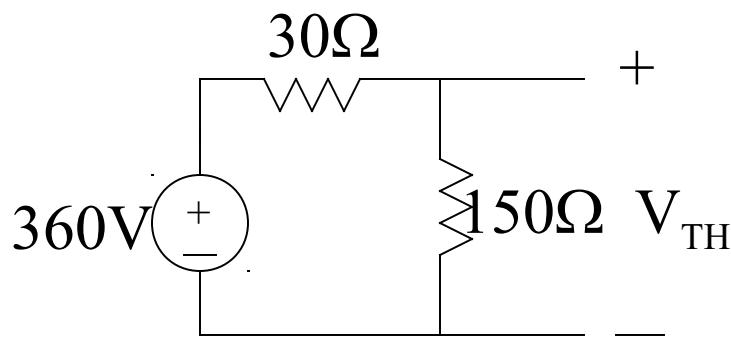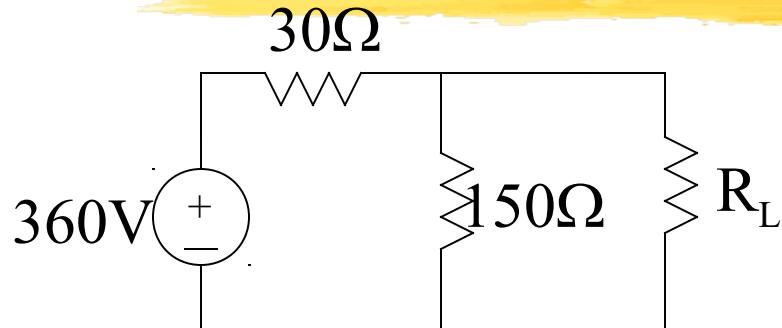

Determine  $R_L$  for maximum power transfer. When  $R_L$  is adjusted for maximum power transfer, what percentage of the power delivered by 360V source reaches  $R_L$ ?

$$V_{TH} = \frac{150}{150 + 30} 360 = 300V$$

$$R_{TH} = 30\parallel 150 = 25\Omega$$

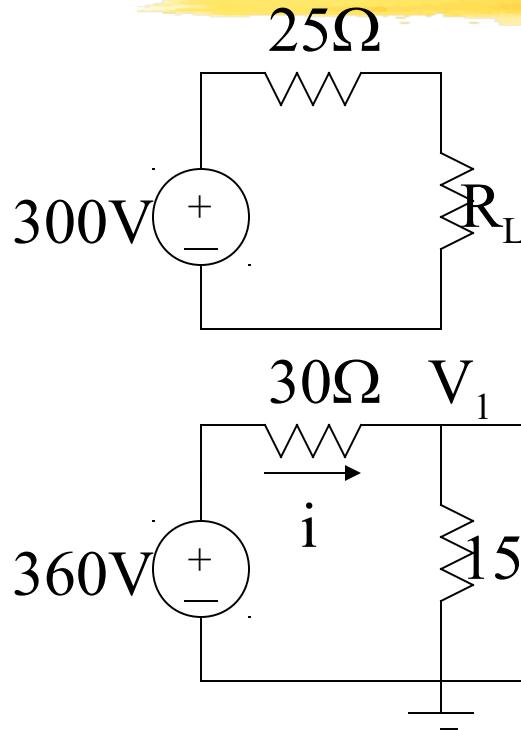

For maximum power transfer  $R_L = 25\Omega$ .

$$P_{\max} = \frac{(300)^2}{4(25)} = 900W$$

$$V_1 = \frac{(150||25)}{(150||25) + 30} 360 = 150V$$

$$i = \frac{360 - 150}{30} = 7A$$

$$P_{360V} = (-7)360 = -2520W$$

$$\frac{900}{2520} \times 100 = 35.71\%$$