
Logic and Computer Design Fundamentals

Chapter 6 – Sequential Circuits

Part 1 – Storage Elements and Sequential Circuit Analysis

Charles Kime & Thomas Kaminski

© 2004 Pearson Education, Inc.

[Terms of Use](#)

(Hyperlinks are active in View Show mode)


Overview

- **Part 1 - Storage Elements and Analysis**
 - Introduction to sequential circuits
 - Types of sequential circuits
 - Storage elements
 - Latches
 - Flip-flops
 - Sequential circuit analysis
 - State tables
 - State diagrams
 - Circuit and System Timing
- **Part 2 - Sequential Circuit Design**
 - Specification
 - Assignment of State Codes
 - Implementation

Introduction to Sequential Circuits

■ A Sequential circuit contains:

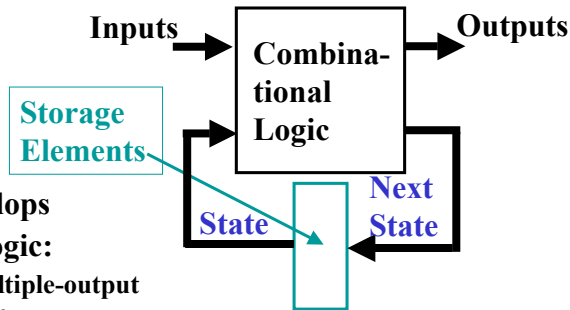- **Storage elements:**
Latches or Flip-Flops
- **Combinatorial Logic:**
 - Implements a multiple-output switching function
 - Inputs are signals from the outside.
 - Outputs are signals to the outside.
 - Other inputs, State or Present State, are signals from storage elements.
 - The remaining outputs, Next State are inputs to storage elements.




Logic and Computer Design Fundamentals
PowerPoint® Slides
© 2004 Pearson Education, Inc.

Chapter 6 - Part 1 3

Introduction to Sequential Circuits

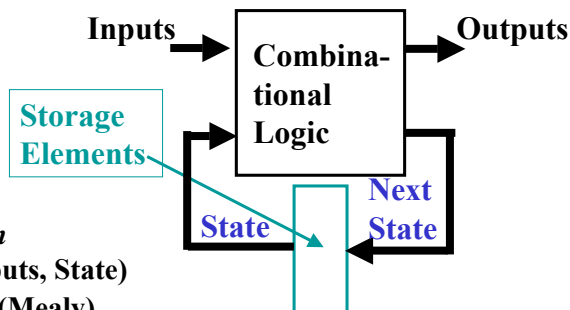- **Combinatorial Logic**
 - *Next state function*
 $\text{Next State} = f(\text{Inputs}, \text{State})$
 - *Output function (Mealy)*
 $\text{Outputs} = g(\text{Inputs}, \text{State})$
 - *Output function (Moore)*
 $\text{Outputs} = h(\text{State})$
- **Output function type depends on specification and affects the design significantly**



Logic and Computer Design Fundamentals
PowerPoint® Slides
© 2004 Pearson Education, Inc.

Chapter 6 - Part 1 4

Types of Sequential Circuits


- Depends on the times at which:
 - storage elements observe their inputs, and
 - storage elements change their state
- Synchronous
 - Behavior defined from knowledge of its signals at discrete instances of time
 - Storage elements observe inputs and can change state only in relation to a timing signal (clock pulses from a clock)
- Asynchronous
 - Behavior defined from knowledge of inputs at any instant of time and the order in continuous time in which inputs change
 - If clock just regarded as another input, all circuits are asynchronous!
 - Nevertheless, the synchronous abstraction makes complex designs tractable!

Discrete Event Simulation

- In order to understand the time behavior of a sequential circuit we use discrete event simulation.
- Rules:
 - Gates modeled by an ideal (instantaneous) function and a fixed gate delay
 - Any change in input values is evaluated to see if it causes a change in output value
 - Changes in output values are scheduled for the fixed gate delay after the input change
 - At the time for a scheduled output change, the output value is changed along with any inputs it drives

Simulated NAND Gate

 - Example: A 2-Input NAND gate with a 0.5 ns. delay:



- Assume A and B have been 1 for a long time
- At time $t=0$, A changes to a 0 at $t=0.8$ ns, back to 1.



t (ns)	A	B	F(I)	F	Comment
$-\infty$	1	1	0	0	A=B=1 for a long time
0	$1 \Rightarrow 0$	1	$1 \Leftarrow 0$	0	F(I) changes to 1
0.5	0	1	1	$1 \Leftarrow 0$	F changes to 1 after a 0.5 ns delay
0.8	$1 \Leftarrow 0$	1	$1 \Rightarrow 0$	1	F(Instantaneous) changes to 0
0.13	1	1	0	$1 \Rightarrow 0$	F changes to 0 after a 0.5 ns delay

Logic and Computer Design Fundamentals
PowerPoint® Slides
© 2004 Pearson Education, Inc.

Chapter 6 - Part 1 7

Gate Delay Models

  - Suppose gates with delay n ns are represented for $n = 0.2$ ns, $n = 0.4$ ns, $n = 0.5$ ns, respectively:



Logic and Computer Design Fundamentals
PowerPoint® Slides
© 2004 Pearson Education, Inc.


Chapter 6 - Part 1 8

Circuit Delay Model

- Consider a simple 2-input multiplexer:

- With function:

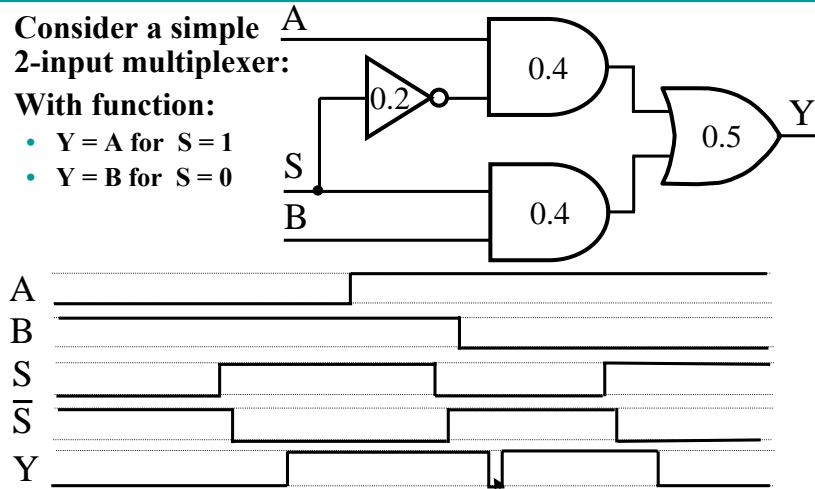- $Y = A$ for $S = 1$
- $Y = B$ for $S = 0$



- “Glitch” is due to delay of inverter

Logic and Computer Design Fundamentals
PowerPoint® Slides
© 2004 Pearson Education, Inc.

Chapter 6 - Part 1 9


Storing State

- What if A connected to Y?

- Circuit becomes:

- With function:

 - $Y = B$ for $S = 1$, and $Y(t)$ dependent on $Y(t - 0.9)$ for $S = 0$



- The simple combinational circuit has now become a sequential circuit because its output is a function of a time sequence of input signals!

Logic and Computer Design Fundamentals
PowerPoint® Slides
© 2004 Pearson Education, Inc.

Y is stored value in shaded area

Chapter 6 - Part 1 10

Storing State (Continued)


- Simulation example as input signals change with time. Changes occur every 100 ns, so that the tenths of ns delays are negligible.

Time	B	S	Y	Comment
↓	1	0	0	Y “remembers” 0
	1	1	1	Y = B when S = 1
	1	0	1	Now Y “remembers” B = 1 for S = 0
	0	0	1	No change in Y when B changes
	0	1	0	Y = B when S = 1
	0	0	0	Y “remembers” B = 0 for S = 0
	1	0	0	No change in Y when B changes

- Y represent the state of the circuit, not just an output.

Storing State (Continued)

 - Suppose we place an inverter in the “feedback path.”




- The following behavior results:

- The circuit is said to be unstable.
- For S = 0, the circuit has become what is called an *oscillator*. Can be used as crude clock.

B	S	Y	Comment
0	1	0	Y = B when S = 1
1	1	1	
1	0	1	Now Y “remembers” A
1	0	0	Y, 1.1 ns later
1	0	1	Y, 1.1 ns later
1	0	0	Y, 1.1 ns later

Basic (NAND) $\bar{S} - \bar{R}$ Latch

 - “Cross-Coupling” two NAND gates gives the $\bar{S} - \bar{R}$ Latch:



- Which has the time sequence behavior:


- $S = 0, R = 0$ is forbidden as input pattern

Time ↓

R	S	Q	\bar{Q}	Comment
1	1	?	?	Stored state unknown
1	0	1	0	“Set” Q to 1
1	1	1	0	Now Q “remembers” 1
0	1	0	1	“Reset” Q to 0
1	1	0	1	Now Q “remembers” 0
0	0	1	1	Both go high
1	1	?	?	Unstable!

Basic (NOR) S – R Latch

 - Cross-coupling two NOR gates gives the S – R Latch:




- Which has the time sequence behavior:

Time ↓

R	S	Q	\bar{Q}	Comment
0	0	?	?	Stored state unknown
0	1	1	0	“Set” Q to 1
0	0	1	0	Now Q “remembers” 1
1	0	0	1	“Reset” Q to 0
0	0	0	1	Now Q “remembers” 0
1	1	0	0	Both go low
0	0	?	?	Unstable!

Clocked S - R Latch

 - Adding two NAND gates to the basic \overline{S} - \overline{R} NAND latch gives the clocked S - R latch:



- Has a time sequence behavior similar to the basic S-R latch except that the S and R inputs are only observed when the line C is high.
- C means “control” or “clock”.

Clocked S - R Latch (continued)

- The Clocked S-R Latch can be described by a table:


S	C	R	Q(t)	S	R	Q(t+1)	Comment
0	0	0	0	0	0	0	No change
0	0	1	0	0	1	0	Clear Q
0	1	0	0	1	0	1	Set Q
0	1	1	0	1	1	???	Indeterminate
1	0	0	1	0	0	1	No change
1	0	1	1	0	1	0	Clear Q
1	1	0	1	1	0	1	Set Q
1	1	1	1	1	1	???	Indeterminate

- The table describes what happens after the clock [at time (t+1)] based on:


- current inputs (S,R) and
- current state Q(t).

D Latch

 - Adding an inverter to the S-R Latch, gives the D Latch:
- Note that there are no “indeterminate” states!



The graphic symbol for a D Latch is:

 

Q	D	Q(t+1)	Comment
0	0	0	No change
0	1	1	Set Q
1	0	0	Clear Q
1	1	1	No Change

Flip-Flops

- The latch timing problem
- Master-slave flip-flop
- Edge-triggered flip-flop
- Standard symbols for storage elements
- Direct inputs to flip-flops
- Flip-flop timing


The Latch Timing Problem


- In a sequential circuit, paths may exist through combinational logic:
 - From one storage element to another
 - From a storage element back to the same storage element
- The combinational logic between a latch output and a latch input may be as simple as an interconnect
- For a clocked D-latch, the output Q depends on the input D whenever the clock input C has value 1

Logic and Computer Design Fundamentals
PowerPoint® Slides
© 2004 Pearson Education, Inc.

Chapter 6 - Part 1 19

The Latch Timing Problem (continued)

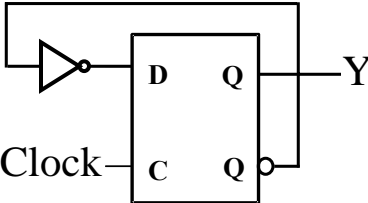- Consider the following circuit:

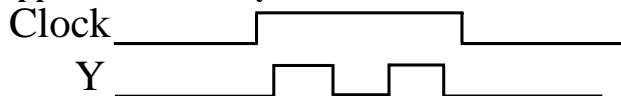The circuit diagram shows a clocked D-latch. The input D is connected to the output Q through an inverter. The clock input C is connected to the output Q. The output is labeled Y.
- Suppose that initially $Y = 0$.

The timing diagram shows two signals: Clock and Y. Clock is a square wave that is high for a period of time. Y is a square wave that changes state (from 0 to 1 and back to 0) whenever Clock is high.
- As long as $C = 1$, the value of Y continues to change!
- The changes are based on the delay present on the loop through the connection from Y back to Y .
- This behavior is clearly unacceptable.
- Desired behavior: Y changes only once per clock pulse

Logic and Computer Design Fundamentals
PowerPoint® Slides
© 2004 Pearson Education, Inc.


Chapter 6 - Part 1 20

The Latch Timing Problem (continued)

- A solution to the latch timing problem is to break the closed path from Y to Y within the storage element
- The commonly-used, path-breaking solutions replace the clocked D-latch with:
 - a master-slave flip-flop
 - an edge-triggered flip-flop

S-R Master-Slave Flip-Flop

- Consists of two clocked S-R latches in series with the clock on the second latch inverted
- The input is observed by the first latch with $C = 1$
- The output is changed by the second latch with $C = 0$
- The path from input to output is broken by the difference in clocking values ($C = 1$ and $C = 0$).
- The behavior demonstrated by the example with D driven by Y given previously is prevented since the clock must change from 1 to 0 before a change in Y based on D can occur.

 

Flip-Flop Problem


- The change in the flip-flop output is delayed by the pulse width which makes the circuit slower or
- S and/or R are permitted to change while $C = 1$
 - Suppose $Q = 0$ and S goes to 1 and then back to 0 with R remaining at 0
 - The master latch sets to 1
 - A 1 is transferred to the slave
 - Suppose $Q = 0$ and S goes to 1 and back to 0 and R goes to 1 and back to 0
 - The master latch sets and then resets
 - A 0 is transferred to the slave
 - This behavior is called *1s catching*

Flip-Flop Solution

- Use edge-triggering instead of master-slave
- An *edge-triggered* flip-flop ignores the pulse while it is at a constant level and triggers only during a transition of the clock signal
- Edge-triggered flip-flops can be built directly at the electronic circuit level, or
- A master-slave D flip-flop which also exhibits edge-triggered behavior can be used.

Edge-Triggered D Flip-Flop

- The edge-triggered D flip-flop is the same as the master-slave D flip-flop
- It can be formed by:
 - Replacing the first clocked S-R latch with a clocked D latch or
 - Adding a D input and inverter to a master-slave S-R flip-flop
- The delay of the S-R master-slave flip-flop can be avoided since the 1s-catching behavior is not present with D replacing S and R inputs
- The change of the D flip-flop output is associated with the negative edge at the end of the pulse
- It is called a *negative-edge triggered flip-flop*

 


Logic and Computer Design Fundamentals
PowerPoint® Slides
© 2004 Pearson Education, Inc.

Chapter 6 - Part 1 25

Positive-Edge Triggered D Flip-Flop

 
- Formed by adding inverter to clock input
- Q changes to the value on D applied at the positive clock edge within timing constraints to be specified
- Our choice as the standard flip-flop for most sequential circuits



Logic and Computer Design Fundamentals
PowerPoint® Slides
© 2004 Pearson Education, Inc.

Chapter 6 - Part 1 26

Standard Symbols for Storage Elements

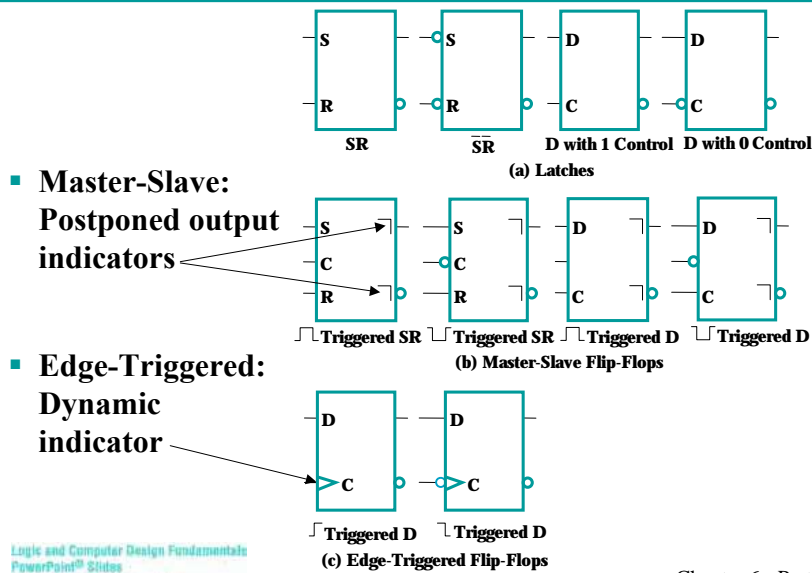


Logic and Computer Design Fundamentals
PowerPoint® Slides
© 2004 Pearson Education, Inc.

Chapter 6 - Part 1 27

Direct Inputs


- At power up or at reset, all or part of a sequential circuit usually is initialized to a known state before it begins operation
- This initialization is often done outside of the clocked behavior of the circuit, i.e., asynchronously.
- Direct R and/or S inputs that control the state of the latches within the flip-flops are used for this initialization.
- For the example flip-flop shown
 - 0 applied to \overline{R} resets the flip-flop to the 0 state
 - 0 applied to \overline{S} sets the flip-flop to the 1 state

 

Logic and Computer Design Fundamentals
PowerPoint® Slides
© 2004 Pearson Education, Inc.

Chapter 6 - Part 1 28

Flip-Flop Timing Parameters

 

(a) Pulse-triggered (positive pulse)

(b) Edge-triggered (negative edge)

Logic and Computer Design Fundamentals
PowerPoint® Slides
© 2004 Pearson Education, Inc.

Chapter 6 - Part 1 29

Flip-Flop Timing Parameters (continued)

- t_s - setup time
 - Master-slave - Equal to the width of the triggering pulse
 - Edge-triggered - Equal to a time interval that is generally much less than the width of the the triggering pulse
- t_h - hold time - Often equal to zero
- t_{px} - propagation delay
 - Same parameters as for gates except
 - Measured from clock edge that triggers the output change to the output change


Logic and Computer Design Fundamentals
PowerPoint® Slides
© 2004 Pearson Education, Inc.

Chapter 6 - Part 1 30

 Example 1 (from Fig. 6-17) (continued)


■ Boolean equations for the functions:

- $A(t+1) = A(t)x(t) + B(t)x(t)$
- $B(t+1) = \bar{A}(t)x(t)$
- $y(t) = \bar{x}(t)(B(t) + A(t))$



 Example 1(from Fig. 6-17) (continued)

■ Where in time are inputs, outputs and states defined?



State Table Characteristics

- **State table** – a multiple variable table with the following four sections:
 - *Present State* – the values of the state variables for each allowed state.
 - *Input* – the input combinations allowed.
 - *Next-state* – the value of the state at time (t+1) based on the present state and the input.
 - *Output* – the value of the output as a function of the present state and (sometimes) the input.
- **From the viewpoint of a truth table:**
 - the inputs are Input, Present State
 - and the outputs are Output, Next State

Example 1: State Table (from Fig. 6-17)

- The state table can be filled in using the next state and output equations: $A(t+1) = A(t)x(t) + B(t)x(t)$
 $= \overline{A}(t)x(t) \quad y(t)$
 $= x(t)(B(t) + A(t))$

Present State	Input	Next State	Output
A(t) B(t)	x(t)	A(t+1) B(t+1)	y(t)
0 0	0	0 0	0
0 0	1	0 1	0
0 1	0	0 0	1
0 1	1	1 1	0
1 0	0	0 0	1
1 0	1	1 0	0
1 1	0	0 0	1
1 1	1	1 0	0

Example 1: Alternate State Table

- 2-dimensional table that matches well to a K-map. Present state rows and input columns in Gray code order.

- $A(t+1) = A(t)x(t) + B(t)x(t)$
- $B(t+1) = \overline{A}(t)x(t)$
- $y(t) = \overline{x}(t)(B(t) + A(t))$

Present State A(t) B(t)	Next State		Output	
	x(t)=0 A(t+1)B(t+1)	x(t)=1 A(t+1)B(t+1)	x(t)=0 y(t)	x(t)=1 y(t)
0 0	0 0	0 1	0	0
0 1	0 0	1 1	1	0
1 0	0 0	1 0	1	0
1 1	0 0	1 0	1	0

Logic and Computer Design Fundamentals
PowerPoint® Slides
© 2004 Pearson Education, Inc.

Chapter 6 - Part 1 37

State Diagrams

- The sequential circuit function can be represented in graphical form as a state diagram with the following components:
 - A circle with the state name in it for each state
 - A directed arc from the Present State to the Next State for each state transition
 - A label on each directed arc with the Input values which causes the state transition, and
 - A label:
 - On each circle with the output value produced, or
 - On each directed arc with the output value produced.

Logic and Computer Design Fundamentals
PowerPoint® Slides
© 2004 Pearson Education, Inc.


Chapter 6 - Part 1 38

State Diagrams

- **Label form:**
 - **On circle with output included:**
 - state/output
 - Moore type output depends only on state
 - **On directed arc with the output included:**
 - input/output
 - Mealy type output depends on state and input

 Example 1: State Diagram

- **Which type?**
- **Diagram gets confusing for large circuits**
- **For small circuits, usually easier to understand than the state table**




Moore and Mealy Models


- Sequential Circuits or Sequential Machines are also called *Finite State Machines (FSMs)*. Two formal models exist:
- Moore Model**
 - Named after E.F. Moore.
 - Outputs are a function **ONLY** of states
 - Usually specified on the states.
- Mealy Model**
 - Named after G. Mealy
 - Outputs are a function of inputs AND states
 - Usually specified on the state transition arcs.
- In contemporary design, models are sometimes mixed Moore and Mealy

Moore and Mealy Example Diagrams

 - Mealy Model State Diagram**
maps inputs and state to outputs



 - Moore Model State Diagram**
maps states to outputs



Moore and Mealy Example Tables

- Mealy Model state table maps inputs and state to outputs


Present State	Next State		Output	
	x=0	x=1	x=0	x=1
0	0	1	0	0
1	0	1	0	1

- Moore Model state table maps state to outputs

Present State	Next State		Output
	x=0	x=1	
0	0	1	0
1	0	2	0
2	0	2	1

Example 2: Sequential Circuit Analysis

- Logic Diagram:

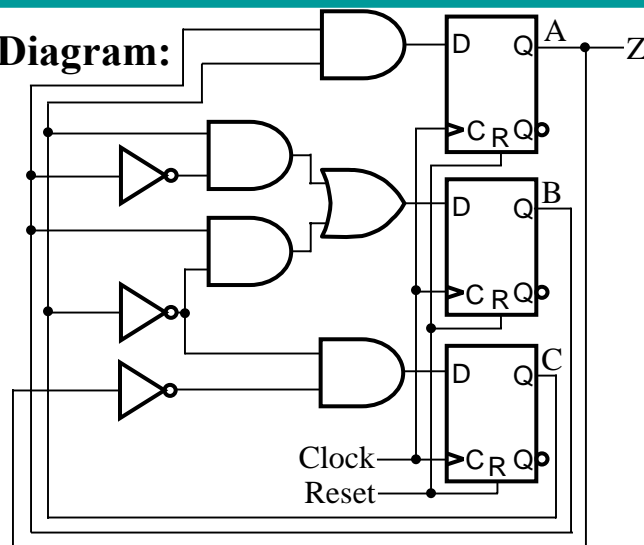

Example 2: Flip-Flop Input Equations

- **Variables**

- **Inputs: None**
- **Outputs: Z**
- **State Variables: A, B, C**

- **Initialization: Reset to (0,0,0)**

- **Equations**


- $A(t+1) =$ $Z =$
- $B(t+1) =$
- $C(t+1) =$

Example 2: State Table

$X' = X(t+1)$

A B C	A'B'C'	Z
0 0 0		
0 0 1		
0 1 0		
0 1 1		
1 0 0		
1 0 1		
1 1 0		
1 1 1		

Example 2: State Diagram

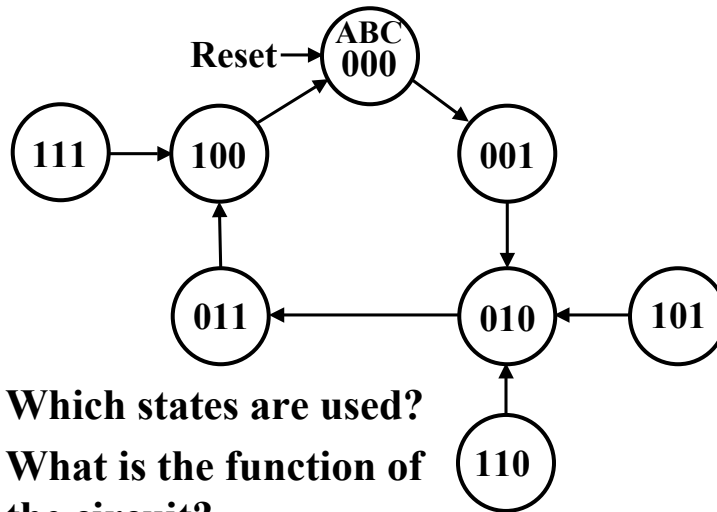


- Which states are used?
- What is the function of the circuit?

Logic and Computer Design Fundamentals
PowerPoint® Slides
© 2004 Pearson Education, Inc.

Chapter 6 - Part 1 47

Circuit and System Level Timing

 - Consider a system comprised of ranks of flip-flops connected by logic:
- If the clock period is too short, some data changes will not propagate through the circuit to flip-flop inputs before the setup time interval begins




Logic and Computer Design Fundamentals
PowerPoint® Slides
© 2004 Pearson Education, Inc.


Chapter 6 - Part 1 48

Circuit and System Level Timing (continued)

 - Timing components along a path from flip-flop to flip-flop



(a) Edge-triggered (positive edge)

 

(b) Pulse-triggered (negative pulse)

Circuit and System Level Timing (continued)

- New Timing Components

- t_p - clock period - The interval between occurrences of a specific clock edge in a periodic clock
- $t_{pd,COMB}$ - total delay of combinational logic along the path from flip-flop output to flip-flop input
- t_{slack} - extra time in the clock period in addition to the sum of the delays and setup time on a path
 - Can be either positive or negative
 - Must be greater than or equal to zero on all paths for correct operation

Circuit and System Level Timing (continued)

- **Timing Equations**

$$t_p = t_{\text{slack}} + (t_{\text{pd,FF}} + t_{\text{pd,COMB}} + t_s)$$

- For t_{slack} greater than or equal to zero,

$$t_p \geq \max (t_{\text{pd,FF}} + t_{\text{pd,COMB}} + t_s)$$

for all paths from flip-flop output to flip-flop input

- Can be calculated more precisely by using t_{PHL} and t_{PLH} values instead of t_{pd} values, but requires consideration of inversions on paths

Calculation of Allowable $t_{\text{pd,COMB}}$

- Compare the allowable combinational delay for a specific circuit:
 - a) Using edge-triggered flip-flops
 - b) Using master-slave flip-flops
- Parameters
 - $t_{\text{pd,FF}}(\text{max}) = 1.0 \text{ ns}$
 - $t_s(\text{max}) = 0.3 \text{ ns}$ for edge-triggered flip-flops
 - $t_s = t_{\text{wH}} = 1.0 \text{ ns}$ for master-slave flip-flops
 - Clock frequency = 250 MHz

Calculation of Allowable $t_{pd,COMB}$ (continued)

- **Calculations: $t_p = 1/\text{clock frequency} = 4.0 \text{ ns}$**
 - **Edge-triggered: $4.0 \geq 1.0 + t_{pd,COMB} + 0.3, t_{pd,COMB} \leq 2.7 \text{ ns}$**
 - **Master-slave: $4.0 \geq 1.0 + t_{pd,COMB} + 1.0, t_{pd,COMB} \leq 2.0 \text{ ns}$**
- **Comparison: Suppose that for a gate, average $t_{pd} = 0.3 \text{ ns}$**
 - **Edge-triggered: Approximately 9 gates allowed on a path**
 - **Master-slave: Approximately 6 to 7 gates allowed on a path**

Terms of Use

- © 2004 by Pearson Education, Inc. All rights reserved.
- The following terms of use apply in addition to the standard Pearson Education [Legal Notice](#).
- Permission is given to incorporate these materials into classroom presentations and handouts only to instructors adopting Logic and Computer Design Fundamentals as the course text.
- Permission is granted to the instructors adopting the book to post these materials on a protected website or protected ftp site in original or modified form. All other website or ftp postings, including those offering the materials for a fee, are prohibited.
- You may not remove or in any way alter this Terms of Use notice or any trademark, copyright, or other proprietary notice, including the copyright watermark on each slide.
- [Return to Title Page](#)