
Logic and Computer Design Fundamentals

Verilog

Part 1 – Chapter 4 – Basics and Types of Descriptions

Charles Kime & Thomas Kaminski

© 2004 Pearson Education, Inc.

[Terms of Use](#)

(Hyperlinks are active in View Show mode)

Overview

■ Part 1

- **Verilog Basics**
 - Notation
 - Keywords & Constructs
 - Operators
- **Types of Descriptions**
 - **Structural**
 - **Dataflow**
 - Boolean Equations
 - Conditions using Binary Combinations
 - Conditions using Binary Decisions
- **Combinational Circuit Testbench**

Verilog Notation - 1

- **Verilog is:**
 - Case sensitive
 - Based on the programming languages C and ADA
- **Comments**
 - **Single Line**
`//` `[end of line]`
 - **Multiple Line**
`/*`

`*/`
- **List element separator:** `,`
- **Statement terminator:** `;`

Verilog Notation - 2

■ Binary Values for Constants and Variables

- 0
- 1
- **X** or **x** – Unknown
- **Z** or **z** – High impedance state (open circuit)

■ Constants

- **n' b[integer]**: **1'b1** = 1, **8'b1** = 000000001, **4'b0101** = 0101, **8'bxxxxxxxx**, **8'bxxxx** = 0000xxxx
- **n' h[integer]**: **8'hA9** = 10101001, **16'hf1** = 0000000011110001

■ Identifier Examples

- **Scalar**: **A**, **C**, **RUN**, **stop**, **m**, **n**
- **Vector**: **sel[0:2]**, **f[0:5]**, **ACC[31:0]**, **SUM[15:0]**,
sum[15:0]

Verilog Keywords & Constructs - 1

- **Keywords are lower case**
- **module** – fundamental building block for Verilog designs
 - Used to construct design hierarchy
 - Cannot be nested
- **endmodule** – ends a module – not a statement
=> no “;”
- **Module Declaration**
 - **module** *module_name* (*module_port, module_port, ...*) ;
 - Example: **module** full_adder (A, B, c_in, c_out, S) ;

Verilog Keywords & Constructs - 2

■ Input Declaration

- Scalar

- `input` *list of input identifiers ;*
- Example: `input A, B, c_in;`

- Vector

- `input [range]` *list of input identifiers ;*
- Example: `input [15:0] A, B, data;`

■ Output Declaration

- Scalar Example: `output c_out, OV, MINUS;`
- Vector Example: `output [7:0] ACC, REG_IN, data_out;`

Verilog Keywords & Constructs - 3

■ Primitive Gates

- `buf`, `not`, `and`, `or`, `nand`, `nor`, `xor`, `xnor`
- Syntax: *gate_operator instance_identifiser (output, input_1, input_2, ...)*
- Examples:

```
and A1 (F, A, B); //F = A B
```

```
or O1 (w, a, b, c)
```

```
    O2 (x, b, c, d, e);
```

```
//w=a+b+c, x=b+c+d+e
```

Verilog Operators - 1

- Bitwise Operators

~ NOT

& AND

| OR

^ XOR

^~ or ~^ XNOR

- Example:


```
input[3:0] A, B;  
output[3:0] Z ;  
assign Z = A | ~B;
```


Verilog Operators - 2

- **Arithmetic Operators**
+, -, (plus others)
- **Logical & Relational Operators**
!, &&, ||, ==, !=, >=, <=, >, < (plus others)
- **Concatenation & Replication Operators**
{identifier_1, identifier_2, ...}
{n{identifier}}
 - Examples: {REG_IN[6:0], Serial_in},
{8 {1'b0}}

1st Example to Illustrate Verilog Description Types

 - IC7283 – a 1-bit adder from a commercial IC



Structural Verilog

- Circuits can be described by a netlist as a text alternative to a diagram – Example IC7283

```
module IC7283 (A0, B0, C0, C1, S0);  
    input A0, B0, C0;  
    output C1, S0;  
    //Seven internal wires needed  
    wire N1, N2, N3, N4, N5, N6, N7;  
    // Ports on primitive gates - output port  
    // is listed first  
    not G1 (N3,C0), G2 (N5,N2), G3 (N6,N3);  
    nand G4 (N1,A0,B0);  
    nor G5 (N2,A0,B0), G6 (C1,N2,N4);  
    and G7 (N4,N1,N3), G8 (N7,N1,N5);  
    xor G9 (S0,N6,N7);  
endmodule
```

Dataflow Verilog - 1

- Circuit function can be described by assign statements using Boolean equations – Example IC7283

```
module IC7283_df1 (A0, B0, C0, C1, S0);  
    input A0, B0, C0;  
    output C1, S0;  
    wire N1, N2;  
    assign N1 = ~(A0 & B0); //Note:  
    // Cannot write ~& for NAND  
    assign N2 = ~(A0 | B0);  
    assign C1 = ~( (N1 & ~C0) | N2);  
    assign S0 = (~N2 & N1) ^ (~(~C0));  
endmodule
```

2nd Example to Illustrate Verilog Description Types

■ Priority Encoder

Inputs					Outputs			
D4	D3	D2	D1	D0	A2	A1	A0	V
0	0	0	0	0	X	X	X	0
0	0	0	0	1	0	0	0	1
0	0	0	1	X	0	0	1	1
0	0	1	X	X	0	1	0	1
0	1	X	X	X	0	1	1	1
1	X	X	X	X	1	0	0	1

Dataflow Verilog - 2

- Circuit function can be described by assign statements using the conditional operator with binary combinations as in a truth table – Example Priority Encoder

```
module priority_encoder_df2 (D, A, V);  
    input[4:0] D;  
    output[2:0] A;  
    output V;  
  
    //Conditional: (X) ? Y: Z - if X is true, then Y, else Z  
    assign A = (D[4] == 1'b1) ? 3'b100 :  
                (D[3] == 1'b1) ? 3'b011 :  
                (D[2] == 1'b1) ? 3'b010 :  
                (D[1] == 1'b1) ? 3'b001 :  
                (D[0] == 1'b1) ? 3'b000 : 3'bxxx;  
  
    assign V = (D == 5'b00000) ? 1'b0 : 1'b1;  
  
endmodule
```

Dataflow Verilog - 3

- Circuit function can be described by assign statements using the conditional operator for binary decisions on inputs

```
module priority_encoder_df3 (D, A, V);  
    input[4:0] D;  
    output[2:0] A;  
    output V;  
    // Conditional: (X) ? Y: Z If X is true,  
    // then Y, else Z  
    assign A = D[4] ? 3'b100: D[3] ? 3'b011: D[2]  
        ? 3'b010: D[1] ? 3'b001: D[0] ? 3'b000: 3'bxxx;  
    assign V = (D == 5'b00000) ? 1'b0: 1'b1;  
endmodule
```

Combinational Circuit Testbench

- ***Testbench*** – a program that is used to verify the correctness of an HDL representation for a circuit
 - Applies a set of input combinations to the circuit that thoroughly tests the HDL representation
 - Assists in verifying the correctness of the corresponding outputs:
 - By displaying the inputs and outputs for manual verification
 - By comparing the outputs to those of a known correct representation for the circuit

Combinational Testbench Example - 1

- **A Verilog testbench for a combinational circuit with n inputs and m outputs that:**
 - **applies all possible binary input combinations as stimuli to the circuit**
 - **provides the circuit outputs for manual verification**
- **Stimuli Generation**
 - **Uses a clocked binary up counter to generate stimuli**
 - **Stops the simulation when all combinations have been applied**

Combinational Testbench Example - 2

■ Verilog code:

```
`timescale 1 ns / 100 ps //sets time unit /  
    // simulation interval (ps - picoseconds (10-12 sec)  
module priority_encoder_testbench;  
reg clk; //clock to advance counter  
reg[4:0] stim; //stimuli counter storage for D[4:0]  
wire[3:0] results; //wires to hold A[1:0],V  
//Following instantiates the circuit being tested  
priority_encoder_df3 x1 (stim[4:0], results [3:1],  
    results[0]);  
initial //initializes clk and stim to 0 and  
//stops simulation after 33 combinations applied  
begin  
    clk <= 0;  
    stim <= 4'b0;  
    #330 $stop;  
end
```

Combinational Testbench Example - 3

■ Verilog code (continued):

```
always
begin
#5 //waits 5 time units before toggling clock
forever
#5 clk <= ~clk; //toggles clock every 5 time units
end

always@(posedge clk)//conditions increment on
// the positive edge of clk
begin
stim <= stim + 1; //increments counter by 1
end
endmodule
```

Terms of Use

- © 2004 by Pearson Education, Inc. All rights reserved.
- The following terms of use apply in addition to the standard Pearson Education [Legal Notice](#).
- Permission is given to incorporate these materials into classroom presentations and handouts only to instructors adopting Logic and Computer Design Fundamentals as the course text.
- Permission is granted to the instructors adopting the book to post these materials on a protected website or protected ftp site in original or modified form. All other website or ftp postings, including those offering the materials for a fee, are prohibited.
- You may not remove or in any way alter this Terms of Use notice or any trademark, copyright, or other proprietary notice, including the copyright watermark on each slide.
- [Return to Title Page](#)