THE TRANSFORMER

Osman Parlaktuna Osmangazi University Eskisehir, TURKEY



- A transformer is a device that is based on magnetic coupling
- In communication, it is used to match impedances and eliminate dc signals.
- In power circuits, it is used to establish alternating current voltage levels that facilitate the transmission, distribution, and consumption of electrical power.



LINEAR TRANSFORMER

A simple transformer is formed when two coils are wound on a single core to ensure magnetic coupling.



The winding connected to the source is the **primary winding**, and the winding connected to the load is the **secondary winding**. Determine I_1 and I_2 as functions of circuit parameters, and also determine the input impedance at the terminals of the transformer.

$$V_{s} = (Z_{s} + R_{1} + j\omega L_{1})I_{1} - j\omega MI_{2}$$

$$0 = -j\omega MI_{1} + (R_{2} + j\omega L_{2} + Z_{L})I_{2}$$

$$Z_{11} = Z_{s} + R_{1} + j\omega L_{1}$$

$$Z_{22} = R_{2} + j\omega L_{2} + Z_{L}$$

$$I_{1} = \frac{Z_{22}}{Z_{11}Z_{22} + \omega^{2}M^{2}}V_{s}$$

$$I_{2} = \frac{j\omega M}{Z_{11}Z_{22} + \omega^{2}M^{2}}V_{s} = \frac{j\omega M}{Z_{22}}I_{1}$$

$$Z_{ab} = R_{1} + j\omega L_{1} + \frac{\omega^{2}M^{2}}{(R_{2} + j\omega L_{2} + Z_{L})}$$

Circuit Analysis II



Reflected Impedance

The last term in the equation for Z_{ab} is called the reflected **impedance** (Z_r) because it is the equivalent impedance of the secondary coil and load impedance reflected to the primary side of the transformer.

$$Z_{L} = R_{L} + jX_{L}$$

$$Z_{r} = \frac{\omega^{2}M^{2}}{R_{2} + R_{L} + j(\omega L_{2} + X_{L})} = \frac{\omega^{2}M^{2}[R_{2} + R_{L} - j(\omega L_{2} + X_{L})]}{(R_{2} + R_{L})^{2} + (\omega L_{2} + X_{L})^{2}}$$

$$= \frac{\omega^{2}M^{2}[(R_{2} + R_{L}) - j(\omega L_{2} + X_{L})]}{|Z_{22}|^{2}}$$

Circuit Analysis II



The parameters of a certain linear transformer are R₁=200 Ω , R₂=100 Ω L₁=9H, L₂=4H, and k=0.5. The transformer couples an impedance consisting of an 800 Ω resistor series with a 1µF capacitor to a sinusoidal voltage source. The 300 Vrms source has an internal impedance of 500+j100 Ω and a frequency of 400 rad/s.

$$j\omega L_1 = j(400)9 = j3600\Omega, \quad j\omega L_1 = j(400)4 = j1600\Omega$$

 $M = 0.5\sqrt{9 \cdot 4} = 3H \Rightarrow j\omega M = j(400)3 = j1200\Omega$

Following figure shows the frequency-domain equivalent circuit



$$\begin{split} &Z_{11} = 500 + j100 + 200 + j3600 = 700 + j3700\Omega \\ &Z_{22} = 100 + j1600 + 800 - j2500 = 900 - j900\Omega \\ &Z_r = \left(\frac{1200}{|900 - j900|}\right)^2 (900 + j900) = 800 + j800\Omega \\ &Z_{ab} = 200 + j3600 + 800 + j800 = 1000 + j4400\Omega \end{split}$$

Circuit Analysis II

Spring 2005

Thevenin equivalent with respect to the secondary terminals Open circuit voltage will be j1200 times the open circuit current \mathbf{I}_1

$$\mathbf{I}_{1} = \frac{300}{700 + j3700} = 79.67 / (-79.29)^{0} mA$$

$$\mathbf{V}_{Th} = j1200(79.67 / (-79.29)^{0}) \times 10^{-3} = 95.6 / (10.71)^{0} V$$

$$Z_{Th} = 100 + j600 + (\frac{1200}{|700 + j3700|})^{2} (700 - j3700) = 171.09 + j1124.26\Omega$$



Osman Parlaktuna

Circuit Analysis II



THE IDEAL TRANSFORMER

- An ideal transformer consist of two magnetically coupled coils having N₁ and N₂ turns.
- The coefficient of coupling is unity (k=1)
- The self-inductance of each coil is infinite $L_1 = L_2 = \infty$
- The coil losses, due to parasitic resistance, are negligible.



Voltage and Current Ratios









Polarity of the voltage and current ratios

 If the coil voltages v₁ and v₂ are both positive or negative at the dot-marked terminals, use a plus sign for the voltage ratio.
 If the coil currents i₁ and i₂ are both directed into or out of the dot-marked terminals use a minus sign for the current ratio.













REFLECTED IMPEDANCE IN IDEAL TRANSFORMER



The ideal transformer's secondary coil reflects the load impedance back to the primary coil, with the scaling factor $1/a^2$.





Find the steady-state values for i_1 , i_2 , v_1 , and v_2 . Use w=400 rad/s

$$2500 = (0.25 + j2)\mathbf{I}_{1} + \mathbf{V}_{1}$$

$$\mathbf{V}_{1} = 10\mathbf{V}_{2} \qquad \mathbf{I}_{2} = 10\mathbf{I}_{1}$$

$$\mathbf{V}_{2} = (0.2375 + j0.05)\mathbf{I}_{2}$$

$$2500 = (24 + j7)\mathbf{I}_{1}$$

$$\mathbf{I}_{1} = 100 \ / -16.26^{0} A$$

$$i_{1} = 100\cos(400t - 16.26^{0})A$$

$$i_{2} = 1000\cos(400t - 16.26^{0})A$$

$$\mathbf{V}_{1} = 2420 - j185 = 2427.06 \ / -4.37^{0} V$$

$$v_{1} = 2427.06\cos(400t - 4.37^{0})V$$

$$v_{2} = 242.71\cos(400t - 4.37^{0})V$$







Determine all indicated voltages and currents in the circuit.

$$\mathbf{V}_{1} = -\frac{\mathbf{V}_{2}}{a}, \quad \mathbf{I}_{1} = -a\mathbf{I}_{2} \quad \text{where } a = \frac{1}{4}$$

$$Z_{ref} = 16(2+j1) = 32+j16\Omega$$

$$\mathbf{I}_{1} = \frac{120}{18-j4+32+j16} = 2.33 \not/ -13.5^{\circ}A$$

$$\mathbf{V}_{1} = \mathbf{I}_{1}Z_{ref} = (2.33 \not/ -13.5^{\circ})(32+j16) = 83.5 \not/ 13.07^{\circ}V$$

$$\mathbf{V}_{2} = -a\mathbf{V}_{1} = 20.88 \not/ 193.07^{\circ}V$$

$$\mathbf{I}_{2} = -\frac{\mathbf{I}_{1}}{a} = 9.32 \not/ 166.5^{\circ}A$$

Circuit Analysis II

 $I_2 =$

Spring 2005

USING THEVENIN THEOREM IN THE ANALYSIS OF IDEAL TRANSFORMER





Determine the Thevenin Equivalent circuit that replaces the transformer and either the primary or secondary circuit.

$$\mathbf{I}_1 = n\mathbf{I}_2 \quad \mathbf{V}_1 = \frac{\mathbf{V}_2}{n}$$

where n is the turns ratio

For open circuit voltage, $\mathbf{I}_2=0$, therefore $\mathbf{I}_1=0$. Then

$$\mathbf{V}_{oc} = \mathbf{V}_2 = n\mathbf{V}_1 = n\mathbf{V}_{s1}$$

 $Z_{Th} = n^2 Z_1$



Thevenin equivalent replacing the transformer and the primary circuit. Each primary voltage is multiplied by n, each primary current is divided by n, and each primary impedance is multiplied by n^2 Thevenin equivalent replacing the transformer and the secondary circuit. Each secondary voltage is divided by n, each secondary current is multiplied by n, and each secondary impedance is divided by n^2

Circuit Analysis II

Spring 2005



EXAMPLE



Determine \mathbf{V}_0

First, let us determine the Thevenin equivalent of the primary.

$$\mathbf{V}_{oc} = \frac{24/0^{0}}{4 - j4}(-j4) - 4/-90^{0}$$
$$= 12 - j8 = 14.42/-33.69^{0}V$$
$$Z_{\text{Th}} = \frac{4(-j4)}{4 - j4} + 2 = 4 - j2\Omega$$

Circuit Analysis II

Spring 2005



Then, reflecting the primary circuit to the secondary results in a one-mesh circuit.

$$\mathbf{V}_{0} = \frac{-28.84 / -33.69^{\circ}}{20 - j5} (2)$$
$$= 2.8 / 160.35^{\circ} V$$



EXAMPLE



Find the value of R₀ for maximum power transfer.

For maximum power transfer, $R_0 = R_{Th}$.

In circuit (b), secondary resistance reflected to primary as 16Ω . Thus,

$$\mathbf{I}_{1} = \frac{48 \underline{0^{0}}}{6+2+16} = 2 \underline{0^{0}} A$$
$$\mathbf{V}_{1} = (2 \underline{0^{0}}) 16 = 32 \underline{0^{0}} V$$
$$\mathbf{I}_{2} = 4 \underline{0^{0}} A \quad \mathbf{V}_{2} = 16 \underline{0^{0}} V$$
$$b_{a} = \mathbf{V}_{a} + \mathbf{V}_{1} - \mathbf{V}_{2} + \mathbf{V}_{b} = 24 \underline{0^{0}} V$$

Circuit Analysis II

Spring 2005

V



$$48 / 0^{0} = 6\mathbf{I}_{1} + 2(\mathbf{I}_{1} - \mathbf{I}_{sc}) + \mathbf{V}_{1}$$

$$48 / 0^{0} = 6\mathbf{I}_{1} + 3[2(\mathbf{I}_{1} - \mathbf{I}_{sc}) + \mathbf{I}_{sc}]$$

$$\mathbf{V}_{2} = (1)[2(\mathbf{I}_{1} - \mathbf{I}_{sc})] + 3[2(\mathbf{I}_{1} - \mathbf{I}_{sc}) + \mathbf{I}_{sc}]$$

$$\mathbf{V}_{1} = 2\mathbf{V}_{2}$$

Solving for $\boldsymbol{I}_{\rm sc}$

$$I_{sc} = \frac{8/0^{0} A}{Z_{Th}} = \frac{\frac{24/0^{0}}{8/0^{0}}}{8/0^{0}} = 3\Omega$$
$$P_{\text{max}} = \left[\frac{24}{2(3)}\right]^{2} (3) = 48W$$

Circuit Analysis II

Spring 2005