


# Sinusoidal Steady-state Power Calculations

---

Osman Parlaktuna  
Osmangazi University  
Eskisehir, TURKEY



# INSTANTANEOUS POWER

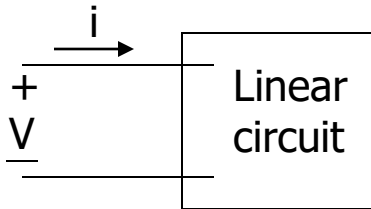

Here,  $v$  and  $i$  are steady-state sinusoidal signals.

The power at any instant of time is  $p=v.i$


If the reference direction of the current is in the direction of the voltage rise, the equation must be written with a minus sign.

$$v = V_m \cos(\omega t + \theta_v)$$


$$i = I_m \cos(\omega t + \theta_i)$$

$$p = V_m \cos(\omega t + \theta_v) I_m \cos(\omega t + \theta_i)$$
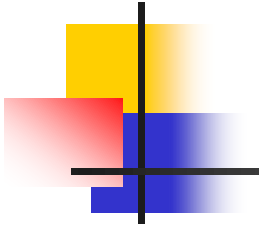
$$p = \frac{V_m I_m}{2} \cos(\theta_v - \theta_i) + \frac{V_m I_m}{2} \cos(2\omega t + \theta_v - \theta_i)$$


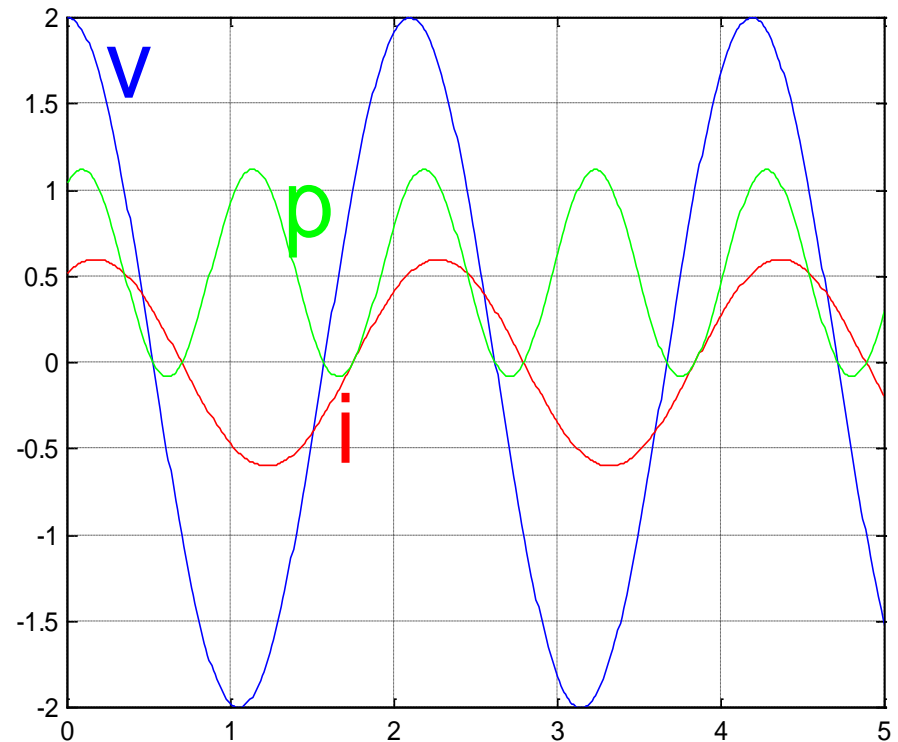
```
t=0:0.01:5;  
v=2*cos(3*t);  
i=0.6*cos(3*t-pi/6);  
p=v.*i;  
figure(1)  
plot(t,v)  
hold on  
plot(t,i,'r')  
plot(t,p,'g')  
grid
```





# AVERAGE AND REACTIVE POWER

$$p = \frac{V_m I_m}{2} \cos(\theta_v - \theta_i) + \frac{V_m I_m}{2} \cos(2\omega t + \theta_v - \theta_i)$$

$$p = \frac{V_m I_m}{2} \cos(\theta_v - \theta_i) + \frac{V_m I_m}{2} \cos(\theta_v - \theta_i) \cos 2\omega t - \frac{V_m I_m}{2} \sin(\theta_v - \theta_i) \sin 2\omega t$$

$$p = P + P \cos 2\omega t - Q \sin 2\omega t$$

P is called the **average (real) power**, and Q is called the **reactive power**.

P is the average power associated with sinusoidal signals  
The average of the instantaneous power over one period is:


$$P = \frac{1}{T} \int_{t_0}^{t_0+T} p dt$$


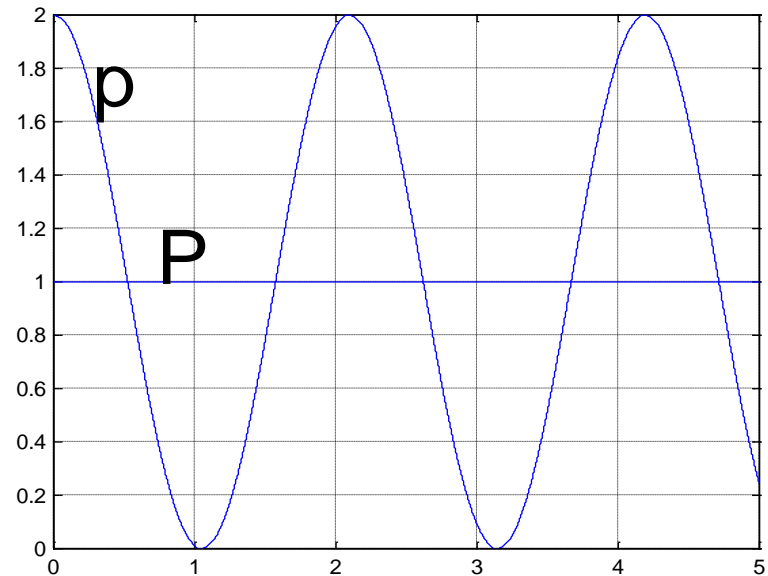
# Purely resistive circuits

If the circuit between the terminals is purely resistive, the voltage and current are in phase,  $\theta_v = \theta_i$ , then  $p = P + P \cos 2\omega t$

Instantaneous real power for a resistor can never be negative. Therefore, power cannot be extracted from a purely resistive circuit.






# Purely Inductive Circuits

If the circuit between the terminals is purely inductive, the voltage and current are out of phase by  $90^\circ$  and the current lags the voltage. Therefore,  $\theta_v - \theta_i = +90^\circ$  and  $p = -Q \sin 2\omega t$

The average power is zero.  $p$  is exchanged between the circuit and the source driving the circuit. When  $p$  is positive, energy is being stored in the inductor, and when  $p$  is negative energy is extracted from the inductor.

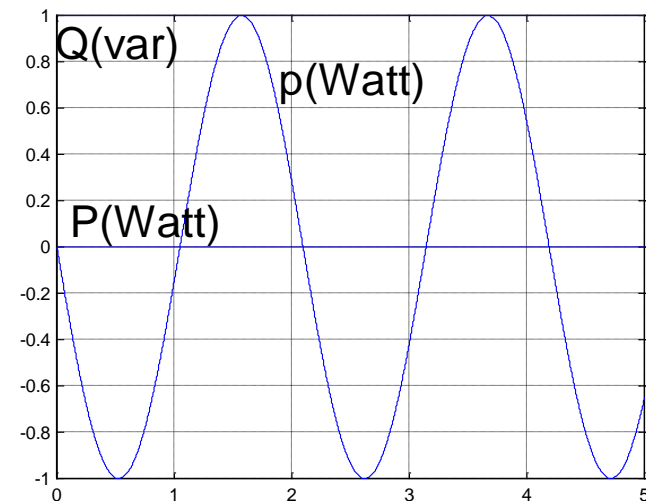$Q$  is the reactive power and its unit is volt-ampere reactive (VAR)







# Purely Capacitive Circuits

If the circuit between the terminals is purely capacitive, the voltage and current are out of phase by  $90^\circ$  and the current leads the voltage.

Therefore,  $\theta_v - \theta_i = -90^\circ$  and  $p = Q \sin 2\omega t$

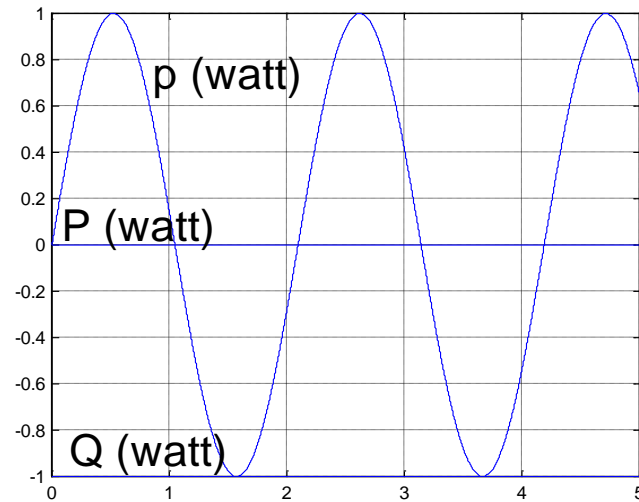Note that  $Q$  is positive for inductors and negative for capacitors. Therefore, we say that inductors demand (or absorb) magnetizing VARs and capacitors furnish (deliver) magnetizing VARs.



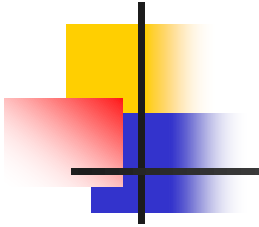

# The Power Factor

The angle  $\theta_v - \theta_i$  plays a role in the computation of both average and reactive power and is referred to as the **power factor angle**. The cosine of this angle is called the **power factor** (pf), and the sine of this angle is called the **reactive factor** (rf)

$$\text{pf} = \cos(\theta_v - \theta_i) \quad \text{rf} = \sin(\theta_v - \theta_i)$$


**Lagging power factor:** Current lags voltage, hence inductive load.

**Leading power factor:** Current leads voltage, hence capacitive load.





# Example

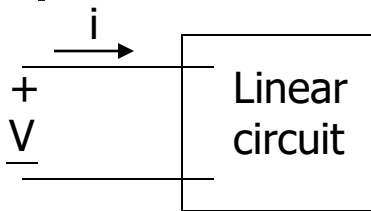

$$v = 100 \cos(\omega t + 15^\circ) V, \quad i = 4 \sin(\omega t - 15^\circ) A$$

Calculate the average and the reactive power.  
Is this circuit absorbs or delivers average power  
and magnetizing VARs?

$$i = 4 \cos(\omega t - 105^\circ) A$$

$$P = \frac{1}{2} (100)(4) \cos(15 - (-105)) = -100 W$$

$$Q = \frac{1}{2} (100)(4) \sin(15 - (-105)) = 173.21 \text{ VAR}$$

Since  $P$  is negative, the circuit delivers average power to the terminals.  
 $Q$  is positive (inductive) and the circuit absorbs magnetizing VARs  
at its terminals



# THE RMS VALUE AND POWER CALCULATIONS

Assume that a sinusoidal voltage  $v = V_m \cos(\omega t + \theta_v)$  is applied to the terminals of a resistor. Determine the average power delivered to the resistor

$$\begin{aligned} P &= \frac{1}{T} \int_{t_0}^{t_0+T} \frac{V_m^2 \cos^2(\omega t + \theta_v)}{R} dt \\ &= \frac{1}{R} \left[ \frac{1}{T} \int_{t_0}^{t_0+T} V_m^2 \cos^2(\omega t + \theta_v) dt \right] = \frac{V_{rms}^2}{R} \end{aligned}$$


If the resistor is carrying a sinusoidal current  $i = I_m \cos(\omega t + \theta_i)$


$$P = I_{rms}^2 R$$


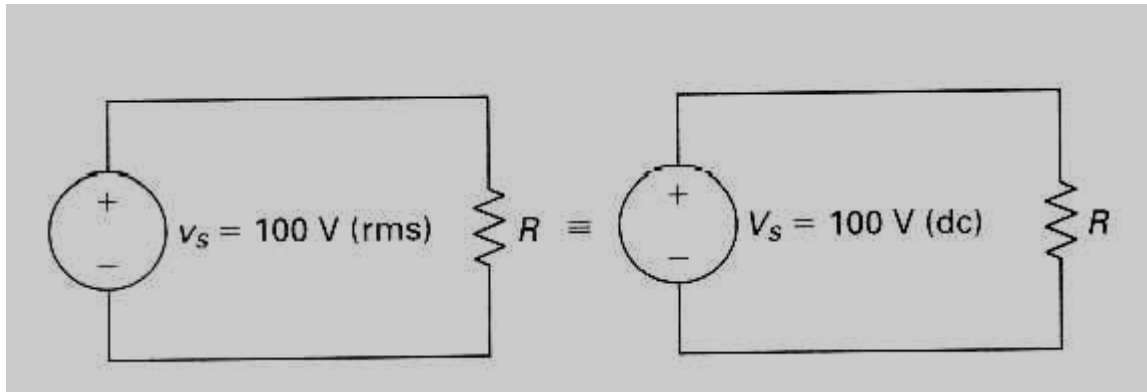
# EFFECTIVE VALUE

The rms value is also referred to as the **effective value** of the sinusoidal signal. Given a resistive load,  $R$ , and a sinusoidal source applied to this load, the rms (effective) value of the source delivers the same energy to  $R$  as does a dc source of the same value.



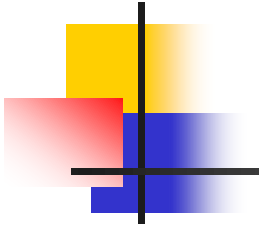

The average power and the reactive power can be written in terms of the reactive values:

$$\begin{aligned} P &= \frac{V_m I_m}{2} \cos(\theta_v - \theta_i) \\ &= \frac{V_m}{\sqrt{2}} \frac{I_m}{\sqrt{2}} \cos(\theta_v - \theta_i) = V_{eff} I_{eff} \cos(\theta_v - \theta_i) \\ Q &= V_{eff} I_{eff} \sin(\theta_v - \theta_i) \end{aligned}$$




# COMPLEX POWER

**Complex power** is the complex sum of real power and reactive power

$S = P + jQ$  We can compute the complex power directly from the voltage and current phasors, then  $P = \text{Re}(S)$  and  $Q = \text{Im}(S)$ .

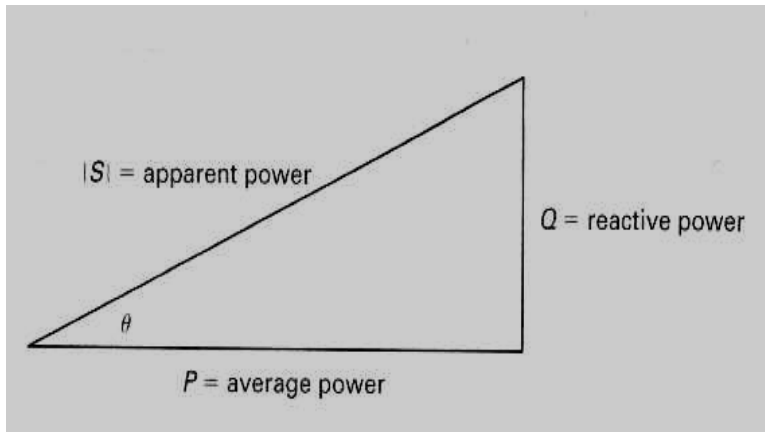Unit of the complex power is **volt-amps** (VA).



Think of  $P$ ,  $Q$ , and  $|S|$  as the sides of a right triangle. Then  $\theta = \tan^{-1} \frac{Q}{P} = \theta_v - \theta_i$

is the power factor angle. The magnitude of the complex power is referred to as **apparent power**

$$|S| = \sqrt{P^2 + Q^2}$$



## EXAMPLE

An electrical load operates at 240Vrms. The load absorbs an average power of 8 kW at a lagging power factor of 0.8. Calculate the complex power and the impedance of the load.

$$P = |S| \cos \theta \Rightarrow |S| = \frac{8000}{0.8} = 10 \text{ kVA}$$

$$Q = |S| \sin \theta = 10 * \sin(\cos^{-1} 0.8) = 6 \text{ kVAR}$$

$$S = 8 + j6 \text{ kVA}$$

$$P = V_{eff} I_{eff} \cos \theta \Rightarrow I_{eff} = \frac{8000}{(240)0.8} = 41.67 \text{ A}_{rms}$$

$$\theta = \cos^{-1} 0.8 = 36.87^\circ$$

$$|Z| = \frac{V_{eff}}{I_{eff}} = \frac{240}{41.67} = 5.76$$

$$Z = 5.76 \angle 36.87^\circ = 4.608 + j3.456 \Omega$$



# POWER CALCULATIONS

$$\begin{aligned} S &= \frac{V_m I_m}{2} \cos(\theta_v - \theta_i) + j \frac{V_m I_m}{2} \sin(\theta_v - \theta_i) \\ &= \frac{V_m I_m}{2} [\cos(\theta_v - \theta_i) + j \sin(\theta_v - \theta_i)] \\ &= \frac{V_m I_m}{2} e^{j(\theta_v - \theta_i)} = \frac{1}{2} V_m I_m \angle (\theta_v - \theta_i) \\ &= V_{eff} I_{eff} \angle (\theta_v - \theta_i) = V_{eff} I_{eff} e^{j(\theta_v - \theta_i)} \\ &= V_{eff} e^{j\theta_v} I_{eff} e^{-j\theta_i} = \mathbf{V}_{eff} \mathbf{I}_{eff}^* \end{aligned}$$



# ALTERNATE FORMS FOR THE COMPLEX POWER

$$\mathbf{V}_{eff} = Z\mathbf{I}_{eff} \Rightarrow S = Z\mathbf{I}_{eff}\mathbf{I}_{eff}^* = |\mathbf{I}_{eff}|^2 Z$$

$$S = |\mathbf{I}_{eff}|^2 (R + jX) = |\mathbf{I}_{eff}|^2 R + j|\mathbf{I}_{eff}|^2 X = P + jQ$$

$$P = |\mathbf{I}_{eff}|^2 R = \frac{1}{2} I_m^2 R$$

$$Q = |\mathbf{I}_{eff}|^2 X = \frac{1}{2} I_m^2 X$$


$$\text{Or } S = \mathbf{V}_{eff} \left( \frac{\mathbf{V}_{eff}}{Z} \right)^* = \frac{|\mathbf{V}_{eff}|^2}{Z^*} = P + jQ$$

$$P = \frac{|\mathbf{V}_{eff}|^2}{R} \quad Q = \frac{|\mathbf{V}_{eff}|^2}{X}$$





# EXAMPLE

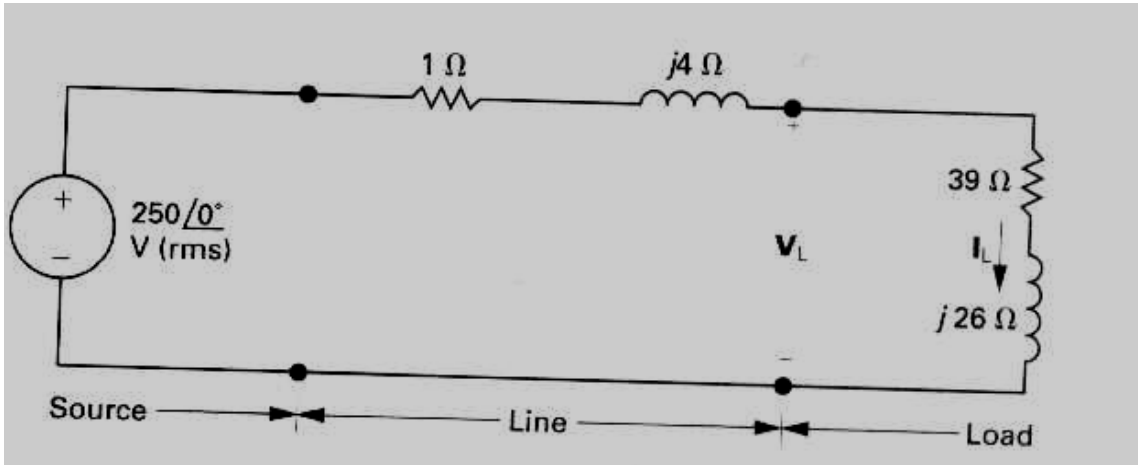

$$\mathbf{I}_L = \frac{250}{40 + j30} = 4 - j3 = 5 \angle -36.87^\circ \text{ A}_{rms}$$

$$\mathbf{V}_L = (39 + j26)\mathbf{I}_L = 234 - j13 = 234.36 \angle -3.18^\circ \text{ V}_{rms}$$

$$\mathbf{S} = \mathbf{V}_L \mathbf{I}_L^* = (234 - j13)(4 + j3) = 975 + j650 \text{ VA}$$

$$P_{line} = (5)^2 1 = 25 \text{ W}$$


$$Q_{line} = (5)^2 4 = 100 \text{ VAR}$$

$$\begin{aligned} \mathbf{S}_s &= 25 + j100 + 975 + j650 \\ &= 1000 + j750 \text{ VA} \end{aligned}$$


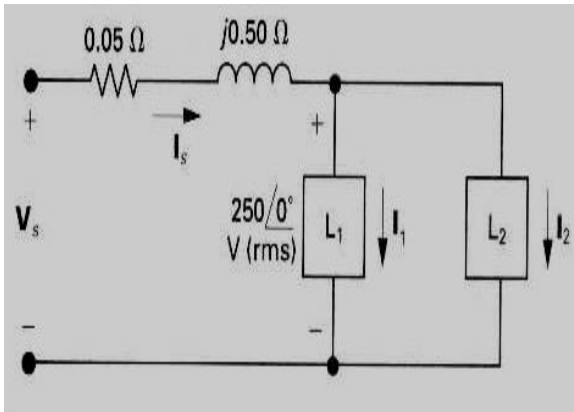
# EXAMPLE

Load 1 absorbs an average power of 8 kW at a leading power factor of 0.8. Load 2 absorbs 20 kVA at a lagging power factor of 0.6.




- Determine the pf of the parallel loads
- Determine the apparent power supplied to the loads, magnitude of  $\mathbf{I}_s$  and  $P_{\text{line}}$
- Determine the value of  $C$  that would correct the pf to 1 if placed in parallel to the loads. Calculate the values in b for the load with the corrected pf.

$$S = (250)\mathbf{I}_s^* = (250)(\mathbf{I}_1 + \mathbf{I}_2)^* = S_1 + S_2$$

$$S_1 = 8000 - j \frac{8000(0.6)}{0.8} = 8000 - j6000\text{VA}$$
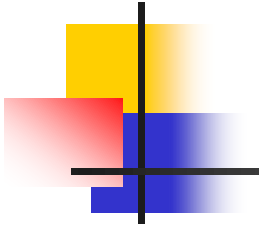
$$S_2 = 20000(0.6) + j20000(0.8) = 12000 + j16000\text{VA}$$



$$S = 20000 + j10000 \text{ VA} \Rightarrow \mathbf{I}_s^* = \frac{20000 + j10000}{250} = 80 + j40 \text{ A}$$

$$\mathbf{I}_s = 80 - j40 = 89.44 \angle -26.57^\circ \text{ A}$$

$$\text{pf} = \cos(0 + 26.57^\circ) = 0.8944 \text{ Lagging}$$

b)  $|S| = |20 + j10| = 22.36 \text{ kVA}$

$$|\mathbf{I}_s| = |80 - j40| = 89.44 \text{ A}$$

$$P_{line} = |\mathbf{I}_s|^2 R = (89.44)^2 (0.05) = 400 \text{ W}$$



c) We can correct the pf to 1 if we place a capacitor in parallel with the existing loads such that the capacitor supplies 10kVAR.

$$X = \frac{|V_{eff}|^2}{Q} = \frac{250^2}{-10000} = -6.25\Omega \quad C = \frac{-1}{\omega X} = \frac{-1}{(2\pi 60)(-6.25)} = 424.4\mu F$$


After correcting the pf to 1.

$$|S| = P = 20kVA \quad \text{and} \quad |I_s| = \frac{20000}{250} = 80A$$

$$P_{line} = |I_s|^2 R = (80)^2 (0.05) = 320W$$




# EXAMPLE

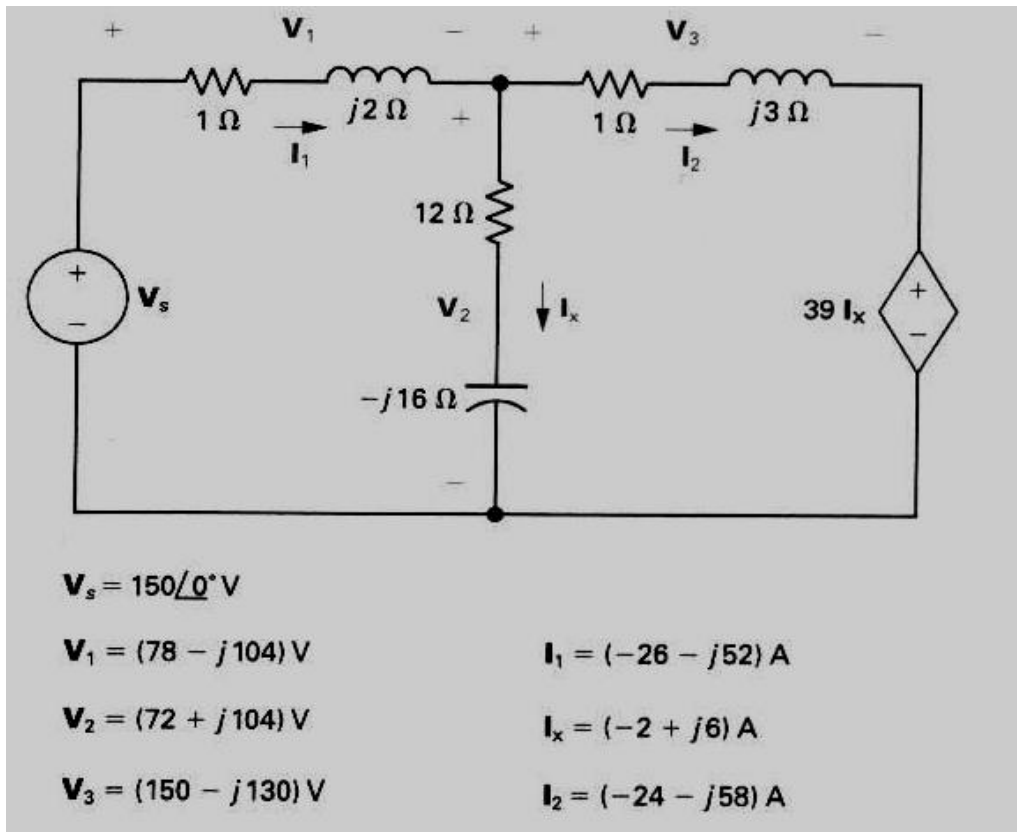

Calculate the average and reactive power of each element in the circuit. Verify consumption of power

$$\begin{aligned} S_1 &= \frac{1}{2} \mathbf{v}_1 \mathbf{i}_1^* = P_1 + jQ_1 \\ &= \frac{1}{2} (78 - j104)(-26 + j52) \\ &= 1690 + j3380 \text{ VA} \end{aligned}$$

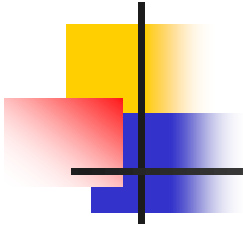1+j2 absorbs both average power and magnetizing VARs



$$\begin{aligned} S_2 &= \frac{1}{2} \mathbf{V}_2 \mathbf{I}_x^* = P_2 + jQ_2 \\ &= \frac{1}{2} (72 + j104)(-2 - j6) \\ &= 240 - j320\text{VA} \end{aligned}$$


12-j16Ω absorbs average power and delivers magnetizing VARS.

$$\begin{aligned} S_s &= \frac{1}{2} \mathbf{V}_s \mathbf{I}_1^* = P_s + jQ_s \\ &= \frac{1}{2} (150)(-26 + j52) \\ &= 1950 - j3900\text{VA} \end{aligned}$$

$$\begin{aligned} S_3 &= \frac{1}{2} \mathbf{V}_3 \mathbf{I}_2^* = P_3 + jQ_3 \\ &= \frac{1}{2} (150 - j130)(-24 + j58) \\ &= 1970 + j5910\text{VA} \end{aligned}$$

1+j3Ω absorbs average power and magnetizing VARS.
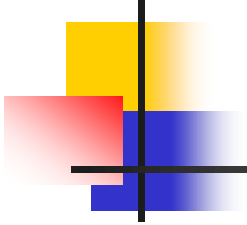
$$\begin{aligned} S_x &= \frac{1}{2} (39 \mathbf{I}_x) \mathbf{I}_2^* = P_x + jQ_x \\ &= \frac{1}{2} (-78 + j234)(-24 + j58) \\ &= -5850 - j5070\text{VA} \end{aligned}$$



Independent voltage source is absorbing average power and delivering magnetizing VARs. Dependent source delivers average power and magnetizing VARs.

$$P_{abs} = P_1 + P_2 + P_3 + P_s = 5850W$$

$$P_{del} = 5850W$$


$$Q_{abs} = Q_1 + Q_3 = 9290VAR$$

$$Q_{del} = Q_2 + Q_s + Q_x = 9290VAR$$


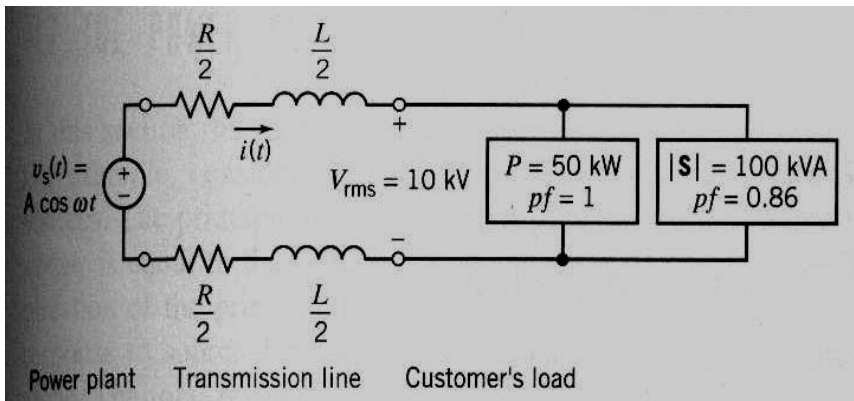
## EXAMPLE

A customer's plant has two parallel loads connected to the power utility's distribution lines. The first load consists of 50 kW of heating and is resistive. The second load is a set of motors that operate at 0.86 lagging power factor. The motor's load is 100 kVA. Power is supplied to the plant at 10000 V<sub>rms</sub>. Determine the total current flowing from the utility's lines into the plant and the plant's overall power factor.



$$S_1 = P_1 = 50 \text{ kW}$$

$$\theta_2 = \cos^{-1}(0.86) = 30.7^\circ$$

$$S_2 = |S_2| \angle \theta_2 = 100 \angle 30.7^\circ \text{ kVA} \\ = 86 + j51 \text{ kVA}$$

$$S = S_1 + S_2 = 136 + j51 = 145.2 \angle 20.6^\circ \text{ kVA}$$

$$\text{Pf} = \cos(20.6^\circ) = 0.94 \text{ lagging}$$


$$I_{rms} = \frac{|S|}{V_{rms}} = \frac{145200}{10000} = 14.52 \text{ Arms}$$




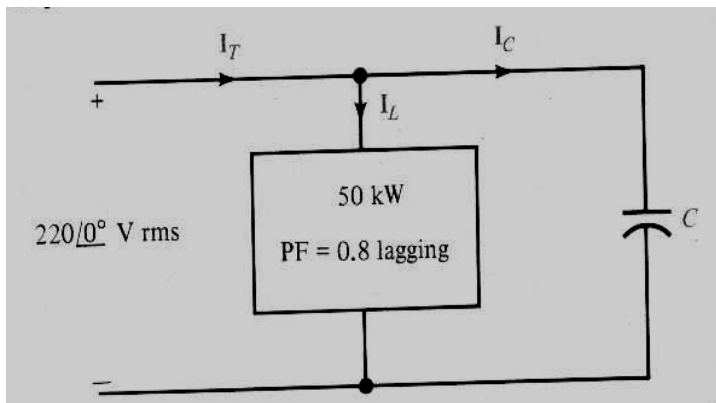
# POWER FACTOR CORRECTION

An industrial load consisting of a bank of induction motors consumes 50 kW at a Pf of 0.8 lagging from a 220-Vrms, 60-Hz line. We wish to raise the Pf to 0.95 lagging by placing a bank of capacitors in parallel to the load.



$$\theta_{\text{old}} = \cos^{-1} 0.8 = 36.87^\circ$$

$$Q_{\text{old}} = |S_{\text{old}}| \sin(\theta_{\text{old}}) = \frac{50}{0.8} \sin(36.87^\circ) = 37.5 \text{ kVAR}$$

$$S_{\text{old}} = 50000 + j37500$$

$$\theta_{\text{new}} = \cos^{-1} 0.95 = 18.19^\circ$$

$$Q_{\text{new}} = |S_{\text{new}}| \sin(\theta_{\text{new}}) = \frac{50}{0.95} \sin(18.19^\circ) = 16.43 \text{ kVAR}$$


$$S_{\text{new}} = 50000 + j16430$$

$$S_{\text{cap}} = S_{\text{new}} - S_{\text{old}} = -j21070$$

$$C = \frac{21070}{(377)(220)^2} = 1155 \mu\text{F}$$



# MAXIMUM POWER TRANSFER

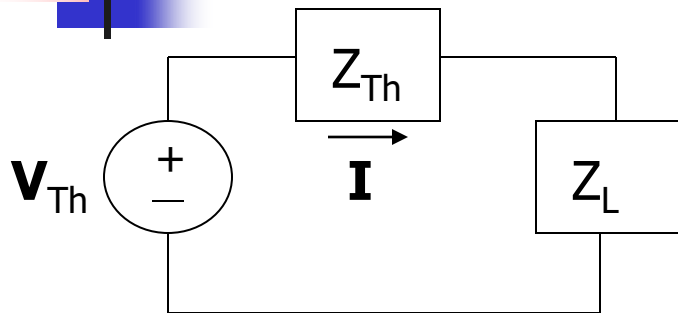


Determine the value of  $Z_L$  for maximum average power transfer

$$Z_{Th} = R_{Th} + jX_{Th} \quad Z_L = R_L + jX_L$$

$$\mathbf{I} = \frac{\mathbf{V}_{Th}}{(R_{Th} + R_L) + j(X_{Th} + X_L)} \quad P = |\mathbf{I}|^2 R_L = \frac{|\mathbf{V}_{Th}|^2}{(R_{Th} + R_L)^2 + (X_{Th} + X_L)^2}$$

$$\frac{\partial P}{\partial X_L} = \frac{-|\mathbf{V}_{Th}|^2 2R_L(X_L + X_{Th})}{[(R_L + R_{Th})^2 + (X_L + X_{Th})^2]^2}$$

$$\frac{\partial P}{\partial R_L} = \frac{|\mathbf{V}_{Th}|^2 [(R_L + R_{Th})^2 + (X_L + X_{Th})^2 - 2R_L(R_L + R_{Th})]}{[(R_L + R_{Th})^2 + (X_L + X_{Th})^2]^2}$$

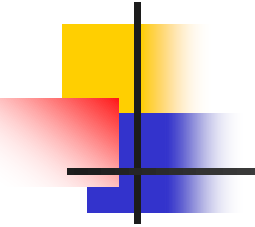

$$\frac{\partial P}{\partial X_L} = 0 \quad \text{when } X_L = -X_{Th}$$

$$\frac{\partial P}{\partial R_L} = 0 \quad \text{when } R_L = \sqrt{R_{Th}^2 + (X_L + X_{Th})^2}$$

Both derivatives are zero when  $Z_L = Z_{Th}^*$

$$P_{\max} = \frac{1}{4} \frac{|\mathbf{V}_{Th}|^2}{R_L}$$

If the Thevenin voltage is expressed in terms of its maximum value rather than its rms amplitude,

$$P_{\max} = \frac{1}{8} \frac{V_m^2}{R_L}$$



# MAXIMUM POWER TRANSFER WHEN $Z$ IS RESTRICTED



When it is not possible to set  $Z_L$  equal to the conjugate of  $Z_{Th}$ :

I)  $R_L$  and  $X_L$  may be restricted to a limited range of values. In this case, the optimum condition for  $R_L$  and  $X_L$  is to adjust  $X_L$  as near to  $-X_{Th}$  as possible and then adjust  $R_L$  as close to  $\sqrt{R_{Th}^2 + (X_L + X_{Th})^2}$  as possible

II) A second type of restriction occurs when the magnitude of  $Z_L$  can be varied but its phase angle cannot. Under this restriction, the greatest amount of power is transferred to the load when the magnitude of  $Z_L$  is set equal to the magnitude of  $Z_{Th}$ .  $|Z_L| = |Z_{Th}|$




# Example

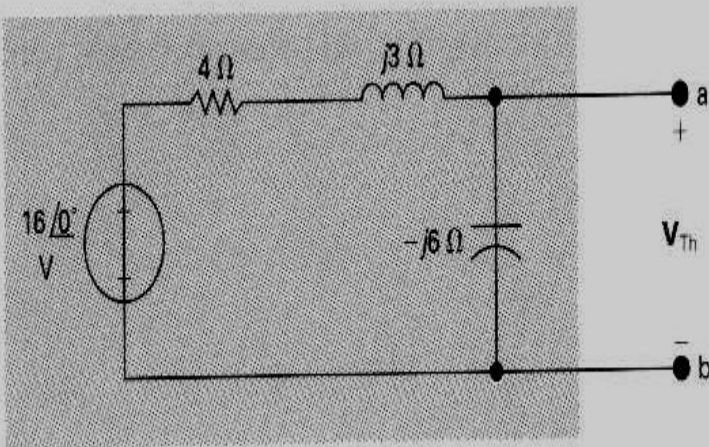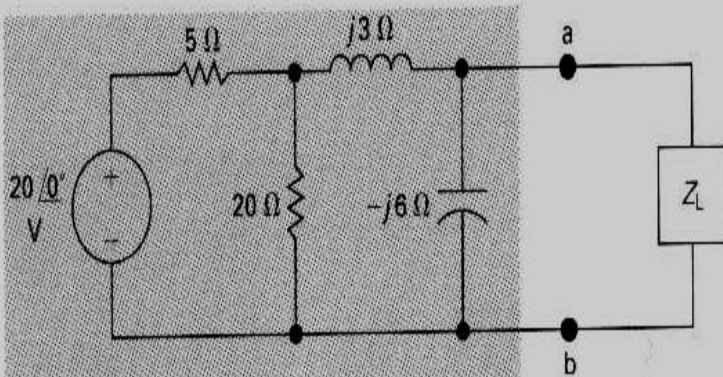

Determine the impedance  $Z_L$  that results in maximum average power transfer to  $Z_L$ .


We need to determine the Thevenin equivalent seen at the terminals a-b. Using 2 successive source transformations, circuit becomes and
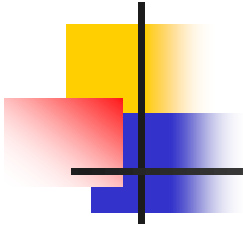
$$\begin{aligned} \mathbf{V}_{Th} &= \frac{16}{4 + j3 - j6} (-j6) \\ &= 19.2 \angle -53.13^\circ = 11.52 - j15.36V \end{aligned}$$



$$Z_{Th} = \frac{(-j6)(4 + j3)}{4 + j3 - j6} = 5.76 - j1.68\Omega$$

$$Z_L = Z_{Th}^* = 5.76 + j1.68\Omega$$

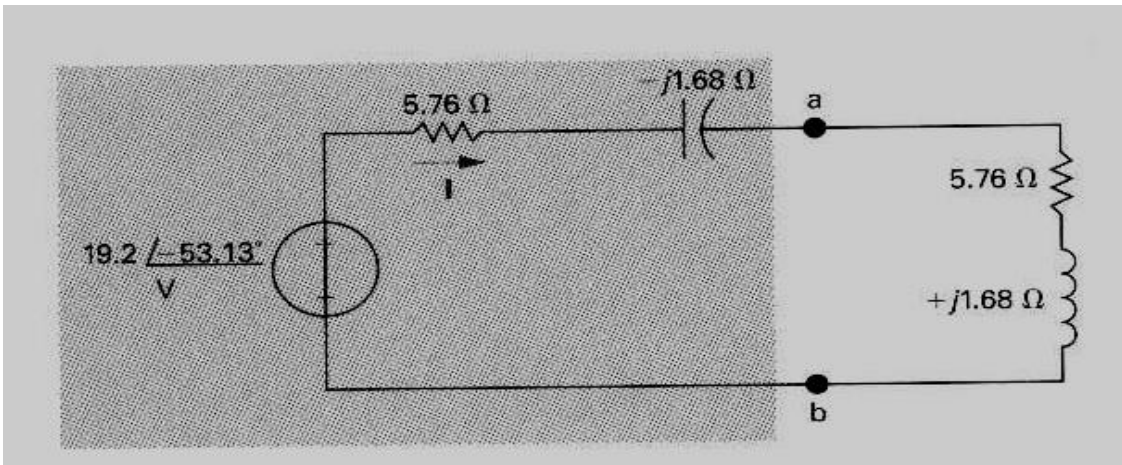


$$I_{eff} = \frac{19.2/\sqrt{2}}{2(5.76)} = 1.1785A$$

$$P = I_{eff}^2 (5.76) = 8W$$



# Example

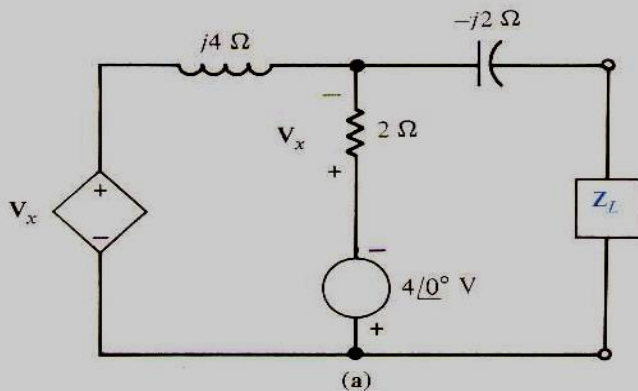


Find the value of  $Z_L$  for maximum power transfer.



$$\mathbf{V}'_x + 4 = (2 + j4)\mathbf{I}_1 \quad \mathbf{V}'_x = -2\mathbf{I}_1$$

$$\mathbf{I}_1 = \frac{1\angle -45^\circ}{\sqrt{2}}$$

$$\mathbf{V}_{oc} = 2\mathbf{I}_1 - 4\angle 0^\circ = \sqrt{2}\angle -45^\circ - 4\angle 0^\circ$$
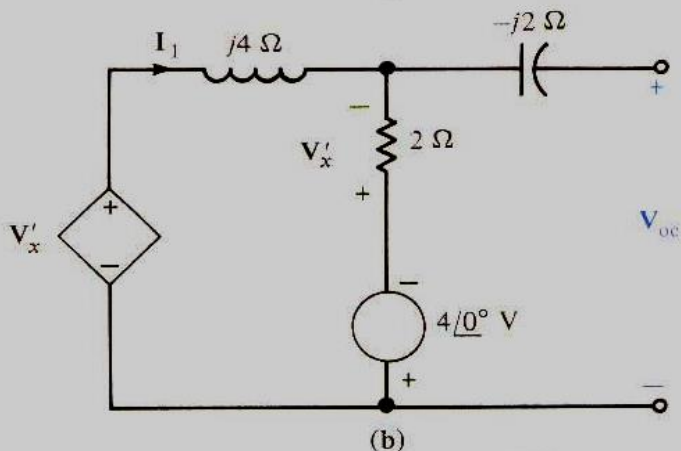
$$= -3 - j1 = -3.16\angle 18.43^\circ \text{ V}$$



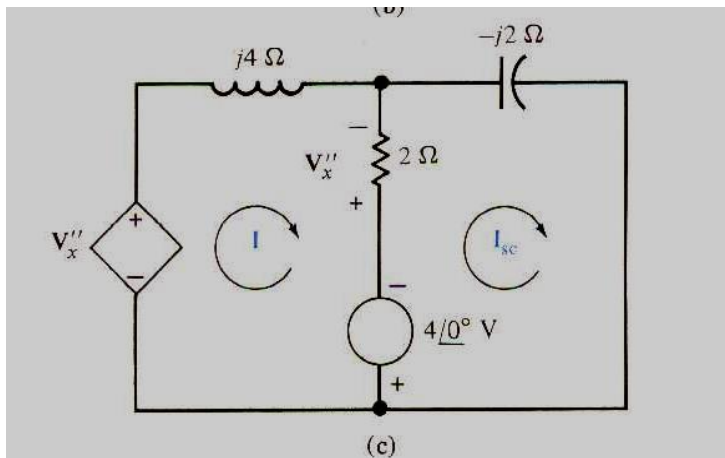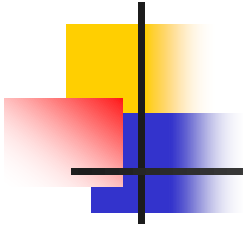

$$\mathbf{V}_x'' + 4 = (2 + j4)\mathbf{I} - 2\mathbf{I}_{sc}$$

$$-4 = -2\mathbf{I} + (2 - j2)\mathbf{I}_{sc}$$

$$\mathbf{V}_x'' = -2(\mathbf{I} - \mathbf{I}_{sc})$$

$$\mathbf{I}_{sc} = -(1 + j2)\text{A} \Rightarrow \mathbf{Z}_{Th} = \frac{\mathbf{V}_{oc}}{\mathbf{I}_{sc}} = \frac{3 + j1}{1 + j2} = 1 - j1\Omega$$

$$\mathbf{Z}_L = \mathbf{Z}_{Th}^* = 1 + j1\Omega$$


$$\mathbf{I}_L = \frac{\mathbf{V}_{oc}}{\mathbf{Z}_L + \mathbf{Z}_{Th}} = \frac{-3 - j1}{2} = -1.58 \angle 18.43^\circ \text{A}$$

$$P_{LMax} = \frac{1}{2} (1.58)^2 (1) = 1.25\text{W}$$





# EXAMPLE

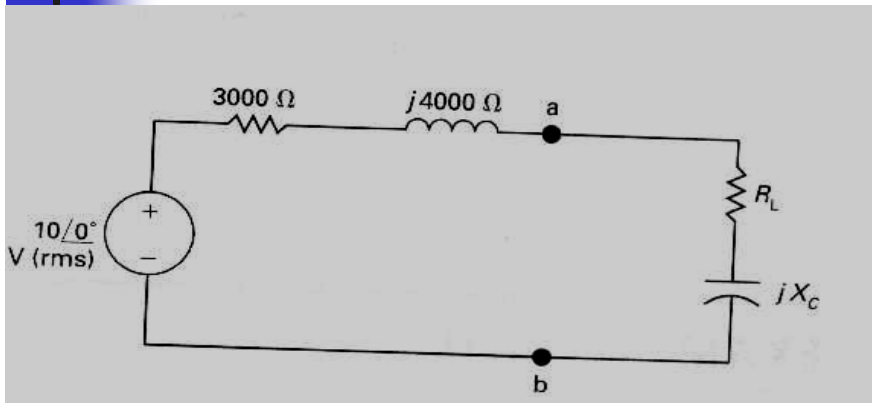

Assume that the load resistance can be varied between 0 and 4000 and that the capacitive reactance of the load can be varied between 0 and -2000. What settings of  $R_L$  and  $X_L$  transfer the most average power to the load?

Set  $X_L = -2000\Omega$ . Then set  $R_L$  as close as possible to

$$R_L = \sqrt{R_{Th}^2 + (X_L + X_{Th})^2} = \sqrt{3000^2 + (-2000 + 4000)^2} = 3605.55\Omega$$



Using  $R_L = 3605.55\Omega$ ,  $Z_L = 3605.55 - j2000\Omega$

$$I_{eff} = \frac{10}{6605.55 + j2000} = 1.4489 \angle -16.85^\circ \text{ mA}$$

$$P = (1.4489 \times 10^{-3})^2 (3605.55) = 7.57 \text{ mW}.$$



# Example

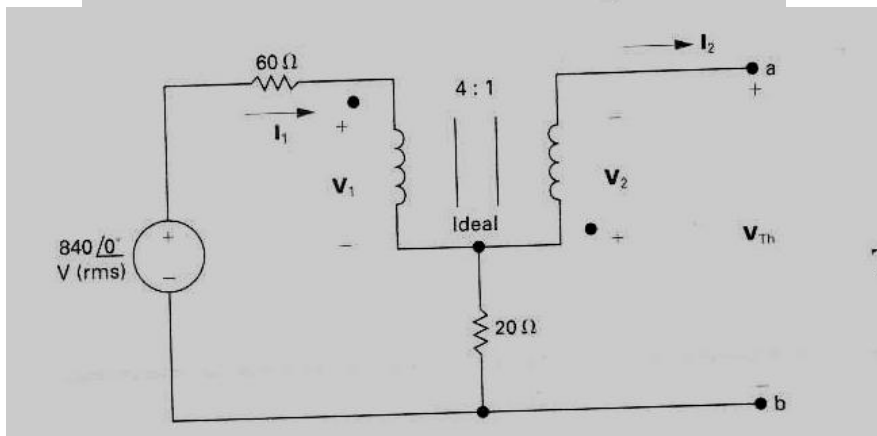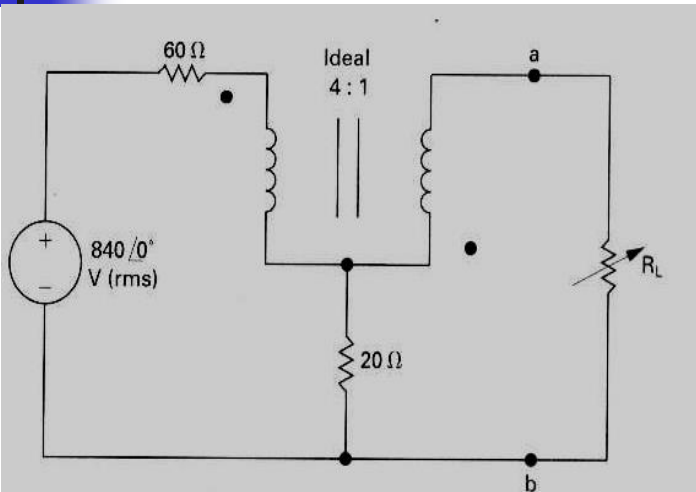

The variable resistor in the circuit is adjusted until maximum average power is delivered to  $R_L$ .


a) What is the value of  $R_L$ ?

b) What is the maximum average power delivered to  $R_L$ ?

$$\mathbf{V}_2 = \frac{1}{4} \mathbf{V}_1, \quad \mathbf{I}_1 = -\frac{1}{4} \mathbf{I}_2$$

Since  $\mathbf{I}_2$  is zero  $\mathbf{I}_1$  is zero and
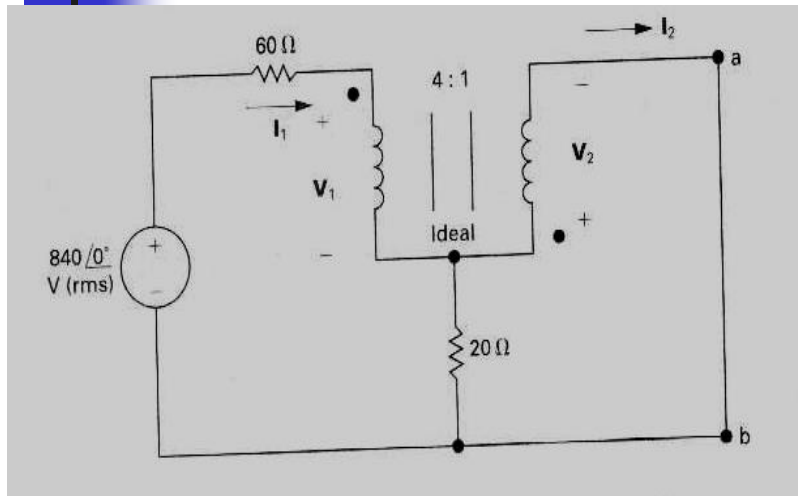
$$\mathbf{V}_{Th} = -\mathbf{V}_2 = -210 \angle 0^\circ$$



$$840\angle 0^\circ = 80\mathbf{i}_1 - 20\mathbf{i}_2 + \mathbf{v}_1 = -40\mathbf{i}_2 + \mathbf{v}_1$$

$$0 = 20\mathbf{i}_2 - 20\mathbf{i}_1 + \mathbf{v}_2 = 25\mathbf{i}_2 + \frac{\mathbf{v}_1}{4}$$

$$\mathbf{i}_2 = -6\text{ A} = \mathbf{i}_{sc}$$

$$R_{Th} = \frac{-210}{-6} = 35\Omega$$

$$P_{\max} = \left(\frac{-210}{70}\right)^2 35 = 315\text{ W}$$

