

DIGITAL SYSTEMS – II SECOND MIDTERM EXAM

Dr. Salih FADIL

April 28, 2009

#1) A sequential circuit with three positive edge-triggered D flip-flops A, B and C and one input COUNT is to be designed. When COUNT=0, the state of the circuit remains the same. When COUNT=1, the circuit goes through state transitions from 000 to 001 to 010 to 011 to 100 to 101 to 110 to 111, back to 000 and then repeats (3-bit binary up counter).


- Draw state diagram of the circuit.
- Draw two-dimensional state table of the circuit.
- Obtain minimum SOP form of flip-flop input equations and realize the circuit by using AND, OR and NOT gates.

#2) Function table for a 4-bit rotator is given as follows;

Mode Control		Register operation
S_1	S_0	
0	0	No change
0	1	Rotate left
1	0	Rotate right
1	1	Load parallel data

Realize the 4-bit rotator by using multiplexers and positive edge triggered D flip-flops.
 
#3 Consider the following sequential circuit. Assume that $S=1$ is made before the first active clock edge. Determine the Q outputs of the D flip-flops after the third active clock edge when $CTR=1$. Determine also $\bar{Q}$ outputs of the D flip flops after the second active clock edge when $CTR=0$. What does this sequential circuit do?




DIGITAL SYSTEMS-II SECOND MIDTERM EXAM

SOLUTION MANUAL

Dr. Salih FADIL

April 28, 2009

 

Value of COUNT (input)


The outputs of the circuit are the Q output of the D flip-flops (A, B and C)

	present state	Next State	
		X=1	X=0
b)	A B C	A B C	A B C
0	0 0 0	0 0 1	0 0 0
1	0 0 1	0 1 0	0 0 1
2	0 1 0	0 1 1	0 1 0
3	0 1 1	1 0 0	0 1 1
4	1 0 0	1 0 1	1 0 0
5	1 0 1	1 1 0	1 0 1
6	1 1 0	1 1 1	1 1 0
7	1 1 1	0 0 0	1 1 1

$$c) D_A(A, B, C, X) = \sum m(8, 10, 12, 14, 7, 9, 11, 13)$$

$$D_B(A, B, C, X) = \sum m(4, 6, 12, 14, 3, 5, 11, 13)$$
 
$$D_C(A, B, C, X) = \sum m(2, 6, 10, 14, 1, 5, 9, 13)$$




for D_A

- step-1) ①
 step-2) None
 step-3) ②, ③, ④ stop.

$$D_A = \bar{A}BCX + A\bar{C} + A\bar{X} + A\bar{B}$$

$$= \bar{A}BCX + A(\bar{B}CX)$$

$$D_A = A \oplus (BCX)$$

 


for D_B

- step-1) None
 step-2) ①
 step-3) ②, ③ stop.

$$D_B = \bar{B}CX + B\bar{C} + B\bar{X}$$

$$= \bar{B}CX + B(\bar{C} \cdot \bar{X})$$


$$D_B = B \oplus (CX)$$

 

for D_C


- step-1) None
 step-2) None
 step-3) ①, ②

 
$$D_C = \bar{C}X + \bar{X}C = C \oplus X$$



#2)

Mode Control		Register operation
S ₁	S ₀	
0	0	No change
0	1	Rotate left
1	0	Rotate right
1	1	Load parallel data

 

 


3) From examination of the given sequential chrt, we can see the following connections

CTR = 1.


$\bar{Q}_0$	$\rightarrow$	C input of	1 st	flip-flop.	} 4-bit ripple <u>up</u> counter
$\bar{Q}_1$	$\rightarrow$	C " "	2 nd	" "	
$\bar{Q}_2$	$\rightarrow$	C " "	3 rd	" "	
$\bar{Q}_3$	$\rightarrow$	C " "			

When CTR = 0

Q_0	$\rightarrow$	C input of	1 st	flip-flop	} 4-bit ripple <u>down</u> counter
Q_1	$\rightarrow$	C " "	2 nd	" "	
Q_2	$\rightarrow$	C " "	3 rd	" "	

 

 When CTR=1, the circuit becomes a 4-bit ripple up counter.



When CTR=0 the circuit becomes a 4-bit ripple down counter