

Name :
Student ID :

24.03.2009

Digital Systems II

Midterm I

2008-09 Spring

No script sheet is allowed.

SOLUTIONS

1.
2.
3.
4.

Good Luck

Sequential Circuit Design

1. A Universal Serial Bus (USB) communication link requires a circuit that produces the sequence 00000001. Design a synchronous sequential circuit that starts producing this sequence for input $E=1$. If $E=1$, during the last output in the sequence, the sequence repeats (Fig. 1). Otherwise, if $E=0$, the output remains constant at 1 (Fig. 2).

- a. Draw the Moore state diagram for the circuit. [15pts]
- b. Find the state table and make state assignments using Gray codes. [10pts]
- c. Design the circuit using D flip-flops and logic gates. Do not draw the logic diagram. [15pts]

 


Fig.1 Repeat the sequence if $E=1$ during the last output sequence


 


Fig.2 $E=0$, the output remains at the logic 1.

 

b.

Present State	Next State		Output
	E=0	E=1	
A	A	B	1
B	C	C	0
C	D	D	0
D	E	E	0
E	F	F	0
F	G	G	0
G	H	H	0
H	A	A	0

A = 000
B = 001
C = 011
D = 010
E = 110
F = 111
G = 101
H = 100

c.

Present State $y_2 y_1 y_0$	Input E	Next State $y_2 y_1 y_0$	Output Z
000	0	000	1
000	1	000	1
001	0	011	0
001	1	011	0
010	0	110	0
010	1	110	0
011	0	101	0
011	1	101	0
100	0	100	0
100	1	100	0
101	0	101	0
101	1	101	0
110	0	110	0
110	1	110	0
111	0	111	0
111	1	111	0

$y_2 y_1$ \ $y_0 E$	00	01	11	10
00				
01	1	1		
11	1	1	1	1
10			1	1

$y_2 y_1$ \ $y_0 E$	00	01	11	10
00				
01	1	1		
11	1	1	1	1
10			1	1

$y_2 y_1$ \ $y_0 E$	00	01	11	10
00				
01			1	1
11	1	1	1	1
10			1	1

$$y_2(t+1) = D_{y_0} = y_1 \bar{y}_0 + y_2 y_0$$

$$y_1(t+1) = D_{y_1} = y_1 \bar{y}_0 + \bar{y}_2 y_0$$

$$y_0(t+1) = D_{y_0} = \bar{y}_2 \bar{y}_1 y_0 + \bar{y}_2 y_1 E + y_2 y_1$$

04 pts

$$\text{Output } Z = \bar{y}_2 \bar{y}_1 \bar{y}_0$$

State Reduction

2. Eliminate the redundant states, if any, from the following state tables using implication table. Make the reduced state table. [20pts]

Present State	Next State		Output (Z)	
	X=0	X=1	X=0	X=1
A	A	B	0	0
B	H	C	1	0
C	H	D	1	0
D	C	D	1	0
E	C	E	1	1
F	D	E	1	1
G	B	F	0	0
H	H	C	1	0

B	X						
C	X	C-D					
D	X	C-H C-D	C-H				
E	X	X	X	X			
F	X	X	X	X	C-D		
G	X A-B X B-F	X	X	X	X	X	
H	X	✓	C-D	C-H C-D	X	X	X
	A	B	C	D	E	F	G

$$B \equiv C \quad C \equiv D \quad D \equiv H \quad E \equiv F$$

$$B \equiv D \quad C \equiv H$$

$$B \equiv H$$

From transitive property
 $B \equiv C \equiv D \equiv H$

$$(A) (B, C, D, H) (E, F) (G)$$

$$q_0 \quad q_1 \quad q_2 \quad q_3$$

	Present State	Next State		Output	
		X=0	X=1	X=0	X=1
A	q_0	q_0	q_1	0	0
B, C, D, H	q_1	q_1	q_1	1	0
E, F	q_2	q_1	q_2	1	1
G	q_3	q_1	q_2	0	0

Hardware Design for Register Transfers

3. Show the diagram of the hardware that implements the following register transfer statements:





C1: $R1 \leftarrow R1 + R2$

C2: $R1 \leftarrow R1 - R2$ (two's complement subtraction)

Use 4-bit adder/subtractor and plus external gates as needed. The control signals, C1 and C2, are mutually exclusive. [20pts]

  Select=0 $\rightarrow$ $S=A+B$ (add),
Select=1 $\rightarrow$ $S=A-B$ (subtract).



Shift Register with Parallel Load

4. 3-bit shift register operates according to the following function table: [20pts]

S1	S0	Register operation
0	0	No change
0	1	Parallel Load
1	0	Arithmetic Shift Right
1	1	Logical Shift Right



Draw logic diagram of the shift register. Implement the register with D flip-flops and 4x1 multiplexers. S1 and S0 are the mode select inputs.

