

Name :  
Student ID :

Digital Systems II, Final Exam  
2008-09 Spring

SOLUTIONS

90 min.


**Sequencing and Control**

1. Design a binary multiplier that multiplies two unsigned binary numbers by the repeated addition method. For example, to multiply 5 by 4, the digital system adds the multiplicand four times:  $5+5+5+5=20$ . The datapath of the multiplier is shown in Fig. 1. In the datapath, the multiplicand is in register BR; the multiplier is register AR; and the product will be register PR. An adder circuit adds the contents of BR to PR and store the sum in PR again,  $PR \leftarrow PR + BR$ . AR is a down-counter. A zero-detection circuit Z checks when AR becomes zero after each time that is decremented.

- a. In the binary multiplier, after signal START goes high, the multiplicand and multiplier are loaded from BUS into the corresponding registers in two successive clock cycles. By repeated addition method, the product is obtained in PR register. Adding BR to PR is stopped when the contents of AR is zero,  $Z=1$ .


Find the ASM chart for the binary multiplier. [20 pts]

- b. Design the control unit by the one flip-flop per state method. [20 pts]

 


**Figure 1** Datapath of the binary multiplier
  
# 1-a. ASM chart




b.



Name:  
Student ID:

### Memory Basics

 
2. Using four 128Kx16 RAM chips and a decoder, construct the block diagram for a 512Kx16 RAM. Find the address range of each RAM. [20pts]



$$512K = 2^9 \cdot 2^{10} = 2^{19}$$

19 address lines.

$$128K = 2^7 \cdot 2^{10} = 2^{17}$$

 

# Address Lines


| 18 | 17 | 16 | 15 | ... | 2 | 1 | 0 |       |        |
|----|----|----|----|-----|---|---|---|-------|--------|
| 0  | 0  | 0  | 0  | ... | 0 | 0 | 0 | 00000 | RAM #0 |
| 0  | 0  | 1  | 1  | ... | 1 | 1 | 1 | 1FFFF |        |
| 0  | 1  | 0  | 0  | ... | 0 | 0 | 0 | 20000 | RAM #1 |
| 0  | 1  | 1  | 1  | ... | 1 | 1 | 1 | 3FFFF |        |
| 1  | 0  | 0  | 0  | ... | 0 | 0 | 0 | 40000 | RAM #2 |
| 1  | 0  | 1  | 0  | ... | 1 | 1 | 1 | 5FFFF |        |
| 1  | 1  | 0  | 0  | ... | 0 | 0 | 0 | 60000 | RAM #3 |
| 1  | 1  | 1  | 1  | ... | 1 | 1 | 1 | 7FFFF |        |

Selects  
one of four  
128Kx16 RAM


17 address lines  
for each 128Kx16 RAM

 3. Specify the 16-bit control word that must be applied to the datapath of Fig. 2 to implement the following microoperations: [ 20 pts]

- $R5 \leftarrow sr R6$
- $R1 \leftarrow R2 + R3$
- $R1 \leftarrow R7 + 1$
- $R2 \leftarrow 0$
- $R2 \leftarrow \text{Data In}$



(a) Block diagram

 

(b) Control word

Figure 2 Datapath with control variables

$R5 \leftarrow sr R6$

101 000 110 0 1101 0 1 = A335 hex

$R1 \leftarrow R2 + R3$

Name:  
Student ID:

$$R1 \leftarrow R7 + 1$$

$$001\ 111\ 000\ 0\ 0001\ 0\ 1 = 3C05\ \text{hex}$$

$$R2 \leftarrow 0 \quad \text{or} \quad R2 \leftarrow R3 \oplus R3$$

$$010\ 011\ 011\ 0\ 1010\ 0\ 1 = 4DA9\ \text{hex}$$

$$R2 \leftarrow \text{Data In}$$

$$010\ 000\ 000\ 0\ 0000\ 1\ 1 = 4003\ \text{hex}$$

#### Single-Cycle Computer

4. Write an assembly-language program using the instructions of the single-cycle computer that performs the arithmetic operation  $2 \cdot N_1 - N_2 + 6$ . The operands  $N_1$  and  $N_2$  are stored in the memory locations 20 and 21(decimal) respectively. Assume that register R2 contains the value of 20(decimal). The result is to be placed in 25(decimal). [20pts]

Give a comment for every instruction in the assembly program.

INC R1            Increment R1 or  $R1 \leftarrow R1 + 1$

**Table 1** Instruction specifications for the single-cycle computer

| Instruction        | Opcode  | Mnemonic | Format   | Description                                  | Status Bits |
|--------------------|---------|----------|----------|----------------------------------------------|-------------|
| Move A             | 0000000 | MOVA     | RD,RA    | $R[DR] \leftarrow R[SA]$                     | N, Z        |
| Increment          | 0000001 | INC      | RD,RA    | $R[DR] \leftarrow R[SA] + 1$                 | N, Z        |
| Add                | 0000010 | ADD      | RD,RA,RB | $R[DR] \leftarrow R[SA] + R[SB]$             | N, Z        |
| Subtract           | 0000101 | SUB      | RD,RA,RB | $R[DR] \leftarrow R[SA] - R[SB]$             | N, Z        |
| Decrement          | 0000110 | DEC      | RD,RA    | $R[DR] \leftarrow R[SA] - 1$                 | N, Z        |
| AND                | 0001000 | AND      | RD,RA,RB | $R[DR] \leftarrow R[SA] \wedge R[SB]$        | N, Z        |
| OR                 | 0001001 | OR       | RD,RA,RB | $R[DR] \leftarrow R[SA] \vee R[SB]$          | N, Z        |
| Exclusive OR       | 0001010 | XOR      | RD,RA,RB | $R[DR] \leftarrow R[SA] \oplus R[SB]$        | N, Z        |
| NOT                | 0001011 | NOT      | RD,RA    | $R[DR] \leftarrow \overline{R[SA]}$          | N, Z        |
| Move B             | 0001100 | MOVB     | RD,RB    | $R[DR] \leftarrow R[SB]$                     |             |
| Shift Right        | 0001101 | SHR      | RD,RB    | $R[DR] \leftarrow sr\ R[SB]$                 |             |
| Shift Left         | 0001110 | SHL      | RD,RB    | $R[DR] \leftarrow sl\ R[SB]$                 |             |
| Load Immediate     | 1001100 | LDI      | RD,OP    | $R[DR] \leftarrow zf\ OP$                    |             |
| Add Immediate      | 1000010 | ADI      | RD,RA,OP | $R[DR] \leftarrow R[SA] + zf\ OP$            |             |
| Load               | 0010000 | LD       | RD,RA    | $R[DR] \leftarrow M[SA]$                     |             |
| Store              | 0100000 | ST       | RA,RB    | $M[SA] \leftarrow R[SB]$                     |             |
| Branch on Zero     | 1100000 | BRZ      | RA,AD    | if $(R[SA] = 0)$ $PC \leftarrow PC + se\ AD$ |             |
| Branch on Negative | 1100001 | BRN      | RA,AD    | if $(R[SA] < 0)$ $PC \leftarrow PC + se\ AD$ |             |
| Jump               | 1110000 | JMP      | RA       | $PC \leftarrow R[SA]$                        |             |

R2: pointer register that holds the address of the operand N1.

LD R3, R2 Load R3 with operand N1  
in memory.

SHL R3, R3 Multiply contents of R3 by 2

INC R2, R2 Increment R2 ( $R2=21$ )

LD R4, R2 Load R4 with operand N2

SUB R3, R3, R4 Subtract R4 from R3

ADI R3, R3, 6 Add 6 to R3

ADI R2, R2, 4 Add 4 to R2 ( $R2=25$ )

ST R2, R3 Store R3 in memory location 25.