 


SOLUTIONS

..... ÖĞRETİM

1. Design a sequential circuit with one input X and one output Z that implements the state diagram in Figure 1. Use D flip-flops. Do not draw the logic diagram. Use Gray codes for state assignment. (40pts)



Y_1, Y_0 : State variable

A = 00
B = 01
C = 11

Figure 1. State diagram

Moore circuit
State Table

PS	NS		Output
	X=0	X=1	
A	A	B	0
B	A	C	0
C	A	C	1

Transition Table

PS $Y_1 Y_0$	NS		Output Z
	X=0	X=1	
00	00	01	0
01	00	11	0
11	00	11	1
10	XX	XX	0

$Y_1 Y_0$	X=0	X=1
00		
01		1
11		1
10	X	X

$Y_1 Y_0$	X
	1
	1
	1
X	X

$$D_{Y_1} = Y_1(t+1) = Y_0 X \quad D_{Y_0} = Y_0(t+1) = X$$

Flip-Flop input equations



Output Equation: $Z = Y_1 Y_0$

2. Show the diagram of the hardware that implements the register transfer statements

C1: $A \leftarrow 2A$

C2: $A \leftarrow B, B \leftarrow A$

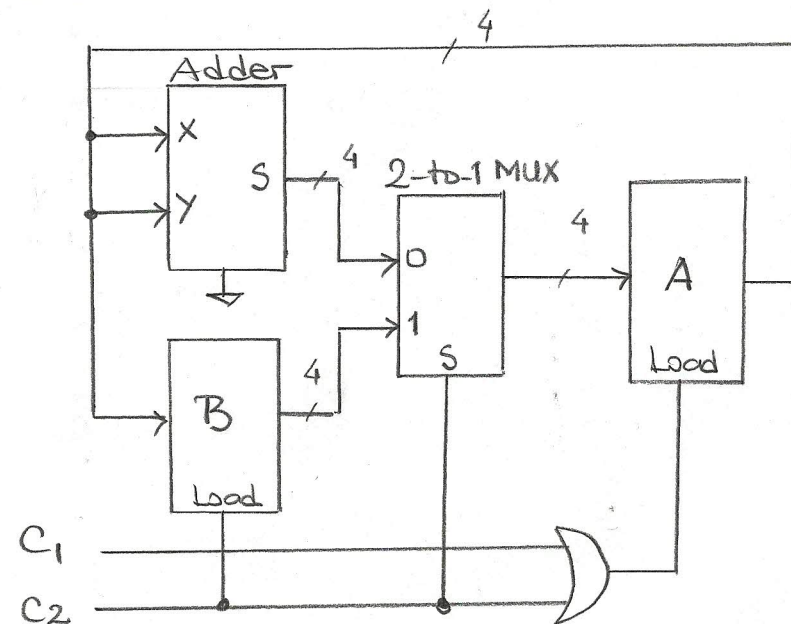 Use the register with parallel load and a 4-bit adder. You can also use additional logic gates or functions in the hardware. (30pts)



3. Register A has the following transfer functions:

- C1: $A \leftarrow sl A$ (logical shift left)
- C2: $A \leftarrow asl A$ (arithmetic shift left)
- C3: $A \leftarrow sr A$ (logical shift right)
- C4: $A \leftarrow asr A$ (arithmetic shift right)
- C5: $A \leftarrow rol A$ (rotate left)
- C6: $A \leftarrow ror A$ (rotate right)

A : n -bit register

For the register cell (A_i), find the flip-flop input equation $D_{i,FF}$ using simple approach technique. The control signals are mutually exclusive. (30pts)

$$D_{i,FF} = \overline{LOAD} A_i + LOAD \cdot D_i$$

$$LOAD = C1 + C2 + C3 + C4 + C5 + C6$$

$$D_i = (C1 + C2 + C5) A_{i-1} + (C3 + C4 + C6) A_{i+1}$$

$$(i = 1, 2, \dots, n-2)$$

$$D_0 = (C3 + C4 + C6) A_1 + C5 \cdot A_{n-1}$$

$$D_{n-1} = (C1 + C2 + C5) A_{n-2} + C4 A_{n-1} + C6 \cdot A_0$$

