

Lab 6 : Part b : Digital to Analog Conversion

Objectives

- To become familiar with digital to analog conversion

Apparatus

DAC0808,
Resistors 4.7 Kohm X 3,
Capacitors 100 nf,
Connection wires or Jumper wires,
Wire Stripper / Cutter,

Background:

A digital to analog converter (DAC) is a device that outputs a voltage proportional to an input binary number. Such a device is frequently required in applications where a digital computer must generate a signal that has an influence on the 'real' world. Real world signals are continuously variable i.e. analogue signals whereas signals within a computer have a finite number of values i.e. discrete signals. A DAC is used to perform the necessary conversion.

Procedure:

- 1- Connect the circuit given in Figure 1. Select $R_{14}=R_{15}=R_L=4.7\text{ Kohm}$, $C=100\text{ nF}$. Also connect digital inputs to the switches on the training set.
- 2- Set $V_{EE} = -15\text{V}$
- 3- Set $V_{ref}=5\text{ V}$.
- 4- By using your OSCILLOSCOPE, measure the corresponding output voltages for the digital input values given in table 1.
- 5- Set $V_{ref}=10\text{ V}$ and repeat Step 4.

Table 1.

DIGITAL INPUT	ANALOG OUTPUT	
	$V_{REF}=10\text{V}$	$V_{REF}=5\text{V}$
0 0 0 0 0 0 0 0		
1 1 1 1 1 1 1 1		
1 0 0 0 0 0 0 0		
0 1 0 0 0 0 0 0		
0 0 1 0 0 0 0 0		
0 0 0 0 0 0 0 1		
0 0 1 1 0 0 1 1		
0 1 0 1 0 0 0 1		
1 0 0 0 0 0 0 1		
0 0 0 1 0 0 0 0		

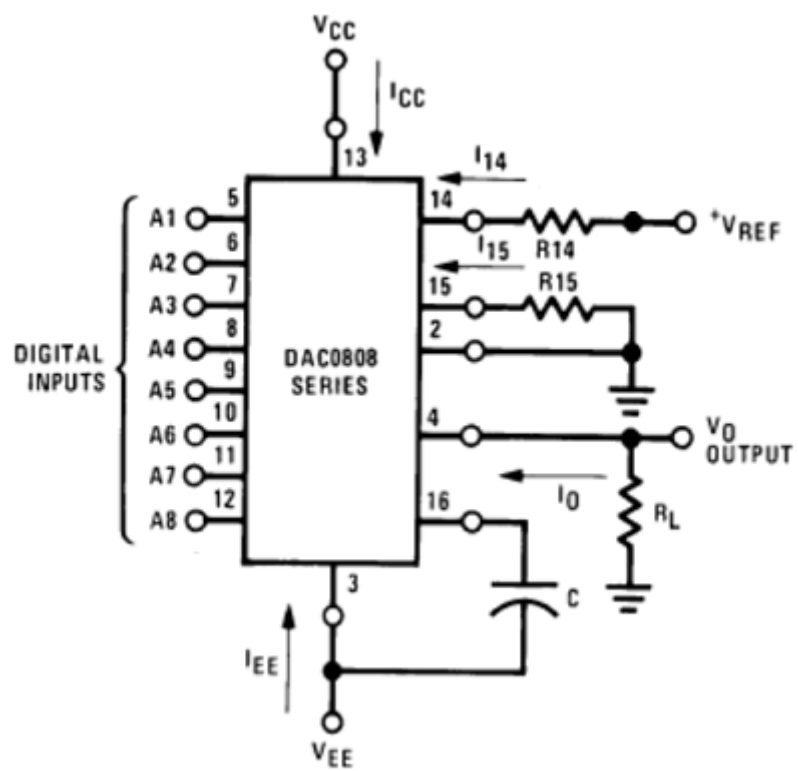


Figure 1