
Logic and Computer Design Fundamentals

Chapter 7 – Registers and Register Transfers

Part 1 – Registers, Microoperations and Implementations

Charles Kime & Thomas Kaminski

© 2004 Pearson Education, Inc.

[Terms of Use](#)

(Hyperlinks are active in View Show mode)

Overview


- **Part 1 - Registers, Microoperations and Implementations**
 - Registers and load enable
 - Register transfer operations
 - Microoperations - arithmetic, logic, and shift
 - Microoperations on a single register
 - Multiplexer-based transfers
 - Shift registers
- **Part 2 - Counters, register cells, buses, & serial operations**
 - Microoperations on single register (continued)
 - Counters
 - Register cell design
 - Multiplexer and bus-based transfers for multiple registers
 - Serial transfers and microoperations

Registers

- Register – a collection of binary storage elements
- In theory, a register is sequential logic which can be defined by a state table
- More often think of a register as storing a vector of binary values
- Frequently used to perform simple data storage and data movement and processing operations

 Example: 2-bit Register

- How many states are there?
- How many input combinations?
Output combinations
- What is the output function?
- What is the next state function?
- Moore or Mealy?
State Table:



Current State A1 A0	Next State A1(t+1) A0(t+1) For I1 I0 =	Output (=A1 A0) Y1 Y0
0 0	00 01 10 11	0 0
0 1	00 01 10 11	0 1
1 0	00 01 10 11	1 0
1 1	00 01 10 11	1 1

- What are the quantities above for an n -bit register?

Register Design Models

- Due to the large numbers of states and input combinations as n becomes large, the state diagram/state table model is not feasible!
- What are methods we can use to design registers?
 - Add predefined combinational circuits to registers
 - Example: To count up, connect the register flip-flops to an incrementer
 - Design individual cells using the state diagram/state table model and combine them into a register
 - A 1-bit cell has just two states
 - Output is usually the state variable

Logic and Computer Design Fundamentals
PowerPoint® Slides
© 2004 Pearson Education, Inc.

Chapter 7 - Part 1 5

Register Storage


- **Expectations:**
 - A register can store information for multiple clock cycles
 - To “store” or “load” information should be controlled by a signal
- **Reality:**
 - A D flip-flop register loads information on every clock cycle
- **Realizing expectations:**
 - Use a signal to block the clock to the register,
 - Use a signal to control feedback of the output of the register back to its inputs, or
 - Use other SR or JK flip-flops which for (0,0) applied store their state
- **Load is a frequent name for the signal that controls register storage and loading**
 - Load = 1: Load the values on the data inputs
 - Load = 0: Store the values in the register

Logic and Computer Design Fundamentals
PowerPoint® Slides
© 2004 Pearson Education, Inc.

Chapter 7 - Part 1 6

Registers with Clock Gating

 - **Load** signal is used to enable the clock signal to pass through if 1 and prevent the clock signal from passing through if 0.
- **Example: For Positive Edge-Triggered or Negative Pulse Master-Slave Flip-flop:**



- What logic is needed for gating? $\text{Gated Clock} = \text{Clock} + \overline{\text{Load}}$
- What is the problem? Clock Skew of gated clocks with respect to clock or each other

Registers with Load-Controlled Feedback


- A more reliable way to selectively load a register:
 - Run the clock continuously, and
 - Selectively use a load control to change the register contents.

- **Example: 2-bit register with Load Control:**

- For Load = 0, loads register contents (hold current values)

- For Load = 1, loads input values (load new values)

 
- Hardware more complex than clock gating, but free of timing problems



Register Transfer Operations

- **Register Transfer Operations** – The movement and processing of data stored in registers
- **Three basic components:**
 - set of registers
 - operations
 - control of operations
- **Elementary Operations** -- load, count, shift, add, bitwise "OR", etc.
 - Elementary operations called *microoperations*

Register Notation

 


- **Letters and numbers** – denotes a register (ex. R2, PC, IR)
- **Parentheses ()** – denotes a range of register bits (ex. R1(1), PC(7:0), AR(L))
- **Arrow (←)** – denotes data transfer (ex. R1 ← R2, PC(L) ← R0)
- **Comma** – separates parallel operations
- **Brackets []** – Specifies a memory address (ex. R0 ← M[AR], R3 M[PC])

Conditional Transfer

- If $(K1 = 1)$ then $(R2 \leftarrow R1)$ K_1 is shortened to

$K1: (R2 \leftarrow R1)$

 where $K1$ is a control variable specifying a conditional execution of the microoperation.



Microoperations

- **Logical Groupings:**
 - Transfer - move data from one set of registers to another
 - Arithmetic - perform arithmetic on data in registers
 - Logic - manipulate data or use bitwise logical operations
 - Shift - shift data in registers

Arithmetic operations

+ Addition
- Subtraction
* Multiplication
/ Division

Logical operations

∨ Logical OR
∧ Logical AND
⊕ Logical Exclusive OR
— Not

Example Microoperations

- Add the content of R1 to the content of R2 and place the result in R1.

$$R1 \leftarrow R1 + R2$$

- Multiply the content of R1 by the content of R6 and place the result in PC.

$$PC \leftarrow R1 * R6$$

- Exclusive OR the content of R1 with the content of R2 and place the result in R1.

$$R1 \leftarrow R1 \oplus R2$$

Example Microoperations (Continued)

- Take the 1's Complement of the contents of R2 and place it in the PC.
- $PC \leftarrow \overline{R2}$
- On condition K1 OR K2, the content of R1 is Logic bitwise Ored with the content of R3 and the result placed in R1.
- $(K1 + K2): R1 \leftarrow R1 \vee R3$
- NOTE: "+" (as in $K_1 + K_2$) and means "OR." In $R1 \leftarrow R1 + R3$, + means "plus."

Control Expressions

- The control expression for an operation appears to the left of the operation and is separated from it by a colon
- Control expressions specify the logical condition for the operation to occur
- Control expression values of:
 - Logic "1" -- the operation occurs.
 - Logic "0" -- the operation is does not occur.
- Example:
 $\overline{X} K1 : R1 \leftarrow R1 + R2$
 $X K1 : R1 \leftarrow R1 + \overline{R2} + 1$
- Variable K1 enables the add or subtract operation.
- If $X = 0$, then $\overline{X} = 1$ so $\overline{X} K1 = 1$, activating the addition of R1 and R2.
- If $X = 1$, then $X K1 = 1$, activating the addition of R1 and the two's complement of R2 (subtract).

Arithmetic Microoperations

From Table 7-3:	Symbolic Designation	Description
	$R0 \leftarrow R1 + R2$	Addition
	$R0 \leftarrow \overline{R1}$	Ones Complement
	$R0 \leftarrow \overline{\overline{R1}} + 1$	Two's Complement
	$R0 \leftarrow R2 + \overline{R1} + 1$	R2 minus R1 (2's Comp)
	$R1 \leftarrow R1 + 1$	Increment (count up)
	$R1 \leftarrow R1 - 1$	Decrement (count down)

- Note that any register may be specified for source 1, source 2, or destination.
- These simple microoperations operate on the whole word

Logical Microoperations

- From Table 7-4:

Symbolic Designation	Description
$R0 \leftarrow \overline{R1}$	Bitwise NOT
$R0 \leftarrow R1 \vee R2$	Bitwise OR (sets bits)
$R0 \leftarrow R1 \wedge R2$	Bitwise AND (clears bits)
$R0 \leftarrow R1 \oplus R2$	Bitwise EXOR (complements bits)

Logical Microoperations (continued)

- Let $R1 = 10101010$,
and $R2 = 11110000$
- Then after the operation, $R0$ becomes:

R0	Operation
01010101	$R0 \leftarrow \overline{R1}$
11111010	$R0 \leftarrow R1 \vee R2$
10100000	$R0 \leftarrow R1 \wedge R2$
01011010	$R0 \leftarrow R1 \oplus R2$

Shift Microoperations

- From Table 7-5:
- Let R2 = 11001001
- Then after the operation, R1 becomes:

Symbolic Designation	Description
$R1 \leftarrow sl\ R2$	Shift Left
$R1 \leftarrow sr\ R2$	Shift Right

R1	Operation
10010010	$R1 \leftarrow sl\ R2$
01100100	$R1 \leftarrow sr\ R2$

- Note: These shifts "zero fill". Sometimes a separate flip-flop is used to provide the data shifted in, or to "catch" the data shifted out.
- Other shifts are possible (rotates, arithmetic) (see Chapter 11).

Logic and Computer Design Fundamentals
PowerPoint® Slides
© 2004 Pearson Education, Inc.

Chapter 7 - Part 1 19

Register Transfer Structures


- Multiplexer-Based Transfers - Multiple inputs are selected by a multiplexer dedicated to the register
- Bus-Based Transfers - Multiple inputs are selected by a shared multiplexer driving a bus that feeds inputs to multiple registers
- Three-State Bus - Multiple inputs are selected by 3-state drivers with outputs connected to a bus that feeds multiple registers
- Other Transfer Structures - Use multiple multiplexers, multiple buses, and combinations of all the above

Logic and Computer Design Fundamentals
PowerPoint® Slides
© 2004 Pearson Education, Inc.

Chapter 7 - Part 1 20

Multiplexer-Based Transfers

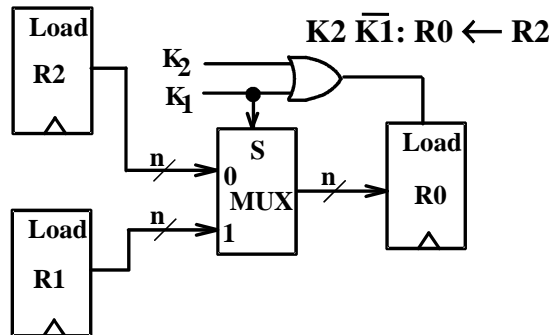- Multiplexers connected to register inputs produce flexible transfer structures (Note: Clocks are omitted for clarity)
- The transfers are: $K1: R0 \leftarrow R1$
 $K2 \bar{K1}: R0 \leftarrow R2$




Logic and Computer Design Fundamentals
 PowerPoint® Slides
 © 2004 Pearson Education, Inc.

Chapter 7 - Part 1 21

Shift Registers

 - Shift Registers move data laterally within the register toward its MSB or LSB position
- In the simplest case, the shift register is simply a set of D flip-flops connected in a row like this:




- Data input, In, is called a *serial input* or the *shift right input*.
- Data output, Out, is often called the *serial output*.
- The vector (A, B, C, Out) is called the *parallel output*.

Logic and Computer Design Fundamentals
 PowerPoint® Slides
 © 2004 Pearson Education, Inc.

Chapter 7 - Part 1 22

Shift Registers (continued)

 - The behavior of the serial shift register is given in the listing on the lower right
- T0 is the register state just before the first clock pulse occurs
- T1 is after the first pulse and before the second.
- Initially unknown states are denoted by “?”
- Complete the last three rows of the table




CP	In	A	B	C	Out
T0	0	?	?	?	?
T1	1	0	?	?	?
T2	1	1	0	?	?
T3	0	1	1	0	?
T4	1				
T5	1				
T6	1				

Logic and Computer Design Fundamentals
PowerPoint® Slides
© 2004 Pearson Education, Inc.

Chapter 7 - Part 1 23

Parallel Load Shift Registers

 - By adding a mux between each shift register stage, data can be shifted or loaded
- If SHIFT is low, A and B are replaced by the data on D_A and D_B lines, else data shifts right on each clock.
- By adding more bits, we can make *n*-bit parallel load shift registers.
- A parallel load shift register with an added “hold” operation that stores data unchanged is given in Figure 7-10 of the text.



Logic and Computer Design Fundamentals
PowerPoint® Slides
© 2004 Pearson Education, Inc.

Chapter 7 - Part 1 24

Shift Registers with Additional Functions

- By placing a 4-input multiplexer in front of each D flip-flop in a shift register, we can implement a circuit with shifts right, shifts left, parallel load, hold.
- Shift registers can also be designed to shift more than a single bit position right or left
- Shift register can be designed to shift a variable number of bit positions specified by a variable called a *shift amount*.

Terms of Use

- © 2004 by Pearson Education, Inc. All rights reserved.
- The following terms of use apply in addition to the standard Pearson Education [Legal Notice](#).
- Permission is given to incorporate these materials into classroom presentations and handouts only to instructors adopting Logic and Computer Design Fundamentals as the course text.
- Permission is granted to the instructors adopting the book to post these materials on a protected website or protected ftp site in original or modified form. All other website or ftp postings, including those offering the materials for a fee, are prohibited.
- You may not remove or in any way alter this Terms of Use notice or any trademark, copyright, or other proprietary notice, including the copyright watermark on each slide.
- [Return to Title Page](#)