

---

# Logic and Computer Design Fundamentals

## Chapter 10 – Computer Design Basics

### Part 2 – A Simple Computer

Charles Kime & Thomas Kaminski

© 2004 Pearson Education, Inc.

[Terms of Use](#)

(Hyperlinks are active in View Show mode)

## Overview

---

- **Part 1 – Datapaths**
  - Introduction
  - Datapath Example
  - Arithmetic Logic Unit (ALU)
  - Shifter
  - Datapath Representation and Control Word
- **Part 2 – A Simple Computer**
  - Instruction Set Architecture (ISA)
  - Single-Cycle Hardwired Control
    - PC Function
    - Instruction Decoder
    - Example Instruction Execution
- **Part 3 – Multiple Cycle Hardwired Control**
  - Single Cycle Computer Issues
  - Sequential Control Design

# Instruction Set Architecture (ISA) for Simple Computer (SC)

---

- A programmable system uses a sequence of *instructions* to control its operation
- An typical instruction specifies:
  - Operation to be performed
  - Operands to use, and
  - Where to place the result, or
  - Which instruction to execute next
- Instructions are stored in RAM or ROM as a *program*
- The addresses for instructions in a computer are provided by a *program counter (PC)* that can
  - Count up
  - Load a new address based on an instruction and, optionally, status information


## Instruction Set Architecture (ISA) (continued)

---

- The PC and associated control logic are part of the Control Unit
- Executing an instruction - activating the necessary sequence of operations specified by the instruction
- Execution is controlled by the control unit and performed:
  - In the datapath
  - In the control unit
  - In external hardware such as memory or input/output
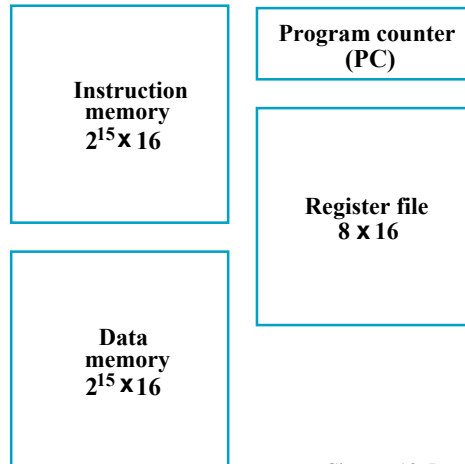
## ISA: Storage Resources

- The storage resources are "visible" to the programmer at the lowest software level (typically, machine or assembly language)
- **Storage resources for the SC =>**
- Separate instruction and data memories imply "Harvard architecture"
- Done to permit use of single clock cycle per instruction implementation
- Due to use of "cache" in modern computer architectures, is a fairly realistic model



Logic and Computer Design Fundamentals  
PowerPoint® Slides  
© 2004 Pearson Education, Inc.

Chapter 10 Part 2 5

## ISA: Instruction Format

- A instruction consists of a bit vector
- The *fields* of an instruction are subvectors representing specific functions and having specific binary codes defined
- The *format* of an instruction defines the subvectors and their function
- An ISA usually contains multiple formats
- The SC ISA contains the three formats presented on the next slide

Logic and Computer Design Fundamentals  
PowerPoint® Slides  
© 2004 Pearson Education, Inc.

Chapter 10 Part 2 6

# ISA: Instruction Format

15	9	8	6	5	3	2	0
Opcode				Destination register (DR)	Source register A (SA)	Source register B (SB)	

(a) Register

15	9	8	6	5	3	2	0
Opcode				Destination register (DR)	Source register A (SA)	Operand (OP)	

(b) Immediate

15	9	8	6	5	3	2	0
Opcode				Address (AD) (Left)	Source register A (SA)	Address (AD) (Right)	

(c) Jump and Branch

- The three formats are: Register, Immediate, and Jump and Branch
- All formats contain an Opcode field in bits 9 through 15.
- The Opcode specifies the operation to be performed
- More details on each format are provided on the next three slides

## ISA: Instruction Format (continued)

15	9	8	6	5	3	2	0
Opcode				Destination register (DR)	Source register A (SA)	Source register B (SB)	

(a) Register

- This format supports instructions represented by:
  - $R1 \leftarrow R2 + R3$
  - $R1 \leftarrow sl\ R2$
- There are three 3-bit register fields:
  - DR - specifies destination register (R1 in the examples)
  - SA - specifies the A source register (R2 in the first example)
  - SB - specifies the B source register (R3 in the first example and R2 in the second example)
- Why is R2 in the second example SB instead of SA?
  - The source for the shifter in our datapath to be used in implementation is Bus B rather than Bus A

## ISA: Instruction Format (continued)

15	9	8	6	5	3	2	0
Opcode				Destination register (DR)	Source register A (SA)	Operand (OP)	

(b) Immediate

- This format supports instructions described by:
  - $R1 \leftarrow R2 + 3$
- The B Source Register field is replaced by an Operand field OP which specifies a constant.
- The Operand:
  - 3-bit constant
  - Values from 0 to 7
- The constant:
  - Zero-fill (on the left of) the Operand to form 16-bit constant
  - 16-bit representation for values 0 through 7

Logic and Computer Design Fundamentals  
PowerPoint® Slides  
© 2004 Pearson Education, Inc.

Chapter 10 Part 2 9

## ISA: Instruction Format (continued)

15	9	8	6	5	3	2	0
Opcode				Address (AD) (Left)	Source register A (SA)	Address (AD) (Right)	

(c) Jump and Branch

- This instruction supports changes in the sequence of instruction execution by adding an extended, 6-bit, signed 2s-complement *address offset* to the PC value
- The 6-bit Address (AD) field replaces the DR and SB fields
  - Example: Suppose that a jump is specified by the Opcode and the PC contains 45 (0...0101101) and Address contains -12 (110100). Then the new PC value will be:  
 $0...0101101 + (1...110100) = 0...0100001$  ( $45 + (-12) = 33$ )
- The SA field is retained to permit jumps and branches on N or Z based on the contents of Source register A

Logic and Computer Design Fundamentals  
PowerPoint® Slides  
© 2004 Pearson Education, Inc.

Chapter 10 Part 2 10

# ISA: Instruction Specifications

- The specifications provide:
  - The name of the instruction
  - The instruction's opcode
  - A shorthand name for the opcode called a *mnemonic*
  - A specification for the instruction format
  - A register transfer description of the instruction, and
  - A listing of the status bits that are meaningful during an instruction's execution (not used in the architectures defined in this chapter)

Logic and Computer Design Fundamentals  
PowerPoint® Slides  
© 2004 Pearson Education, Inc.

Chapter 10 Part 2 11

## ISA: Instruction Specifications (continued)

### Instruction Specifications for the SimpleComputer - Part 1

Instruction	Opcode	Mnemonic	Format	Description	Status Bits
Move A	0000000	MOVA	RD,RA	$R[DR] \leftarrow R[SA]$	N, Z
Increment	0000001	INC	RD,RA	$R[DR] \leftarrow R[SA] + 1$	N, Z
Add	0000010	ADD	RD,RA,RB	$R[DR] \leftarrow R[SA] + R[SB]$	N, Z
Subtract	0000101	SUB	RD,RA,RB	$R[DR] \leftarrow R[SA] - R[SB]$	N, Z
Decrement	0000110	DEC	RD,RA	$R[DR] \leftarrow R[SA] - 1$	N, Z
AND	0001000	AND	RD,RA,RB	$R[DR] \leftarrow R[SA] \wedge R[SB]$	N, Z
OR	0001001	OR	RD,RA,RB	$R[DR] \leftarrow R[SA] \vee R[SB]$	N, Z
Exclusive OR	0001010	XOR	RD,RA,RB	$R[DR] \leftarrow R[SA] \oplus R[SB]$	N, Z
NOT	0001011	NOT	RD,RA	$R[DR] \leftarrow \overline{R[SA]}$	N, Z

Logic and Computer Design Fundamentals  
PowerPoint® Slides  
© 2004 Pearson Education, Inc.

Chapter 10 Part 2 12

# ISA: Instruction Specifications (continued)

## Instruction Specifications for the Simple Computer - Part 2

Instruction	Opcode	Mnemonic	Format	Description	Status Bits
Move B	0001100	MOVB	RD,RB	$R[DR] \leftarrow R[SB]$	
Shift Right	0001101	SHR	RD,RB	$R[DR] \leftarrow sr\ R[SB]$	
Shift Left	0001110	SHL	RD,RB	$R[DR] \leftarrow sl\ R[SB]$	
Load Immediate	1001100	LDI	RD, OP	$R[DR] \leftarrow zf\ OP$	
Add Immediate	1000010	ADI	RD,RA,OP	$R[DR] \leftarrow R[SA] + zf\ OP$	
Load	0010000	LD	RD,RA	$R[DR] \leftarrow M[SA]$	
Store	0100000	ST	RA,RB	$M[SA] \leftarrow R[SB]$	
Branch on Zero	1100000	BRZ	RA,AD	if $(R[SA] = 0)$ $PC \leftarrow PC + se\ AD$	
Branch on Negative	1100001	BRN	RA,AD	if $(R[SA] < 0)$ $PC \leftarrow PC + se\ AD$	
Jump	1110000	JMP	RA	$PC \leftarrow R[SA]$	


## ISA: Example Instructions and Data in Memory

### Memory Representation of Instructions and Data

Decimal Address	Memory Contents	Decimal Opcode	Other Fields	Operation
25	0000101 001 010 011	5 (Subtract)	DR:1, SA:2, SB:3	$R1 \leftarrow R2 - R3$
35	0100000 000 100 101	32 (Store)	SA:4, SB:5	$M[R4] \leftarrow R5$
45	1000010 010 111 011	66 (Add Immediate)	DR:2, SA:7, OP:3	$R2 \leftarrow R7 + 3$
55	1100000 101 110 100	96 (Branch on Zero)	AD: 44, SA:6	If $R6 = 0$ , $PC \leftarrow PC - 20$
70	00000000011000000	Data = 192. After execution of instruction in 35, Data = 80.		
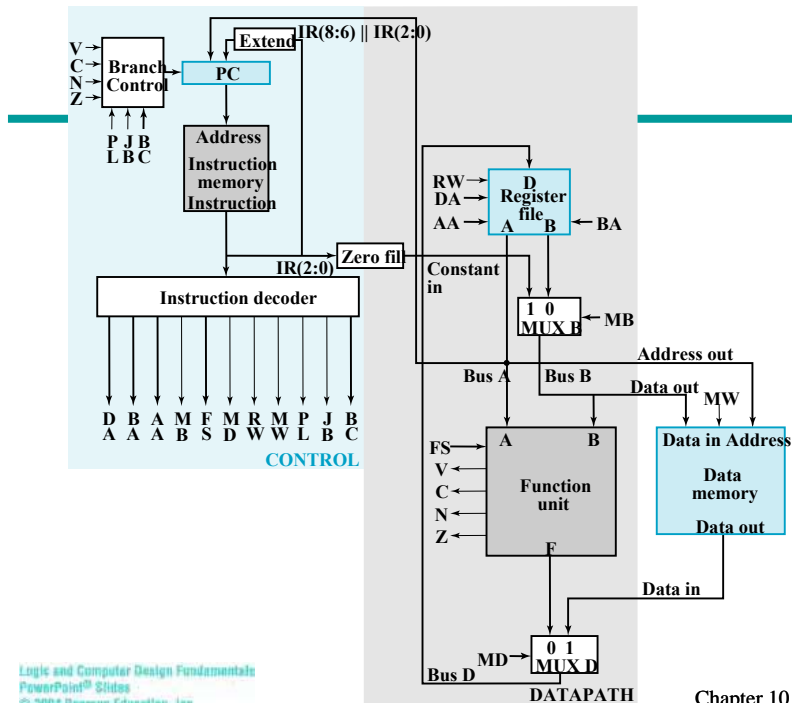
# Single-Cycle Hardwired Control

- Based on the ISA defined, design a computer architecture to support the ISA
- The architecture is to fetch and execute each instruction in a single clock cycle
- The datapath from Figure 10-11 will be used
- The control unit will be defined as a part of the design
- The block diagram is shown on the next slide





# The Control Unit

- The Data Memory has been attached to the Address Out and Data Out and Data In lines of the Datapath.
- The MW input to the Data Memory is the Memory Write signal from the Control Unit.
- For convenience, the Instruction Memory, which is not usually a part of the Control Unit is shown within it.
- The Instruction Memory address input is provided by the PC and its instruction output feeds the Instruction Decoder.
- Zero-filled IR(2:0) becomes Constant In
- Extended IR(8:6) || IR(2:0) and Bus A are address inputs to the PC.
- The PC is controlled by Branch Control logic

Logic and Computer Design Fundamentals  
PowerPoint® Slides  
© 2004 Pearson Education, Inc.

Chapter 10 Part 2 17

## PC Function

- PC function is based on instruction specifications involving jumps and branches taken from Slide 13:

Branch on Zero	BRZ	if (R[SA] = 0) $PC \leftarrow PC + se\ AD$
Branch on Negative	BRN	if (R[SA] < 0) $PC \leftarrow PC + se\ AD$
Jump	JMP	$PC \leftarrow R[SA]$
- In addition to the above register transfers, the PC must also implement:  $PC \leftarrow PC + 1$
- The first two transfers above require addition to the PC of: Address Offset = Extended IR(8:6) || IR(2:0)
- The third transfer requires that the PC be loaded with: Jump Address = Bus A = R[SA]
- The counting function of the PC requires addition to the PC of 1

Logic and Computer Design Fundamentals  
PowerPoint® Slides  
© 2004 Pearson Education, Inc.

Chapter 10 Part 2 18

## PC Function (continued)

- **Branch Control determines the PC transfers based on five of its inputs defined as follows:**
  - N,Z – negative and zero status bits
  - PL – load enable for the PC
  - JB – Jump/Branch select: If JB = 1, Jump, else Branch
  - BC – Branch Condition select: If BC = 1, branch for N = 1, else branch for Z = 1.

- **The above is summarize by the following table:**

PC Operation	PL	JB	BC
Count Up	0	X	X
Jump	1	1	X
Branch on Negative (else Count Up)	1	0	1
Branch on Zero (else Count Up)	1	0	0

- **Sufficient information is provided here to design the PC**

Logic and Computer Design Fundamentals  
PowerPoint® Slides  
© 2004 Pearson Education, Inc.

Chapter 10 Part 2 19

## Instruction Decoder

- **The combinational instruction decoder converts the instruction into the signals necessary to control all parts of the computer during the single cycle execution**
- **The input is the 16-bit Instruction**
- **The outputs are control signals:**
  - Register file addresses DA, AA, and BA,
  - Function Unit Select FS
  - Multiplexer Select Controls MB and MD,
  - Register file and Data Memory Write Controls RW and MW, and
  - PC Controls PL, JB, and BC
- **The register file outputs are simply pass-through signals:**  
**DA = DR, AA = SA, and BA = SB**  
**Determination of the remaining signals is more complex.**

Logic and Computer Design Fundamentals  
PowerPoint® Slides  
© 2004 Pearson Education, Inc.

Chapter 10 Part 2 20

## Instruction Decoder (continued)

- The remaining control signals do not depend on the addresses, so must be a function of IR(13:9)
- Formulation requires examining relationships between the outputs and the opcodes given in Slides 12 and 13.
- Observe that for other than branches and jumps, FS = IR(12:9)
- This implies that the other control signals should depend as much as possible on IR(15:13) (which actually were assigned with decoding in mind!)
- To make some sense of this, we divide instructions into types as shown in the table on the next page

## Instruction Decoder (continued)

Truth Table for Instruction Decoder Logic


Instruction Function Type	Instruction Bits				Control Word Bits							
	15	14	13	9	MB	MD	RW	MW	PL	JB	BC	
Function unit operations using registers	0	0	0	X	0	0	1	0	0	X	X	
Memory read	0	0	1	X	0	1	1	0	0	X	X	
Memory write	0	1	0	X	0	X	0	1	0	X	X	
Function unit operations using register and constant	1	0	0	X	1	0	1	0	0	X	X	
Conditional branch on zero (Z)	1	1	0	0	X	X	0	0	1	0	0	
Conditional branch on negative (N)	1	1	0	1	X	X	0	0	1	0	1	
Unconditional Jump	1	1	1	X	X	X	0	0	1	1	X	

## Instruction Decoder (continued)

- The types are based on the blocks controlled and the seven signals to be generated; types can be divided into two groups:
  - Datapath and Memory Control (First 4 types)
  - PC Control (Last 3 types)
- In Datapath and Memory Control blocks controlled are considered:
  - Mux B (1st and 4th types)
  - Memory and Mux D (2nd and 3rd types)
  - By assigning codes with no or only one 1 for these, implementation of MB, MD, RW and MW are simplified.
- In Control Unit more of a bit setting approach was used:
  - Bit 15 = Bit 14 = 1 were assigned to generate PL
  - Bit 13 values were assigned to generate JB.
  - Bit 9 was used as BC which contradicts FS = 0000 needed for branches. To force FS(6) to 0 for branches, Bit 9 into FS(6) is disabled by PL.
- Also, useful bit correlations between values in the two groups were exploited in assigning the codes.

## Instruction Decoder (continued)

- The end result by use of the types, careful assignment of codes, and use of don't cares, yields very simple logic:
  - This completes the design of most of the essential parts of the single-cycle simple computer
- 
- | Instruction |    |    |    |    |    |   |   |    |   |   |   |    |   |   |    |
|-------------|----|----|----|----|----|---|---|----|---|---|---|----|---|---|----|
| Opcode      |    |    |    |    |    |   |   | DR |   |   |   | SA |   |   | SB |
| 15          | 14 | 13 | 12 | 11 | 10 | 9 | 8 | 7  | 6 | 5 | 4 | 3  | 2 | 1 | 0  |
|             |    |    |    |    |    |   |   |    |   |   |   |    |   |   |    |

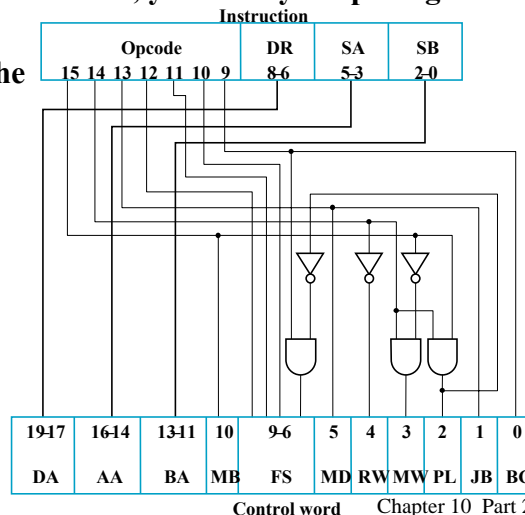

# Example Instruction Execution

## Six Instructions for the Single-Cycle Computer


Operation code	Symbolic name	Format	Description	Function	MB	MD	RW	MW	PL	JB	BC
1000010	ADI	Immediate	Add immediate operand	$R[DR] \leftarrow R[SA] + zf \ll (2:0)$	1	0	1	0	0	0	0
0010000	LD	Register	Load memory content into register	$R[DR] \leftarrow M[R[SA]]$	0	1	1	0	0	1	0
0100000	ST	Register	Store register content in memory	$M[R[SA]] \leftarrow R[SB]$	0	1	0	1	0	0	0
0001110	SL	Register	Shift left	$R[DR] \leftarrow sl R[SB]$	0	0	1	0	0	1	0
0001011	NOF	Register	Complement register	$R[DR] \leftarrow \overline{R[SA]}$	0	0	1	0	0	0	1
1100000	BRZ	Jump/Branch	If $R[SA] = 0$ , branch to PC + se AD	If $R[SA] = 0$ , $PC \leftarrow PC + se AD$ If $R[SA] \neq 0$ , $PC \leftarrow PC + 1$	1	0	0	0	1	0	0

- Decoding, control inputs and paths shown for **ADI**, **RD** and **BRZ** on next 6 slides

Logic and Computer Design Fundamentals  
PowerPoint® Slides  
© 2004 Pearson Education, Inc.


Chapter 10 Part 2 25

## Decoding for ADI

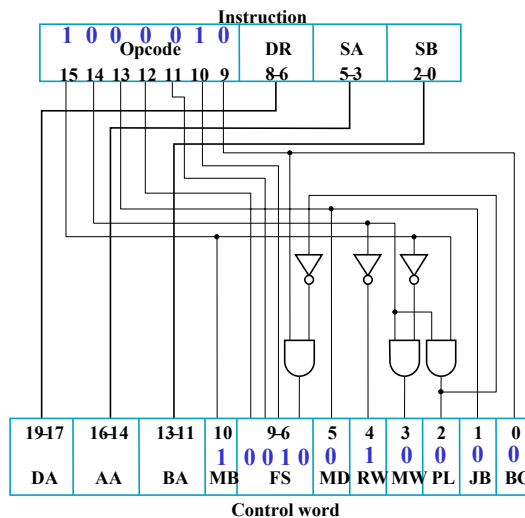


Logic and Computer Design Fundamentals  
PowerPoint® Slides  
© 2004 Pearson Education, Inc.

Chapter 10 Part 2 26

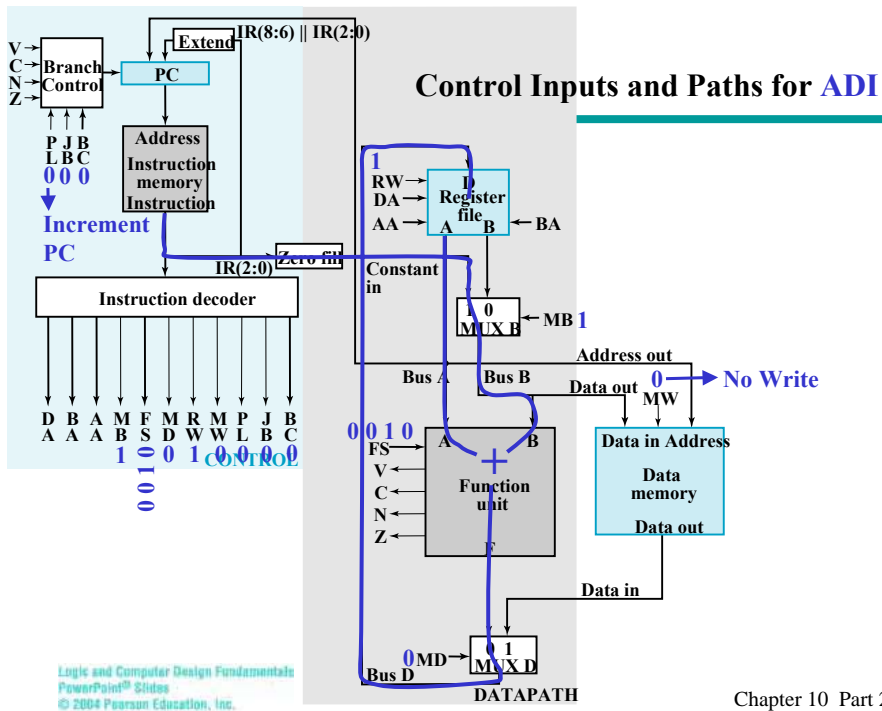


Chapter 10 Part 2 27

## Decoding for LD

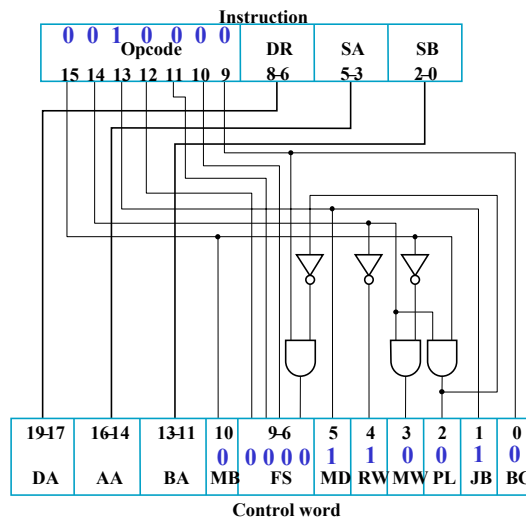


Chapter 10 Part 2 28

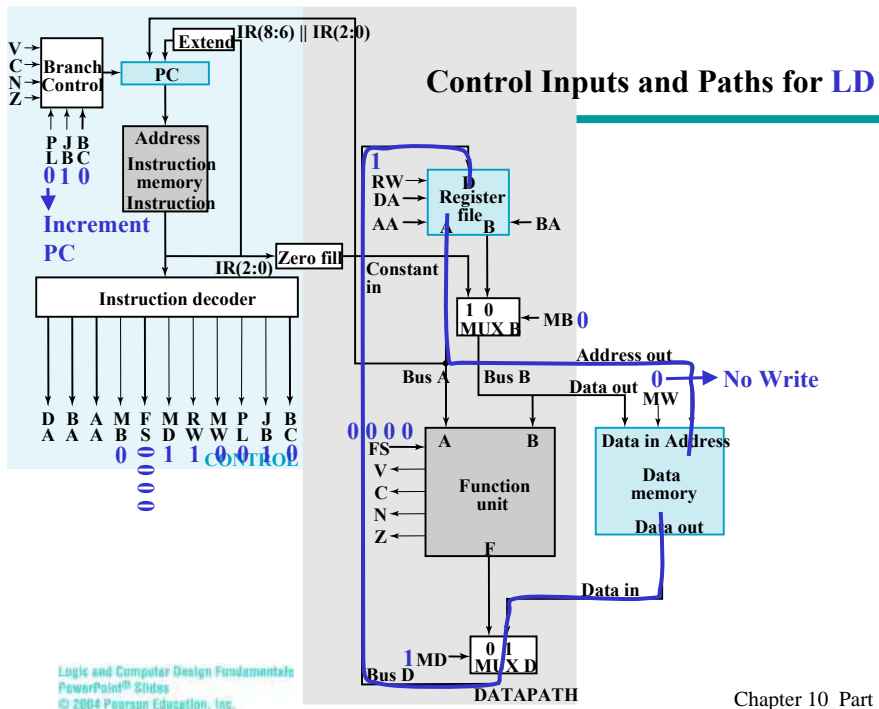

Chapter 10 Part 2 29

## Decoding for BRZ

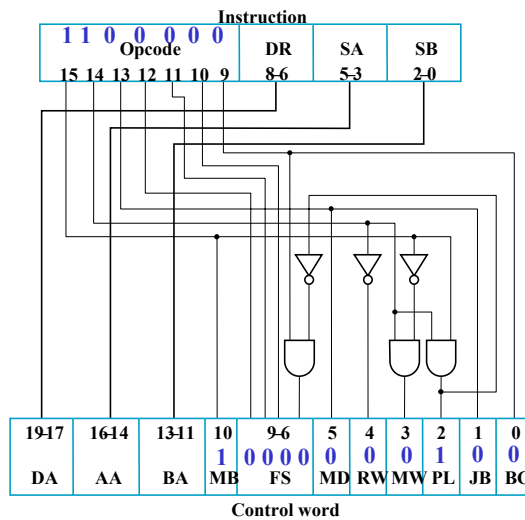

Chapter 10 Part 2 30

